

Enumerate States

Last updated 1/22/21

Enumerated States

- These slides introduce Enumerated States
- Upon completion: You should be able to create a state machine using enumerated states

Enumerated States

- Enumerated States
 - Similar to enumerated types in C
 - Define a new TYPE with a fixed set of recognized values

`type STATE_TYPE is (A, B, C, D, E, F, G, H, I, J);`

- Each state can be identified by its position (integer)
 - A – 0
 - B – 1
 - ...
 - J – 9
- `STATE_TYPE'pos(D) → 3`

Enumerated States


- Enumerated States
 - Create signals of the enumerated type

```
signal state:          STATE_TYPE;  
signal state_next:   STATE_TYPE;
```

- Synthesis is done using the enumerated states with the corresponding encoding
 - Binary
 - One Hot
 - Gray
 - Johnson
 - Auto

Enumerated States

Mod 10 Counter using Enumerated States

 

Enumerated States

- Mod 10 Counter – Enumerated States

```
-----  
-- counter_mod10_fsmc.vhdl  
-- created 3/30/18  
-- tj  
-- rev 0  
-----  
-- mod 10 up-counter - state machine with case statement  
-- enumerated states  
-----  
-- Inputs: i_rstb, i_clk  
-- Outputs: o_cnt[3:0]  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
entity counter_mod10_fsmc is  
  port (  
    i_clk : in std_logic;  
    i_rstb : in std_logic;  
    o_cnt : out std_logic_vector(3 downto 0)  
  );  
end entity;
```

```
architecture behavioral of counter_mod10_fsmc is  
  -- internal signals  
  type STATE_TYPE is (A, B, C, D, E, F, G, H, I, J);  
  signal state: STATE_TYPE;  
  signal state_next: STATE_TYPE;  
begin  
  -- next state logic  
  process(all)  
  begin  
    case state is  
      when A => state_next <= B;  
      when B => state_next <= C;  
      when C => state_next <= D;  
      when D => state_next <= E;  
      when E => state_next <= F;  
      when F => state_next <= G;  
      when G => state_next <= H;  
      when H => state_next <= I;  
      when I => state_next <= J;  
      when J => state_next <= A;  
      when others => state_next <= A;  
    end case;  
  end process;
```

```
-- Register logic  
process(i_clk, i_rstb)  
begin  
  -- reset  
  if (i_rstb = '0') then  
    state <= A;  
  -- rising i_clk edge  
  elsif (rising_edge(i_clk)) then  
    state <= state_next;  
  end if;  
end process;  
  
-- Output logic  
process(all)  
begin  
  case state is  
    when A => o_cnt <= "0000";  
    when B => o_cnt <= "0001";  
    when C => o_cnt <= "0010";  
    when D => o_cnt <= "0011";  
    when E => o_cnt <= "0100";  
    when F => o_cnt <= "0101";  
    when G => o_cnt <= "0110";  
    when H => o_cnt <= "0111";  
    when I => o_cnt <= "1000";  
    when J => o_cnt <= "1001";  
    when others => o_cnt <= "0000";  
  end case;  
end process;  
end behavioral;
```

Enumerated state declaration


State initialization and update (register logic)

Next state logic

Output logic

Enumerated States



- Mod 10 Counter –Enumerated States

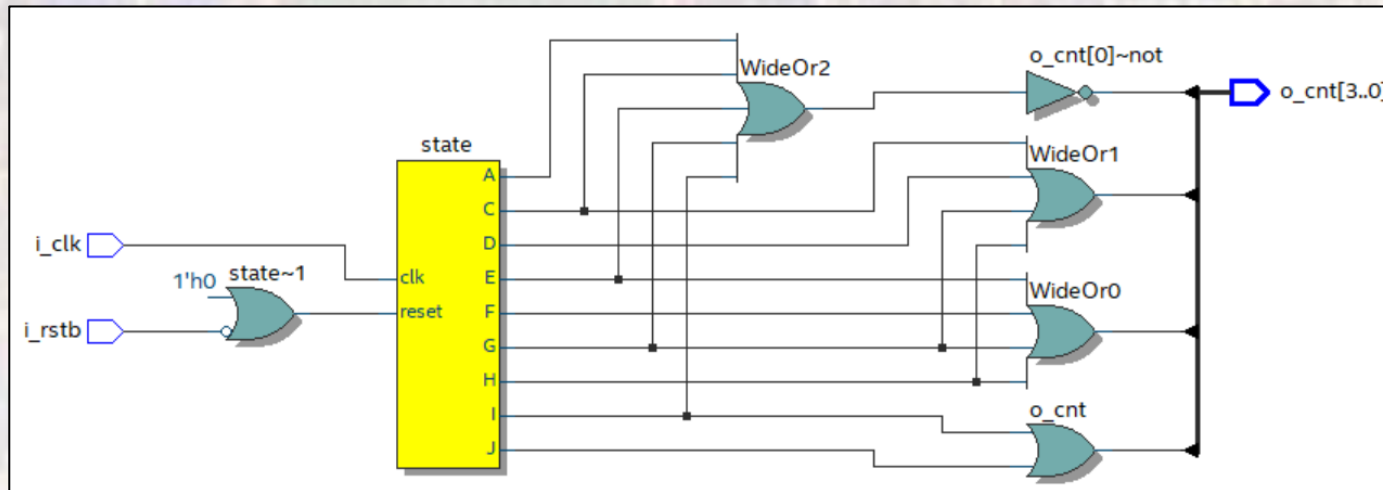

Quartus recognized part of the code
as a state machine


Enumerated States

- Mod 10 Counter –Enumerated States

 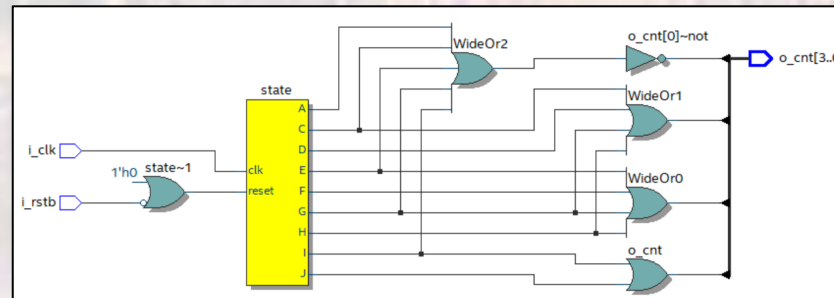

Enumerated States

- Mod 10 Counter –Enumerated States

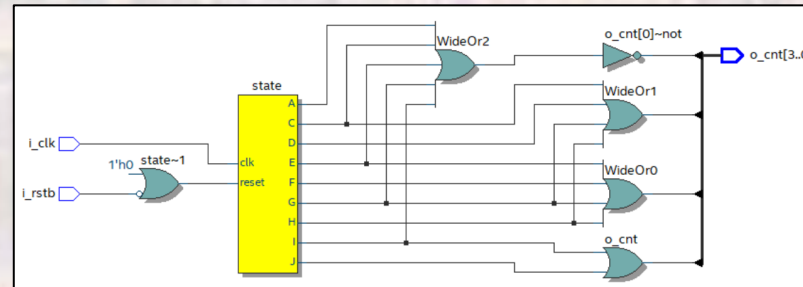


	Source State	Destination State	Condition
1	A	B	
2	B	C	
3	C	D	
4	D	E	
5	E	F	
6	F	G	
7	G	H	
8	H	I	
9	I	J	
10	J	A	

Transitions / Encoding /

Enumerated States

- Mod 10 Counter –Enumerated States

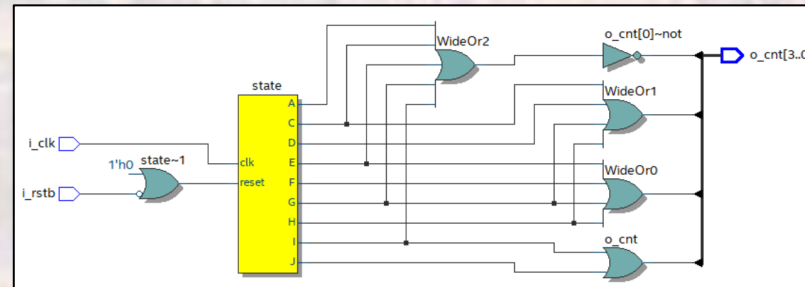

Default encoding is a
modified 1-hot

