

Flip-Flop Basics





Last updated 1/11/21

Flip-Flop Basics

- D Latch (data)

Level Sensitive Latch

   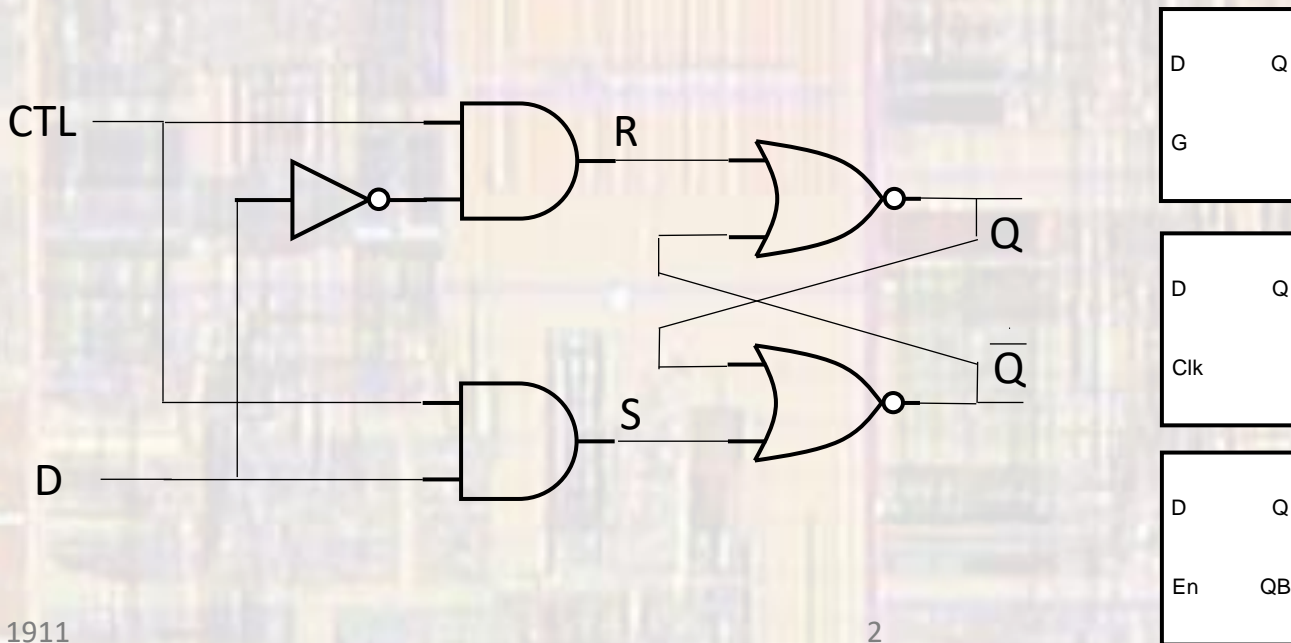CTL = low \rightarrow latched
 CTL = high \rightarrow Transfer



CTL	D	Q
0	X	Q_{old}
1	D	D

Flip-Flop Basics


- D Flip-Flop (data)
 - Sequential
 - Bi-stable circuit
 - Synchronous – outputs change on a (rising) clk edge
 - Output changes limited to specific input conditions

Flip-Flop Basics

- D Flip-Flop (data)

- Sequential

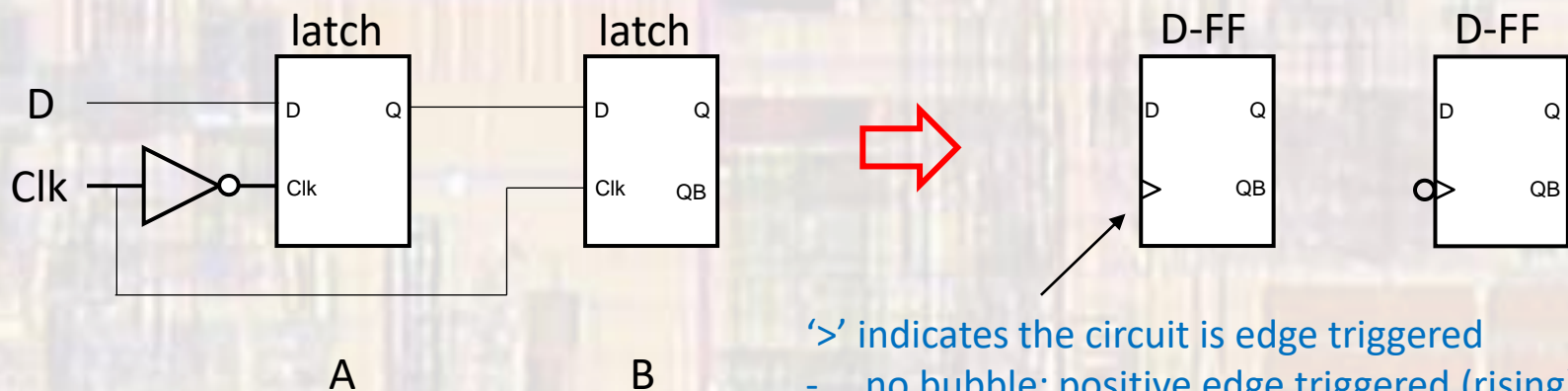- Bi-stable circuit
- Synchronous – outputs change on a (rising) clk edge
- Output changes limited to specific input conditions




- '>' indicates the circuit is edge triggered
- no bubble: positive edge triggered (rising)
- bubble: negative edge triggered (falling)

Flip-Flop Basics

D-Latch

CTL CLK	D	Q
0	x	Q_{old}
1	D	D

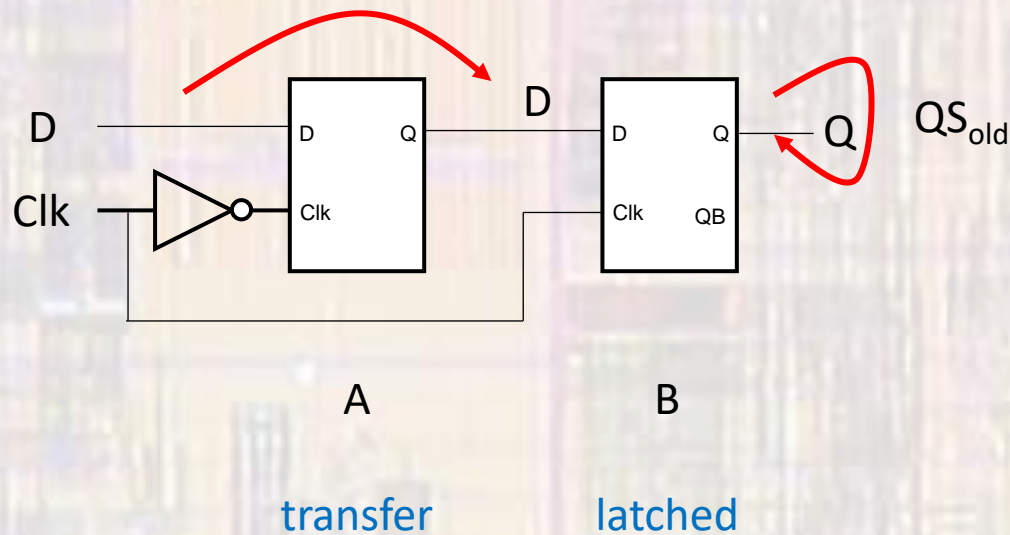- D Flip-Flop (data)
- Clock low – after a short time
 - A is enabled and passes D to it's Q output
 - B is in latch mode and retains it's state - Q_{old}




D	Clk	Q
x	0	Q_{old}

Flip-Flop Basics

- D Flip-Flop (data)

- Clock high – after a short time

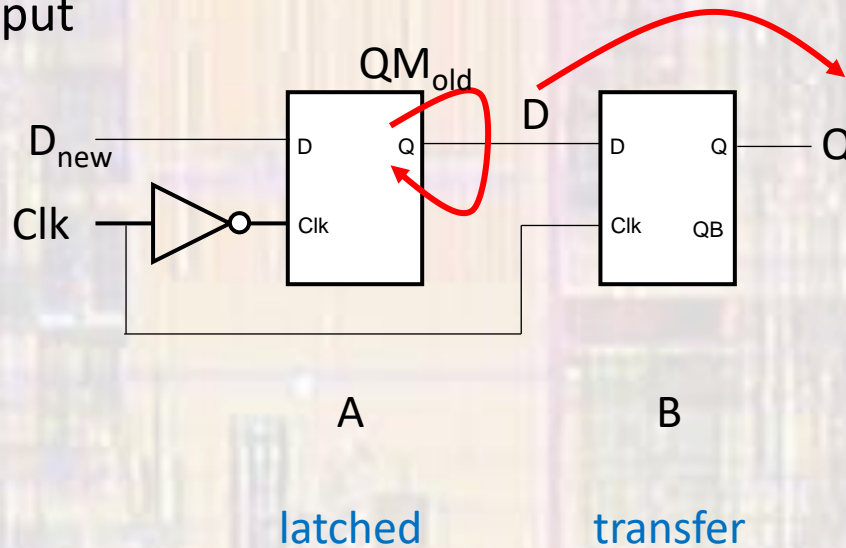- A is latched and retains it's state – $Q_{m_{old}}$ (original value of D)
- B is in transfer mode and would have already passed D to it's Q output




D	Clk	Q
x	0	Q_{old}
x	1	$Q_{m_{old}}$ (D_{old})

Flip-Flop Basics

- D Flip-Flop (data)

- Clock **Low** → **High**

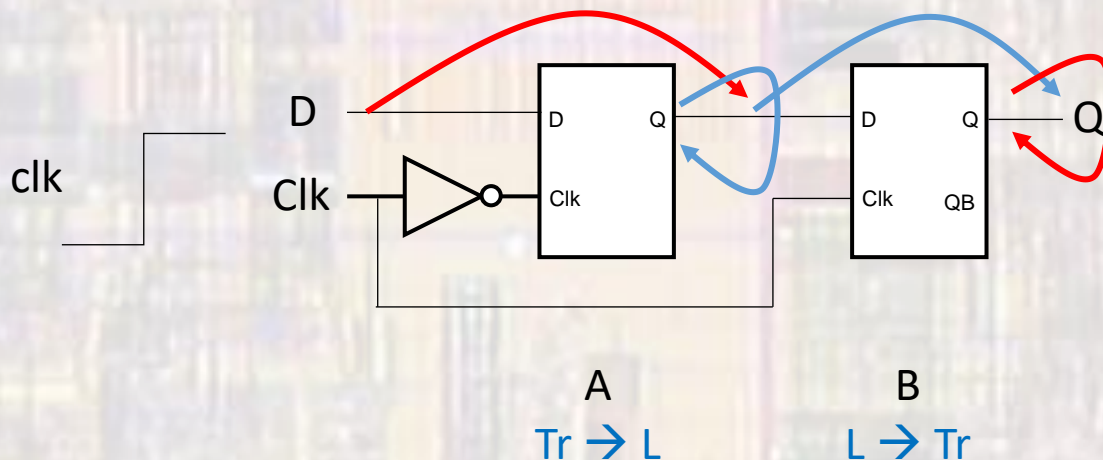- D has previously been passed to the intermediate node
- When clk transitions high, the intermediate value (D) is passed to the output while simultaneously the A becomes latched
- Further changes of the D input are blocked by the latched A




D	Clk	Q
x	0	Q_{old}
x	1	QM_{old}
D	↑	D

Flip-Flop Basics

- D Flip-Flop (data)

- Clock **High** \rightarrow **Low**

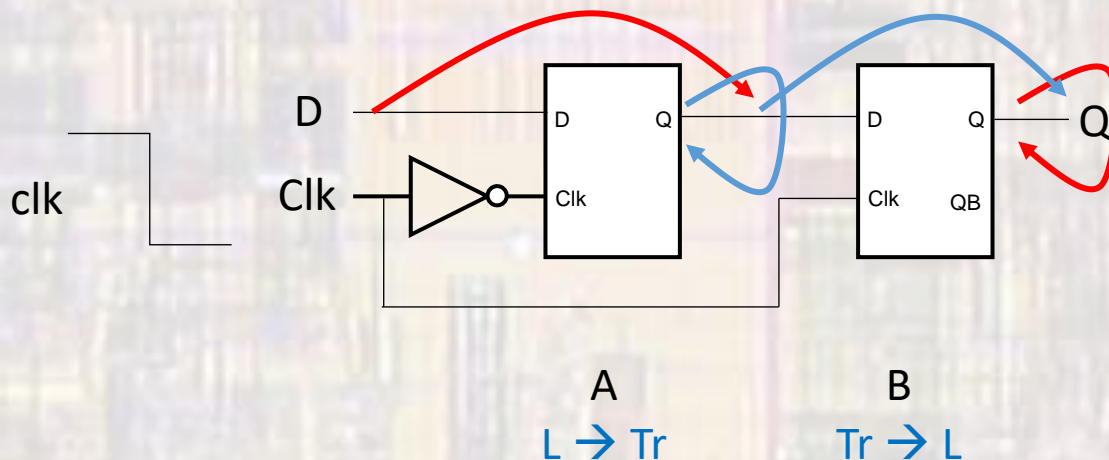- The output is latched by the B
- The new D input is allowed to transfer to the intermediate node but no further





D	Clk	Q
x	0	Q_{old}
x	1	QM_{old}
D	\uparrow	D
x	\downarrow	QM_{old}

Flip-Flop Basics

- D Flip-Flop (data)

- Truth Table

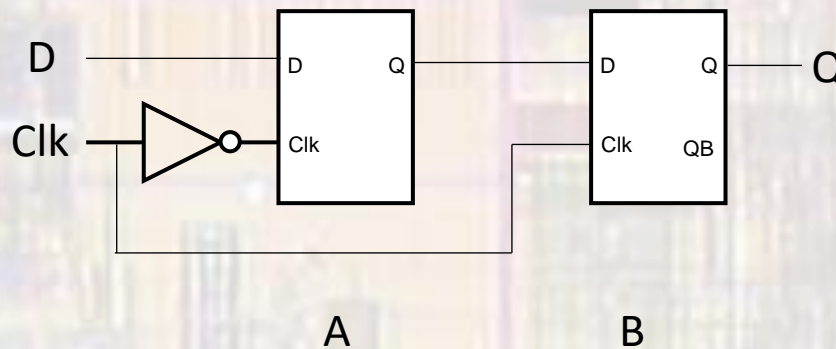 - Positive Edge Triggered D Flip-Flop
 - (typically, just called a D Flip-flop)



D	Clk	Q
x	0	Q_{old}
x	1	Q_{old}
D	↑	D
x	↓	Q_{old}