
 


Flip-Flop Circuits

Last updated 1/14/21



Flip Flop Circuits

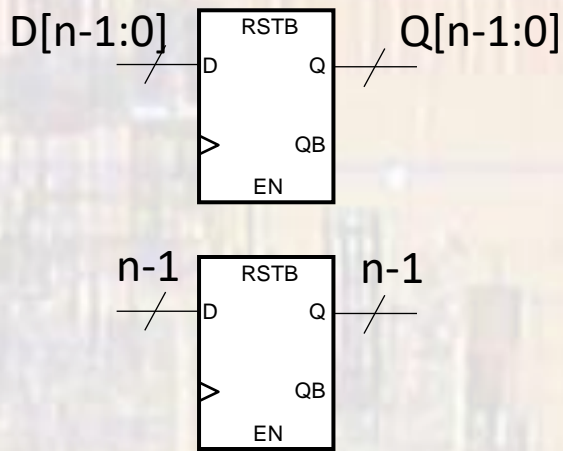- Register
 - Collection of n Flip-Flops
 - Configured in parallel
 - Common clock, set/reset, enable
 - Stores n state variables





Flip Flop Circuits

- Register
 - I/O Port on MSP432

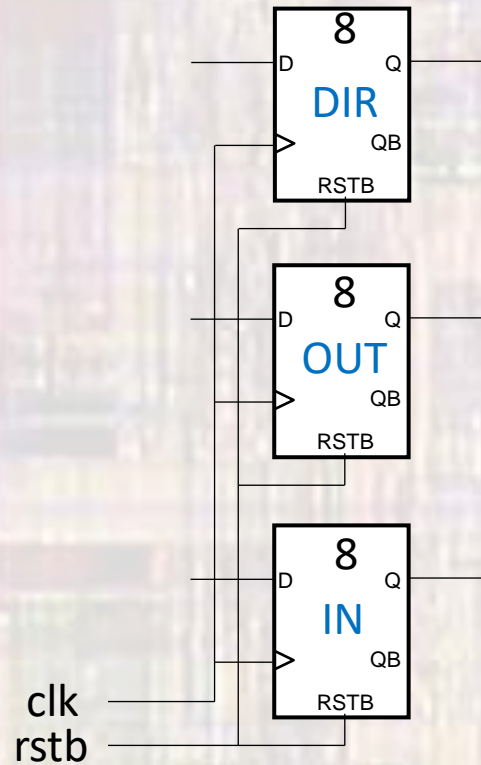 


Flip Flop Circuits

- Register
 - With Load (enable)

  

Flip Flop Circuits


 
- Shift Register
 - Shift a series of bits within a register (1 element L/R)



Flip Flop Circuits


- Shift Register

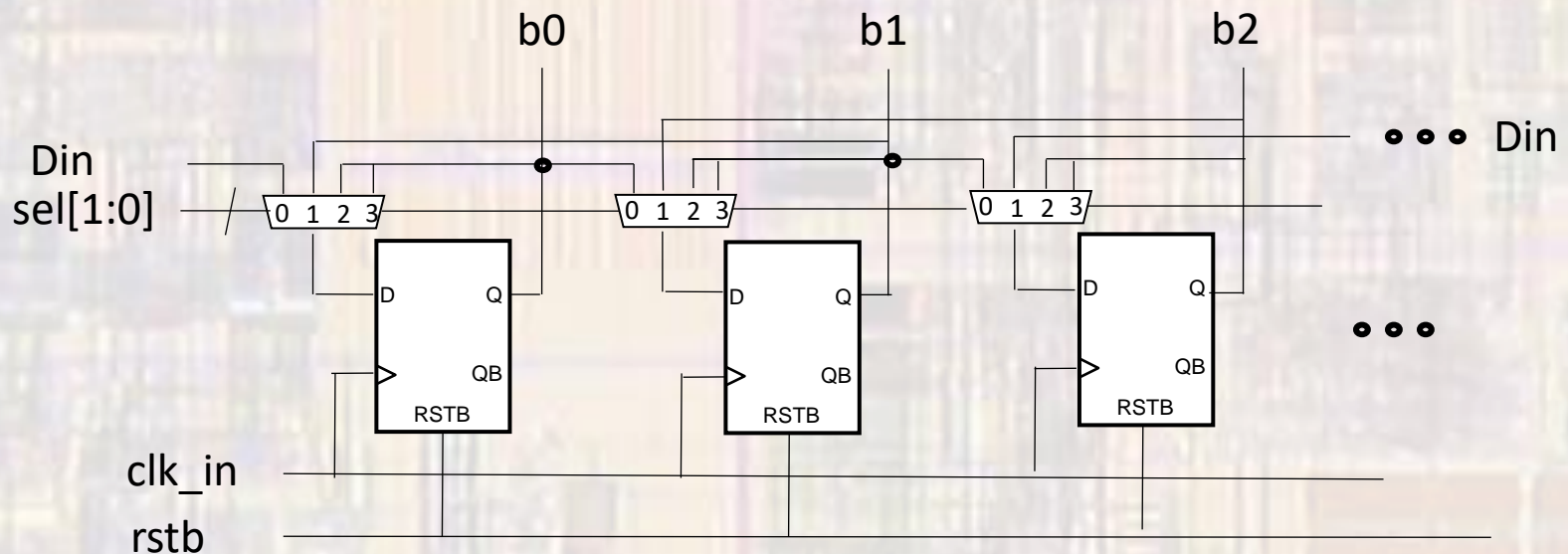 - Shift a series of bits within a register (1 element L/R)
- sel[0]: (0) shift right, (1) shift left
- sel[1]: (0) shift, (1) no-shift



Flip Flop Circuits

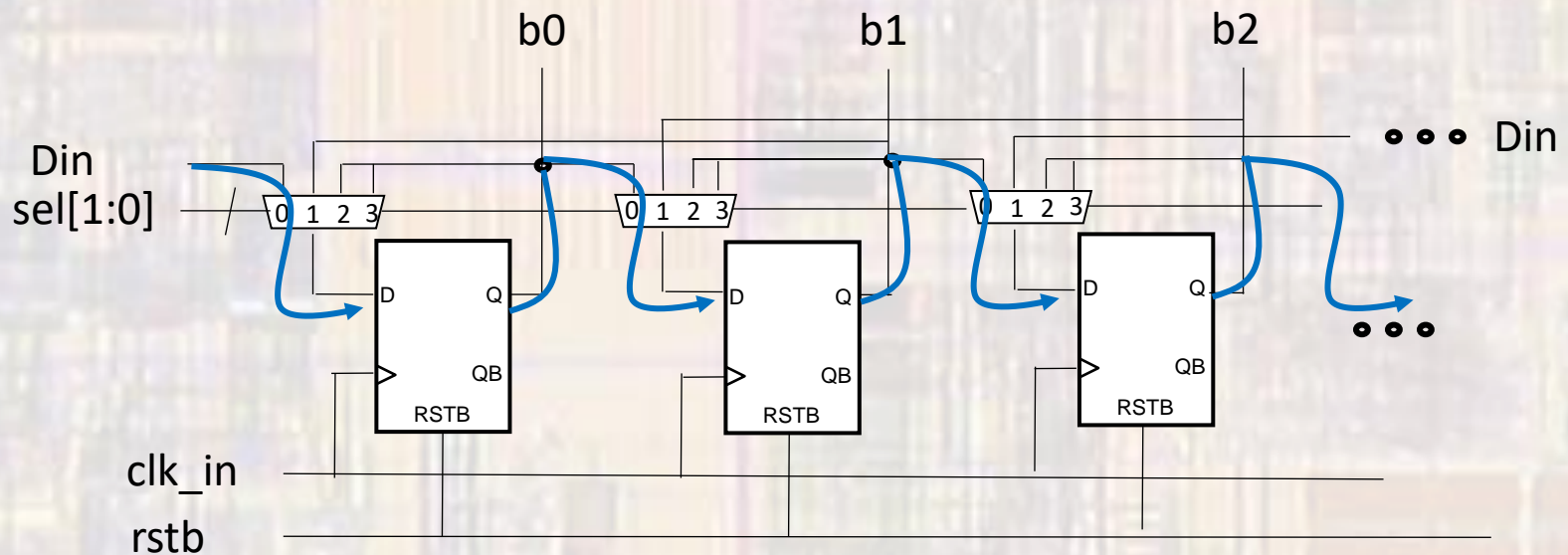
- Shift Register
 - Shift a series of bits within a register (1 element L/R)
 - sel = 0,0 shift left



Flip Flop Circuits

- Shift Register

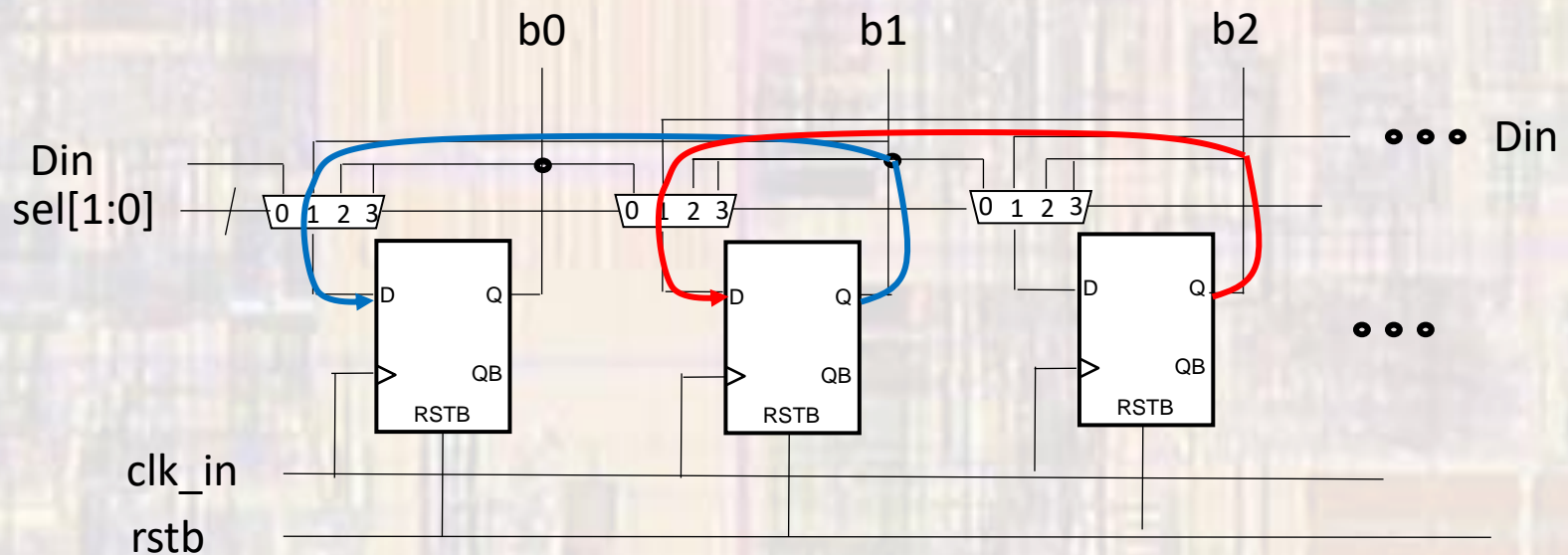
- Shift a series of bits within a register (1 element L/R)
- sel = 0,1 shift right



Our circuit does not indicate what to shift into the last bit location

Flip Flop Circuits

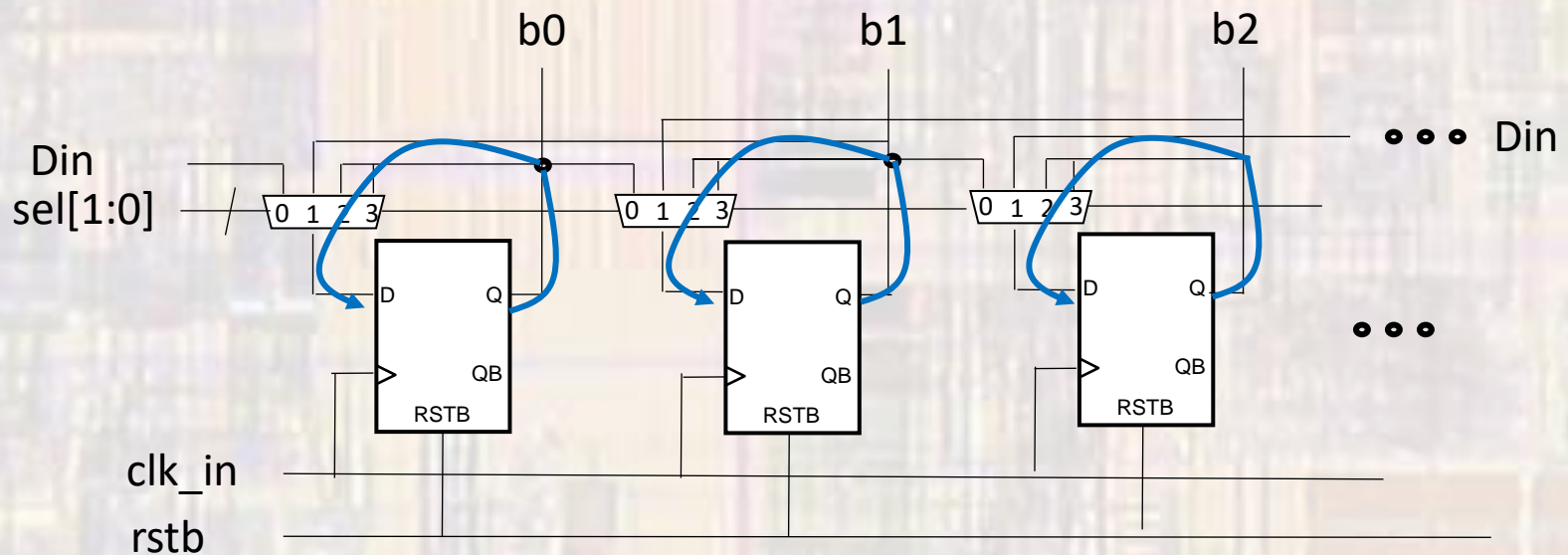- Shift Register
 - Shift a series of bits within a register (1 element L/R)
 - sel = 1,0 or 1,1 no shift




Flip Flop Circuits

- Counter

- Count in binary

- 0000 → 0001 → 0010 → 0011 → 0100 ... 1111 → 0000 ...


Note: bit order reversed

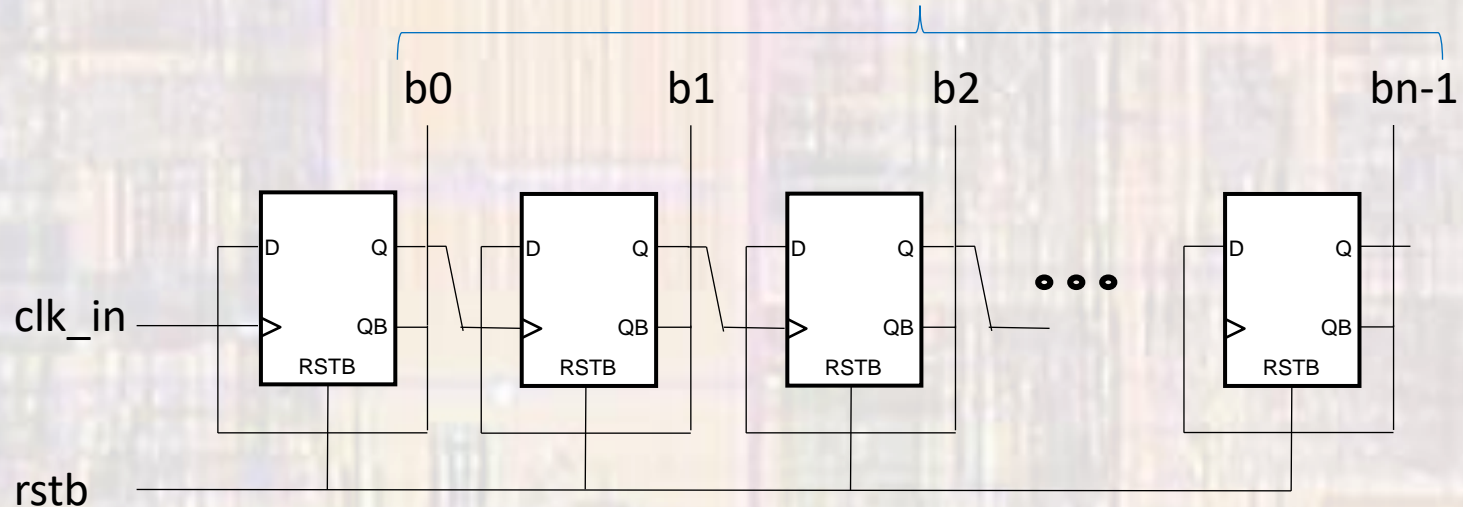

Flip Flop Circuits

- Counter

	0	0	0	0
clk ↑	1	0	0	0
clk ↑ Q1 ↑	0	1	0	0
clk ↑	1	1	0	0
clk ↑ Q1 ↑ Q2 ↑	0	0	1	0

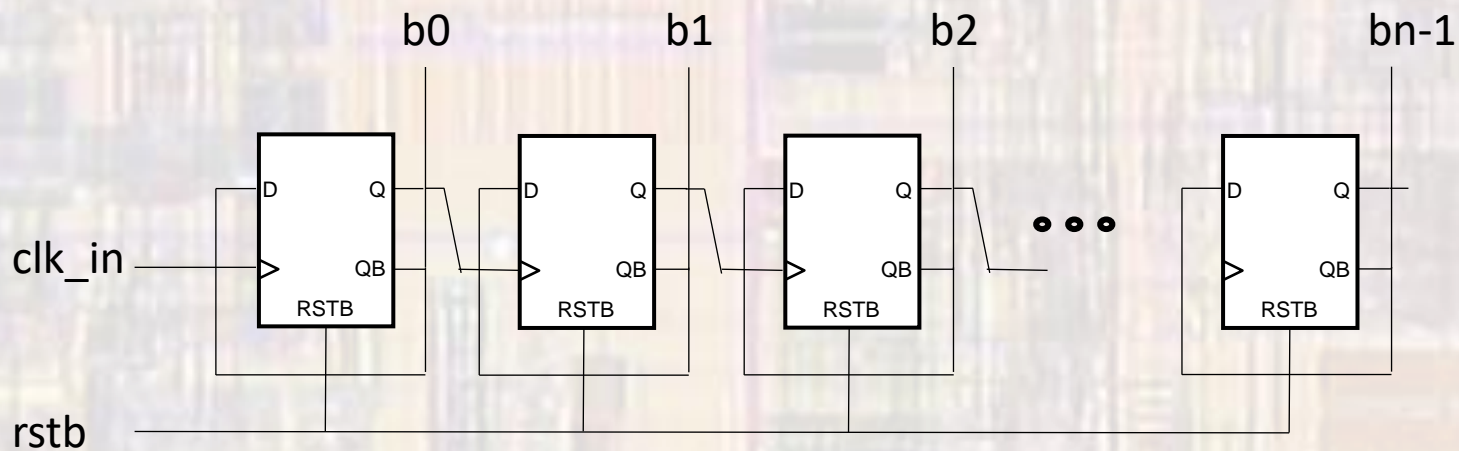


What's wrong with this solution

Flip Flop Circuits

- Counter

- Count in binary

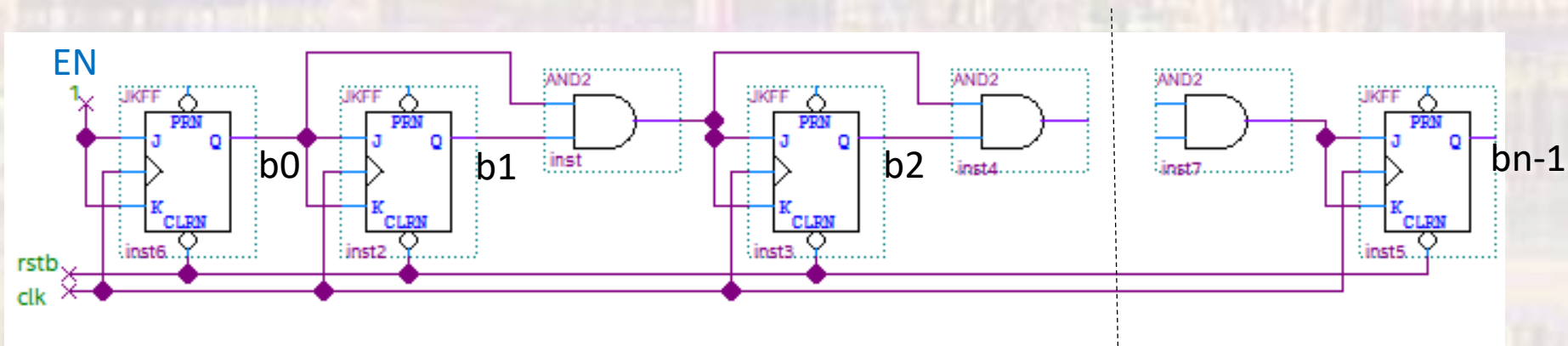- 0000 → 0001 → 0010 → 0011 → 0100 ... 1111 → 0000 ...





en	b0	b1	b2	b3	bn-1
1	0	0	0	0	0
1	1	0	0	0	0
1	0	1	0	0	0
1	1	1	0	0	0
1	0	0	1	0	0
1	1	0	1	0	0
1	0	1	1	0	0
1	1	1	1	0	0
1	0	0	0	1	0

Flip Flop Circuits

- Modulo 10 Counter
 - Mod 10
 - Counts from 0 to 9, then back to 0, ...
 - If output is 9 (1001), want next value to be 0 (0000)
 - 1001 \rightarrow 1010 but we want 1001 \rightarrow 0000
 - no change in LSB
 - don't allow bit 1 to change (force JK to 0 – *and* with B3 *not*)
 - this works since no B1 change between 1000 and 1001
 - no change in bit 2
 - force bit 3 to zero (force JK to 1 – add in a path with B0 *and* B1)
- once in 0 state – progresses normally


Flip Flop Circuits

 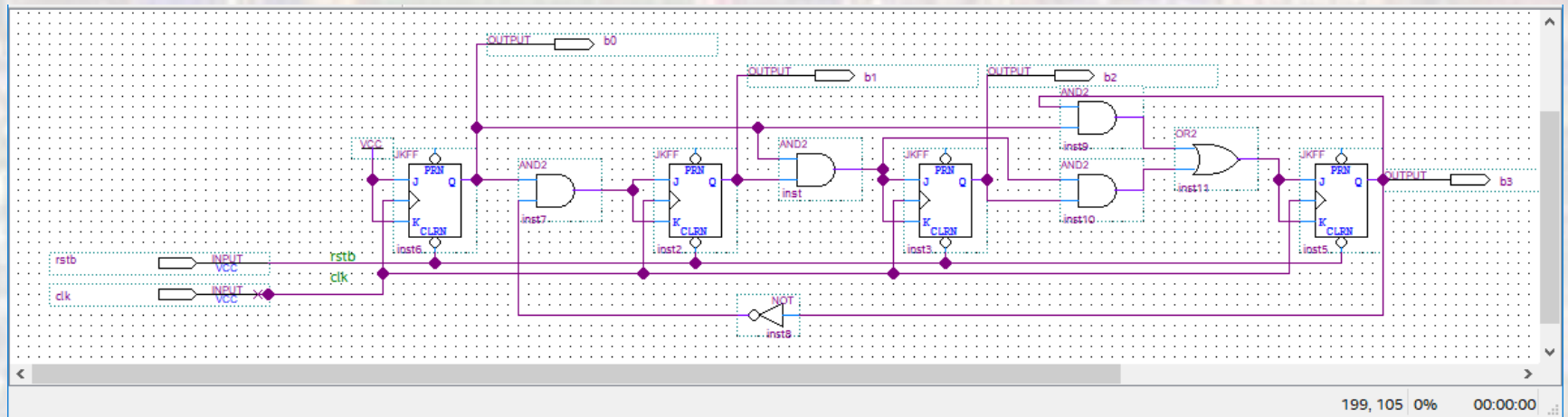- Modulo 10 Counter
 - Mod 10
 - Counts from 0 to 9, then back to 0, ...



Flip Flop Circuits

 
- Register File – simple
 - Group of n-bit registers
 - Accessed via a multiplexor (address)



Flip Flop Circuits

- Register File - simple

	we_b	addr	data_in	data_out
	1	7	472	?
clk ↑ →	0	7	472	?
	1	7	472	472
	1	7	93	472
	1	12	93	?
clk ↑ →	0	12	93	?
	1	12	93	93
	1	23	0	?
clk ↑ →	0	23	0	?
	1	23	0	0
	1	7	55	472
	1	12	55	93

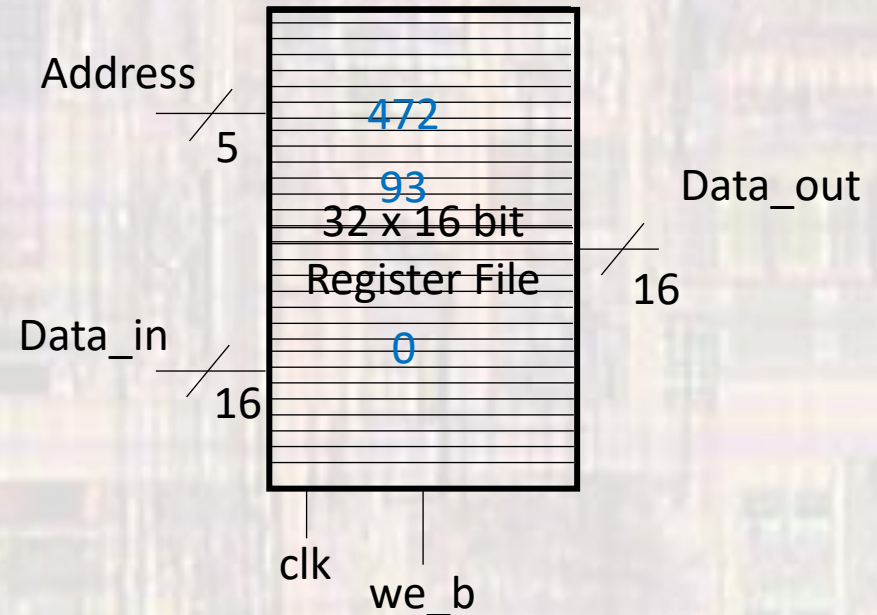


clk only required for writes, reads are asynchronous

In normal application, clock would always be running

Flip Flop Circuits

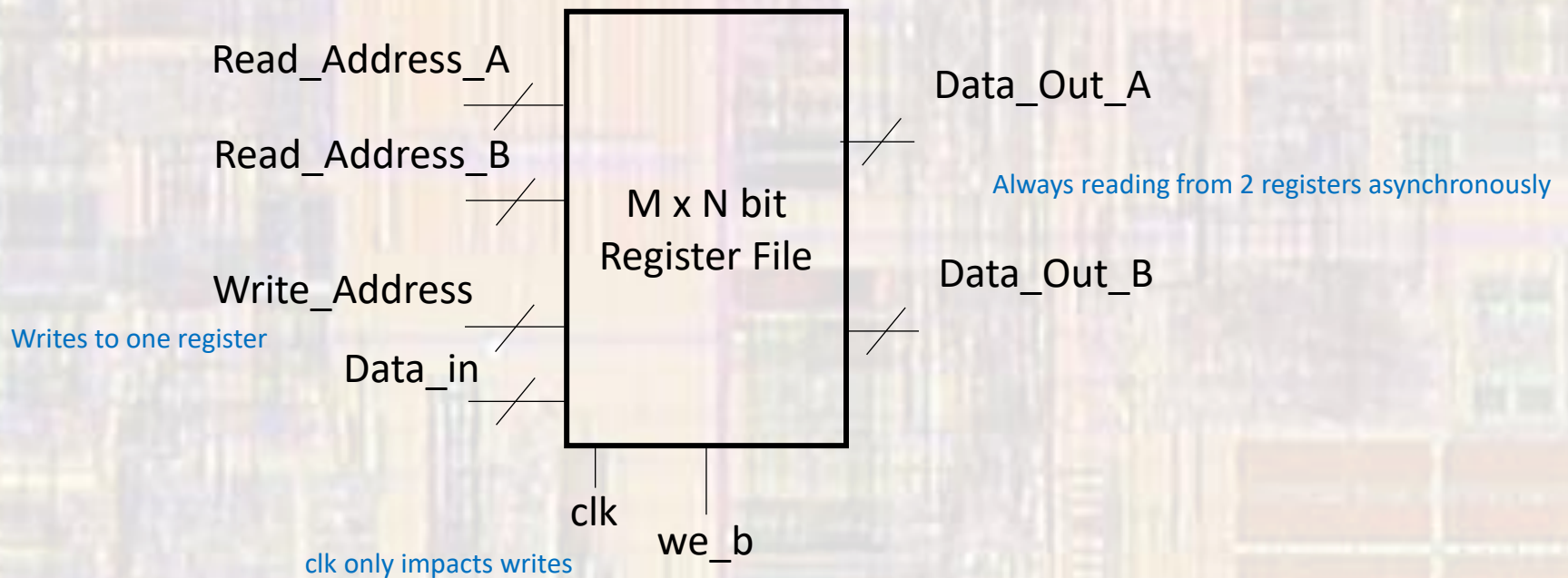- Register File – multi-port
 - Group of n-bit registers
 - Accessed via a multiplexor
 - Can have multiple inputs and outputs



Flip Flop Circuits

- Clock Divider
 - Modulo counter
 - XOR gate to toggle the output clock
- Divide by 24
 - Modulo 12 counter
 - XOR gate that toggles the output every time the counter hits 0