
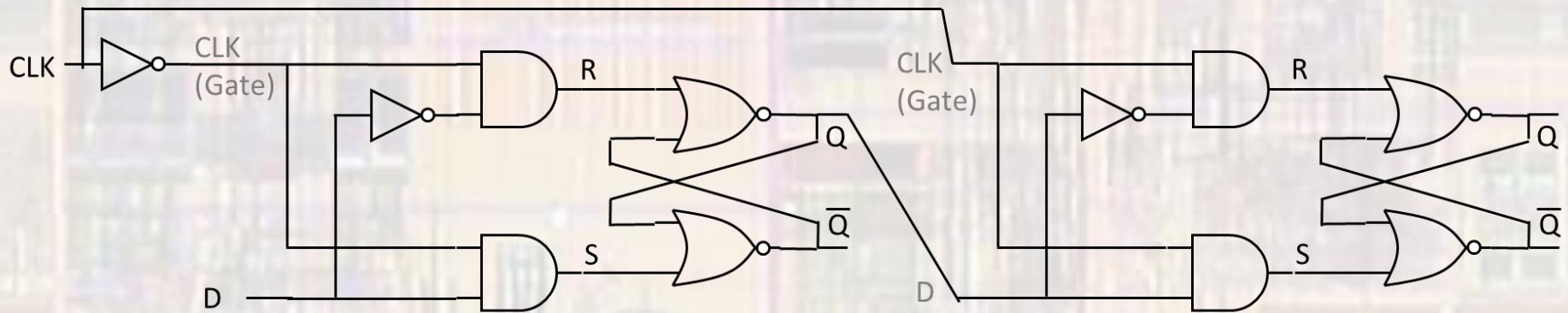


# Flip-Flop Enhancements

Last updated 1/11/21

# Flip-Flop Enhancements


- D Flip-Flop – SR Latch based

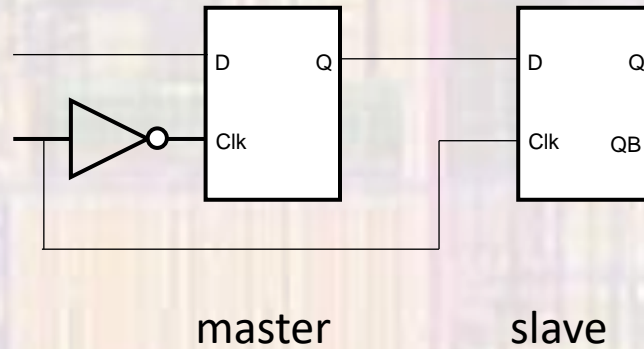

How many Transistors ???
 
# Flip-Flop Enhancements


- D Flip-Flop – Pass Gate based
- D latch



src: Harris & Harris

# Flip-Flop Enhancements

- D Flip-Flop – Pass Gate Based

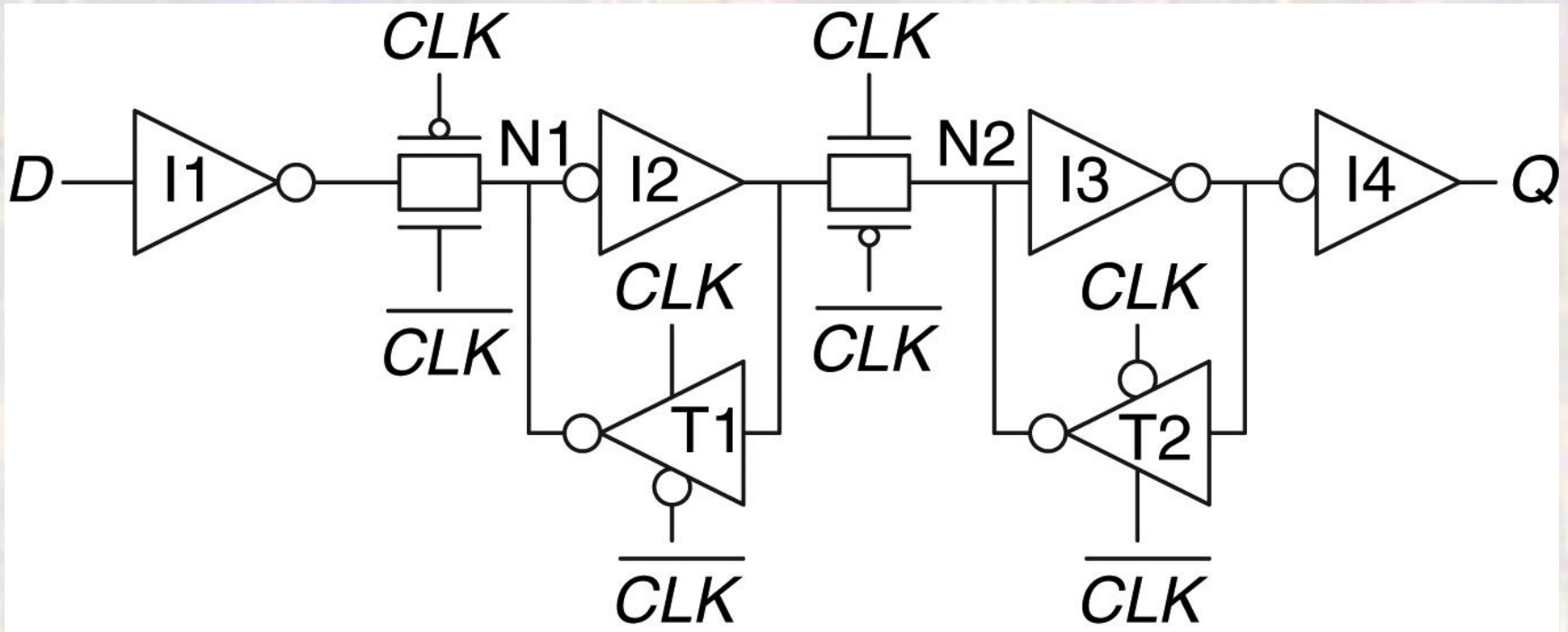

src: Harris & Harris


How many Gates ???

# Flip-Flop Enhancements

- Enhanced D Flip-Flops
  - Enable – limit when the FF responds to the clk
  - Set – force the FF into the  $Q=1$  state, independent of D
  - Reset – force the FF into the  $Q=0$  state, independent of D
  - Set/Reset can be asynchronous or synchronous
  - Enable/Set/Reset – can be active high or active low
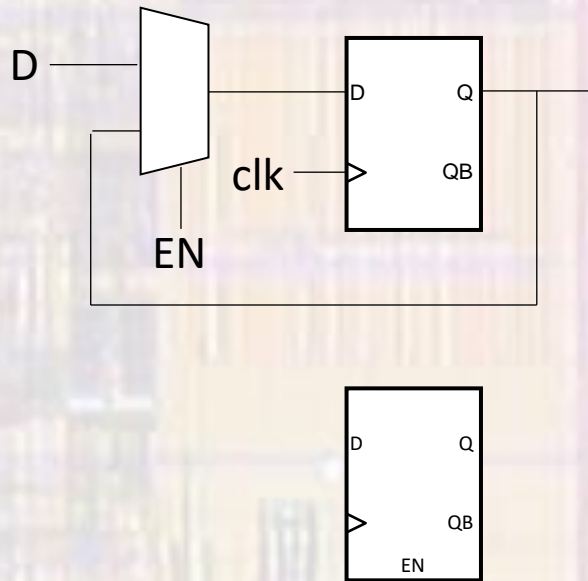
# Flip-Flop Enhancements


- Enhanced D Flip-Flops
  - Synchronous Enable - mux




D	Clk	EN	Q
x	x	0	$Q_{old}$
x	0	1	$Q_{old}$
x	1	1	$Q_{old}$
x	↓	1	$Q_{old}$
D	↑	1	D
 
# Flip-Flop Enhancements

- Enhanced D Flip-Flops
  - Synchronous Enable – gated clock



Requires EN only changes when clk is low

 


D	Clk	EN	Q
x	x	0	$Q_{old}$
x	0	1	$Q_{old}$
x	1	1	$Q_{old}$
x	↓	1	$Q_{old}$
D	↑	1	D

**Normally clock gating is considered bad practice at the system level**


# Flip-Flop Enhancements

- Enhanced D Flip-Flops


- Synchronous Set

 

- Synchronous Reset - RST

 


- Reset\_bar – RSTB

 


 
# Flip-Flop Enhancements

- Enhanced D Flip-Flops
- Synchronous Set/Reset – **very uncommon**



D	Clk	SET	RST	Q
x	0	x	x	$Q_{old}$
x	1	x	x	$Q_{old}$
x	↓	x	x	$Q_{old}$
D	↑	0	0	D
x	↑	1	-	1
x	↑	-	1	0


SETB / RSTB operate in active low mode

# Flip-Flop Enhancements

- Enhanced D Flip-Flops

- Asynchronous Set/Reset**

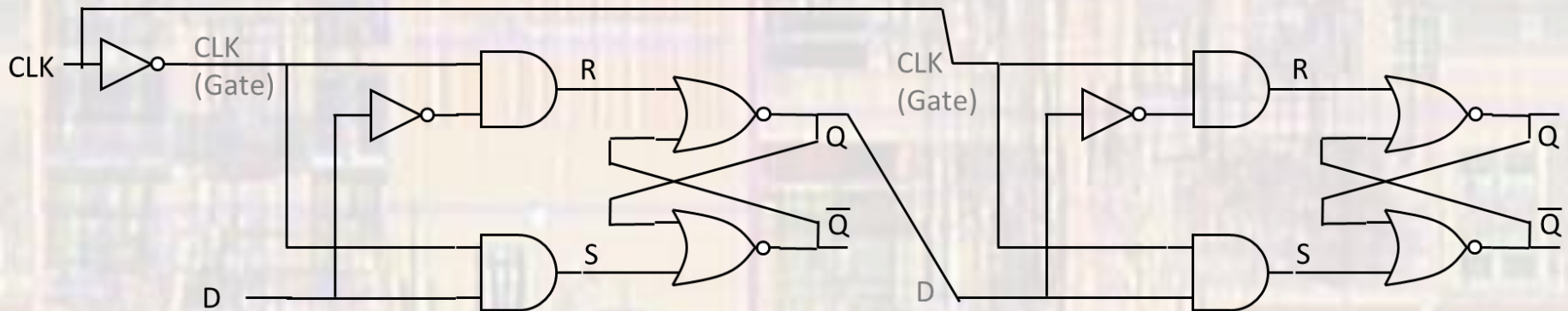- Due to the latching behavior of the DFF – require internal circuit changes




# Flip-Flop Enhancements

- Enhanced D Flip-Flops


- Asynchronous Set

 - Due to the latching behavior of the DFF – require internal circuit changes


 
# Flip-Flop Enhancements

- Enhanced D Flip-Flops
  - Asynchronous Set/Reset




D	Clk	SET	RST	Q
x	0	0	0	$Q_{old}$
x	1	0	0	$Q_{old}$
x	↓	0	0	$Q_{old}$
D	↑	0	0	D
x	x	1	-	1
x	x	-	1	0

SETB / RSTB operate in active low mode
 
# Flip-Flop Enhancements


- Additional Flip-Flops
  - T – Flip-Flop (Toggle)



T	Clk	Q
x	0	$Q_{old}$
x	1	$Q_{old}$
x	↓	$Q_{old}$
0	↑	$Q_{old}$
1	↑	$\overline{Q_{old}}$
 
# Flip-Flop Enhancements

- Additional Flip-Flops
  - JK – Flip-Flop



J	K	clk	Q
x	x	0	$Q_{old}$
x	x	1	$Q_{old}$
x	x	↓	$Q_{old}$
0	0	↑	$Q_{old}$
0	1	↑	0
1	0	↑	1
1	1	↑	$\overline{Q_{old}}$

} Matches the J input