

Flip-Flop HDL

Last updated 1/18/21

Flip-Flop HDL

- Latches are recognized by a pre-defined VHDL template

```
process (clock signal)
begin
  if(clock signal) then
    actions
  end if;
end process;
```

note:

- If statement without an else

```
process (i_clk, i_d)
begin
  if(i_clk = '1') then
    o_q <= i_d;
  end if;
end process;
```


- what happens when the clock signal is false case is not defined
- the synthesizer must assume you meant to create a latch

Flip-Flop HDL

- Latches are recognized by a pre-defined VHDL template

```
--  
-- latches.vhd1  
--  
-- created: 1/26/18  
-- by: johnsontim  
-- rev: 0  
--  
-- file to synthesize latches for lecture slides  
--  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
  
entity latches is  
  port(  
    i_clk : in std_logic;  
    i_d   : in std_logic;  
  
    o_q : out std_logic  
  );  
end entity latches;
```
 
```
-- latch generated-----  
architecture behavioral of latches is  
begin  
  process(i_clk, i_d)  
  begin  
    if(i_clk = '1') then  
      o_q <= i_d;  
    end if;  
  end process;  
end architecture;
```



Type	ID	Message
Warning	10631	VHDL Process Statement warning at latches.vhd1(27): inferring latch(es) for signal or variable "o_q", which holds its previous value in one or more paths through the process
Warning	10041	Inferred latch for "o_q" at latches.vhd1(27)
Info	quartus Prime Analysis & Elaboration was successful. 0 errors, 2 warnings	

Flip-Flop HDL

- ~~Latches~~ are recognized by a pre-defined VHDL template

```
process (clock signal)
begin
  if(clock signal) then
    actions
  else
    actions
  end if;
end process;
```

```
process (i_clk)
begin
  if(i_clk = 1) then
    o_q <= i_d;
  else
    o_q <= 1;
  end if;
end process;
```

if a valid else
statement is
included then
something
other than a
latch will be
created

Flip-Flop HDL


- Latches are recognized by a pre-defined VHDL template

```
-----  
--  
-- latches.vhdl  
--  
-- created: 1/26/18  
-- by: johnsontim  
-- rev: 0  
--  
-- file to synthesize latches for lecture slides  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
  
entity latches is  
  port(  
    i_clk : in std_logic;  
    i_d   : in std_logic;  
  
    o_q : out std_logic  
  );  
end entity latches;
```

```
-----  
-- no latch generated-----  
architecture behavioral of latches is  
begin  
  process(i_clk, i_d)  
  begin  
    if(i_clk = '1') then  
      o_q <= i_d;  
    else  
      o_q <= '0';  
    end if;  
  end process;  
end architecture;  
-----
```

note:

 - if a valid else statement is included then something other than a latch will be created



18236 Number of processors has not been specified which may cause overloading on shared machines. set the global assignment NUM_P
Quartus Prime Netlist Viewers Preprocess was successful. 0 errors, 1 warning

Flip-Flop HDL

- Warning – warning – warning
- Most (maybe all) of the times you do not complete an if-else a latch will be created
- **We do not want latches - EVER**



Flip-Flop HDL

- Flip-Flops are recognized by a pre-defined VHDL template

```
process (clock signal)
begin
  if(clock edge detection) then
    actions
  end if;
end process;
```

note:

- here the else is not required because the synthesizer recognizes the edge detection

- you can include an else for clarity

```
process (i_clk)
begin
  if(i_clk'event and i_clk = 1) then
    o_q <= i_d;
  end if;
end process;
```



```
process (i_clk)
begin
  if(rising_edge(i_clk)) then
    o_q <= i_d;
  end if;
end process;
```

2008 release

Flip-Flop HDL


Note rstb IS in the sensitivity list

- D-FF w/ asynchronous rstb

```
-----  
-- flops.vhdl  
--  
-- created: 1/26/18  
-- by: johnsontim  
-- rev: 0  
--  
-- file to synthesize flip-flops for lecture slides  
--  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
  
entity flops is  
  port(  
    i_clk: in std_logic;  
    i_d : in std_logic;  
    i_rstb: in std_logic;  
  
    o_q : out std_logic  
  );  
end entity flops;
```

```
-----  
-- flop generated-----  
architecture behavioral of flops is  
begin  
  process (i_clk, i_rstb)  
  begin  
    if (i_rstb = '0') then  
      o_q <= '0';  
    elsif (rising_edge(i_clk)) then  
      o_q <= i_d;  
    end if;  
  end process;  
end architecture;
```

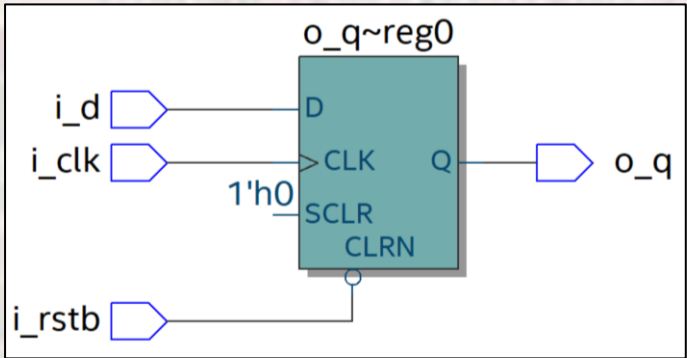Asynchronous inputs are outside the rising_edge



Most of our designs will use DFFs with an asynchronous reset


Flip-Flop HDL

Note rstb, set, and en are NOT in the sensitivity list

- D-FF w/ synchronous set, rstb, en

```
-----  
-- flops.vhdl  
-- created: 1/26/18  
-- by: johnsontim  
-- rev: 0  
-- file to synthesize flip-flops for lecture slides  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
  
entity flops is  
  port(  
    i_clk: in std_logic;  
    i_d : in std_logic;  
    i_set: in std_logic;  
    i_en: in std_logic;  
    i_rstb: in std_logic;  
  
    o_q : out std_logic  
  );  
end entity flops;
```
 
```
-- fancy flop generated-----  
architecture behavioral of flops is  
begin  
  process (i_clk)  
  begin  
    if (rising_edge(i_clk)) then  
      if (i_rstb = '0') then  
        o_q <= '0';  
      elsif (i_set = '1') then  
        o_q <= '1';  
      elsif (i_en = '1') then  
        o_q <= i_d;  
      end if;  
    end if;  
  end process;  
end architecture;
```



Synchronous inputs are inside the rising_edge

priority
rstb > set > en

Flip-Flop HDL

- Process concurrency

```
-----  
-- process_concurrency.vhd1  
-- created: 1/26/18  
-- by: johnsontim  
-- rev: 0  
-- file to show concurrency of processes  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
entity process_concurrency is  
  port(  
    i_clka: in std_logic;  
    i_clkb: in std_logic;  
    i_d1 : in std_logic;  
    i_d2 : in std_logic;  
    i_d3 : in std_logic;  
    i_rstb: in std_logic;  
  
    o_q1 : out std_logic;  
    o_q2 : out std_logic;  
    o_q3 : out std_logic  
  );  
end entity process_concurrency;
```

```
architecture behavioral of process_concurrency is  
begin  
  process (i_clka, i_rstb)  
  begin  
    if (i_rstb = '0') then  
      o_q1 <= '0';  
    elsif (rising_edge(i_clka)) then  
      o_q1 <= i_d1;  
    end if;  
  end process;  
  
  process (i_clka, i_rstb)  
  begin  
    if (i_rstb = '0') then  
      o_q2 <= '0';  
    elsif (rising_edge(i_clka)) then  
      o_q2 <= i_d2;  
    end if;  
  end process;  
  
  process (i_clkb, i_rstb)  
  begin  
    if (i_rstb = '0') then  
      o_q3 <= '0';  
    elsif (rising_edge(i_clkb)) then  
      o_q3 <= i_d3;  
    end if;  
  end process;  
end architecture;
```

