 


# Flip-Flop Timing Analysis

Last updated 2/14/21

# Flip-Flop Timing Analysis

- Typical Flip-Flop Circuit




- Need the data to get from point A to point B before the next clock edge occurs

# Flip-Flop Timing Analysis

- Flip-Flop Example

- $t_{PD\ INV} = 10ps$
- $t_{CQ} = 22ps$
- $t_{setup} = 4ps$
- $t_{hold} = 2ps$

All values already account for loading

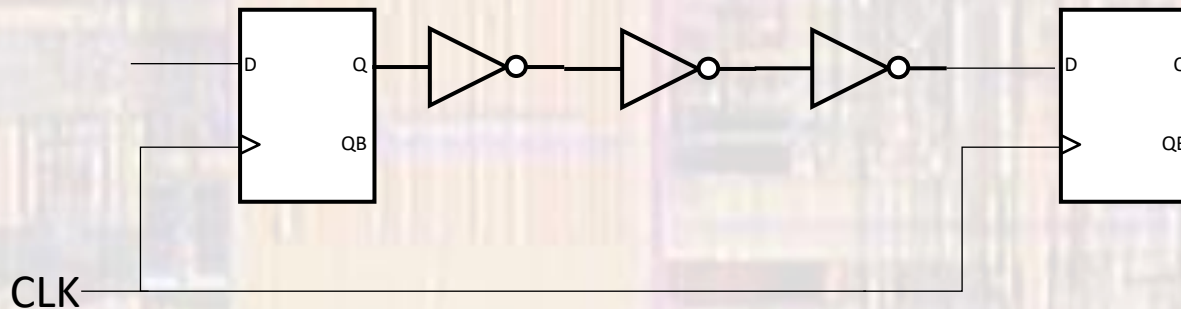


Shortest clock period  
Fastest clock speed



# Flip-Flop Timing Analysis

- Register Transfer Architecture
  - Timing

All values already account for loading

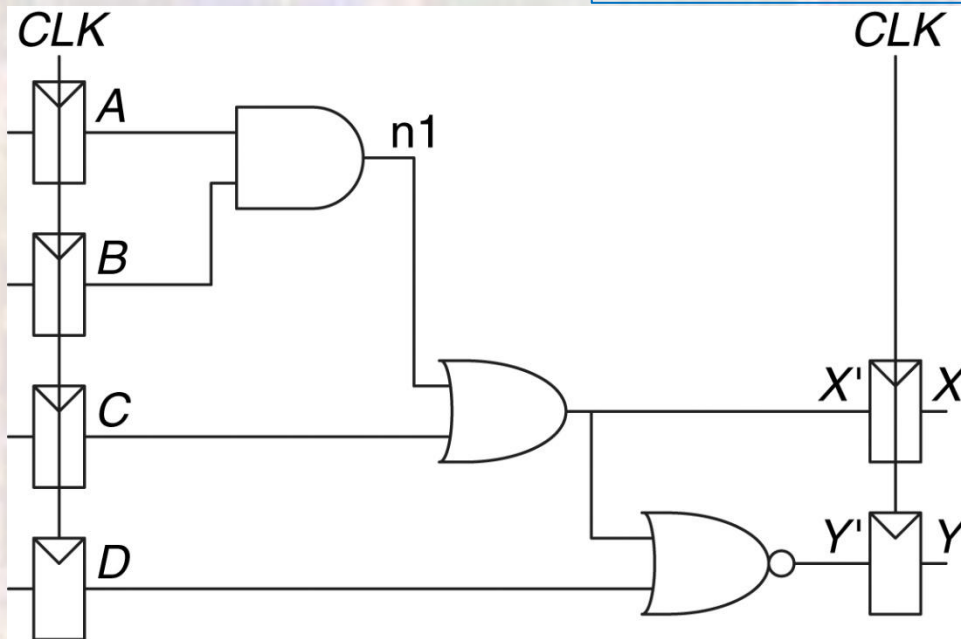

src: Harris & Harris

$$t_{CQ\_min} = 30ps$$

$$t_{CQ\_max} = 80ps$$

$$t_{setup} = 50ps$$

$$t_{hold} = 60ps$$



$$t_{pd\_min} \text{ Logic} = 25ps$$

$$t_{pd\_max} \text{ Logic} = 40ps$$

# Flip-Flop Timing Analysis

- Register Transfer Architecture
  - Timing

All values already account for loading

 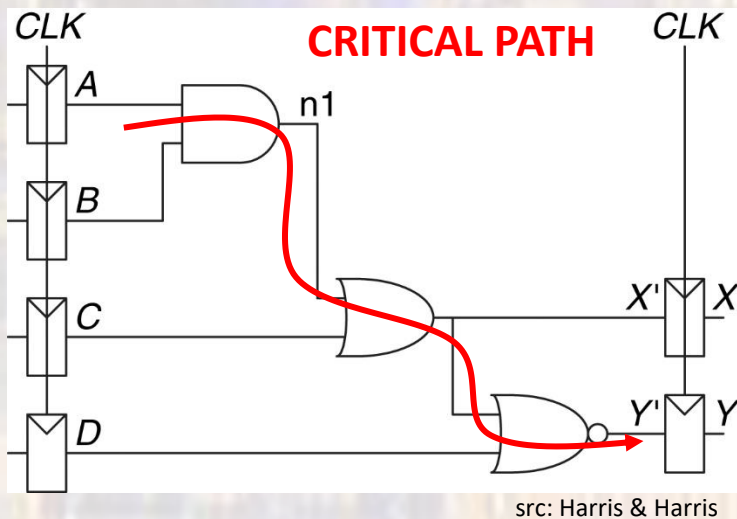

$$t_{CQ\_min} = 30ps$$

$$t_{CQ\_max} = 80ps$$

$$t_{setup} = 50ps$$

$$t_{hold} = 60ps$$

$$t_{pd\_min} \text{ Logic} = 25ps$$

$$t_{pd\_max} \text{ Logic} = 40ps$$

$$t_{crit} = t_{CQ\_max} + 3 * t_{pd\_max} + t_{setup}$$

$$t_{crit} = 80ps + 3 * 40ps + 50ps = 250ps$$


$$F_{max} = 1/250ps = 4GHz$$

# Flip-Flop Timing Analysis


- Register Transfer Architecture

- Timing

All values already account for loading

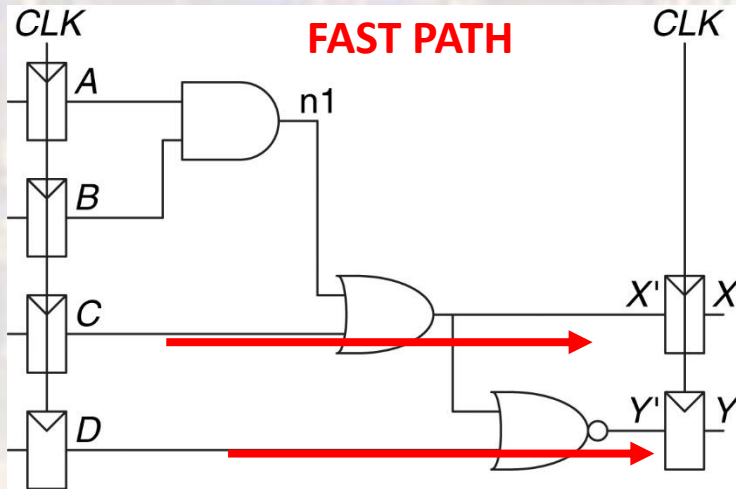

src: Harris & Harris

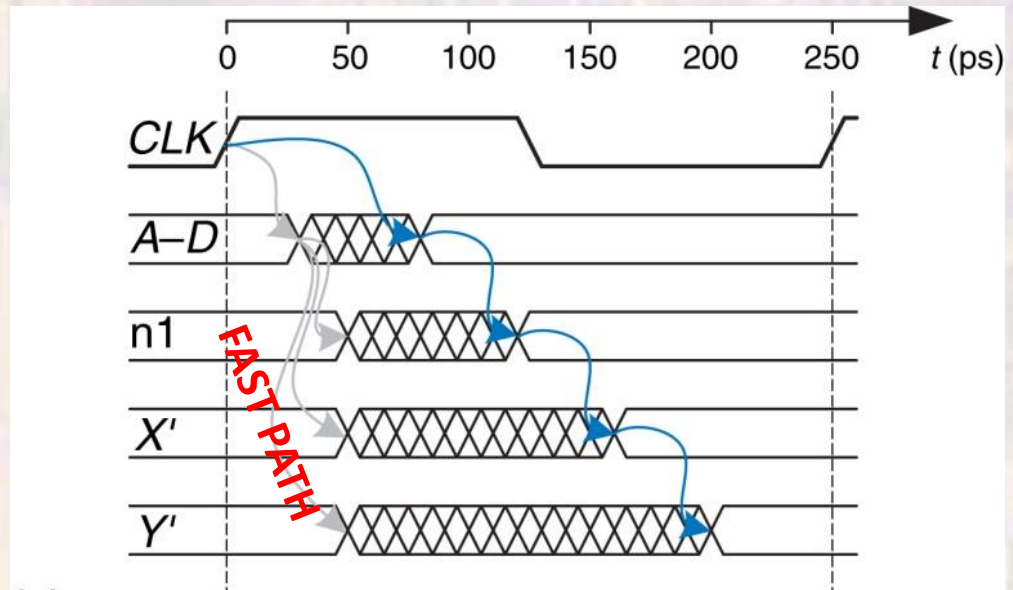

$$t_{CQ\_min} = 30ps$$

$$t_{CQ\_max} = 80ps$$

$$t_{setup} = 50ps$$

$$t_{hold} = 60ps$$

$$t_{pd\_min} \text{ Logic} = 25ps$$

$$t_{pd\_max} \text{ Logic} = 40ps$$

$$t'_{fast} = t_{CQ\_min} + t_{pd\_min}$$

$$t'_{fast} = 30ps + 25ps = 55ps$$


$$t'_{fast} < \text{hold time} \rightarrow \text{unpredictable output}$$

# Flip-Flop Timing Analysis


- Register Transfer Architecture

- Timing

All values already account for loading

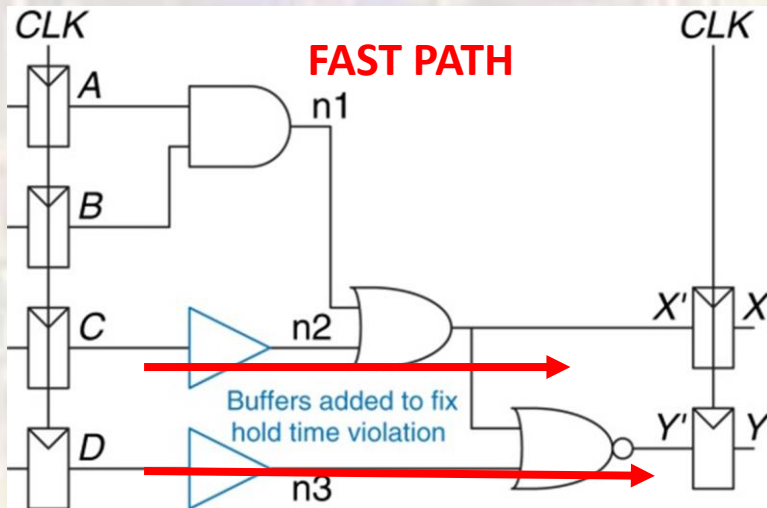

src: Harris & Harris

 

$$t_{CQ\_min} = 30ps$$

$$t_{CQ\_max} = 80ps$$

$$t_{setup} = 50ps$$

$$t_{hold} = 60ps$$

$$t_{pd\_min} \text{ Logic} = 25ps$$

$$t_{pd\_max} \text{ Logic} = 40ps$$

$$t'_{fast} = t_{CQ\_min} + 2 * t_{pd\_min}$$

$$t'_{fast} = 30ps + 2 * 25ps = 80ps$$

$$t'_{fast} > \text{hold time} \rightarrow \text{predictable output}$$

# Flip-Flop Timing Analysis

- Additional Timing Issues
  - Clock skew
    - Variation in clock edge arrival time
    - Due to path variations (capacitances)
    - Reduces maximum clock frequency
    - Can create hold time issues
  - Clock Gating
    - Creates clock skew




# Flip-Flop Timing Analysis

- Timing Verification
  - Static Timing Analysis
    - Testing for setup and hold violations
    - Check all paths
    - Estimate delays based on worst case assumptions
    - No specific input values are used
    - Logical operation IS NOT checked
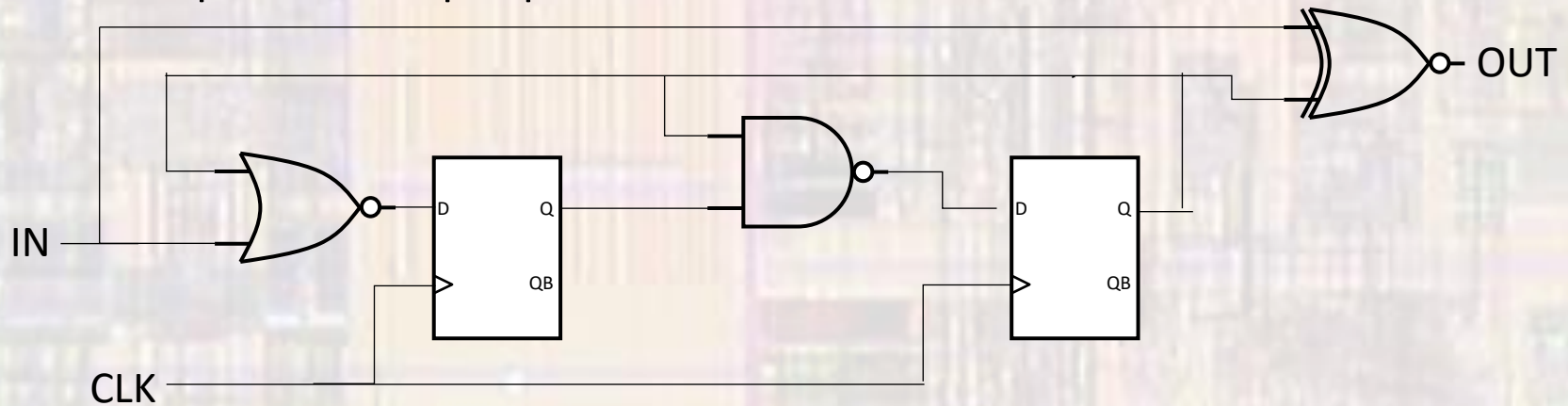
# Flip-Flop Timing Analysis


- Timing Verification
  - Static Timing Analysis Path
    - Input of source FlipFlop to Input of destination FlipFlop
    - Input and Output paths



How many static timing paths ?
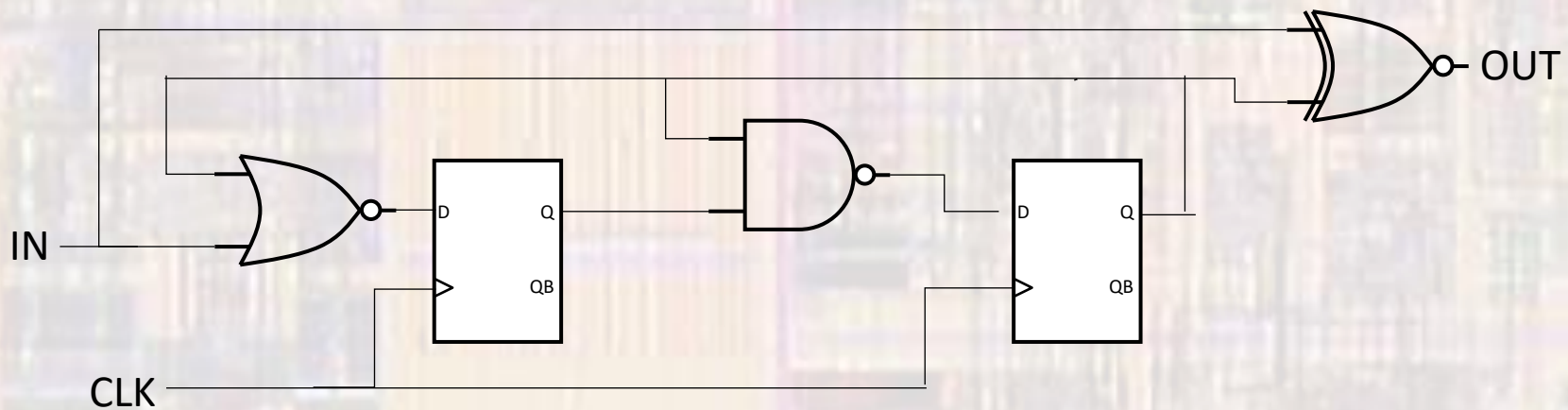
# Flip-Flop Timing Analysis

- Timing Verification
  - Static Timing Analysis Path
    - Input of source FlipFlop to Input of destination FlipFlop
    - Input and Output paths



IN to D1  
D1 to D2  
D2 to D2  
D2 to D1  
D2 to OUT  
IN to OUT

# Flip-Flop Timing Analysis

- Timing Verification
  - Static Timing Analysis Path
    - Input of source FlipFlop to Input of destination FlipFlop
    - Setup time violations
    - Hold time violations
    - Slack – gap between estimated time and violation