

FSMD Multiplier

Last updated 1/28/21

FSMD Multiplier

- Multiplication
 - Want a process that is repetitive
 - Repetitive addition multiplication

$5 \times 4 = 5 + 5 + 5 + 5$ i.e. the **multiplicand** added the **multiplier** times

- Requires integers – or non-fractional binary numbers for the multiplier

FSMD Multiplier


- Multiplication
 - Must sign extend to sum of # bits

$$\begin{array}{r} 1110 \\ \times 0011 \\ \hline \end{array} \quad \Rightarrow \quad \begin{array}{r} 11111110 \\ \times 00000011 \\ \hline \end{array}$$

$$\begin{array}{r} 11111110 \\ \times 00000011 \\ \hline 11111110 \\ 11111110 \\ 00000000 \\ 00000000 \\ 00000000 \\ 00000000 \\ 00000000 \\ 00000000 \\ \hline 11111010 \end{array}$$


FSMD Multiplier

- Multiplier

 

FSMD Multiplier


- Multiplier – ASM
- Control Path

 

FSMD Multiplier


- Multiplier – ASM

- Data Path

 

FSMD Multiplier

- Multiplier – ASM

 

FSMD Multiplier

- Multiplier - FSM

```
-----  
-- mult_rep_add_4bit_fsm.vhdl  
--  
-- created 9/12/18  
-- tj  
-- rev 0  
-----  
--  
-- FSM for repetitive addition multiplier  
-- tells the datapath when to calculate (calc) and uses  
-- done from the datapath to know its complete  
-----  
--  
-- Inputs: rstb, clk, startb, done  
-- Outputs: calc, complete  
--  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
  
entity mult_rep_add_4bit_fsm is  
  port (  
    i_clk          : in std_logic;  
    i_rstb         : in std_logic;  
    i_startb       : in std_logic;  
    i_done         : in std_logic;  
  
    o_calc         : out std_logic;  
    o_complete     : out std_logic  
  );  
end entity;
```

```
architecture behavioral of mult_rep_add_4bit_fsm is  
  --  
  -- State Types  
  --  
  type STATE_TYPE is (Idle, Run, Finish);  
  signal state:      STATE_TYPE;  
  signal state_next: STATE_TYPE;  
  
begin  
  --  
  -- next state logic  
  --  
  process(all)  
  begin  
    case state is  
      when Idle=>  
        if(i_startb = '0') then  
          state_next <= Run;  
        else  
          state_next <= Idle;  
        end if;  
      when Run =>  
        if(i_done = '1') then  
          state_next <= Finish;  
        else  
          state_next <= Run;  
        end if;  
      when Finish =>  
        state_next <= Idle;  
    end case;  
  end process;
```

FSMD Multiplier

- Multiplier - FSM

```
--  
-- State Register logic  
--  
process(i_clk, i_rstb)  
begin  
    -- reset  
    if (i_rstb = '0') then  
        state <= Idle;  
    -- rising clk edge  
    elsif (rising_edge(i_clk)) then  
        state <= state_next;  
    end if;  
end process;
```

```
--  
-- output logic  
--  
process(all)  
begin  
    case state is  
        when Idle=>  
            o_complete <= '1';  
            o_calc <= '0';  
        when Run =>  
            o_complete <= '0';  
            o_calc <= '1';  
        when Finish =>  
            o_complete <= '1';  
            o_calc <= '0';  
    end case;  
end process;  
end behavioral;
```

FSMD Multiplier

- Multiplier – Data path

```
-----  
-- mult_rep_add_4bit_datapath.vhdl  
-- created 9/12/18  
-- tj  
-- rev 0  
-----  
-- Data Path for repetitive addition multiplier  
-- adds the multiplicand multiplier number of times  
-----  
-- Inputs: clk, start, multiplicand, multiplier  
-- Outputs: result, complete  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
entity mult_rep_add_4bit_datapath is  
  port (  
    i_clk      : in std_logic;  
    i_multiplicand : in std_logic_vector(3 downto 0);  
    i_multiplier : in std_logic_vector(3 downto 0);  
    i_calc     : in std_logic;  
  
    o_result : out std_logic_vector(7 downto 0);  
    o_done   : out std_logic  
  );  
end entity;
```

```
architecture behavioral of mult_rep_add_4bit_datapath is  
  -- structural signals  
  signal multiplicand_sig: unsigned(3 downto 0);  
  signal multiplier_sig:  unsigned(3 downto 0);  
  signal multiplier_sig_next: unsigned(3 downto 0);  
  signal result_sig:      unsigned(7 downto 0);  
  signal result_sig_next: unsigned(7 downto 0);  
  signal zero_fill:       unsigned(7 downto 0);  
  
begin  
  -- datapath registers  
  process(i_clk)  
  begin  
    if (rising_edge(i_clk)) then  
      if(i_calc = '0') then  
        multiplicand_sig <= unsigned(i_multiplicand);  
        multiplier_sig <= unsigned(i_multiplier);  
        result_sig <= (others => '0'); --result_sig;  
      else  
        multiplicand_sig <= unsigned(i_multiplicand);  
        multiplier_sig <= multiplier_sig_next;  
        result_sig <= result_sig_next;  
      end if;  
    end if;  
  end process;
```

FSMD Multiplier

- Multiplier – Data path

```
--  
-- next state logic  
--  
process(all)  
begin  
    if(multiplier_sig = 0) then  
        multiplier_sig_next <= multiplier_sig;  
        result_sig_next <= result_sig;  
        o_done <= '1';  
    else  
        multiplier_sig_next <= multiplier_sig - 1;  
        result_sig_next <= ("0000" & multiplicand_sig) + result_sig;  
        o_done <= '0';  
    end if;  
end process;  
  
--  
-- output logic  
--  
o_result <= std_logic_vector(result_sig);  
end behavioral;
```

FSMD Multiplier

- Multiplier – FSMD

```
-----  
-- mult_rep_add_4bit_fsmd.vhdl  
-- created 9/7/18  
-- tj  
-- rev 0  
-----  
--  
-- FSMD for repetitive addition multiplier  
-- adds the multiplicand multiplier number of times  
-----  
--  
-- Inputs: rstb, clk, start, multiplicand, multiplier  
-- Outputs: result, complete  
--  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
  
entity mult_rep_add_4bit_fsmd is  
  port (  
    i_clk          : in std_logic;  
    i_rstb         : in std_logic;  
    i_startb       : in std_logic;  
    i_multiplicand : in std_logic_vector(3 downto 0);  
    i_multiplier   : in std_logic_vector(3 downto 0);  
  
    o_result_latched : out std_logic_vector(7 downto 0);  
    o_complete       : out std_logic  
  );  
end entity;
```

```
architecture behavioral of mult_rep_add_4bit_fsmd is  
  -- structural signals  
  --  
  signal calc:          std_logic;  
  signal done:          std_logic;  
  signal complete_sig:  std_logic;  
  signal result:        std_logic_vector(7 downto 0);  
  
  -----  
  -- Component prototype  
  -----  
  COMPONENT mult_rep_add_4bit_fsm  
  PORT(  
    i_clk      : IN STD_LOGIC;  
    i_rstb     : IN STD_LOGIC;  
    i_startb   : IN STD_LOGIC;  
    i_done     : IN STD_LOGIC;  
    o_calc     : OUT STD_LOGIC;  
    o_complete : OUT STD_LOGIC  
  );  
END COMPONENT;  
  
  COMPONENT mult_rep_add_4bit_datapath  
  port (  
    i_clk          : in std_logic;  
    i_calc         : in std_logic;  
    i_multiplicand : in std_logic_vector(3 downto 0);  
    i_multiplier   : in std_logic_vector(3 downto 0);  
  
    o_done         : out std_logic;  
    o_result       : out std_logic_vector(7 downto 0)  
  );  
END COMPONENT;
```





FSMD Multiplier

- Multiplier – FSMD

```
-----  
-- Device instantiations  
-----  
fsm: mult_rep_add_4bit_fsm  
  port map(  
    i_clk      => i_clk,  
    i_rstb    => i_rstb,  
    i_startb  => i_startb,  
    i_done    => done,  
    o_calc    => calc,  
    o_complete => complete_sig  
  );  
  
datapath: mult_rep_add_4bit_datapath  
  port map(  
    i_clk      => i_clk,  
    i_calc     => calc,  
    i_multiplicand => i_multiplicand,  
    i_multiplier => i_multiplier,  
    o_done     => done,  
    o_result   => result  
  );  
  
--  
-- latch the result so it doesnt reset  
--  
process(i_clk)  
begin  
  if(rising_edge(i_clk)) then  
    if (complete_sig = '0') then  
      o_result_latched <= result;  
    end if;  
  end if;  
end process;  
  
--  
-- output logic  
--  
o_complete <= complete_sig;  
end behavioral;
```

FSMD Multiplier

- RTL

  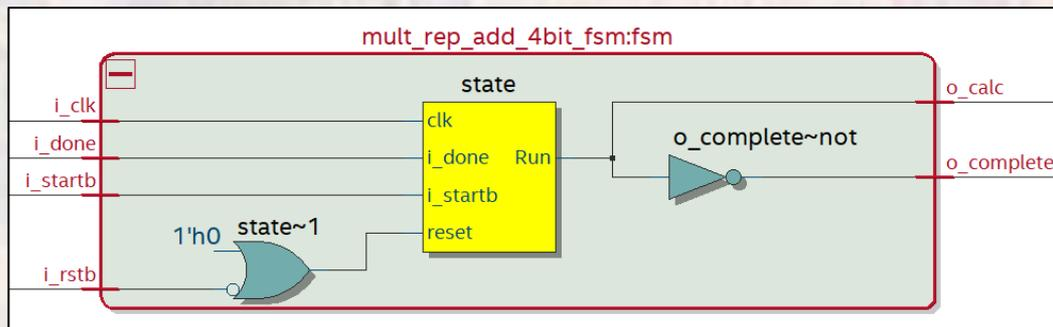 

FSMD Multiplier

- Verification

Results and intermediate values



Note: Takes “multiplier” number of clock cycles
Takes a variable number of clock cycles