

HDL FSM Examples


Last updated 1/22/21

State Machine Intro

- These slides present VHDL FSM examples using enumerated states

HDL FSM Examples

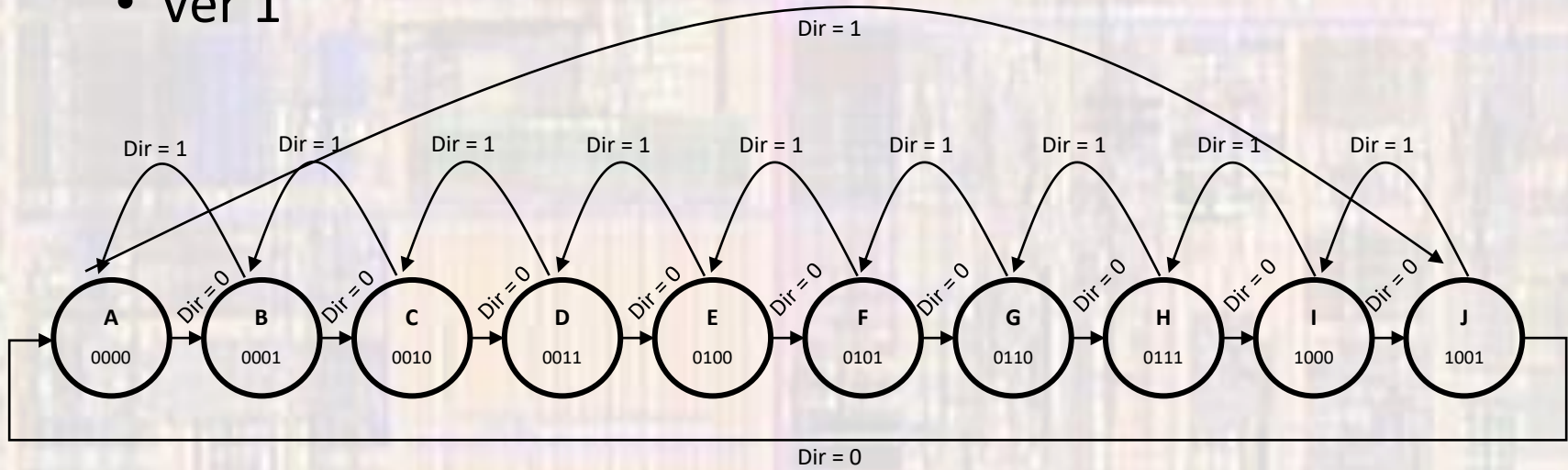- Mod 10 u/d Counter – Enumerated States
 - Ver 1



Note: this is for illustrative purpose - we would never make a counting state machine like this

HDL FSM Examples

- Mod 10 u/d Counter – Enumerated States
 - Ver 1


```
-----  
-- counter_mod10_ud_fsm.vhd1  
-- created 3/30/18  
-- tj  
-- rev 0  
-----  
-- mod 10 up/dn-counter - state machine with case statement  
-- enumerated states  
-----  
-- Inputs: i_rstb, i_clk, i_dir (0=up)  
-- Outputs: o_cnt[3:0]  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
entity counter_mod10_ud_fsm is  
  port (  
    i_clk : in std_logic;  
    i_rstb : in std_logic;  
    i_dir : in std_logic;  
    o_cnt : out std_logic_vector(3 downto 0)  
  );  
end entity;
```

```
architecture behavioral of counter_mod10_ud_fsm is  
  -- internal signals  
  type STATE_TYPE is (A, B, C, D, E, F, G, H, I, J);  
  signal state : STATE_TYPE;  
  signal state_next : STATE_TYPE;  
begin  
  -- next state logic  
  process(all)  
  begin  
    if(i_dir = '0') then  
      case state is  
        when A => state_next <= B;  
        when B => state_next <= C;  
        when C => state_next <= D;  
        when D => state_next <= E;  
        when E => state_next <= F;  
        when F => state_next <= G;  
        when G => state_next <= H;  
        when H => state_next <= I;  
        when I => state_next <= J;  
        when J => state_next <= A;  
        when others => state_next <= A;  
      end case;  
    else  
      case state is  
        when A => state_next <= J;  
        when B => state_next <= A;  
        when C => state_next <= B;  
        when D => state_next <= C;  
        when E => state_next <= D;  
        when F => state_next <= E;  
        when G => state_next <= F;  
        when H => state_next <= G;  
        when I => state_next <= H;  
        when J => state_next <= I;  
        when others => state_next <= A;  
      end case;  
    end if;  
  end process;
```

```
-- Register Logic  
process(i_clk, i_rstb)  
begin  
  -- reset  
  if (i_rstb = '0') then  
    state <= A;  
  -- rising i_clk edge  
  elsif (rising_edge(i_clk)) then  
    state <= state_next;  
  end if;  
end process;  
  
-- output logic  
process(all)  
begin  
  case state is  
    when A => o_cnt <= "0000";  
    when B => o_cnt <= "0001";  
    when C => o_cnt <= "0010";  
    when D => o_cnt <= "0011";  
    when E => o_cnt <= "0100";  
    when F => o_cnt <= "0101";  
    when G => o_cnt <= "0110";  
    when H => o_cnt <= "0111";  
    when I => o_cnt <= "1000";  
    when J => o_cnt <= "1001";  
    when others => o_cnt <= "0000";  
  end case;  
end process;  
end behavioral;
```

HDL FSM Examples


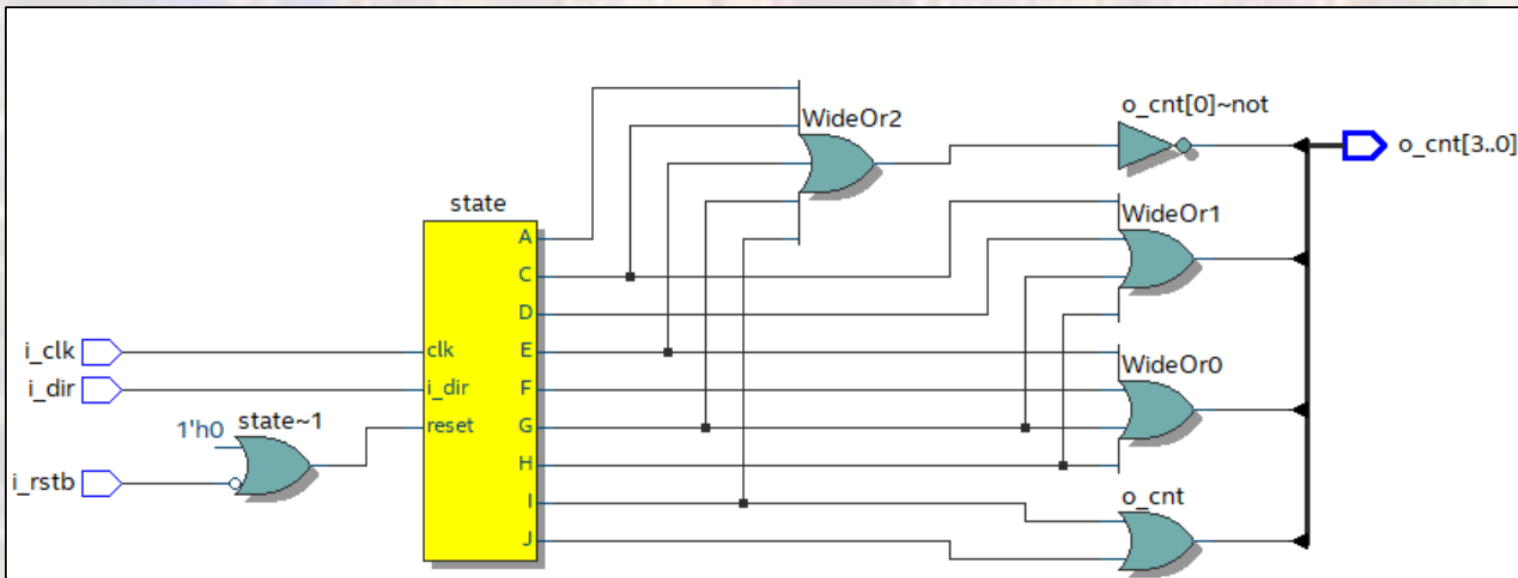
- Mod 10 u/d Counter – Enumerated States
 - Ver 1



Quartus recognized part of the code
as a state machine


HDL FSM Examples

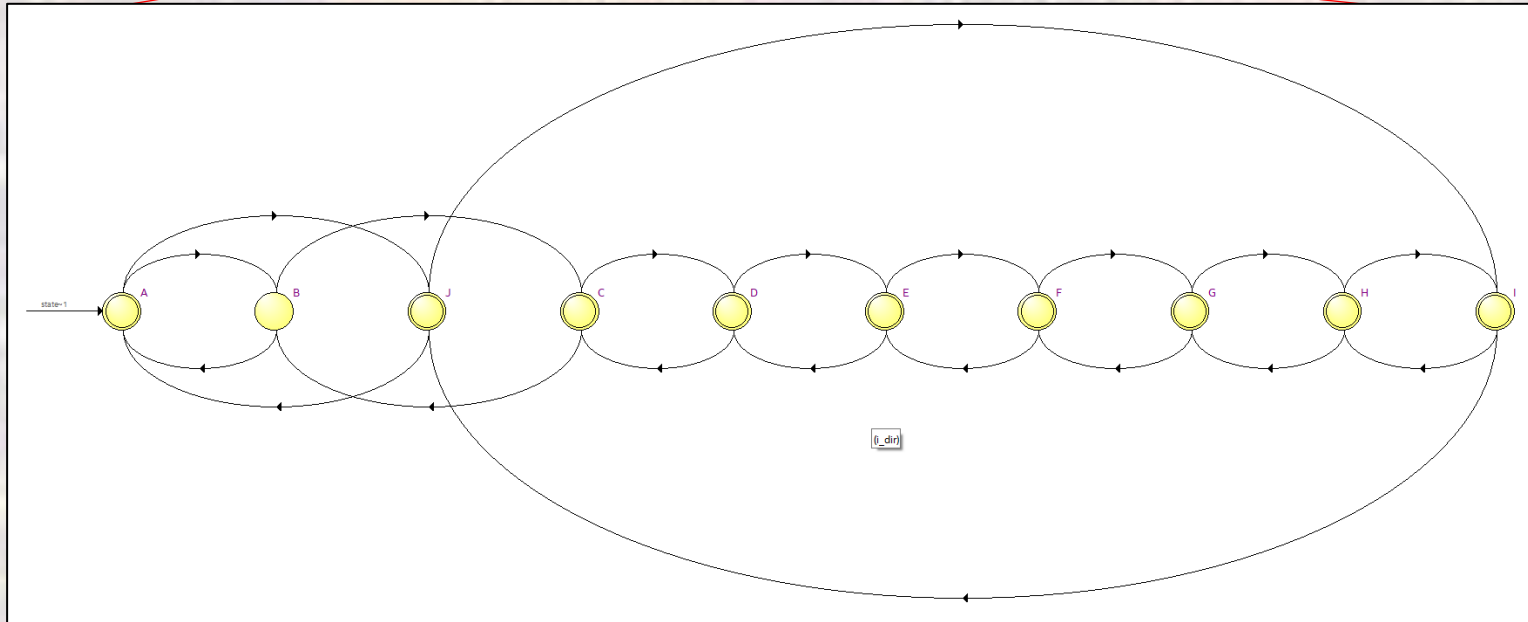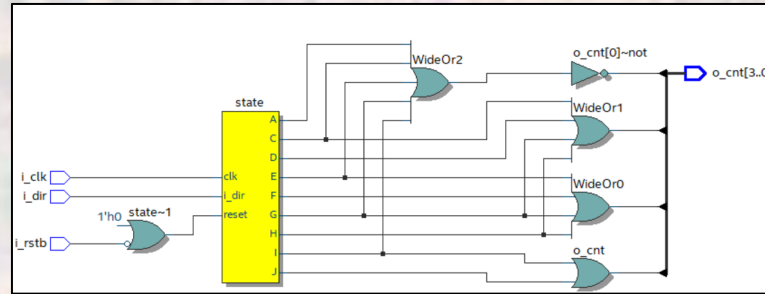- Mod 10 u/d Counter – Enumerated States
 - Ver 1



HDL FSM Examples

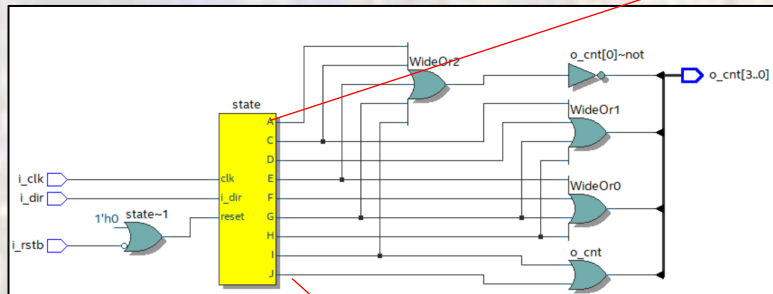- Mod 10 u/d Counter – Enumerated States
 - Ver 1




	Source State	Destination State	Condition
1	A	J	(dir)
2	A	B	(!dir)
3	B	C	(!dir)
4	B	A	(dir)
5	C	D	(!dir)
6	C	B	(dir)
7	D	E	(!dir)
8	D	C	(dir)
9	E	F	(!dir)
10	E	D	(dir)
11	F	G	(!dir)
12	F	E	(dir)
13	G	H	(!dir)
14	G	F	(dir)
15	H	I	(!dir)
16	H	G	(dir)
17	I	J	(!dir)
18	I	H	(dir)
19	J	I	(dir)
20	J	A	(!dir)

Transitions / Encoding

HDL FSM Examples

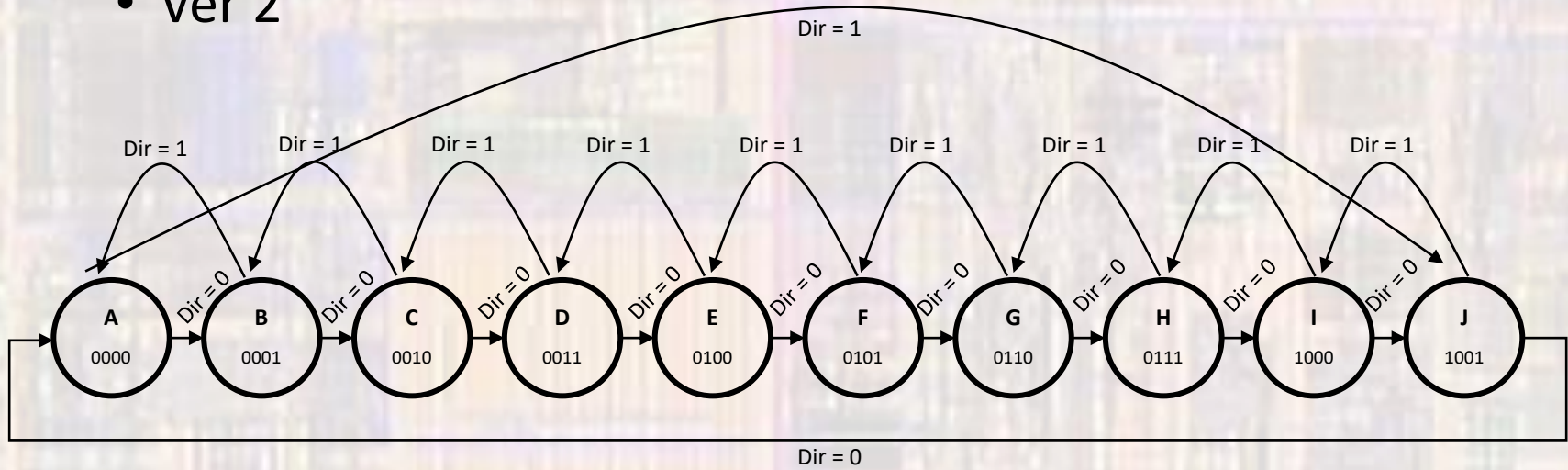- Mod 10 u/d Counter – Enumerated States
 - Ver 2



Note: this is for illustrative purpose - we would never make a counting state machine like this

HDL FSM Examples

- Mod 10 u/d Counter –
- Ver 2

```
-----  
-- counter_mod10_ud_fsmA.vhdl  
-- created 3/30/18  
-- tj  
-- rev 0  
-----  
-- mod 10 up/dn-counter - state machine with case statement  
-- enumerated states  
-----  
-- Inputs: i_rstb, i_clk, i_dir(0=up)  
-- Outputs: o_cnt[3:0]  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
entity counter_mod10_ud_fsmA is  
  port (  
    i_clk : in std_logic;  
    i_rstb : in std_logic;  
    i_dir : in std_logic;  
  
    o_cnt : out std_logic_vector(3 downto 0)  
  );  
end entity;  
architecture behavioral of counter_mod10_ud_fsmA is  
  --  
  -- internal signals  
  --  
  type STATE_TYPE is (A, B, C, D, E, F, G, H, I, J);  
  signal state: STATE_TYPE;  
  signal state_next: STATE_TYPE;  
begin
```


```
--  
-- next state logic  
--  
process(all)  
begin  
  case state is  
    when A =>  
      if(i_dir = '0') then  
        state_next <= B;  
      else  
        state_next <= J;  
      end if;  
    when B =>  
      if(i_dir = '0') then  
        state_next <= C;  
      else  
        state_next <= A;  
      end if;  
    when C =>  
      if(i_dir = '0') then  
        state_next <= D;  
      else  
        state_next <= B;  
      end if;  
    when D =>  
      if(i_dir = '0') then  
        state_next <= E;  
      else  
        state_next <= C;  
      end if;  
    when E =>  
      if(i_dir = '0') then  
        state_next <= F;  
      else  
        state_next <= D;  
      end if;  
    when F =>  
      if(i_dir = '0') then  
        state_next <= G;  
      else  
        state_next <= E;  
      end if;  
    when G =>  
      if(i_dir = '0') then  
        state_next <= H;  
      else  
        state_next <= F;  
      end if;  
    when H =>  
      if(i_dir = '0') then  
        state_next <= I;  
      else  
        state_next <= G;  
      end if;  
    when I =>  
      if(i_dir = '0') then  
        state_next <= J;  
      else  
        state_next <= H;  
      end if;  
    when J =>  
      if(i_dir = '0') then  
        state_next <= A;  
      else  
        state_next <= I;  
      end if;  
    when others =>  
      state_next <= A;  
  end case;  
end process;
```

and States

```
--  
-- Register logic  
--  
process(i_clk, i_rstb)  
begin  
  -- reset  
  if (i_rstb = '0') then  
    state <= A;  
  -- rising i_clk edge  
  elsif (rising_edge(i_clk)) then  
    state <= state_next;  
  end if;  
end process;  
--  
-- Output logic  
--  
process(all)  
begin  
  case state is  
    when A => o_cnt <= "0000";  
    when B => o_cnt <= "0001";  
    when C => o_cnt <= "0010";  
    when D => o_cnt <= "0011";  
    when E => o_cnt <= "0100";  
    when F => o_cnt <= "0101";  
    when G => o_cnt <= "0110";  
    when H => o_cnt <= "0111";  
    when I => o_cnt <= "1000";  
    when J => o_cnt <= "1001";  
    when others => o_cnt <= "0000";  
  end case;  
end process;  
end behavioral;
```

HDL FSM Examples

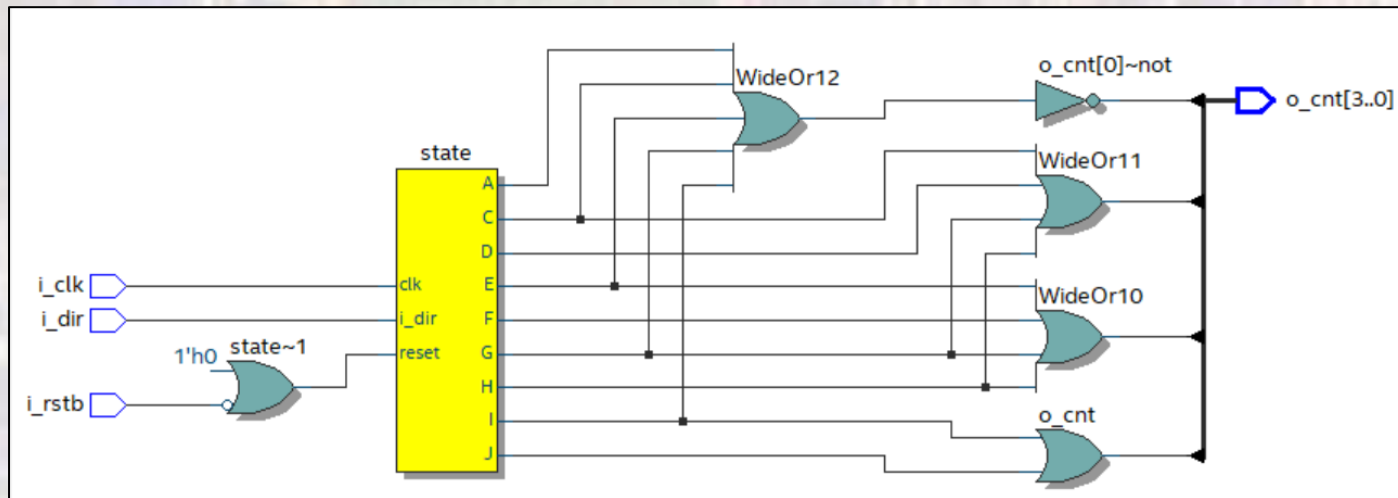
- Mod 10 u/d Counter – Enumerated States
 - Ver 2



Quartus recognized part of the code
as a state machine

HDL FSM Examples

- Priority Stoplight - revisited

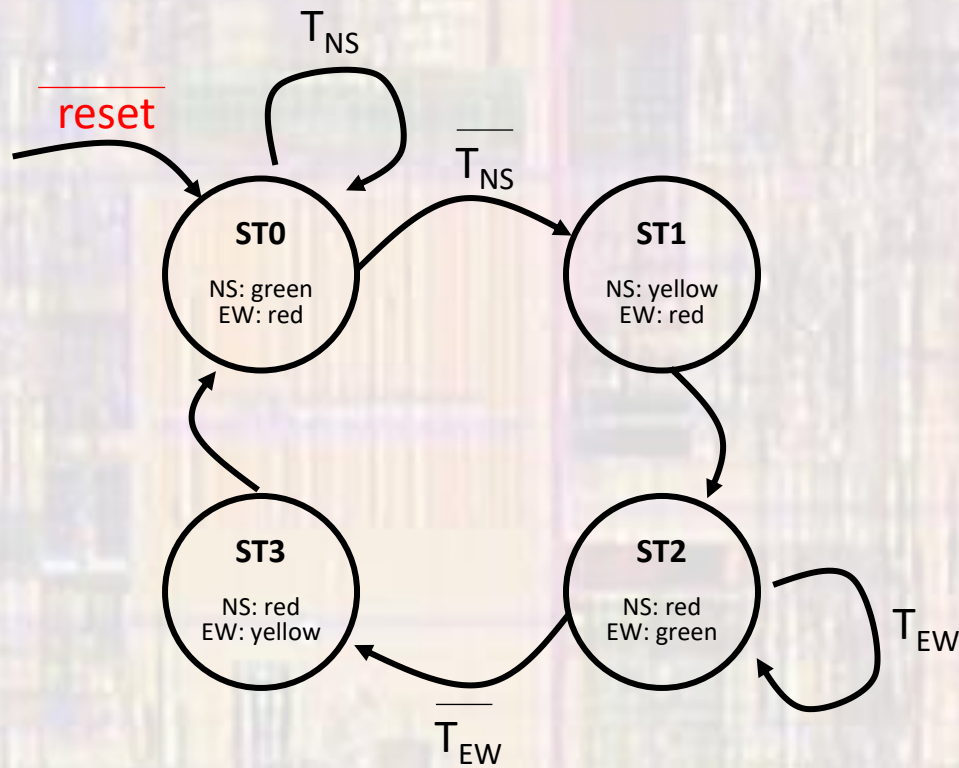

HDL FSM Examples

- Priority Stoplight - revisited


```
-----  
-- stoplight_nsew_fsm.vhdl  
-- created 3/30/18  
-- tj  
-- rev 0  
-----  
-- NS/EW stoplight  
-----  
-- Inputs: i_rstb, i_clk, i_tns, i_tew  
-- Outputs: oLights_ew, oLights_ns  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
entity stoplight_nsew_fsm is  
    port (  
        i_clk : in std_logic;  
        i_rstb : in std_logic;  
        i_tns : in std_logic;  
        i_tew : in std_logic;  
  
        oLights_ns : out std_logic_vector(1 downto 0);  
        oLights_ew : out std_logic_vector(1 downto 0)  
    );  
end entity;
```

```
architecture behavioral of stoplight_nsew_fsm is  
    -- internal signals  
    --  
    type STATE_TYPE is (ST0, ST1, ST2, ST3);  
    signal state: STATE_TYPE;  
    signal state_next: STATE_TYPE;  
    --  
    constant green: std_logic_vector := "00";  
    constant yellow: std_logic_vector := "01";  
    constant red: std_logic_vector := "10";  
begin  
    -- next state logic  
    process(all)  
    begin  
        case state is  
            when ST0 =>  
                if(i_tns = '1') then  
                    state_next <= ST0;  
                else  
                    state_next <= ST1;  
                end if;  
  
            when ST1 =>  
                state_next <= ST2;  
  
            when ST2 =>  
                if(i_tew = '1') then  
                    state_next <= ST2;  
                else  
                    state_next <= ST3;  
                end if;  
  
            when ST3 =>  
                state_next <= ST0;  
        end case;  
    end process;
```

```
-- Register logic  
--  
process(i_clk, i_rstb)  
begin  
    -- reset  
    if (i_rstb = '0') then  
        state <= ST0;  
    -- rising clk edge  
    elsif (rising_edge(i_clk)) then  
        state <= state_next;  
    end if;  
end process;  
  
-- Output logic  
--  
process(all)  
begin  
    case state is  
        when ST0 =>  
            oLights_ns <= green;  
            oLights_ew <= red;  
        when ST1 =>  
            oLights_ns <= yellow;  
            oLights_ew <= red;  
        when ST2 =>  
            oLights_ns <= red;  
            oLights_ew <= green;  
        when ST3 =>  
            oLights_ns <= red;  
            oLights_ew <= yellow;  
        end case;  
    end process;  
end behavioral;
```


HDL FSM Examples

- Priority Stoplight - revisited

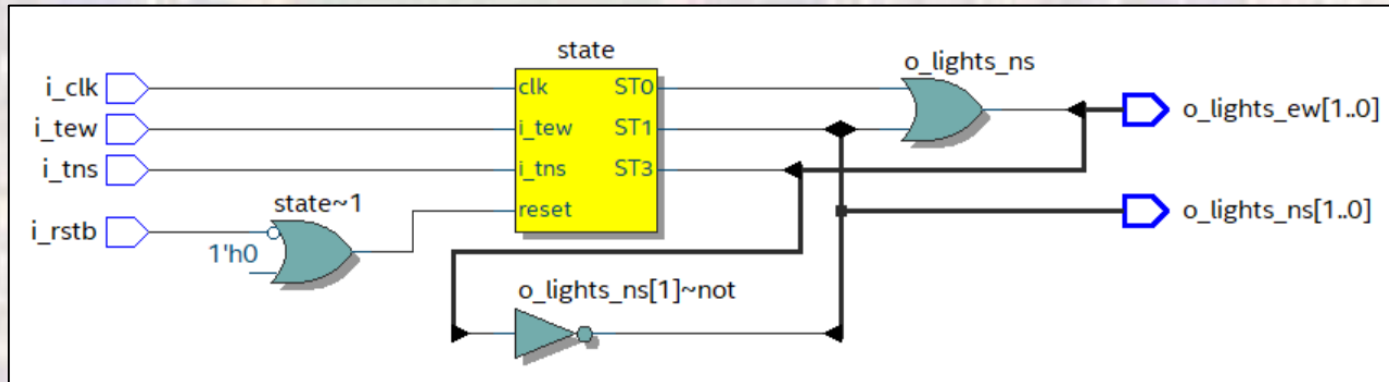



HDL FSM Examples

- Priority Stoplight - revisited

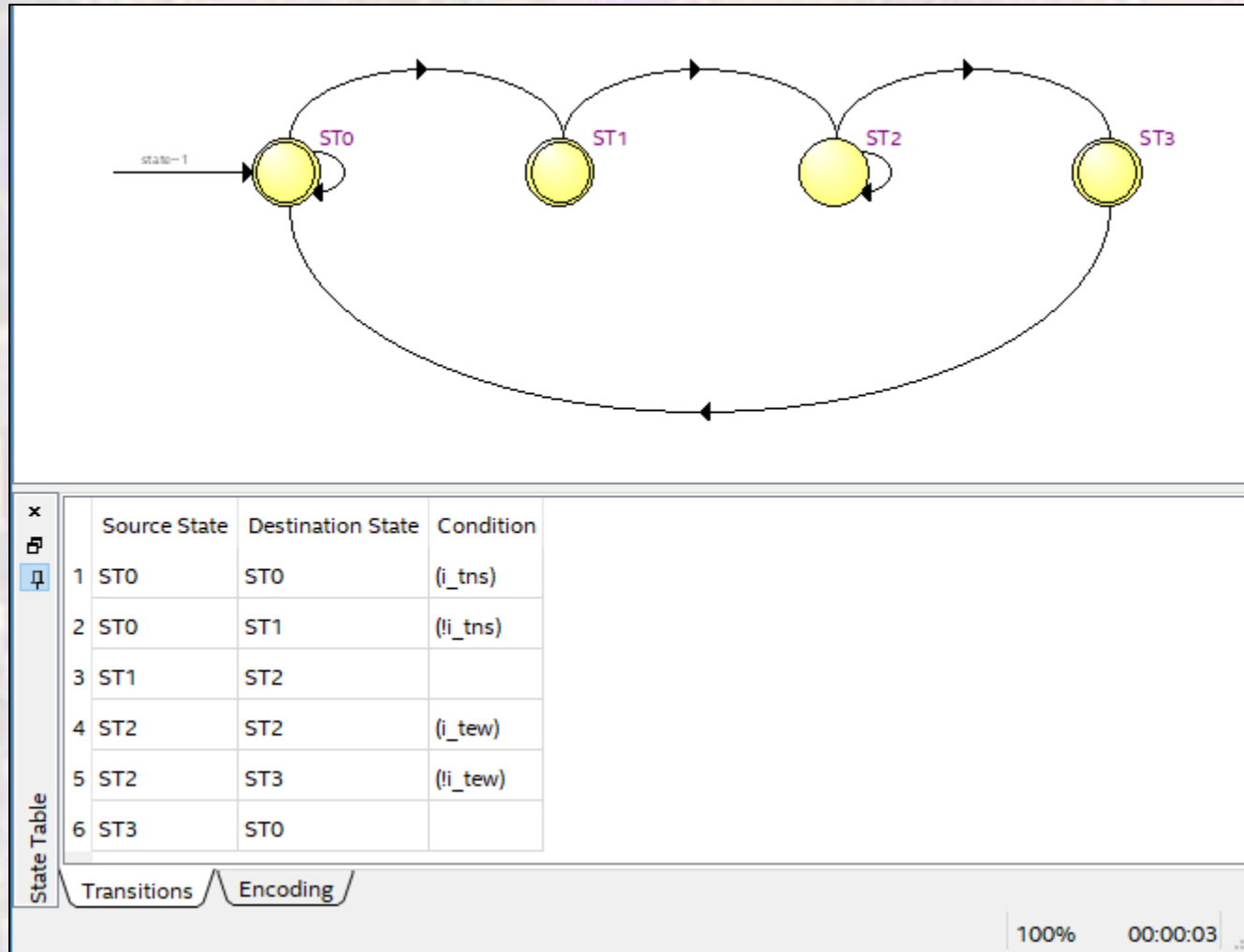


HDL FSM Examples

- Priority Stoplight - revisited

 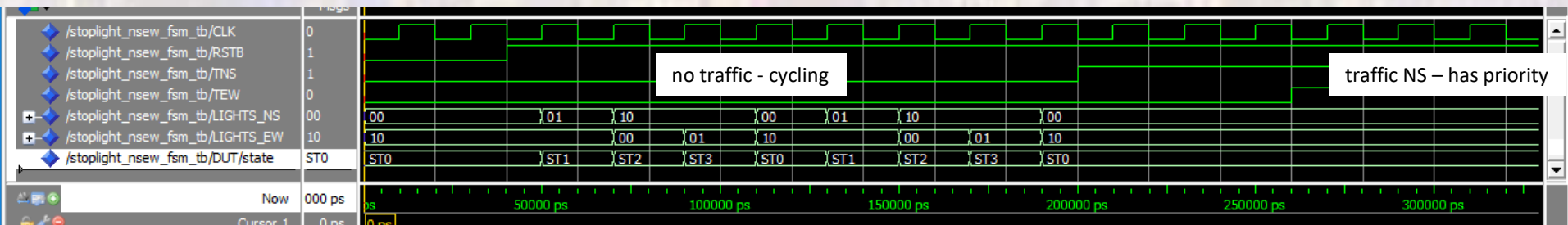

HDL FSM Examples

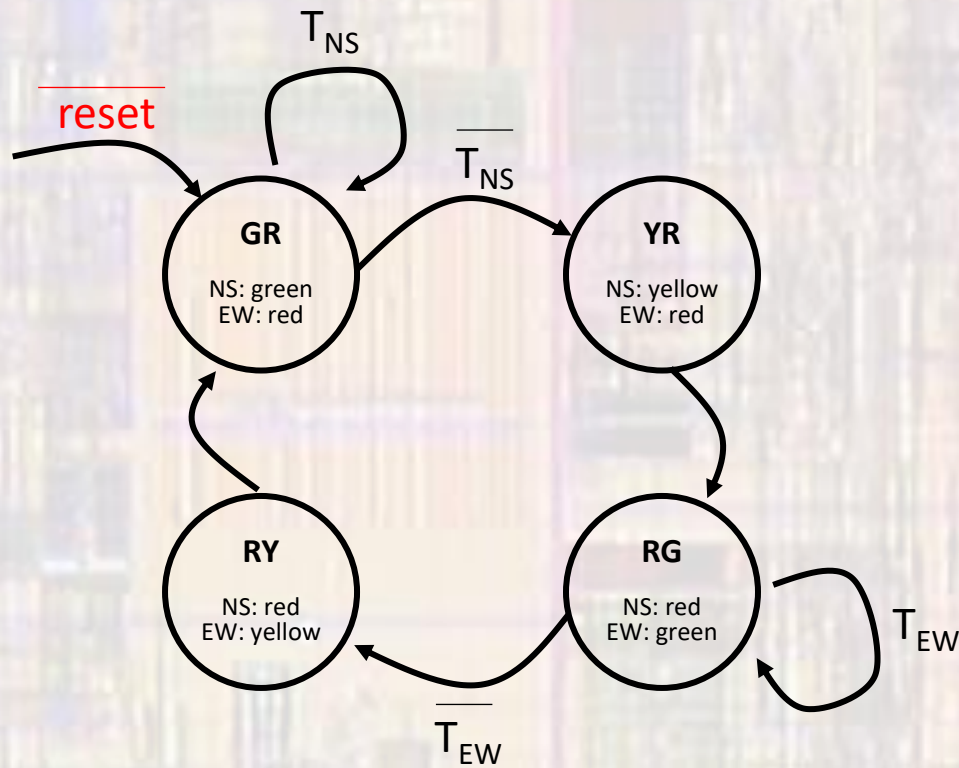- Priority Stoplight – revisited - revisited



HDL FSM Examples

- Priority Stoplight – revisited - revisited


```
-----  
-- stoplight_nsew_fsm2.vhd1  
-- created 3/30/18  
-- tj  
-- rev 0  
-----  
-- NS/EW Stoplight with o_lights enumerated  
-----  
-- Inputs: i_rstb, i_clk, i_tns, i_tew  
-- Outputs: o_lights_ew, o_lights_ns  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
entity stoplight_nsew_fsm2 is  
  port (  
    i_clk : in std_logic;  
    i_rstb : in std_logic;  
    i_tns : in std_logic;  
    i_tew : in std_logic;  
  
    o_lights_ns : out std_logic_vector(1 downto 0);  
    o_lights_ew : out std_logic_vector(1 downto 0)  
  );  
end entity;
```

```
architecture behavioral of stoplight_nsew_fsm2 is  
  -- internal signals  
  type STATE_TYPE is (GR, YR, RG, RY);  
  signal state : STATE_TYPE;  
  signal state_next : STATE_TYPE;  
  
  type LIGHT is (G, Y, R);  
  signal light_ns : LIGHT;  
  signal light_ew : LIGHT;  
  
begin  
  -- next state logic  
  process(all)  
  begin  
    case state is  
      when GR =>  
        if(i_tns = '1') then  
          state_next <= GR;  
        else  
          state_next <= YR;  
        end if;  
      when YR =>  
        state_next <= RG;  
      when RG =>  
        if(i_tew = '1') then  
          state_next <= RG;  
        else  
          state_next <= RY;  
        end if;  
      when RY =>  
        state_next <= GR;  
    end case;  
    state_next <= GR;  
  end process;
```

```
  -- Register logic  
  process(i_clk, i_rstb)  
  begin  
    -- reset  
    if (i_rstb = '0') then  
      state <= GR;  
    -- rising clk edge  
    elsif (rising_edge(i_clk)) then  
      state <= state_next;  
    end if;  
  end process;  
  
  -- Output logic  
  process(all)  
  begin  
    case state is  
      when GR =>  
        light_ns <= G;  
        light_ew <= R;  
      when YR =>  
        light_ns <= Y;  
        light_ew <= R;  
      when RG =>  
        light_ns <= R;  
        light_ew <= G;  
      when RY =>  
        light_ns <= R;  
        light_ew <= Y;  
    end case;  
  end process;  
  o_lights_ns <= std_logic_vector(to_unsigned(LIGHT'pos(light_ns), 2));  
  o_lights_ew <= std_logic_vector(to_unsigned(LIGHT'pos(light_ew), 2));  
end behavioral;
```


HDL FSM Examples

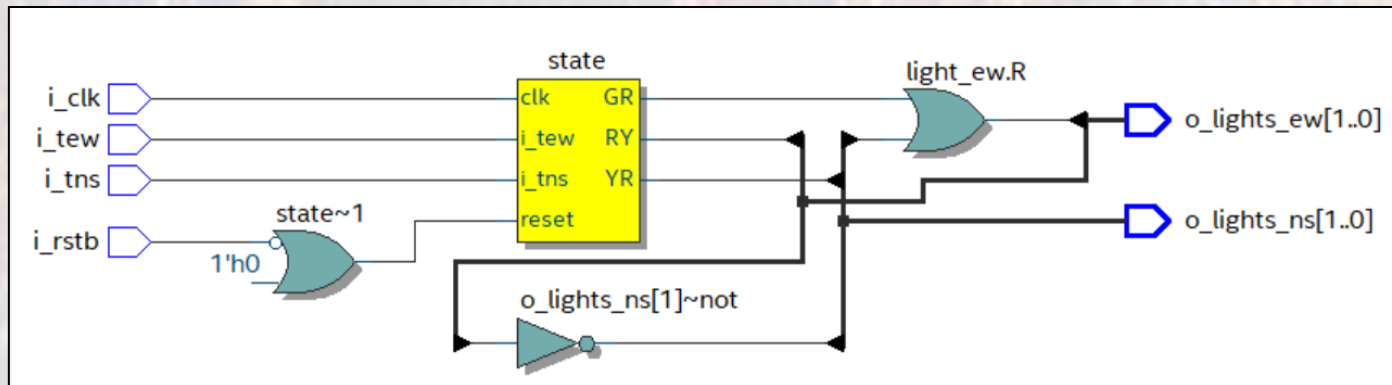- Priority Stoplight – revisited - revisited



HDL FSM Examples

 - Priority Stoplight – revisited - revisited



HDL FSM Examples

- Sequence detector -


```
-----  
-- sequence_detector_CD_fsm.vhdl  
-- created 4/12/2018  
-- tj  
-- rev 0  
-----  
-- sequence detector state machine  
-----  
-- Inputs: i_rstb, i_clk, i_data_in  
-- Outputs: Detect  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
  
entity sequence_detector_CD_fsm is  
  port (  
    i_clk:      in std_logic;  
    i_rstb:     in std_logic;  
    i_data_in:  in std_logic;  
  
    o_detect:   out std_logic  
  );  
end entity;  
  
architecture behavioral of sequence_detector_CD_fsm is  
  
  -- internal signals  
  type STATETYPE is (rst,A,B,C,D,E,F,G,det);  
  signal state:    STATETYPE;  
  signal state_next: STATETYPE;  
  
begin
```

```
-- next state logic  
--  
process(all)  
begin  
  case state is  
    when rst =>  
      if i_data_in = '1' then  
        state_next <= A;  
      else  
        state_next <= rst;  
      end if;  
    when A =>  
      if i_data_in = '1' then  
        state_next <= B;  
      else  
        state_next <= rst;  
      end if;  
    when B =>  
      if i_data_in = '0' then  
        state_next <= C;  
      else  
        state_next <= B;  
      end if;  
    when C =>  
      if i_data_in = '0' then  
        state_next <= D;  
      else  
        state_next <= A;  
      end if;  
    when D =>  
      if i_data_in = '1' then  
        state_next <= E;  
      else  
        state_next <= rst;  
      end if;  
    when E =>  
      if i_data_in = '1' then  
        state_next <= F;  
      else  
        state_next <= rst;  
      end if;  
    when F =>  
      if i_data_in = '0' then  
        state_next <= G;  
      else  
        state_next <= B;  
      end if;  
    when G =>  
      if i_data_in = '1' then  
        state_next <= det;  
      else  
        state_next <= D;  
      end if;  
    when det =>  
      state_next <= rst;  
  end case;  
end process;
```

```
-- Register logic  
--  
process(i_clk, i_rstb)  
begin  
  -- reset  
  if (i_rstb = '0') then  
    state <= rst;  
    -- rising i_clk edge  
    elsif (rising_edge(i_clk)) then  
      state <= state_next;  
    end if;  
end process;  
  
-- Output logic  
--  
process(state)  
begin  
  case state is  
    when rst => o_detect <= '0';  
    when A => o_detect <= '0';  
    when B => o_detect <= '0';  
    when C => o_detect <= '0';  
    when D => o_detect <= '0';  
    when E => o_detect <= '0';  
    when F => o_detect <= '0';  
    when G => o_detect <= '0';  
    when det => o_detect <= '1';  
  end case;  
end process;  
end behavioral;
```


HDL FSM Examples

- Sequence detector - revisited

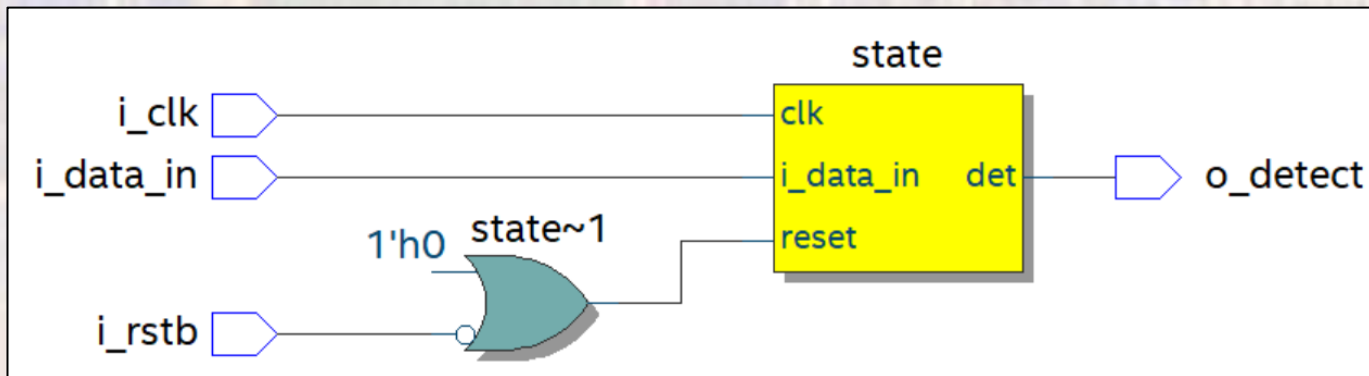


HDL FSM Examples

- Sequence detector - revisited

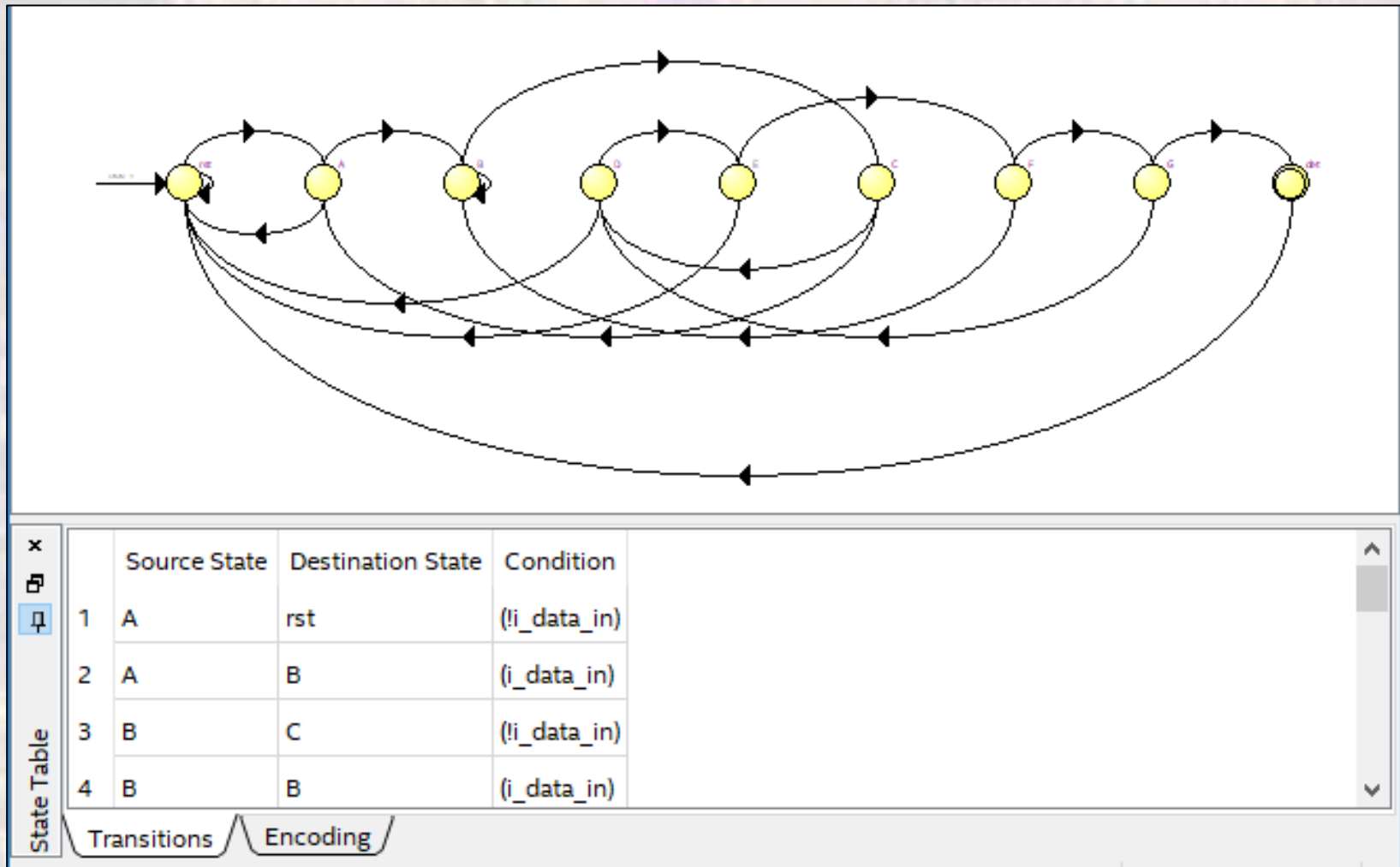


HDL FSM Examples

- Sequence detector - revisited

 

full sequence

re-start

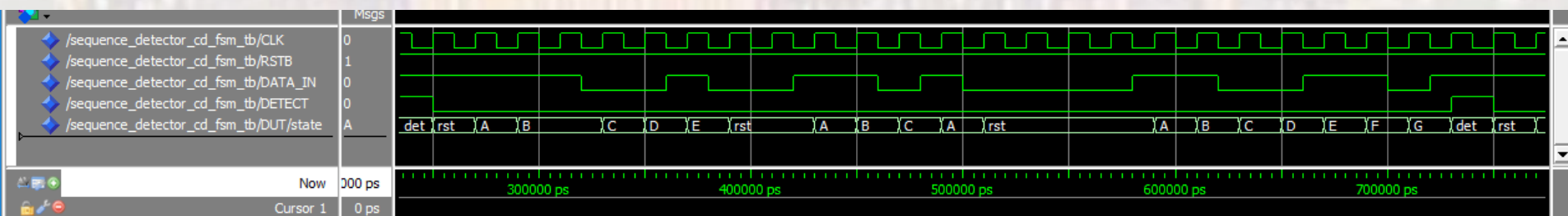

↑
repeat B

↗
Back to start

↑
Back to A

↖
Back to start

full sequence