

HDL FSM Intro

Direct Implementation


Last updated 2/18/21

HDL FSM Intro

- These slides introduce the basics of HDL based State Machines
- Upon completion: You should be able to create a direct implementation of a State Machine in VHDL


HDL FSM Intro

 - Finite State Machine
 - Moore Machine
 - Outputs depend only on the current state(S)



HDL FSM Intro

 
- Finite State Machine
 - Mealy Machine
 - Outputs depend on the current state(S) and the inputs



HDL FSM Intro

- Mod 10 Counter

 Note: this is for illustrative purpose - we would never make a counting state machine like this



HDL FSM Intro

- Mod 10 Counter
 - Next State Logic

Current State	Inputs	Next State
A		B
B		C
C		D
D		E
E		F
F		G
G		H
H		I
I		J
J		A

Binary Encoding

Current State	Inputs	Next State
0000		0001
0001		0010
0010		0011
0011		0100
0100		0101
0101		0110
0110		0111
0111		1000
1000		1001
1001		0000

HDL FSM Intro

- Mod 10 Counter
 - Output Logic

Current State	Output
A	0000
B	0001
C	0010
D	0011
E	0100
F	0101
G	0110
H	0111
I	1000
J	1001

Binary Encoding

Current State	Output
0000	0000
0001	0001
0010	0010
0011	0011
0100	0100
0101	0101
0110	0110
0111	0111
1000	1000
1001	1001

HDL FSM Intro

- FSM general structure - HDL

```

-- counter_mod10_fsm.vhd
-- created 3/30/18
-- tj
-- rev 0
-----
-- mod 10 up-counter - state machine
-----
-- Inputs: i_rstb, i_clk
-- Outputs: o_cnt[3:0]
--
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity counter_mod10_fsm is
    port (
        i_rstb : in std_logic;
        i_clk  : in std_logic;
        o_cnt  : out std_logic_vector(3 downto 0)
    );
end entity;
    
```

Entity declaration

```

architecture behavioral of counter_mod10_fsm is
    -- in
    -- out
    signal state : unsigned(3 downto 0);
    signal state_next : unsigned(3 downto 0);
begin
    -- next state logic
    with state select
        state_next <= "0001" when "0000",
                    "0010" when "0001",
                    "0110" when "0101",
                    "0111" when "0110",
                    "1000" when "0111",
                    "1001" when "1000",
                    "0000" when "1001",
                    "0000" when others;
    
```

State signal declaration


Next state logic

```

-- Register logic
process(i_clk, i_rstb)
begin
    state <= state_next;
end process;
-- Output logic
with state select
    o_cnt <= "0000" when "0000",
           "0001" when "0001",
           "0101" when "0101",
           "0110" when "0110",
           "0111" when "0111",
           "1000" when "1000",
           "1001" when "1001",
           "0000" when others;
end behavioral;
    
```

State initialization and Update (register)

Output logic

 

HDL FSM Intro

- Mod 10 Counter

Made these unsigned since they represent a count

```

-- counter_mod10_fsm.vhd1
-- created 3/30/18
-- tj
-- rev 0
-----
-- mod 10 up-counter - state machine
-----
--
-- Inputs: i_rstb, i_clk
-- Outputs: o_cnt[3:0]
--
-----
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity counter_mod10_fsm is
  port (
    i_clk : in std_logic;
    i_rstb : in std_logic;
    o_cnt : out std_logic_vector(3 downto 0)
  );
end entity;

```

```

architecture behavioral of counter_mod10_fsm is
  -- internal signals
  --
  signal state:      unsigned(3 downto 0);
  signal state_next: unsigned(3 downto 0);
begin
  -- next state logic
  with state select
    state_next <= "0001" when "0000",
                  "0010" when "0001",
                  "0011" when "0010",
                  "0100" when "0011",
                  "0101" when "0100",
                  "0110" when "0101",
                  "0111" when "0110",
                  "1000" when "0111",
                  "1001" when "1000",
                  "0000" when "1001",
                  "0000" when others;


```

```

-- Register logic
process(i_clk, i_rstb)
begin
  -- reset
  if (i_rstb = '0') then
    state <= (others => '0');
  -- rising i_clk edge
  elsif (rising_edge(i_clk)) then
    state <= state_next;
  end if;
end process;


-- Output logic
with state select
  o_cnt <= "0000" when "0000",
           "0001" when "0001",
           "0010" when "0010",
           "0011" when "0011",
           "0100" when "0100",
           "0101" when "0101",
           "0110" when "0110",
           "0111" when "0111",
           "1000" when "1000",
           "1001" when "1001",
           "0000" when others;
end behavioral;

```

 


HDL FSM Intro

- Mod 10 Counter

 

HDL FSM Intro

 - Mod 10 Counter
 - 4 16bit values instead of 16 4bit values



16'h180
 0x0180
 0000 0001 1000 0000

 0000 0001 1000 0000
 0000 0000 0111 1000
 0000 0000 0110 0110
 0000 0001 0101 0101

 0001 0100 0000
 SEL (State)

"0001" when "0000",
 "0010" when "0001",

HDL FSM Intro

- Mod 10 Counter – test bench



```
-----  
-- counter_mod10_fsm_tb.vhd1  
--  
-- created: 3/30/18  
-- by: johnsontimoj  
-- rev: 0  
--  
-- testbench for mod 10 FSM counter  
-- of counter_mod10_fsm_tb.vhd1  
--  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
  
entity counter_mod10_fsm_tb is  
  -- no port entry - testbench  
end entity;  
  
architecture testbench of counter_mod10_fsm_tb is  
  signal CLK: std_logic;  
  signal RSTB: std_logic;  
  
  signal CNT: std_logic_vector(3 downto 0);  
  
  constant PER: time:= 20 ns;
```

```
-----  
-- Component prototype  
-----  
COMPONENT counter_mod10_fsm  
  PORT  
  (  
    i_rstb      : IN STD_LOGIC;  
    i_clk       : IN STD_LOGIC;  
    o_cnt       : OUT STD_LOGIC_VECTOR(3 downto 0)  
  );  
END COMPONENT;  
  
begin  
  
-----  
-- Device under test (DUT)  
-----  
DUT: counter_mod10_fsm  
  port map(  
    i_clk => CLK,  
    i_rstb => RSTB,  
    o_cnt => CNT  
  );
```

```
-----  
-- Test processes  
-----  
  
-- Clock process  
clock: process -- note - no sensitivity list  
begin  
  CLK <= '0';  
  wait for PER/2;  
  infinite: loop  
    CLK <= not CLK; wait for PER/2;  
  end loop;  
end process;  
  
-- Reset process  
reset: process -- note - no sensitivity list  
begin  
  RSTB <= '0'; wait for 2*PER;  
  RSTB <= '1'; wait;  
end process reset;  
  
-- Run Process  
-- no run process needed - run sim to 250 ns  
  
-----  
-- End test processes  
-----  
  
end architecture;
```

HDL FSM Intro

- Mod 10 Counter

  

radix set to unsigned

HDL FSM Intro

Mod 10 Counter using a case statement

HDL FSM Intro

- Mod 10 Counter – case statement

Made these unsigned since they represent a count

```

-----
-- counter_mod10_fsmA.vhdl
-- created 3/30/18
-- tj
-- rev 0
-----
-- mod 10 up-counter - state machine with case statement
-----
-- Inputs: i_rstb, i_clk
-- Outputs: o_cnt[3:0]
-----
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity counter_mod10_fsmA is
  port (
    i_clk : in std_logic;
    i_rstb : in std_logic;
    o_cnt : out std_logic_vector(3 downto 0)
  );
end entity;

```

```

architecture behavioral of counter_mod10_fsmA is
  -- internal signals
  signal state: unsigned(3 downto 0);
  signal state_next: unsigned(3 downto 0);
begin
  -- next state logic
  process(all)
  begin
    case state is
      when "0000" => state_next <= "0001";
      when "0001" => state_next <= "0010";
      when "0010" => state_next <= "0011";
      when "0011" => state_next <= "0100";
      when "0100" => state_next <= "0101";
      when "0101" => state_next <= "0110";
      when "0110" => state_next <= "0111";
      when "0111" => state_next <= "1000";
      when "1000" => state_next <= "1001";
      when "1001" => state_next <= "0000";
      when others => state_next <= "0000";
    end case;
  end process;
end behavioral;


```

```

-- Register logic
process(i_clk, i_rstb)
begin
  -- reset
  if (i_rstb = '0') then
    state <= (others => '0');
  -- rising i_clk edge
  elsif (rising_edge(i_clk)) then
    state <= state_next;
  end if;
end process;


-- output logic
with state select
  o_cnt <= "0000" when "0000",
           "0001" when "0001",
           "0010" when "0010",
           "0011" when "0011",
           "0100" when "0100",
           "0101" when "0101",
           "0110" when "0110",
           "0111" when "0111",
           "1000" when "1000",
           "1001" when "1001",
           "0000" when others;
end behavioral;

```

 

HDL FSM Intro

- Mod 10 Counter –with case statement

 

HDL FSM Intro

Mod 10 Counter using a case statement X 2

HDL FSM Intro

- Mod 10 Counter – case statement X 2

Made these unsigned since they represent a count

```

-----
-- counter_mod10_fsmB.vhd1
-- created 3/30/18
-- tj
-- rev 0
-----
-- mod 10 up-counter - state machine with case statement
-- case statement for output logic
-----
--
-- Inputs: i_rstb, i_clk
-- Outputs: o_cnt[3:0]
-----
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity counter_mod10_fsmB is
  port (
    i_clk : in std_logic;
    i_rstb : in std_logic;
    o_cnt : out std_logic_vector(3 downto 0)
  );
end entity;

```

```

architecture behavioral of counter_mod10_fsmB is
  --
  -- internal signals
  signal state:      unsigned(3 downto 0);
  signal state_next: unsigned(3 downto 0);
begin
  --
  -- next state logic
  --
  process(all)
  begin
    case state is
      when "0000" => state_next <= "0001";
      when "0001" => state_next <= "0010";
      when "0010" => state_next <= "0011";
      when "0011" => state_next <= "0100";
      when "0100" => state_next <= "0101";
      when "0101" => state_next <= "0110";
      when "0110" => state_next <= "0111";
      when "0111" => state_next <= "1000";
      when "1000" => state_next <= "1001";
      when "1001" => state_next <= "0000";
      when others => state_next <= "0000";
    end case;
  end process;
end architecture;


```

```

--
-- Register logic
--
process(i_clk, i_rstb)
begin
  -- reset
  if (i_rstb = '0') then
    state <= (others => '0');
  -- rising i_clk edge
  elsif (rising_edge(i_clk)) then
    state <= state_next;
  end if;
end process;

--
-- output logic
--
process(all)
begin
  case state is
    when "0000" => o_cnt <= "0000";
    when "0001" => o_cnt <= "0001";
    when "0010" => o_cnt <= "0010";
    when "0011" => o_cnt <= "0011";
    when "0100" => o_cnt <= "0100";
    when "0101" => o_cnt <= "0101";
    when "0110" => o_cnt <= "0110";
    when "0111" => o_cnt <= "0111";
    when "1000" => o_cnt <= "1000";
    when "1001" => o_cnt <= "1001";
    when others => o_cnt <= "0000";
  end case;
end process;
end behavioral;

```

 

HDL FSM Intro

- Mod 10 Counter –with case statement X 2

