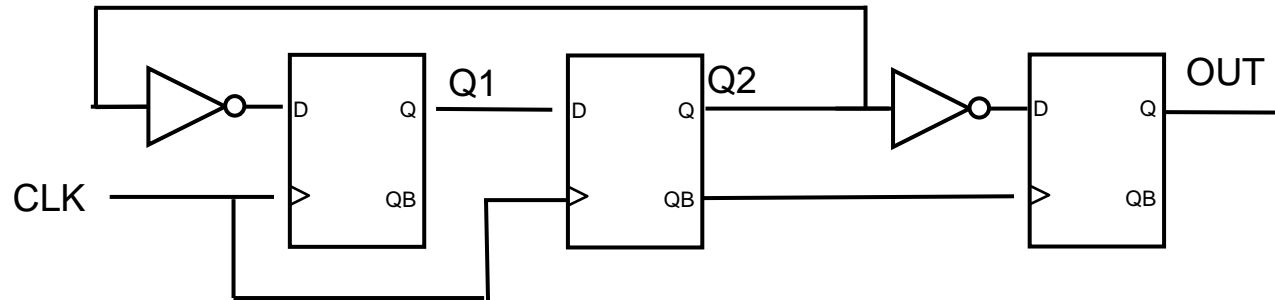


CE 1911


Homework 2

1 – Create a transition table and determine the value of OUT
(Assume all Qs = 0 initially)

30pts



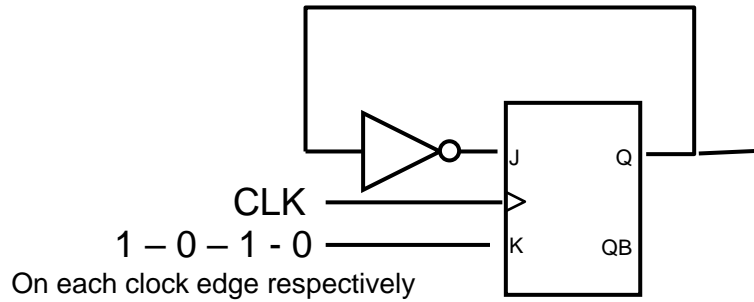
2 – Create a transition table and determine the value of Q after each clock cycle
(Assume Q = 0 initially and include it in the table) 30pts




On each clock edge respectively
K=1 on 1st clock edge
K=0 on 2nd clock edge
K=1 on 3rd clock edge
K=0 on 4th clock edge

3 – Identify the period, frequency and duty cycle of each waveform
use engineering notation and without a calculator


20pts

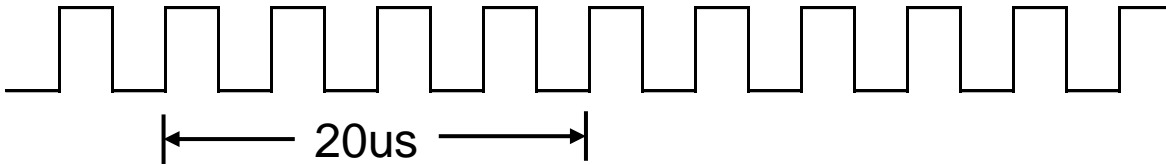


T = _____
F = _____
Duty = _____

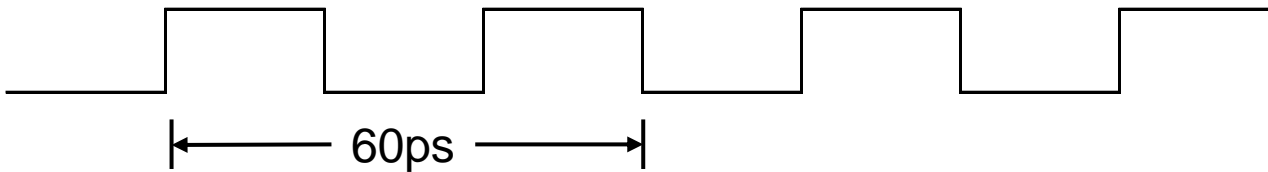

T = _____
F = _____
Duty = _____

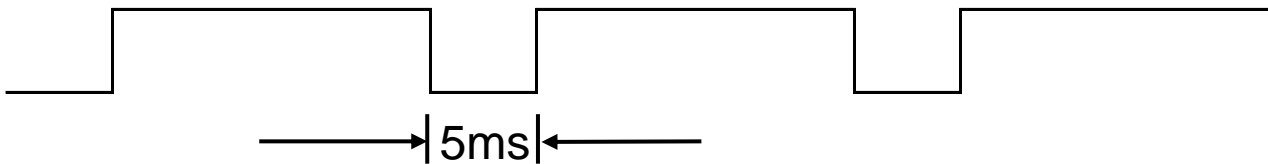

T = _____
F = _____
Duty = _____

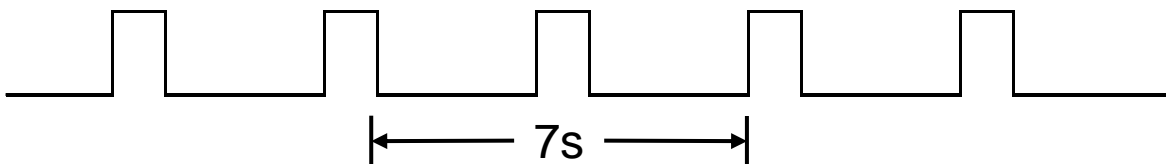

T = _____
F = _____
Duty = _____

4 – Write a short description of each of the following flip-flops

20pts

