

CE 1911

Homework 4

1 – Write behavioral VHDL code for a D-FF with asynchronous resetb and synchronous set. Provide code, test-bench and a simulation

50pts

```
--
-- created 2/1/2018
-- tj
--
-- rev 0
-----
--
-- special DFF with synchronous set
--
-----
--
-- Inputs: clk, rstb, din, set
-- Outputs: q
--
-----
library ieee;
use ieee.std_logic_1164.all;

entity dffws is
port (
    i_clk :    in std_logic;
    i_rstb :   in std_logic;
    i_din  :   in std_logic;
    i_set  :   in std_logic;

    o_q    :   out std_logic
);
end entity;

architecture behavioral of dffws is
```

architecture
~14 lines

1 – Write behavioral VHDL code for a D-FF with asynchronous resetb and synchronous set. Provide code, test-bench and a simulation 50pts

testbench

```

--
-- created: 1/26/18
-- by: johnsontimoj
-- rev: 0
--
-- testbench for dff with set
-- of dffws.vhdl
--
-----
library ieee;
use ieee.std_logic_1164.all;

entity dffws_tb is
  -- no entry - testbench
end entity;

architecture testbench of dffws_tb is
  signal CLK:      std_logic;
  signal RSTB:     std_logic;
  signal DIN:      std_logic;
  signal SET:      std_logic;

  signal Q:        std_logic;

  constant PER:    time := 20 ns;

  -----
  -- Component prototype
  -----
  COMPONENT dffws
  PORT
  (
    i_clk   : IN STD_LOGIC;
    i_rstb  : IN STD_LOGIC;
    i_din   : IN STD_LOGIC;
    i_set   : IN STD_LOGIC;
    o_q     : OUT STD_LOGIC
  );
END COMPONENT;

-----
begin

-----
-- Device under test (DUT)
-----
DUT: dffws
  port map(
    i_clk   => CLK,
    i_rstb  => RSTB,
    i_din   => DIN,
    i_set   => SET,

    o_q     => Q
  );

-----
-- Test processes
-----

```

Clock process

Reset process

```

-- Run process
run: process      -- note - no sensitivity
begin
  -----
  -- Initialize inputs
  DIN <= '0';
  SET <= '0';
  wait for 3*PER;  -- wait for reset

  -- verify normal operation
  DIN <= '1'; wait for 3*PER;
  DIN <= '0'; wait for 3*PER;
  DIN <= '1'; wait for 3*PER;
  DIN <= '0'; wait for 3*PER;

  -- verify set operation
  SET <= '1';
  DIN <= '1'; wait for 3*PER;
  DIN <= '0'; wait for 3*PER;


  -- verify normal operation
  SET <= '0';
  DIN <= '1'; wait for 3*PER;
  DIN <= '0'; wait for 3*PER;
  DIN <= '1'; wait for 3*PER;
  DIN <= '0'; wait for 3*PER;
end process run;

-----
-- End test processes
-----
end architecture;

```

1 – Write behavioral VHDL code for a D-FF with asynchronous resetb and synchronous set. Provide code, schematic, test-bench and a simulation 50pts

Simulation Results

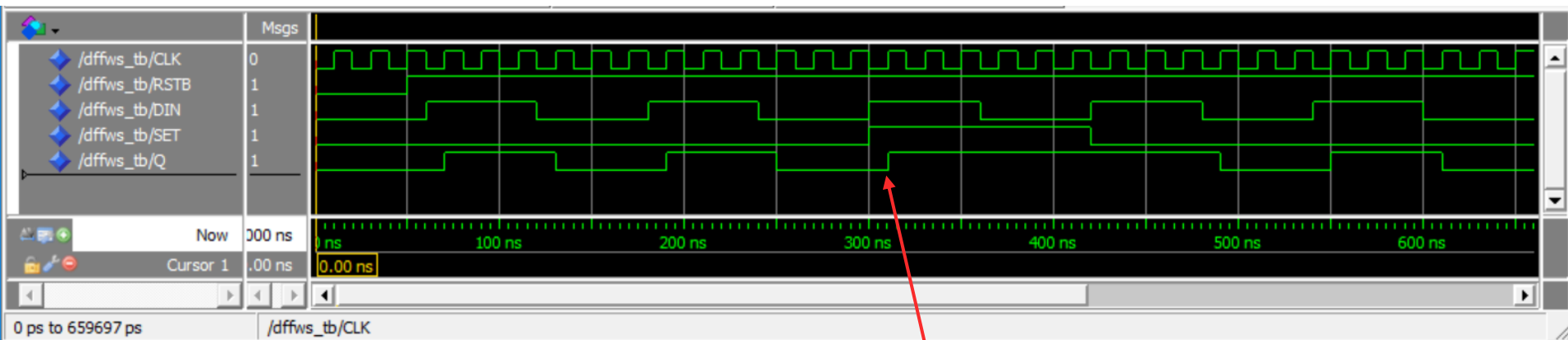

data mode

Set mode

data mode

note – no set until clk - synchronous

2 – Write behavioral VHDL code for a special new FlipFlop you have conceived of – this FlipFlop has a second data input called Toggle(T). When T is low, the DFF operates normally, when T is high, the DFF ignores the D input and synchronously toggles the output. Provide code and a simulation 50pts

```
--
-- created 2/1/2018
-- tj
--
-- rev 0
-----
--
-- special DFF with toggle mode
--
-----
--
-- Inputs: clk, rstb, din, t
-- Outputs: q
--
-----
library ieee;
use ieee.std_logic_1164.all;

entity dffwT is
  port (
    i_clk : in std_logic;
    i_rstb : in std_logic;
    i_din : in std_logic;
    i_t : in std_logic;

    o_q : out std_logic
  );
end entity;

architecture behavioral of dffwT is
```

architecture
~14 lines

2 – Write behavioral VHDL code for a special new FlipFlop you have conceived of – this FlipFlop has a second data input called Toggle(T). When T is low, the DFF operates normally, when T is high, the DFF ignores the D input and synchronously toggles the output. Provide code and a simulation 50pts

testbench

```
-- Run process
run: process      -- note - no sensitivity list allowed
begin
-----
-- Initialize inputs
DIN <= '0';
T <= '0';
wait for 2*PER;  -- wait for reset

-- verify normal operation
DIN <= '1'; wait for 3*PER;
DIN <= '0'; wait for 3*PER;
DIN <= '1'; wait for 3*PER;
DIN <= '0'; wait for 3*PER;

-- verify toggle operation
T <= '1';
DIN <= '1'; wait for 4*PER;
DIN <= '0'; wait for 4*PER;


-- verify normal operation
T <= '0';
DIN <= '1'; wait for 3*PER;
DIN <= '0'; wait for 3*PER;
DIN <= '1'; wait for 3*PER;
DIN <= '0'; wait for 3*PER;
end process run;

-----
-- End test processes
-----

end architecture;
```

2 – Write behavioral VHDL code for a special new FlipFlop you have conceived of – this FlipFlop has a second data input called Toggle(T). When T is low, the DFF operates normally, when T is high, the DFF ignores the D input and synchronously toggles the output. Provide code and a simulation 50pts

Simulation Results

 

data mode

toggle mode

data mode