

CE 1911 Week 6 Lab: FSM HDL Design

Name: _____

Objectives

- Design a moderately complex Finite State Machines using VHDL
- Develop a DE10 implementation using switches and seven segment displays

Prelab

- Create a working directory and project in Quartus for W6Lab
- Review HDL FSM class notes
- Review CE1901 notes on using the seven segment displays
- **Create a state transition diagram for your design**

student
check off

Assignment

Part 1: **Create and simulate a full function stoplight system using a timer based FSM.**

- 1) Normal operation cycles from
RR – 1 clk, RG – 7 clks, RY – 3 clks, RR – 1 clk, GR – 7 clks, YR – 3 clks, ...
- 2) Maintenance mode – solid RR based on signal “maint”
- 3) Power fail mode – flashing RR (1 clk on, 1 clk off) based on signal “pwr_fail”
- 4) Emergency vehicle mode – **safely** transition to GR or RG in direction A or B based on 2 signals “emergency_A” or “emergency_B”
- 5) Use the following priority – power fail >> maintenance >> emergency >> normal

Be sure to check the example simulation plot for testbench expectations

Part 2: **Implement your design on the DE10 board.**

Use a 3Hz clock divider to slow down the clock

Use switches as the control inputs

Use 3 LEDs for each direction A and B


Use 4 seven segment displays to indicate the status of your system using letters

Normal operation – 2 sseg for each direction (A and B) – **rd, ye, gr**

Maintenance mode – **main**

Power out mode – **fail** – flashing

 Emergency vehicle mode – **em** in the emergency direction, normal operation in the second direction



Check Off

- Demo and document your stoplight schematic and simulation 50%
- Demo and document your DE10 implementation 50%

Lab Report (informal)

- Due at 4:00 pm, Monday after lab – in the box
- Include a properly documented informal lab report.