
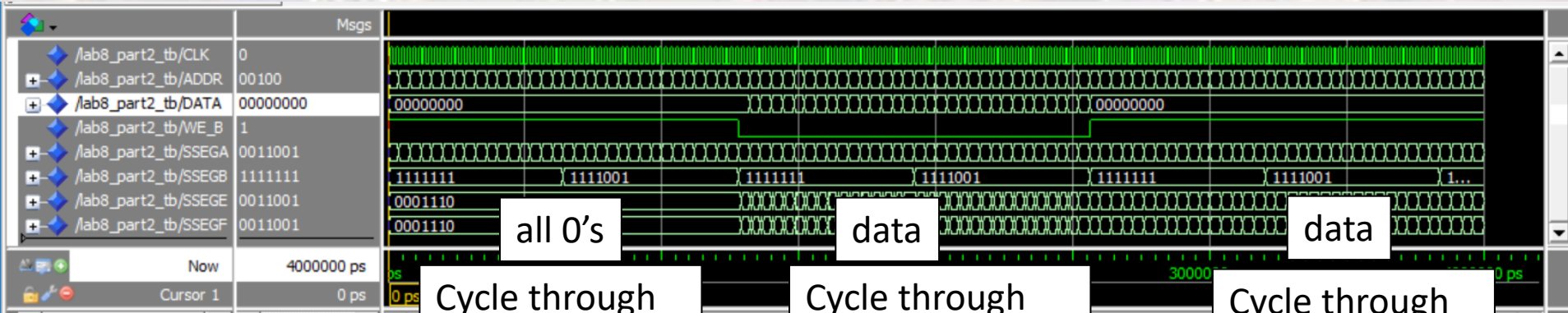


Lab8 – Part2

```

entity lab8_part2 is
port(
    i_clk:      in    std_logic;
    i_we_b:     in    std_logic;
    i_addr:     in    std_logic_vector(4 downto 0);
    i_data:     in    std_logic_vector(7 downto 0);

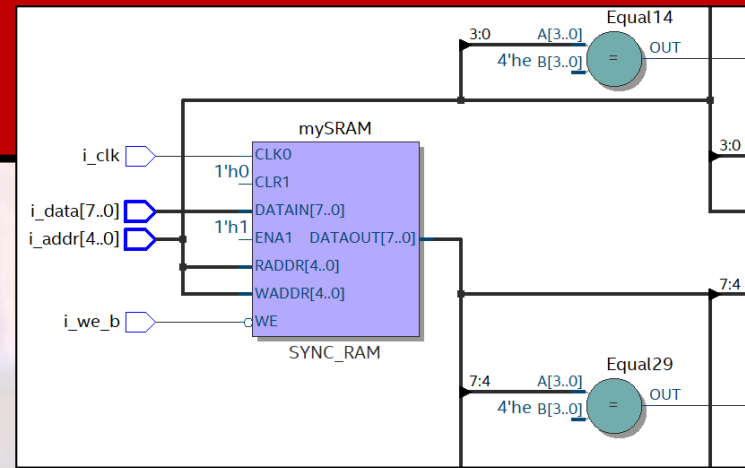    o_addr_sseg_A: out  std_logic_vector(6 downto 0);
    o_addr_sseg_B: out  std_logic_vector(6 downto 0);
    o_data_sseg_E: out  std_logic_vector(6 downto 0);
    o_data_sseg_F: out  std_logic_vector(6 downto 0)
);
end;
    
```



all 0's
Cycle through addresses – no write


data
Cycle through addresses – and write data

data
Cycle through addresses – no write

```

entity lab8_part2_de10 is
port(
    CLOCK_50: in    std_logic;
    SW:       in    std_logic_vector(9 downto 0);
    KEY:      in    std_logic_vector(0 downto 0);

     HEX0:     out  std_logic_vector(6 downto 0);
    HEX1:     out  std_logic_vector(6 downto 0);
    HEX4:     out  std_logic_vector(6 downto 0);
    HEX5:     out  std_logic_vector(6 downto 0)
);
end entity;
    
```



Only 4 data input switches but data is 8 bits wide I doubled up on the input bits b3 b2 b1 b0 to form the data input b3 b3 b2 b2 b1 b1 b0 b0 e.g. if I input 1010, I store 11001100 and read out CC