

# Lab Project Notes

- Implementation Notes
  - Normally the Register file would only have Read\_Data\_1 and Read\_Data\_2 outputs – but – because we want to see the internal register values you need to also have outputs for RegA, RegB, RegC, and RegD

```
entity reg_file is
  port (
    i_clk : in std_logic;
    i_reg1_addr : in std_logic_vector(1 downto 0);
    i_reg2_addr : in std_logic_vector(1 downto 0);
    i_wreg_addr : in std_logic_vector(1 downto 0);
    i_wreg_data : in std_logic_vector(7 downto 0);
    i_we_b: in std_logic;

    o_reg1_data: out std_logic_vector(7 downto 0);
    o_reg2_data: out std_logic_vector(7 downto 0);

    o_regA_data: out std_logic_vector(7 downto 0);
    o_regB_data: out std_logic_vector(7 downto 0);
    o_regC_data: out std_logic_vector(7 downto 0);
    o_regD_data: out std_logic_vector(7 downto 0)
  );
end entity;
```

# Lab Project Notes



- Implementation Notes

- Create a sseg output block to do the conversion from binary to sseg display and place 6 of them in the DE10 top level design
  - Takes the nibble from the register and converts it to a sseg display value
  - 2 for each register value
  - See the DE10 RTL view later in the notes

```
entity sseg is
  port(
    i_blank:      in    std_logic;
    i_nibble_in: in    std_logic_vector(3 downto 0);
    o_sseg_out:   out   std_logic_vector(6 downto 0)
  );
end;
```

# Lab Project Notes


- Sequencer Simulation

  
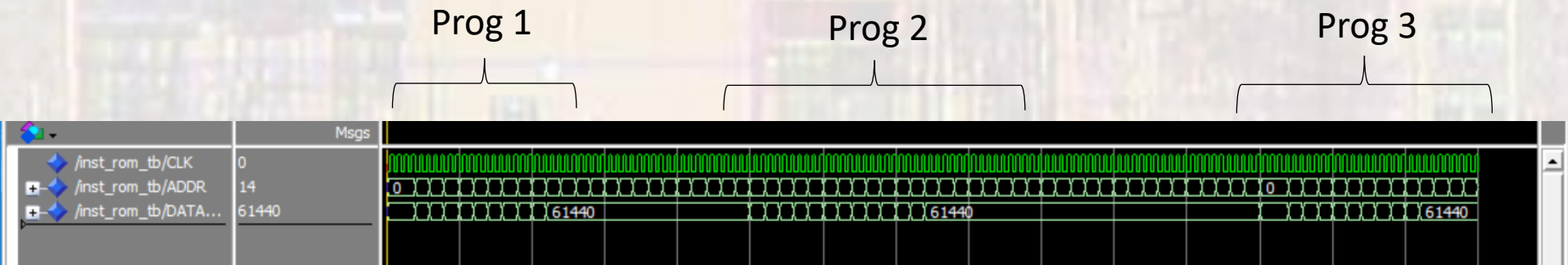
# Lab Project Notes



- Instruction ROM
  - Inferred using HDL ROM, slide 4
  - Add addresses to the constant section
    - Only the addresses you are using
    - Others go to NOP: x"F000"

```
-- ROM contents
constant instr_ROM: rom_type:=(
  0 =>    X"C010",
  1 =>    X"C04A",
  2 =>    X"5180",
  ...
  64 =>   x"C002",
  65 =>   x"C044",
  66 =>   x"C088",
  ...
  others => x"F000"
);
```




# Lab Project Notes

- Register File Simulation

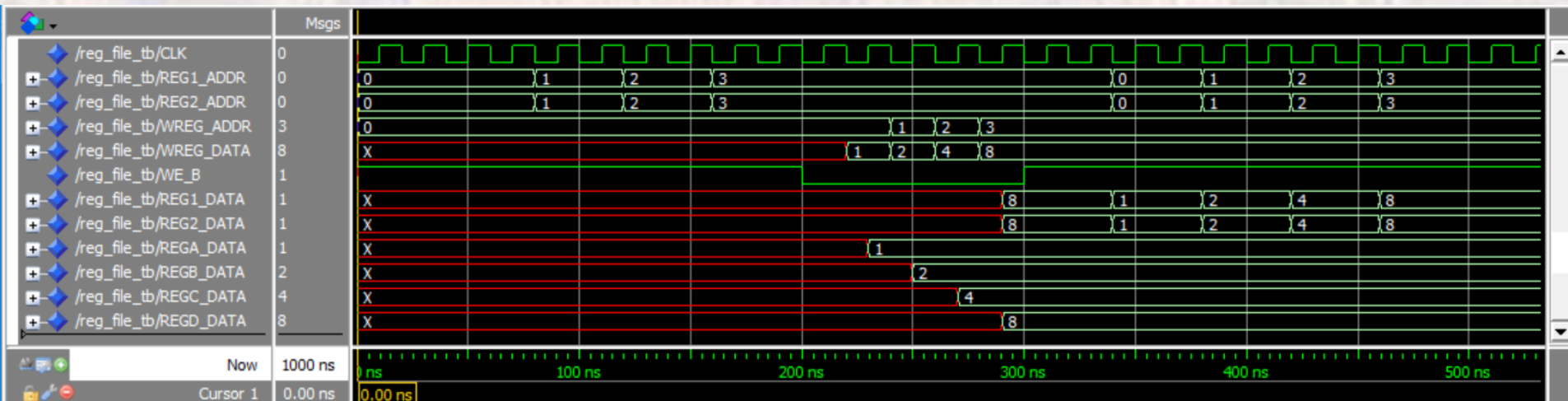 


# Lab Project Notes

- ALU Simulation

 


- Data RAM Simulation

 


# Lab Project Notes

- Decoder Simulation

 

# Lab Project Notes


- Processor RTL view

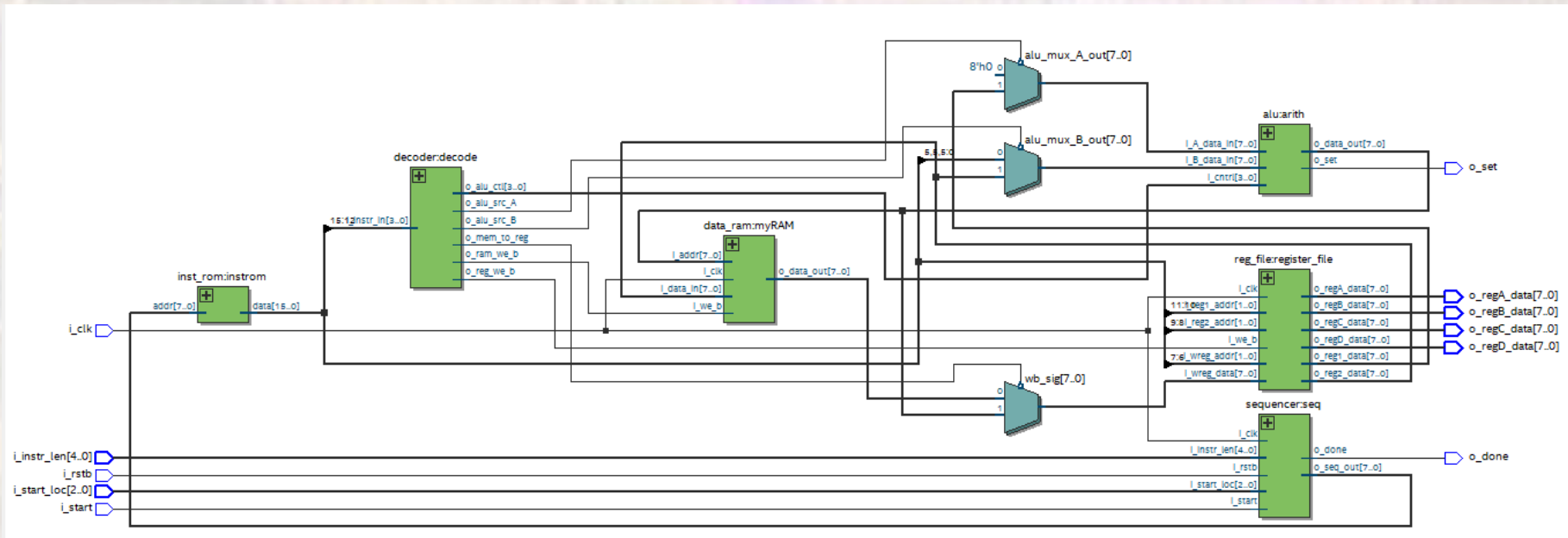



# Lab Project Notes

- Processor Simulation

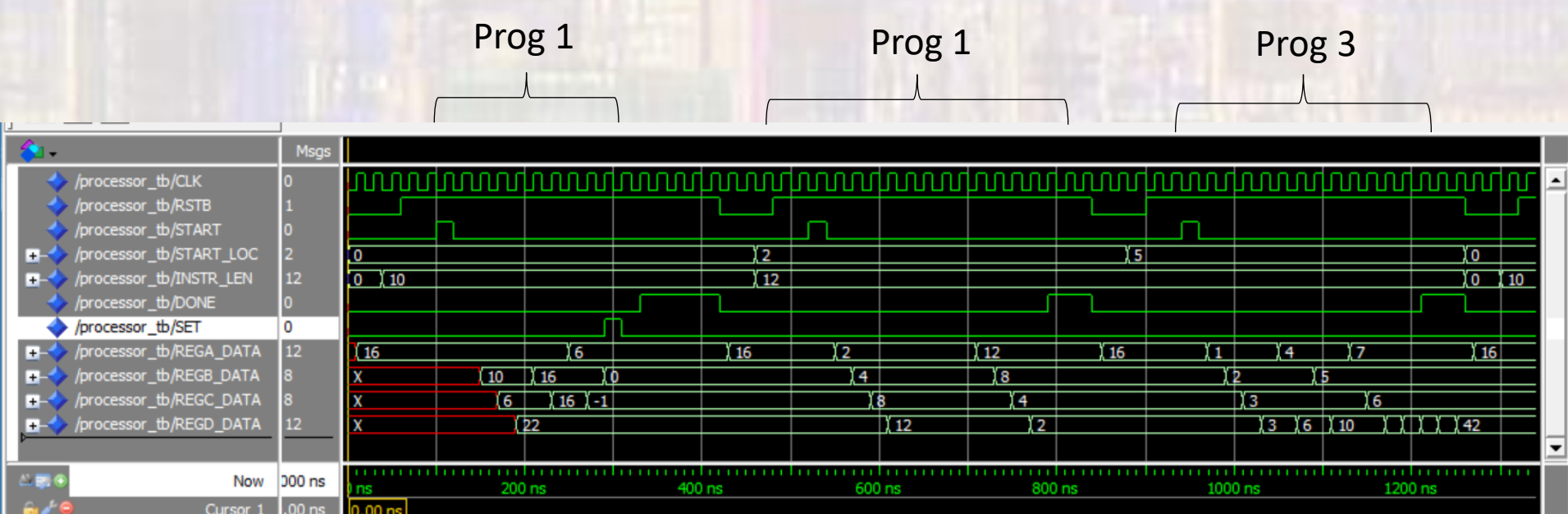

# Lab Project Notes

- DE10 RTL view

