 


# Latches

Last updated 1/11/21



# Latches

- Shortcuts


  
# Latches

- Bi-stable circuit
  - Circuit with 2 stable operating points
  - Holds 1 element of memory
    - 1 state variable
    - 2 values for the state variable
      - 1 bit – 0 or 1





	state variable	
State	A	B
1	0	1
2	1	0

	state variable	
State	Q	$\overline{Q}$
1	0	1
2	1	0
  
# Latches

- Bi-stable circuit

- Circuit with 2 stable operating points
- Holds 1 element of memory
  - 1 state variable
  - 1 bit




*What's wrong with this circuit*

State	A	B
1	0	1
2	1	0

State	Q	$\overline{Q}$
1	0	1
2	1	0
 
# Latches


- SR Latch (set/reset)
  - Bi-stable circuit
  - Added ability to set the state



R : Reset  
S : Set

# Latches

- SR Latch (set/reset)
- 0,0 Inputs

 


S	R	Q
0	0	$Q_{old}$

Latch

# Latches

- SR Latch (set/reset)

- 0,1 Inputs

 


S	R	Q
0	0	$Q_{old}$
0	1	0

Reset

# Latches

- SR Latch (set/reset)

- 1,0 Inputs

 

S	R	Q
0	0	$Q_{old}$
0	1	0
1	0	1


Set



# Latches

- SR Latch (set/reset)

- 1,1 Inputs

 

S	R	Q
0	0	$Q_{old}$
0	1	0
1	0	1
1	1	0



Fault?

# Latches

- SR Latch (set/reset)

- Sequential

  
- Output depends on Inputs and 1 state variable  $Q$  ( $Q_{old}$ )
- Asynchronous – output changes occur when inputs change
- Memory is in the bi-stable latch



S	R	Q
0	0	$Q_{old}$
0	1	0
1	0	1
1	1	0
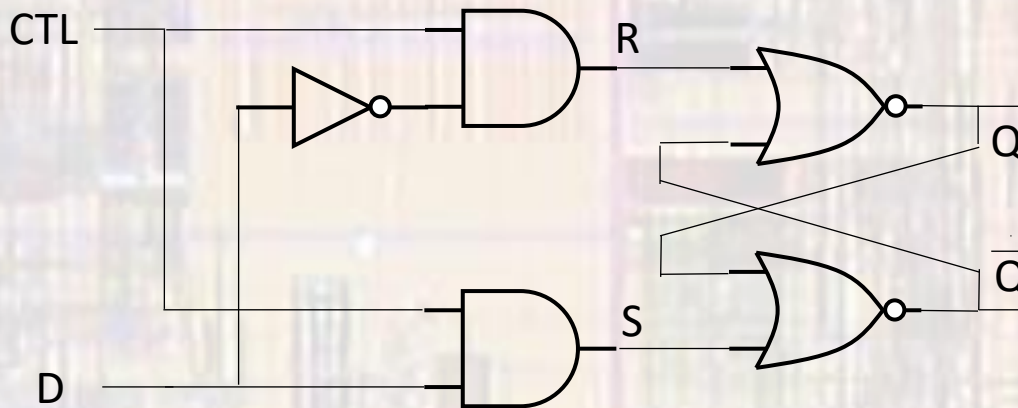
# Latches

- D Latch (data)
  - Bi-stable circuit
  - Added ability to set the state
  - Output changes limited to specific input conditions





# Latches

- D Latch (data)

- 0,0 inputs – control (CTL), data (D)

CTL	D	Q
0	0	$Q_{old}$

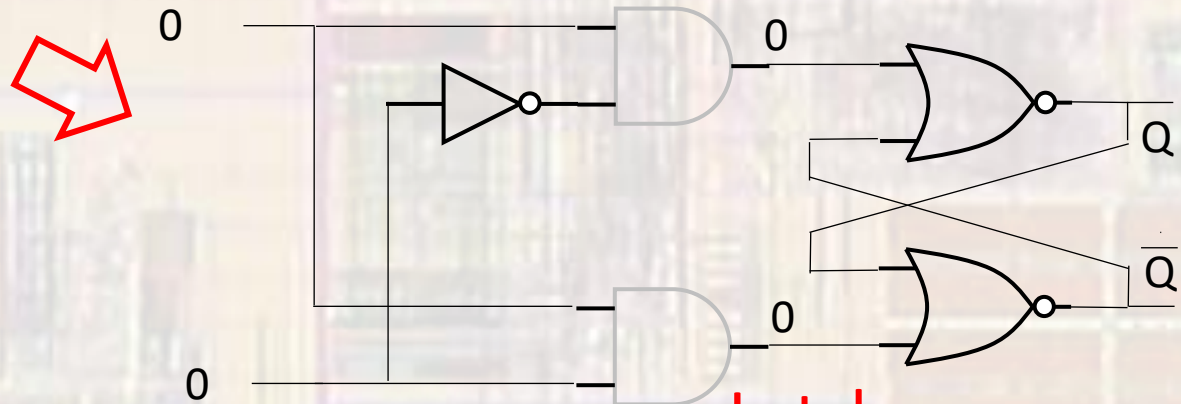 


Latch


# Latches

- D Latch (data)

- 0,1 inputs – control, data

 


CTL	D	Q
0	0	$Q_{old}$
0	1	$Q_{old}$

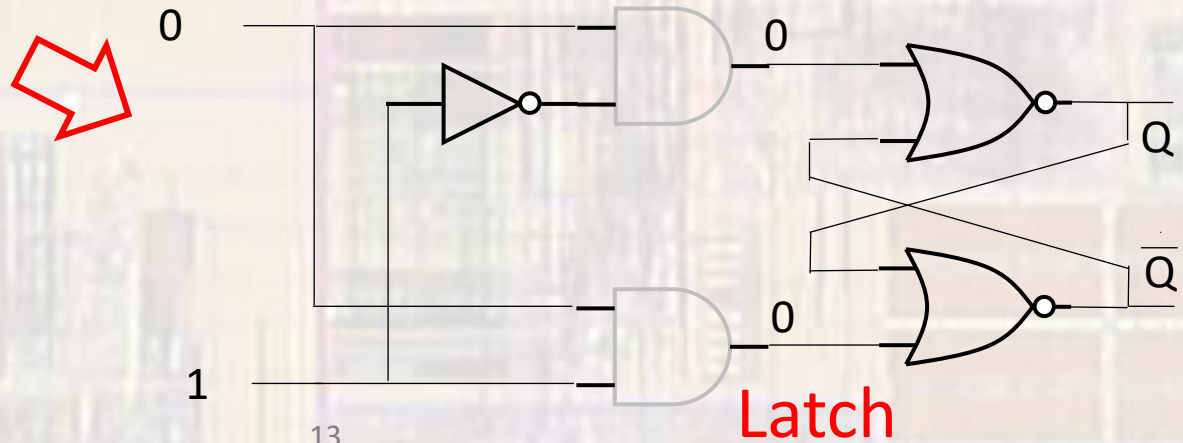


# Latches

- D Latch (data)

- 1,0 inputs – control, data

 

CTL	D	Q
0	0	$Q_{old}$
0	1	$Q_{old}$
1	0	0 (D)


 


# Latches

- D Latch (data)


- 1,1 inputs – control, data

CTL	D	Q
0	0	$Q_{old}$
0	1	$Q_{old}$
1	0	0 (D)
1	1	1 (D)


 
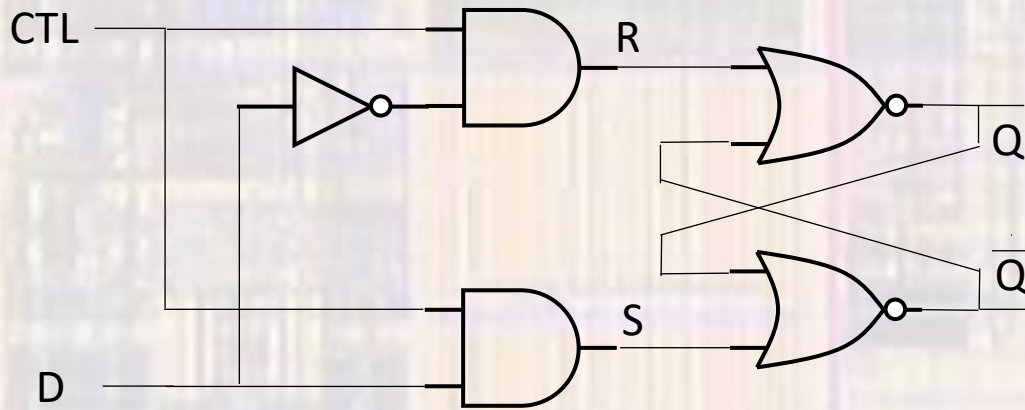

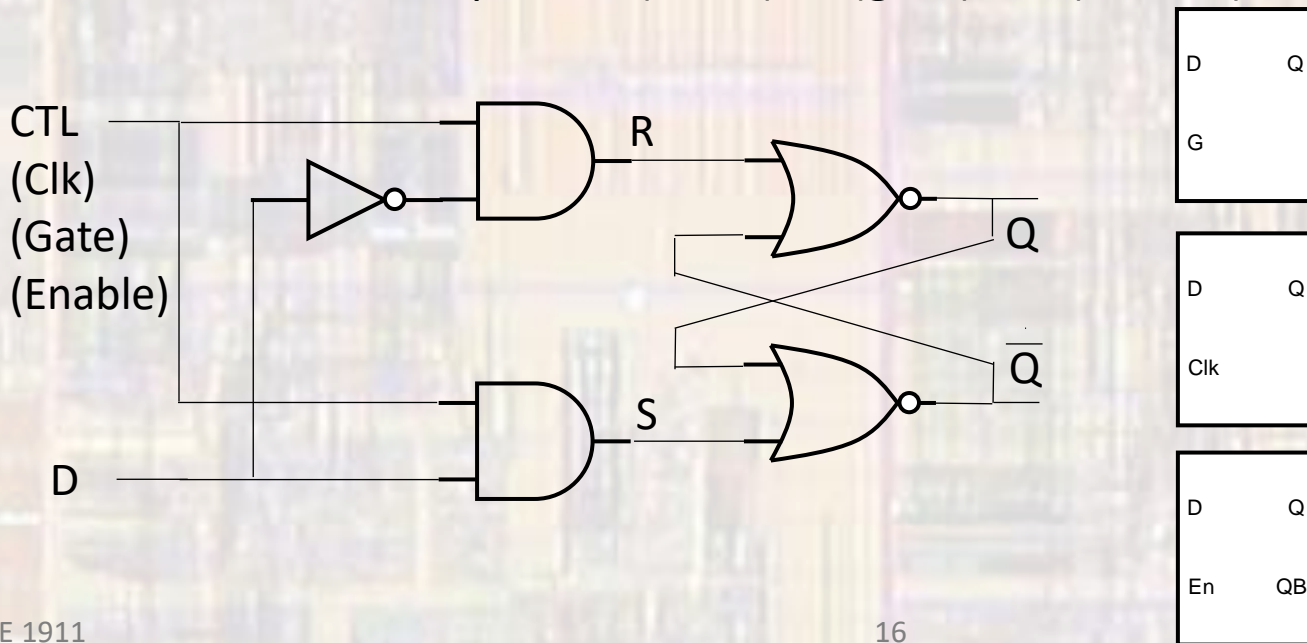
# Latches

- D Latch (data)
  - Sequential
    - Output depends on Inputs and 1 state variable (Q)
    - Asynchronous – output changes occur when inputs change
    - Memory is in the bi-stable latch
  - Control input: Clk(clock), G (gate), En (enable)



CTL	D	Q
0	x	$Q_{old}$
1	D	D

   







# Latches

- D Latch (data)
   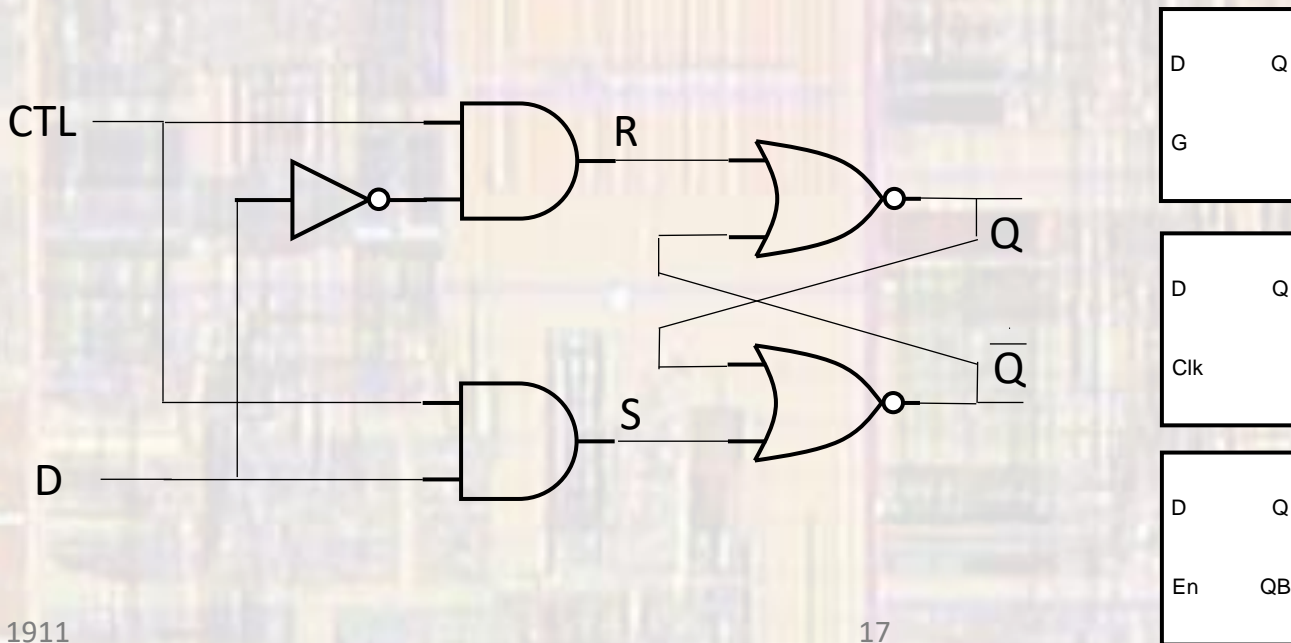
## Level Sensitive Latch

CTL = low  $\rightarrow$  latched  
 CTL = high  $\rightarrow$  Transfer



CTL	D	Q
0	x	$Q_{old}$
1	D	D