
Last updated 1/25/21

- Read Only Memory ROM
 - Key Attributes
 - Sequential vs. Random Access
 - Read only vs. Read/Write
 - Static s. Dynamic
 - Volatile vs non-Volatile
 - Key Measures
 - Density +
 - Speed
 - Power
 - Cost / bit +

- ROM Read Only Memory
 - Memory cell (1 bit) is based on whether a MOSFET is or is not connected between the bit line and word line
 - The MOSFET structure is always part of the bit cell
 - It can be connected to the bit line through a contact or via (via ROM)
 - It can be disable by removing the S/D diffusion (diffusion ROM)
 - Cannot be modified once the part is built
 - Typically used as Boot memory or to hold chip configuration data

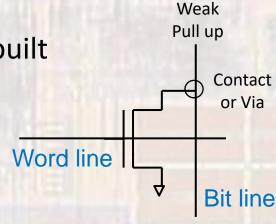



CE 1911 3

- ROM Read Only Memory
 - Read
 - Read Enable (RE) high
 - Sense amplifiers on
 - Apply an address
 - Select the desired word line (high)
 - Sense amplifiers read the value of the bit lines

If connected – will read a "0"


If not connected – will read a "1"

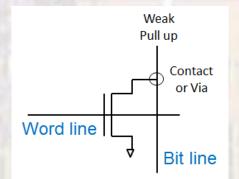

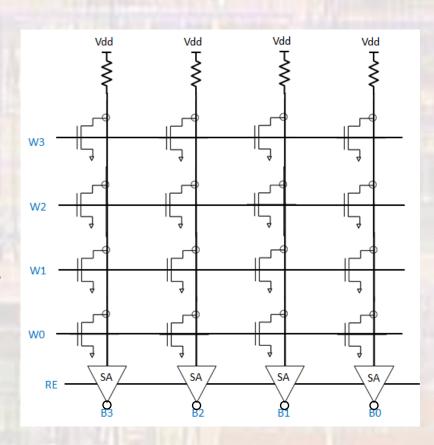

© ti

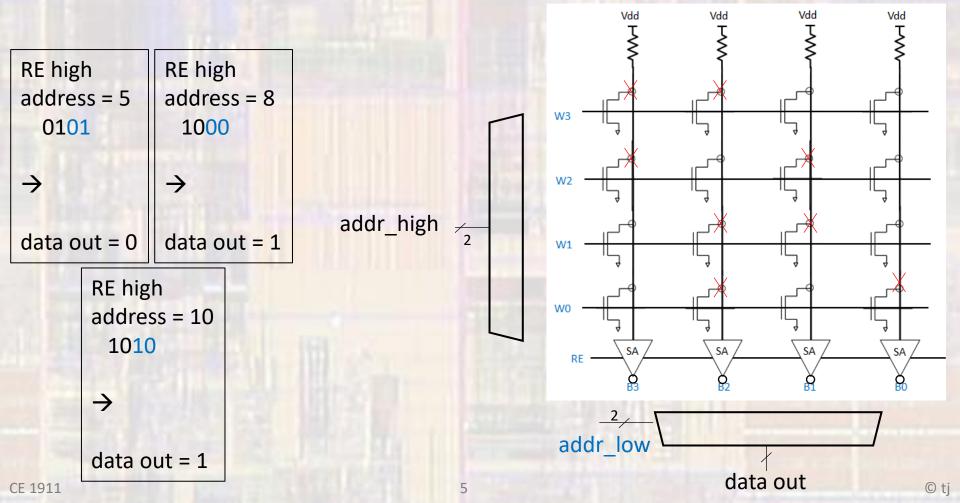
- ROM Read Only Memory
 - Read x1 configuration






Read – x4 configuration – 4 x 8 x 4


RE high RE high RE high address = 21address = 5address = 2911101 10101 00101 \rightarrow \rightarrow \rightarrow data out = data out = data out = 0011 0101 1010

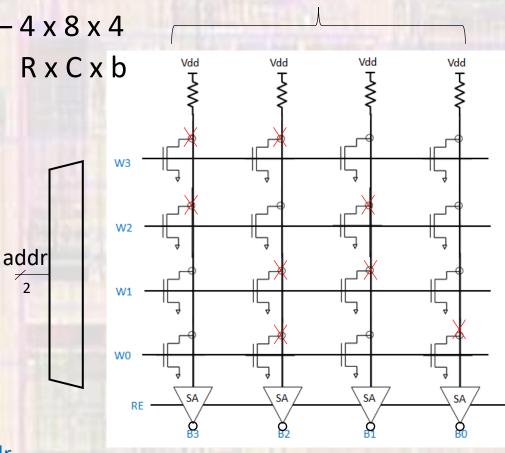


column 5

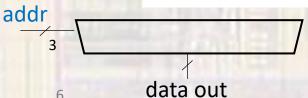

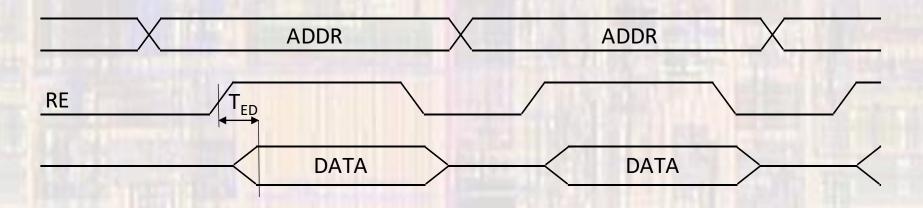
- ROM Read Only Memory
 - Timing Read enable




Timing – no Read enable

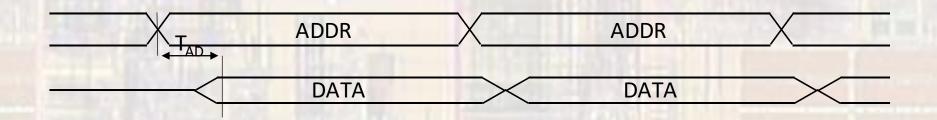

ROM – Read Only Memory – Diffusion ROM

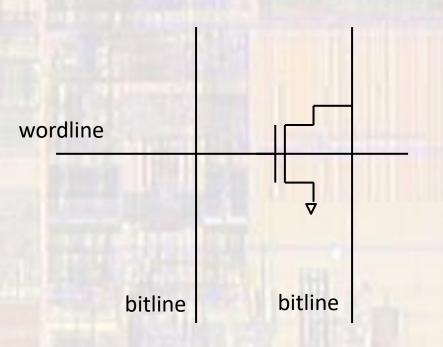

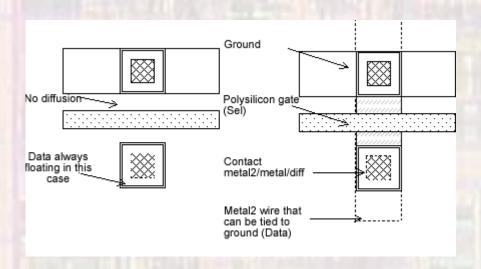

ROM – Read Only Memory – Via (contact) ROM

