

Memory - SDRAM

Last updated 1/25/21


Memory - SDRAM

- Dynamic Random Access Memory – DRAM
- **Synchronous** DRAM - SDRAM
 - Key Attributes
 - Sequential vs. **Random Access**
 - Read only vs. **Read/Write**
 - Static vs. **Dynamic**
 - **Volatile** vs. non-Volatile
 - Key Measures
 - Density +
 - Speed
 - Power
 - Cost / bit +

Memory - SDRAM


- DRAM/SDRAM – Synchronous Dynamic Random Access Memory
 - Memory cell (1 bit) is based on capacitor charge storage
 - Bit value decays over time
 - must be recharged – called a refresh cycle
 - Standard SDRAM transfers 1 word each array access
 - DDR – double data rate – transfers 2 words each array access
 - DDR2, DDR3, DDR4 – transfer 4,8,16 words each array access
 - Medium speed
 - Highest density
 - Used as main memory

Bit line

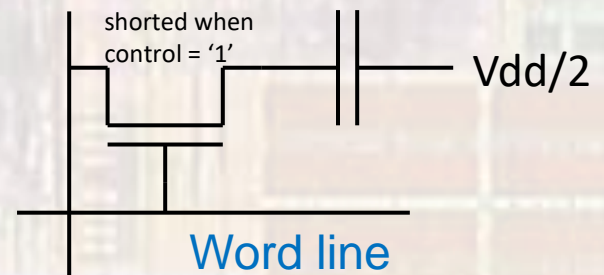

Memory - SDRAM

- SDRAM – Cell

 


Src: IEDM

Memory - SDRAM

- General Memory Topology

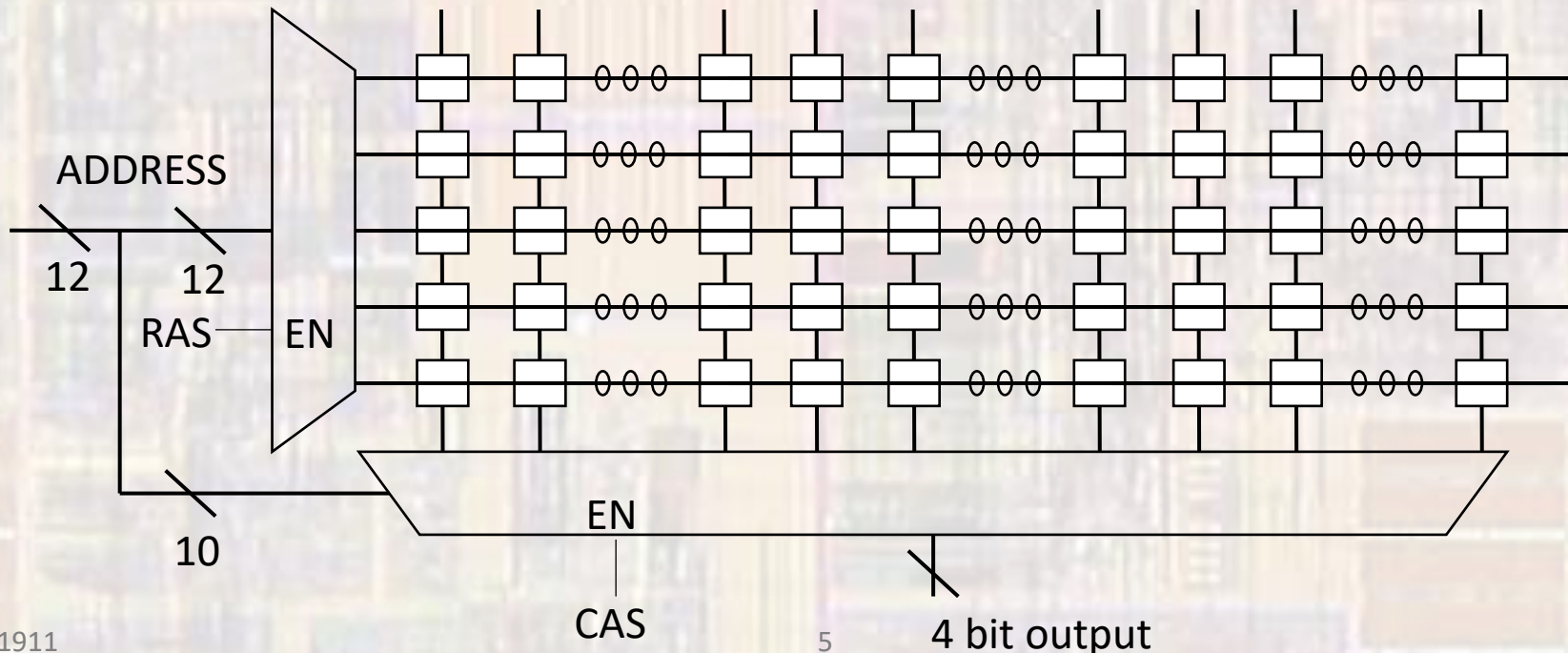
- Reduce I/O by sharing the address inputs between Row addresses and Column addresses
- 22 bit address \rightarrow 12 bit address + RAS and CAS
- RAS – Row Address Strobe (current address is for row decode)
- CAS – Column Address Strobe (current address is for column decode)




Memory - SDRAM

- Write

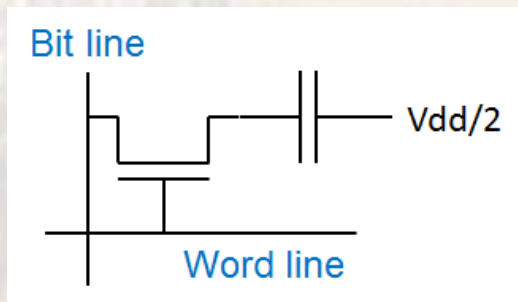- Read Enable (RE) disabled (low)
- Place $\overline{B0}$, $\overline{B1}$, $\overline{B2}$, $\overline{B3}$ on inputs (data in)
- Apply Address (RAS then CAS)
 - Select the desired word line (high)
 - Select the desired column to input to
- Strobe (clk) write enable bar (WE) low
- Bit lines write to the bit cell capacitors




4 bits of 1 column

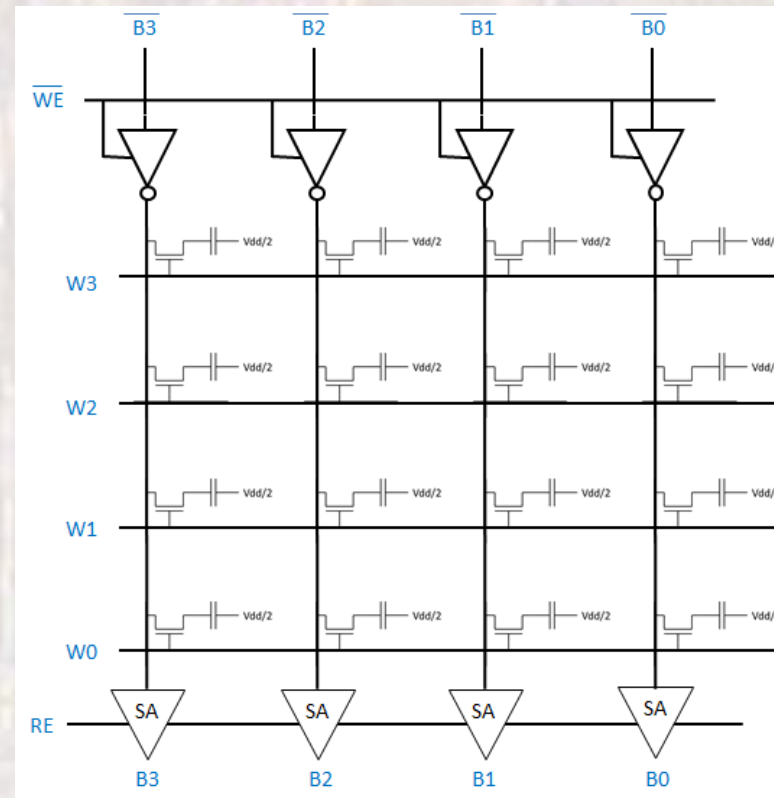

Memory - SDRAM

- Read
 - Write enable bar (\overline{WE}) high
 - inverters tristated
 - Read Enable (RE) high
 - Apply Address (RAS then CAS)
 - Select the desired word line (high)
 - Select the desired column to output
 - Sense amplifiers read the value of the capacitors
 - Clk to output the value
 - The read process is destructive !
 - **WHY?**


4 bits of 1 column

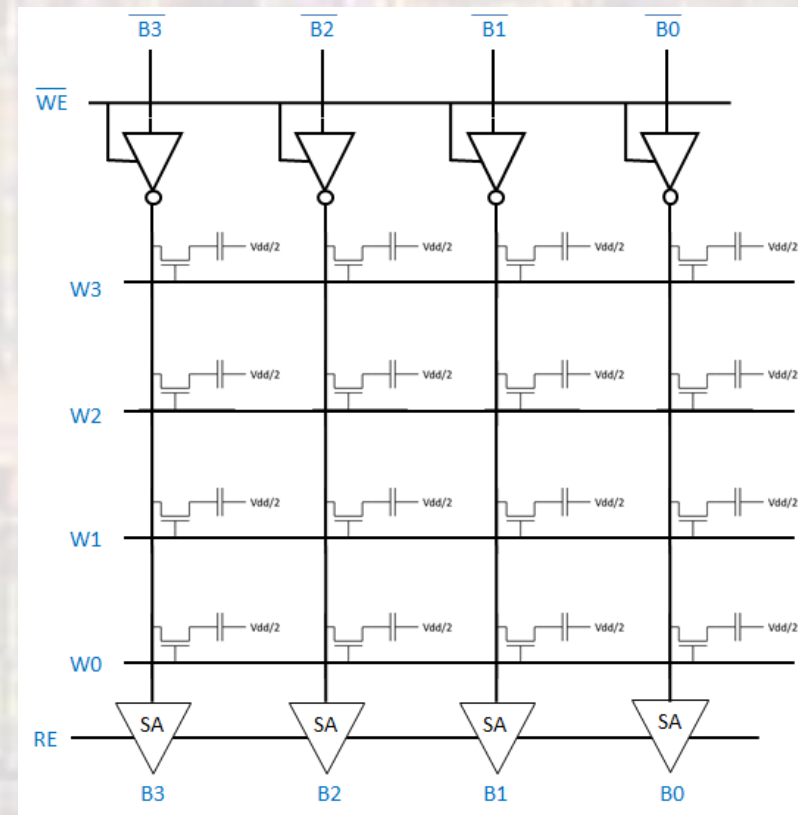


Memory - SDRAM

- SDRAM – Timing

WRITE

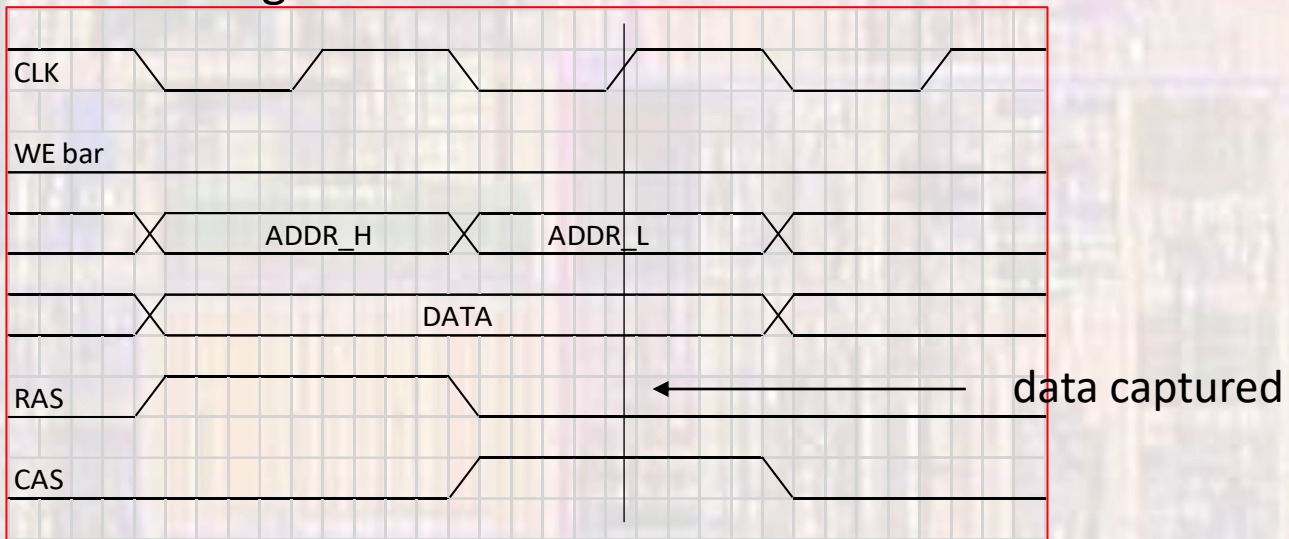


READ

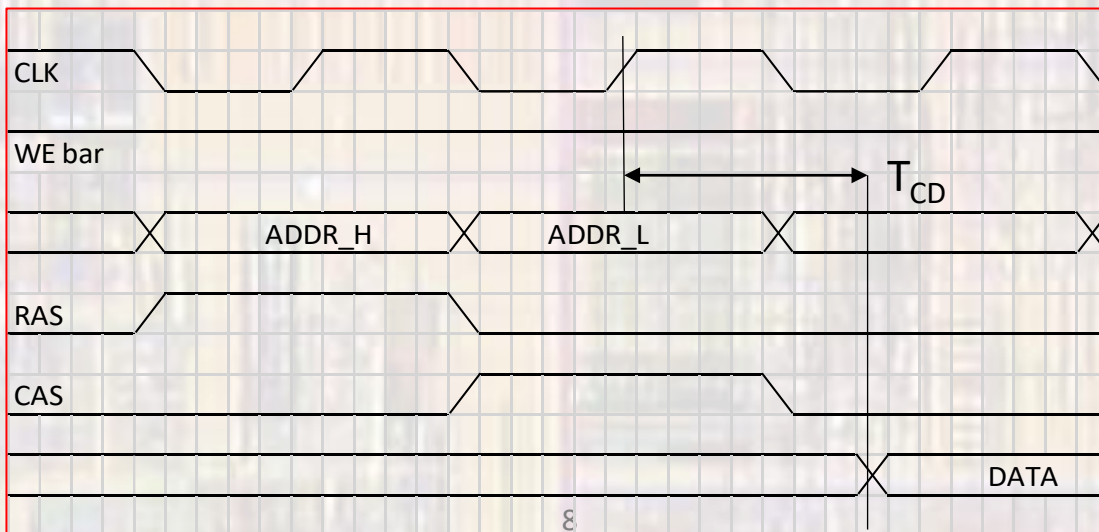

Memory - SDRAM

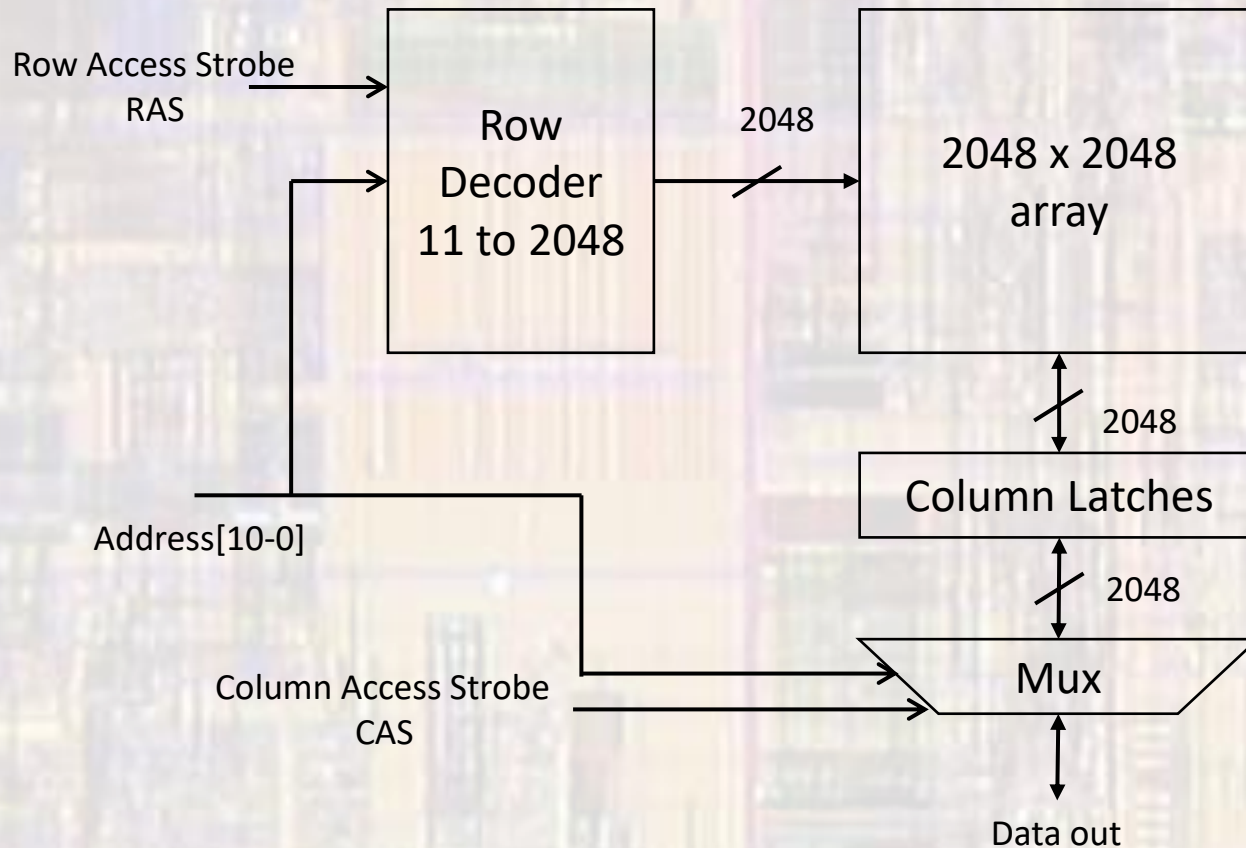- SDRAM – Complex Configuration
 - 4Mb in a x1 configuration



Memory - SDRAM


- SDRAM – Complex Configuration

- Random Access

- 4M bits → 22 address bits


- Operation

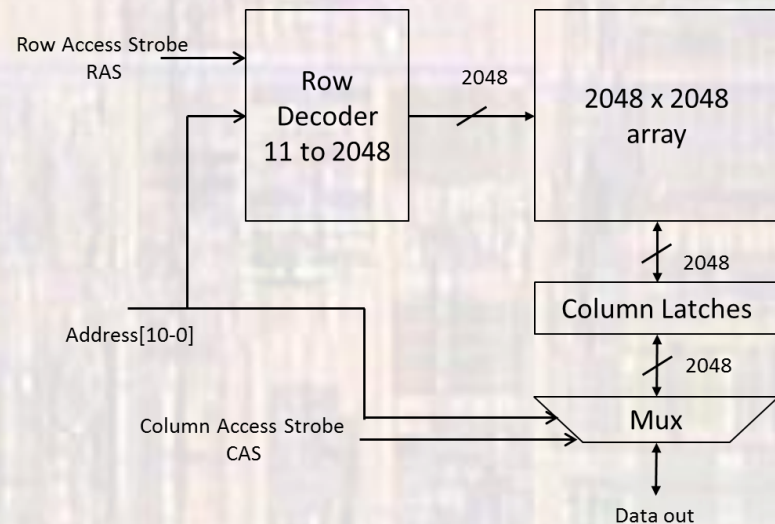- Place upper 11 bits on address bus
- Strobe RAS
 - 2048 bits are latched
- Place lower 11 bits on address bus
- Strobe CAS
 - Selected bit is fed out



Memory - SDRAM

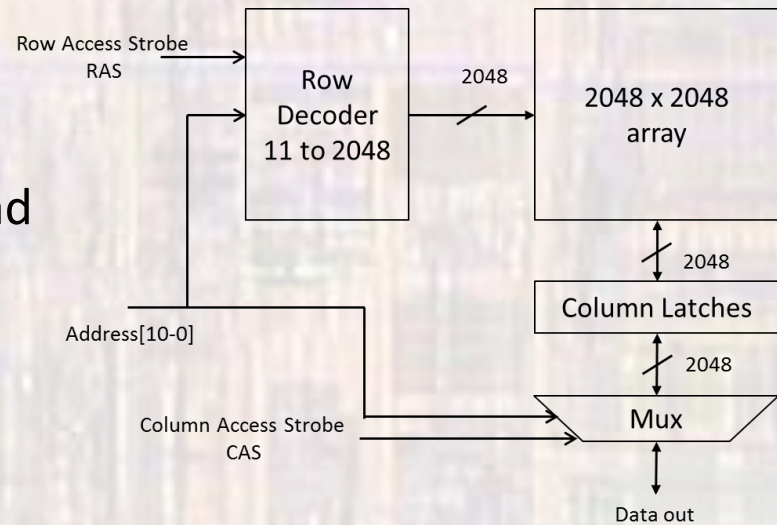- Refresh
- Operation
 - Controller selects a row address - Read
 - 2048 bits are latched
 - The read circuit also re-writes the DRAM cells at the same time




Memory - SDRAM

- Burst Operation

- 4M bits \rightarrow 22 address bits


- Operation

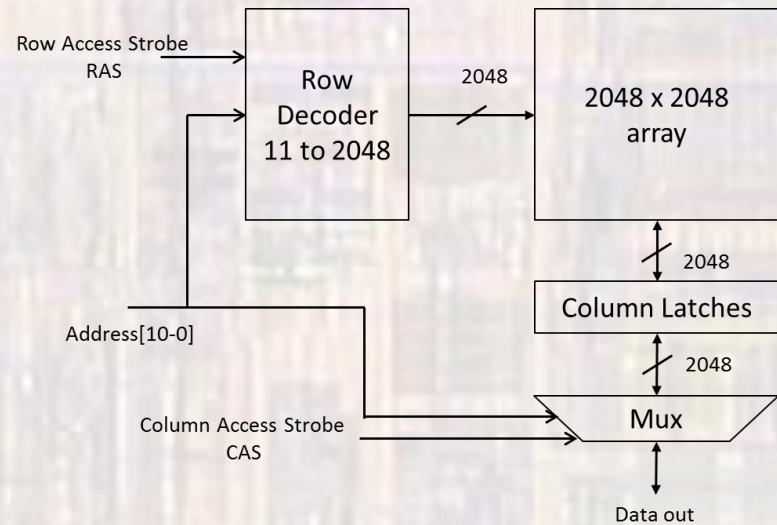- Place upper 11 bits on address bus
- Strobe RAS
 - 2048 bits are latched
- Place lower 11 bits on address bus
- Strobe CAS
 - Selected bit is fed out
- On-chip - Automatically Increment address latch
- Next clock
 - Next bit is fed out
- ...




Memory - SDRAM

- Array Layout – 4M X 8 DRAM

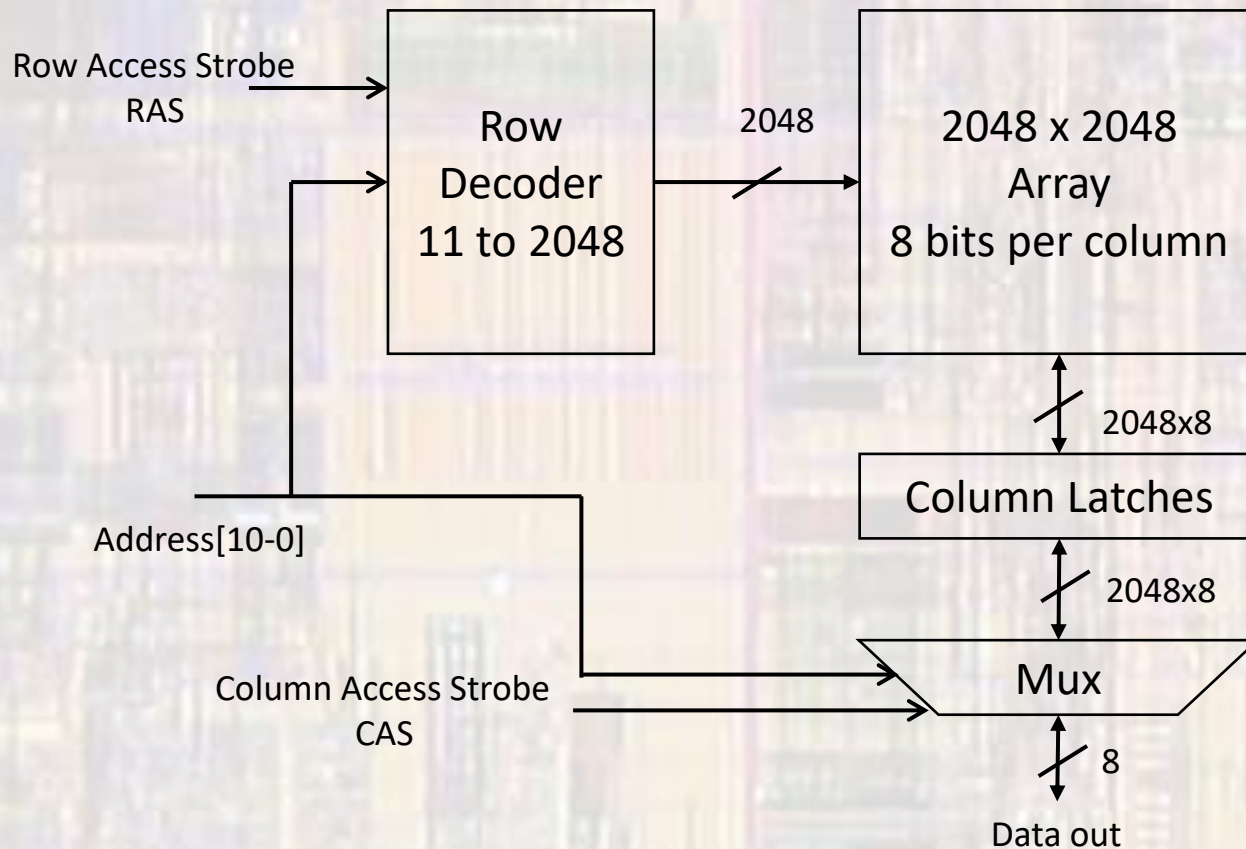


Memory - SDRAM

- Array Layout – 16M X 1 DRAM

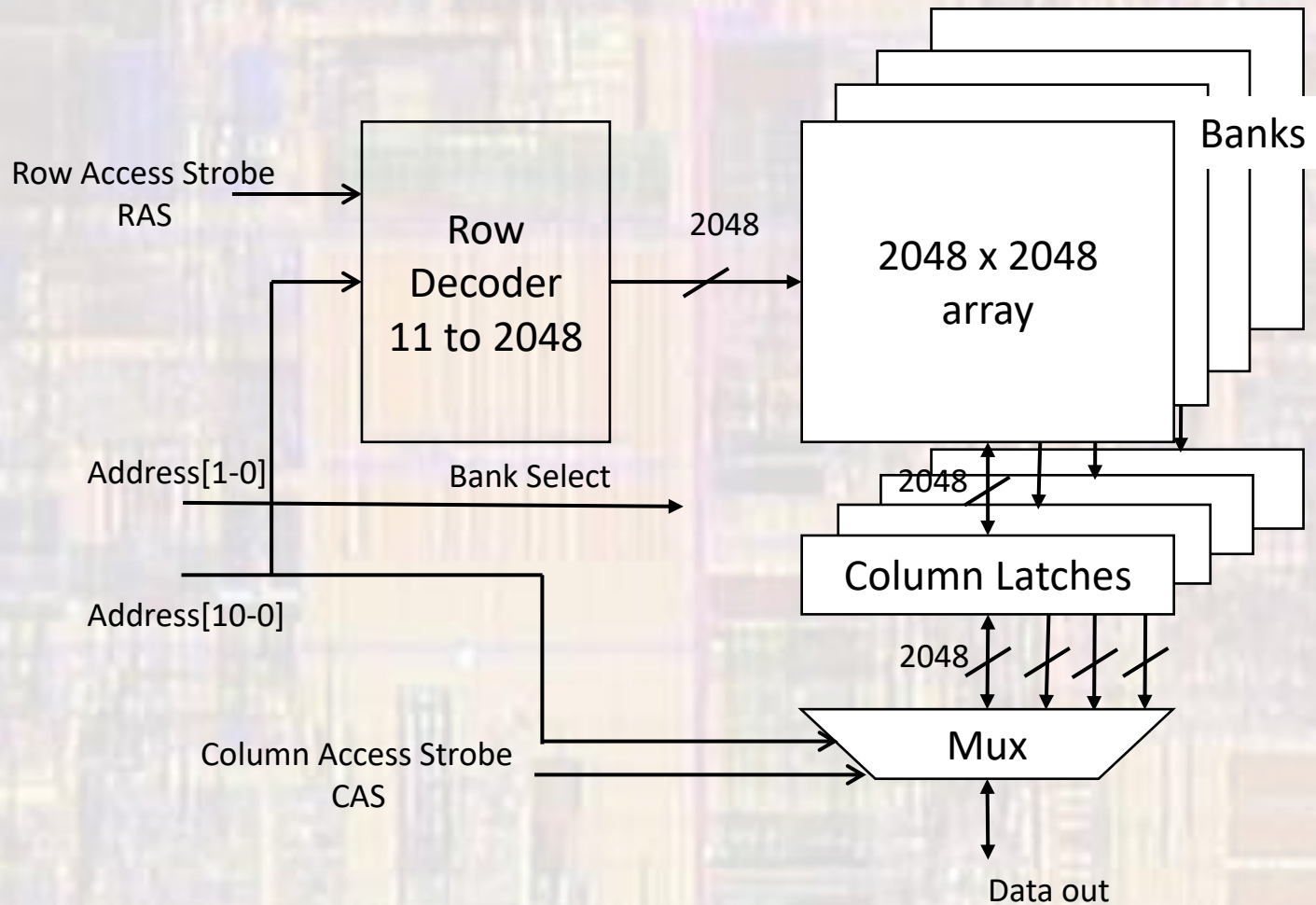


Memory - SDRAM

1Gb DDR SDRAM - 64M x 16

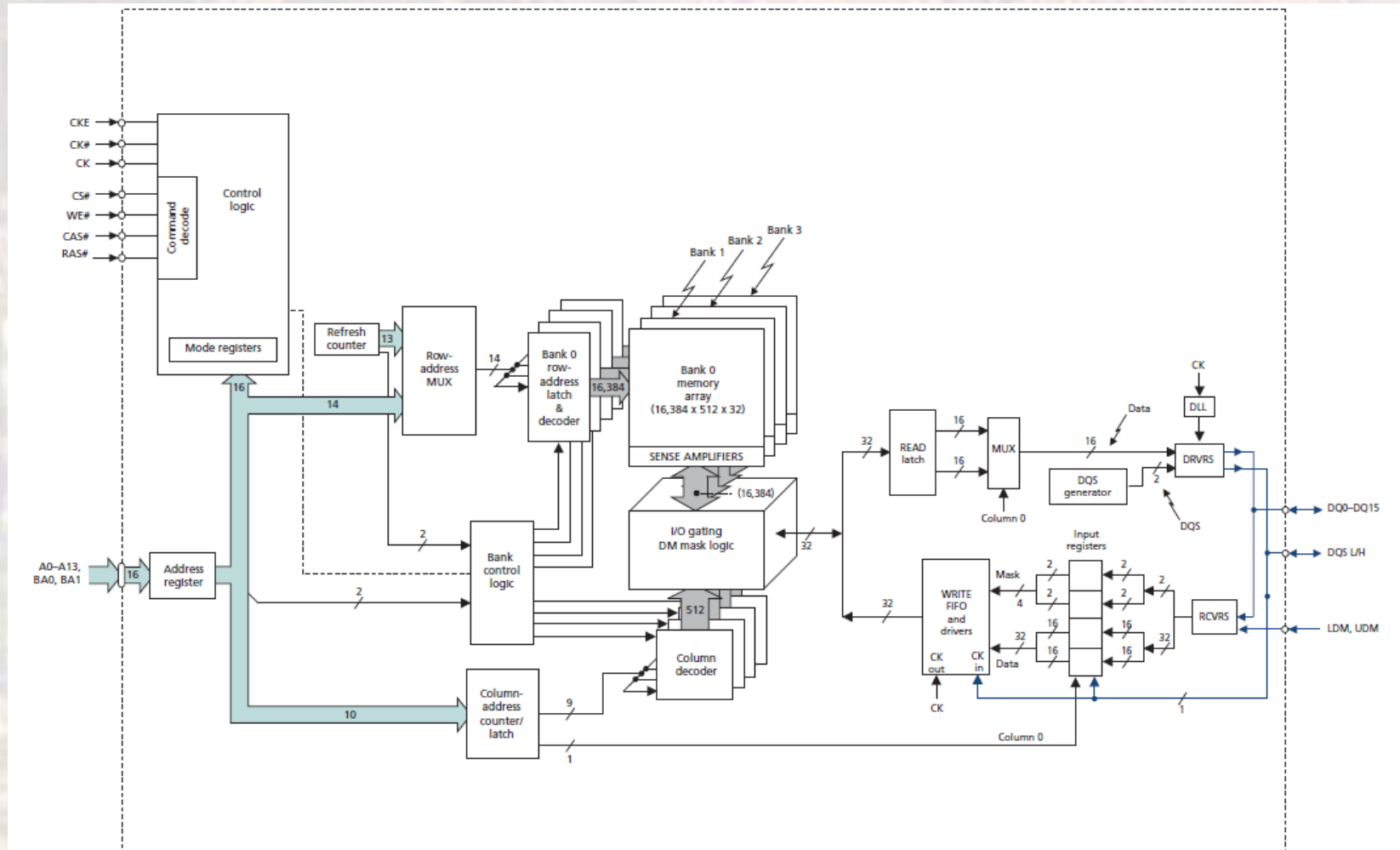

Memory - SDRAM

1Gb DDR2 SDRAM - 64M x 16

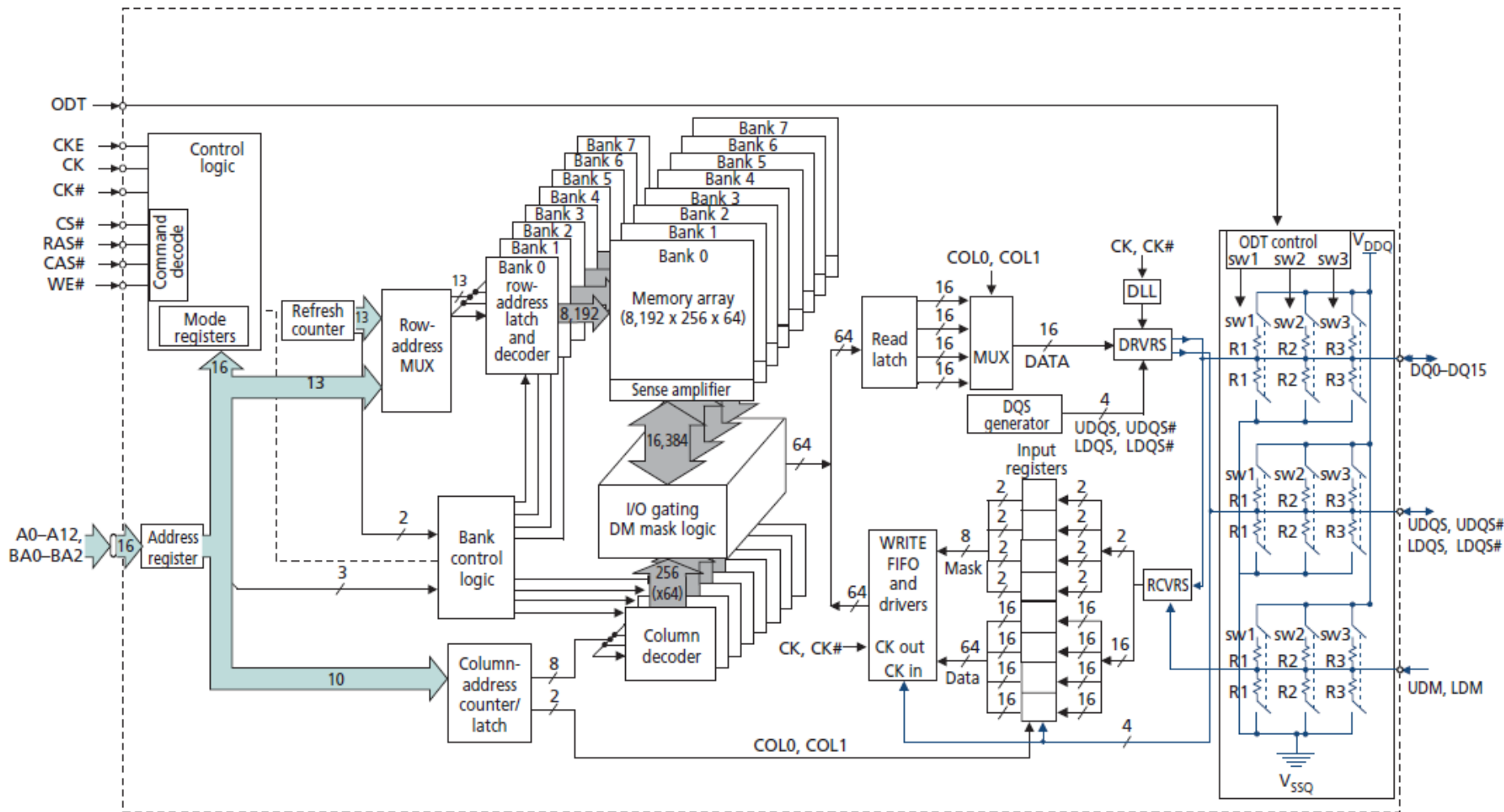

Memory - SDRAM

1Gb DDR3 SDRAM - 64M x 16

