

Memory - SRAM


Last updated 4/14/21

Memory - SRAM

- Static Random Access Memory - SRAM
 - Key Attributes
 - Sequential vs. **Random Access**
 - Read only vs. **Read/Write**
 - **Static** vs. Dynamic
 - **Volatile** vs. non-Volatile
 - Key Measures
 - Density -
 - Speed +
 - Power -
 - Cost / bit -


Memory - SRAM

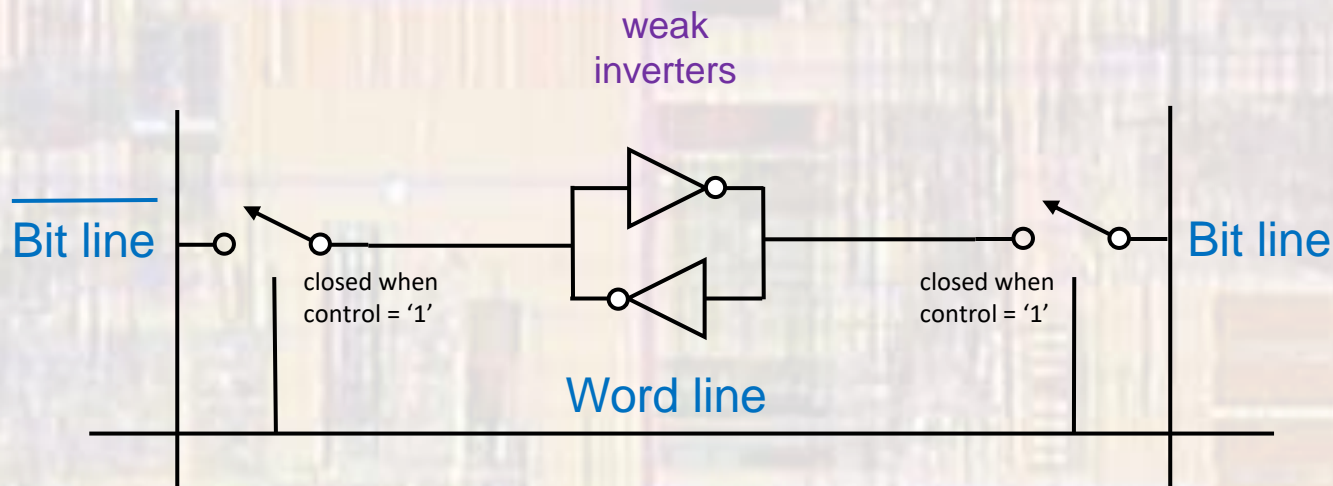- SRAM – Circuit
 - Memory cell (1 bit) is based on a feedback circuit
 - Bit value is retained as long as power is maintained
 - Fastest read/write (R/W)
 - Highest power
 - Lowest density
 - Used in caches and small data memories



Memory - SRAM


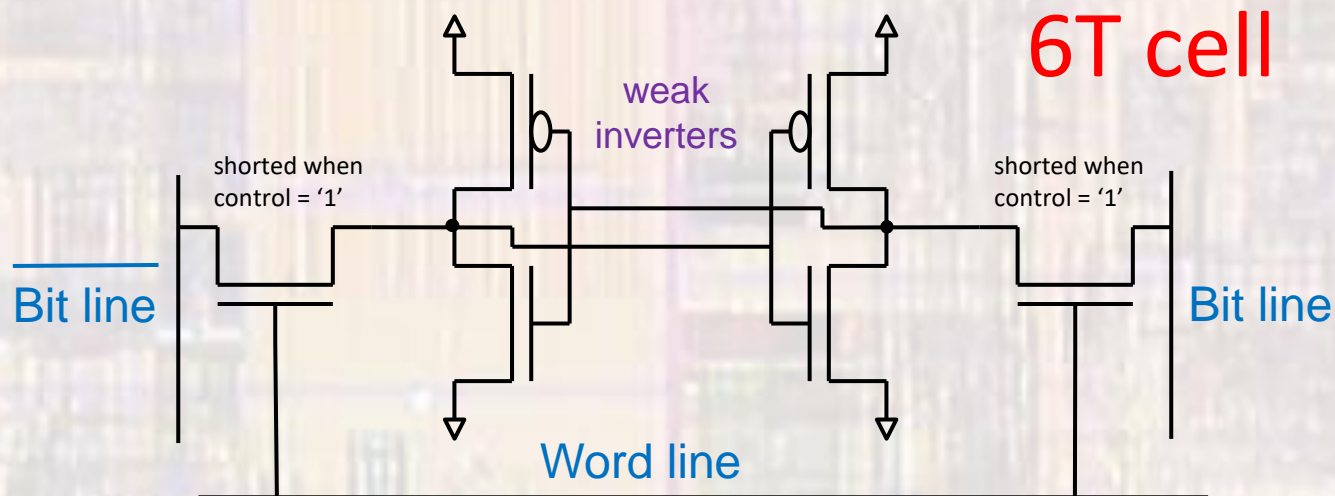
- SRAM – Circuit
 - Memory cell (1 bit) is based on a feedback circuit
 - Bit value is retained as long as power is maintained



Memory - SRAM

- SRAM – Write

 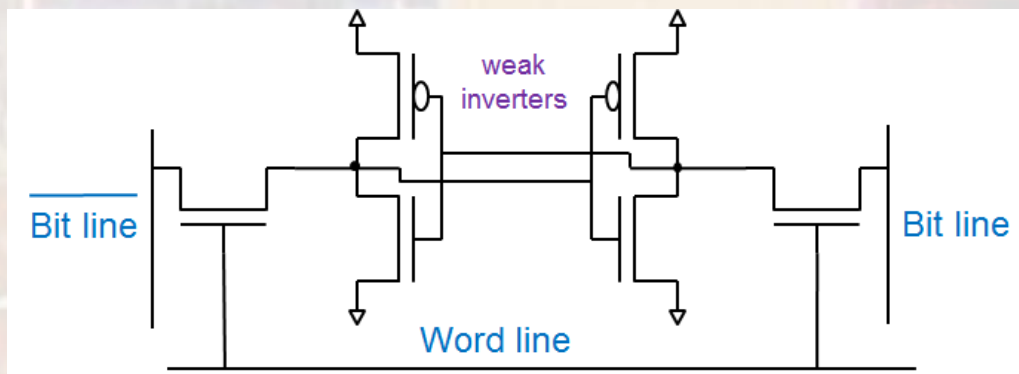- Read Enable (RE) disabled (low)
- Place B0, B1, B2, B3 on inputs (data in)
- Apply Address
 - Select the desired word line (high)
 - Select the desired column to input to
- Strobe write enable bar (\overline{WE}) low
- Bit lines override the bit cell inverters and store the new value in the cell



Memory - SRAM



- Write – x4 configuration – 16 x 16 x 4

R x C x b

RE low
data in =
0011
address = 35
00110101
WE – strobe

RE low
data in =
0101
address = 25
00100101
WE – strobe

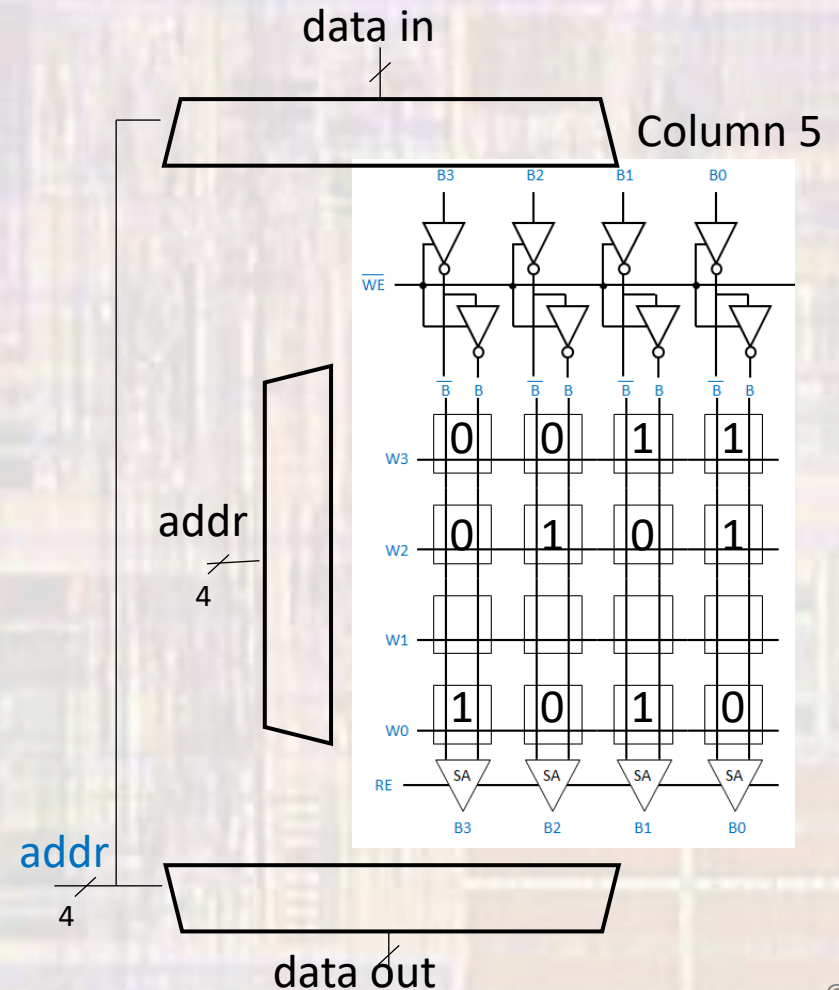
 
RE low
data in =
1010
address = 5
00000101
WE – strobe



Memory - SRAM

- Read

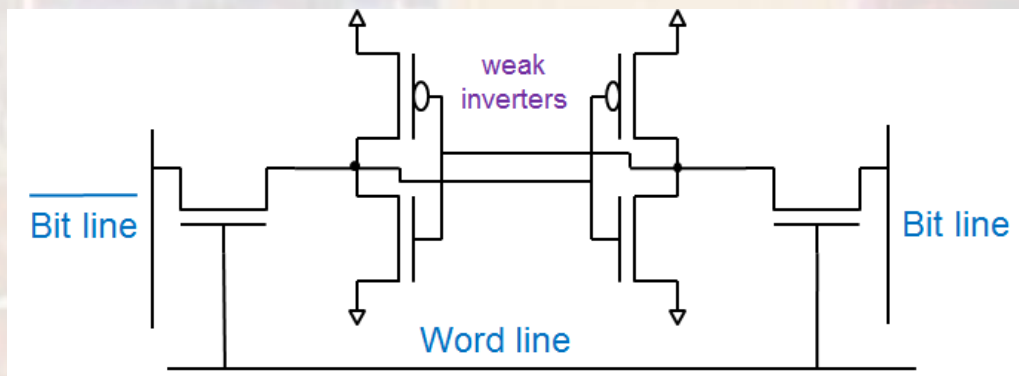
 
- Write enable bar (\overline{WE}) high
 - inverters tristated
- Read Enable (RE) high
- Apply Address
 - Select the desired word line (high)
 - Select the desired column to output
- Bit cell inverters drive the bit lines and sense amplifiers read the value



Memory - SRAM


- Read – x4 configuration – 16 x 16 x 4
R x C x b

WE' high RE high address = 35 00110101	WE' high RE high address = 25 00100101	WE' high RE high address = 5 00000101
→	→	→
data out = 0011	data out = 0101	data out = 1010

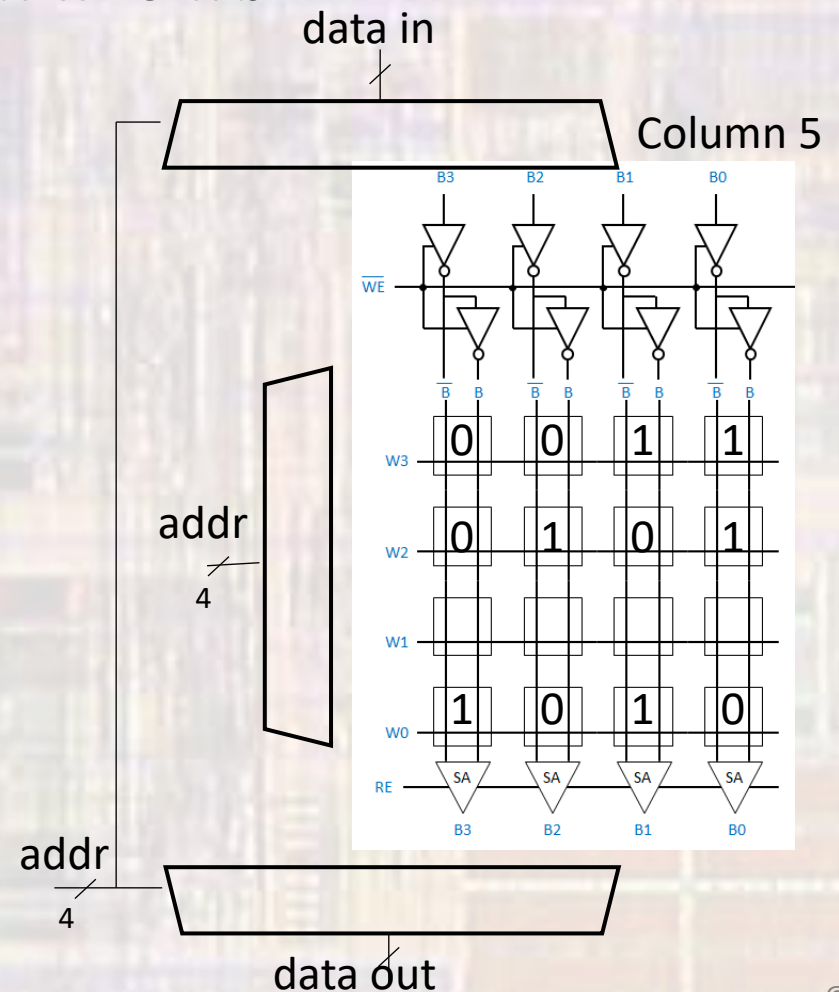 


Memory - SRAM

- SRAM – Timing

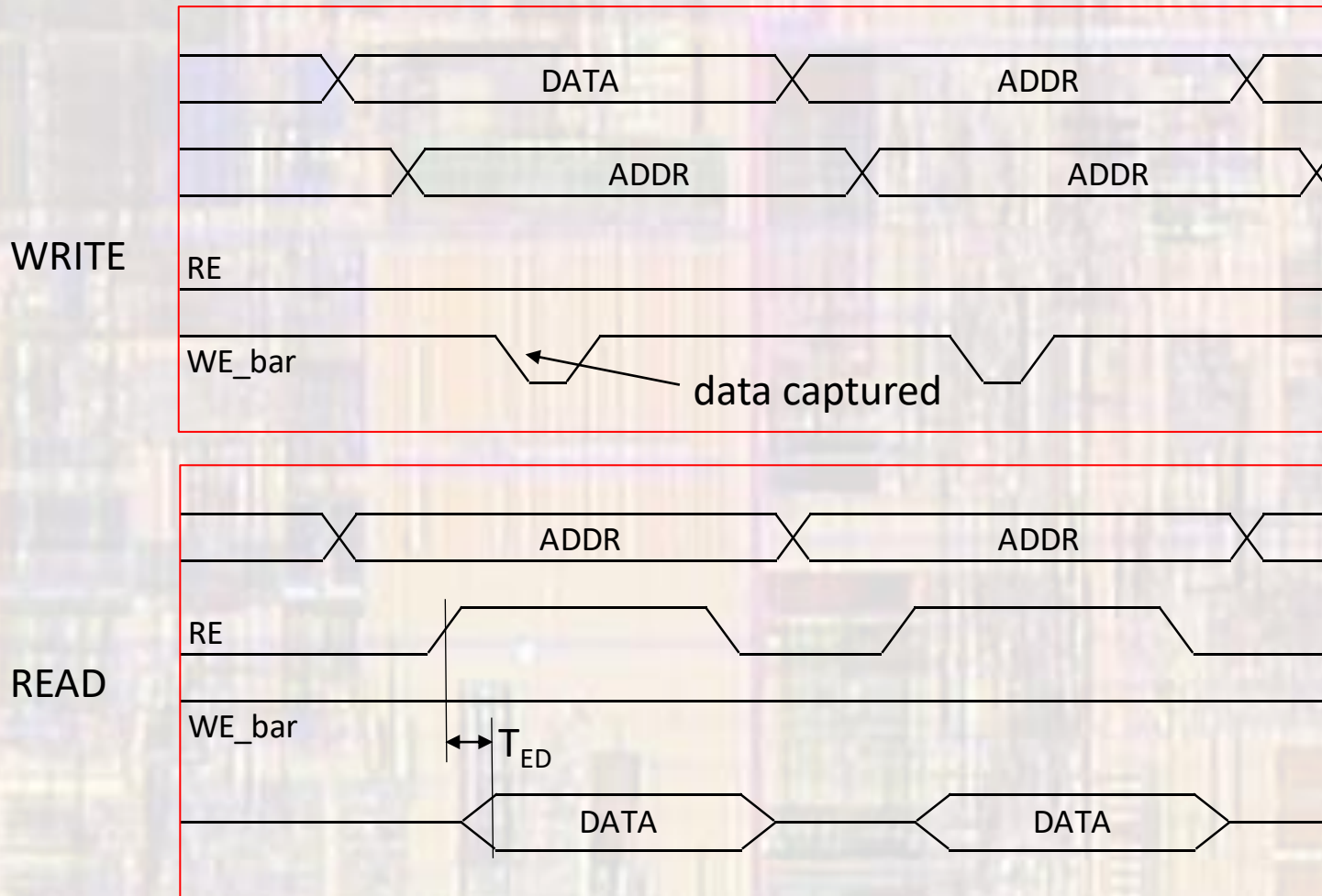

Memory - SRAM

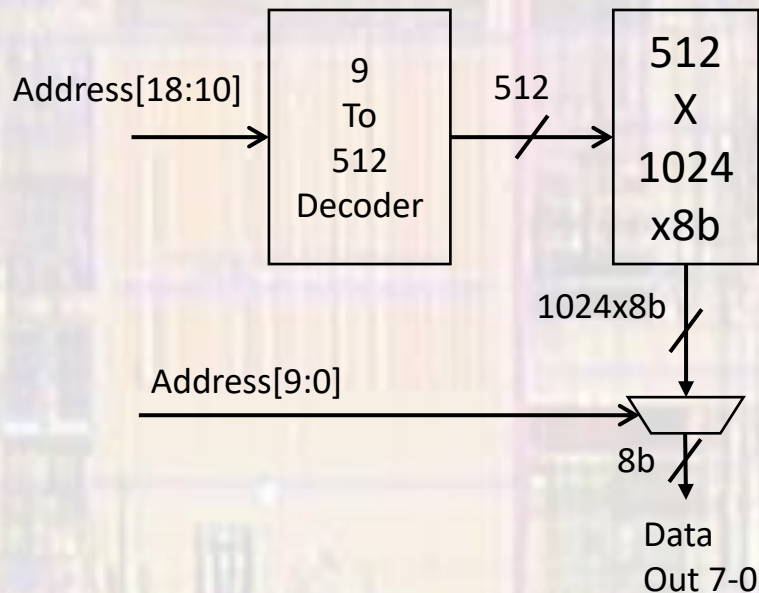- SRAM – Complex configuration
 - Array Layout – 4Mb, in a x8 (4Mb, x8)
 - No address line sharing



Memory - SRAM

- SRAM – Complex configuration
 - Array Layout – 4Mb X 8 (4Mx8b) (implicit x1 format)
 - No address line sharing

