

# CE 1911 Week 9/10 Lab: Single Cycle Processor

Name: \_\_\_\_\_

## Objectives

- Pull together everything from CE1910 and CE1911
- Combinational Logic Design
- Sequential Logic Design
- State Machine Design
- Memory Integration

## Prelab

- None

**student  
check off**

## Assignment

**This lab is to be done individually - no collaboration.**

This assignment involves the development of a single cycle processor similar to the one discussed in class. You will need to design each of the processor components AND a state machine to drive the front end (FETCH) portion of the processor. You may do your design as a single HDL file or you may design your processor as a collection of components that are integrated at the top level.

Top Level Inputs: rstb, clk, start, start\_address, instruction\_count, output\_select

Outputs: done, register\_A,B,C,D, set

Processor Components:

- 256 Word, 16bit/word Instruction Memory (inferred – see HDL ROM, slide 4)
- 4 register (8 bit), Register File with 2 read ports and 1 write port
- 8 bit ALU with support for ADD, SUB, AND, OR, NAND, NOR, SLT, NOP
- 256 Word, 8 bit/word Data Memory (RAM) (inferred – see HDL SRAM, slide 2)
- Control Block
- Support for LD, ST, and LDI memory instructions
- Program Control State Machine (Sequence Selector)

Additional Components:

- Clock Divider for demonstration purposes – 1Hz configuration
- Output Selector

#### Sequence Selector:

The Sequence Selector replaces all the normal program flow control with a state machine. The selector accepts a 3 bit starting address along with a 5 bit program length value. The Sequence selector will provide addresses for the Instruction Memory starting at the modified start address, incrementing by 1 for “program\_length ” clock cycles. The selector multiplies the starting address by 32 to allow for 8 – 32 instruction programs to be accessed from the Program Memory. The program length value determines the actual program length to be executed. Program execution starts on the rising edge of clock after the Start signal is asserted and indicates completion by raising the Done signal. Each program will end with a NOP instruction. The sequencer is to stay at this instruction until reset.

#### Output Selector:

The Output Selector is used to present either the values for Register A and Register B to 4 7-segment displays or the values for Register C and Register D to 4 7-segment displays. This will be toggled by the user after a program has completed to see all 4 register values.

#### Program Memory:

You must preload your Program Memory with instructions for each of the test cases. You are responsible for encoding the instructions in our simplified instruction format. (Embed the programs into your ROM HDL to allow simulation)

#### Signal Mapping:

- RSTB – switch 3
- CLK – 50MHz for simulation, 1Hz for demonstration
- Start\_Address – switches 2-0
- Inst\_Count – switches 9-5
- Start – pushbutton 0
- Done – LED 9-0
- Output\_select – switch 4
- Register A – 7 seg 0-1 (hex)
- Register B – 7 seg 2-3 (hex)
- Register C – 7 seg 0-1 (hex)
- Register D – 7 seg 2-3 (hex)
- Set – 7 seg 5 (0 or 1 displayed) (hex)

Wk 1: Your goal for week 1 should be to get each block working independently in simulation.

Wk 2: Your goal for week 2 should be to integrate all the pieces and verify full operation

#### Test Cases:

On the website

