


Register Transfer Architecture

Last updated 1/18/21

Register Transfer Architecture

- Combinational Logic

 - Outputs are dependent only on current inputs
- Output changes can be triggered by any input change



Register Transfer Architecture


- Sequential Logic
 - Outputs are dependent on inputs and current STATE
 - State
 - Collection of outputs and intermediate values stored within the system
 - Requires some sort of memory
 - Asynchronous - Output changes can be triggered by some input changes
 - Synchronous – Outputs changes triggered by a synchronous event – usually a clock

Register Transfer Architecture

- State memory elements
 - Bi-stable circuit
 - Latches
 - Flip-flops
 - Registers
 - Memories
 - ROM
 - RAM
 - SRAM
 - SDRAM
 - Flash

Register Transfer Architecture

- Typical Flip-Flop Circuit

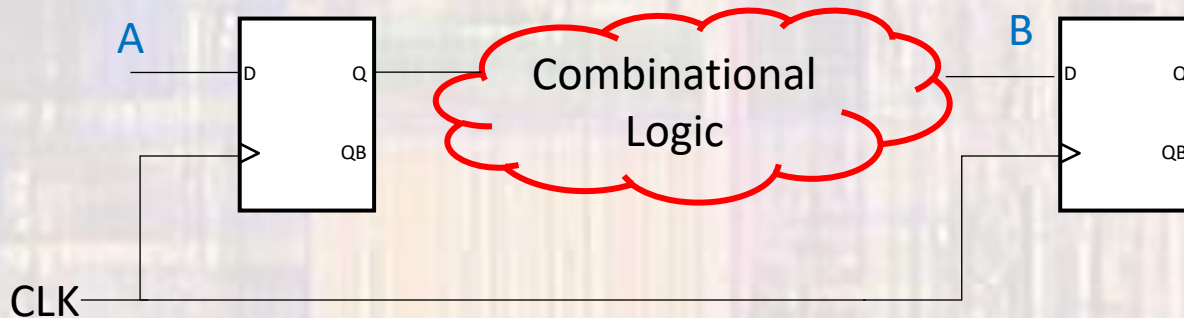

- Need the data to get from point A to point B before the next clock edge occurs


Register Transfer Architecture

- Register Transfer Architecture
 - Synchronous System
 - Blocks of combinational logic and registers
 - Every intermediate state is captured in a register




Register Transfer Architecture

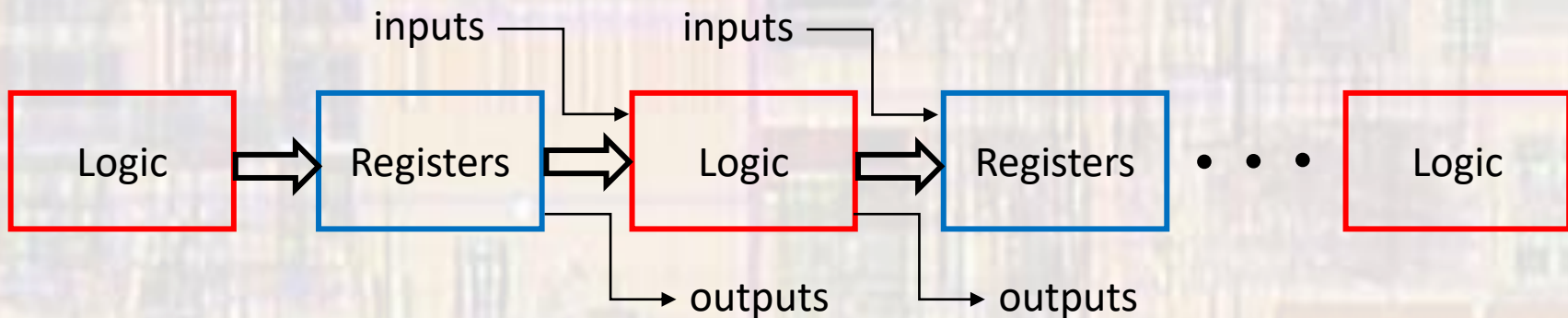- Register Transfer Architecture
 - Synchronous System
 - Blocks of combinational logic and registers
 - Every intermediate state is captured in a register
 - Many I/O paths




Register Transfer Architecture

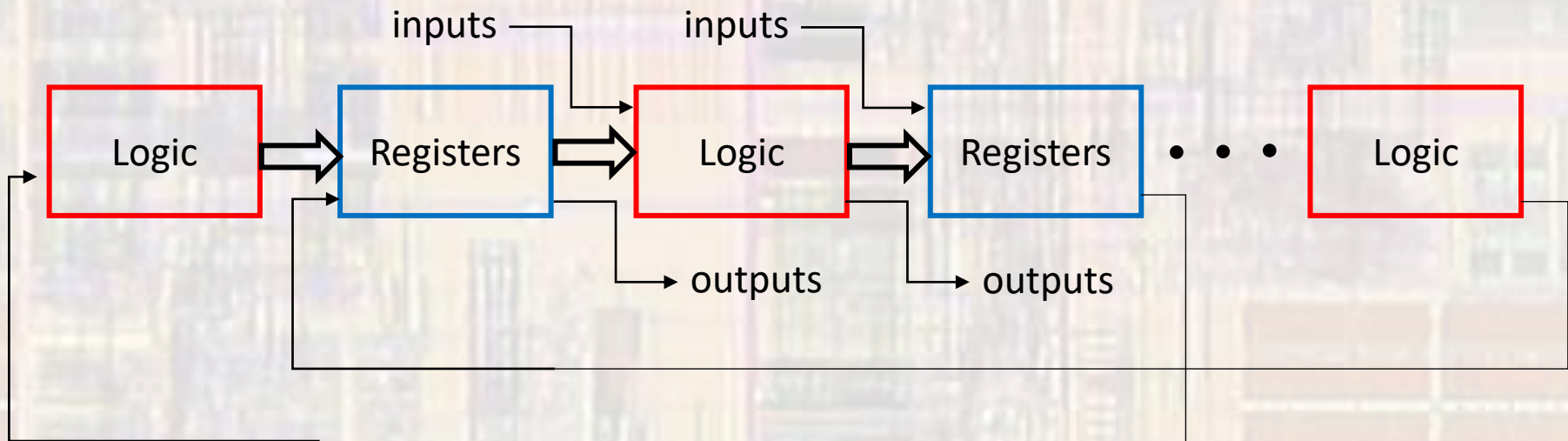- Register Transfer Architecture
 - Synchronous System
 - Blocks of combinational logic and registers
 - Every intermediate state is captured in a register
 - Many I/O paths
 - Many feedback paths



Register Transfer Architecture


- Timing

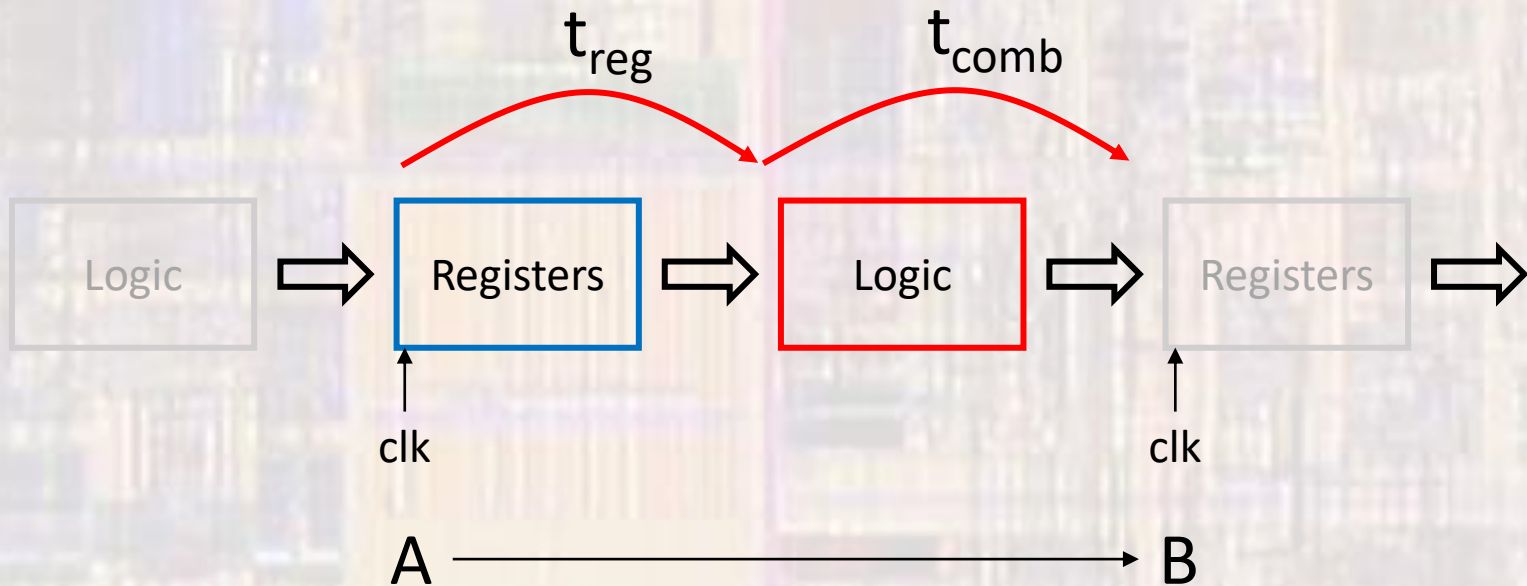

Data must make it from A to B before the next active clock edge (rising)

Register Transfer Architecture

- Timing

 

$$T_{nom} = t_{CQ} + t_{comb}$$

$$T_{nom} = t_{CQ} + t_{interconnect1} + t_{comb} + t_{interconnect2} + t_{setup}$$