


Registers - HDL

Last updated 1/18/21


Registers - HDL

- Register
 - Collection of n Flip-Flops
 - Configured in parallel
 - Common clock, set/reset, enable
 - Stores an n-bit state variable


n-bit register

 

n bit wide bus

 

signal indices n-1 down to 0

 


Registers - HDL

- 8 bit register w/enable

```
-----  
-- reg_8_bit_en.vhdl  
-- created: 1/26/18  
-- by: johnsontimoj  
-- rev: 0  
--  
-- 8 bit register w/enable example  
--  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
----- fixed 8 bit register -----  
entity reg_8_bit_en is  
  port (  
    i_d   : in std_logic_vector(7 downto 0);  
    i_en  : in std_logic;  
    i_clk : in std_logic;  
    i_rstb: in std_logic;  
  
    o_q   : out std_logic_vector(7 downto 0)  
  );  
end entity;
```

```
architecture behavioral of reg_8_bit_en is  
begin  
  process(i_clk, i_rstb)  
  begin  
    if (i_rstb = '0') then  
      o_q <= "00000000";  
    elsif (rising_edge(i_clk)) then  
      if (i_en = '1') then  
        o_q <= i_d;  
      else  
        null;  
      end if;  
    else  
      null;  
    end if;  
  end process;  
end behavioral;
```

not necessary

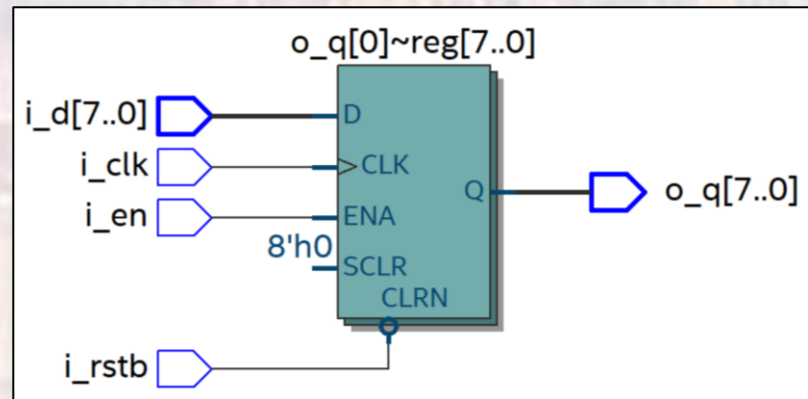


Registers - HDL

- 8 bit register – no enable

Note: no elses - matches template

```
-----  
-- reg_8_bit.vhdl  
--  
-- created: 1/26/18  
-- by: johnsontim  
-- rev: 0  
--  
-- 8 bit register example  
--  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
  
----- fixed 8 bit register -----  
entity reg_8_bit is  
    port (  
        i_d      : in std_logic_vector(7 downto 0);  
        i_clk    : in std_logic;  
        i_rstb   : in std_logic;  
  
        o_q      : out std_logic_vector(7 downto 0)  
    );  
end entity;
```
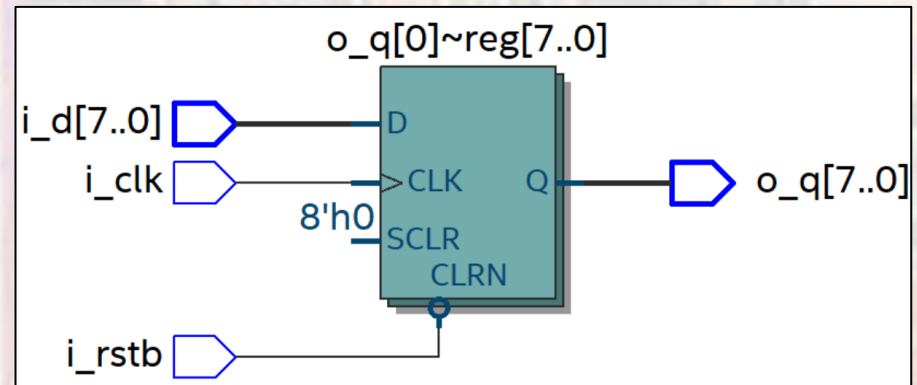
```
architecture behavioral of reg_8_bit is  
begin  
    process(i_clk, i_rstb)  
    begin  
        if (i_rstb = '0') then  
            o_q <= "00000000";  
        elsif (rising_edge(i_clk)) then  
            o_q <= i_d;  
        end if;  
    end process;  
end behavioral;
```



Registers - HDL

- N bit register

```
---
--- reg_n_bit.vhdl
--- created: 1/26/18
--- by: johnsontimoj
--- rev: 0
---
--- n bit register example
---
-----
library ieee;
use ieee.std_logic_1164.all;

-----
--- generic N bit register
entity reg_n_bit is
  generic(
    N: integer := 8
  );
  port (
    i_d   : in std_logic_vector((N - 1) downto 0);
    i_clk : in std_logic;
    i_rstb: in std_logic;


    o_q   : out std_logic_vector((N - 1) downto 0)
  );
end entity;

architecture behavioral of reg_n_bit is
begin
  process(i_clk, i_rstb)
  begin
    if (i_rstb = '0') then
      o_q <= (others => '0');
    elsif (rising_edge(i_clk)) then
      o_q <= i_d;
    end if;
  end process;
end behavioral;
```

generic section added

- defines N
- defaults N to 8
- can be overwritten when instantiated

Vector sizes now defined with N

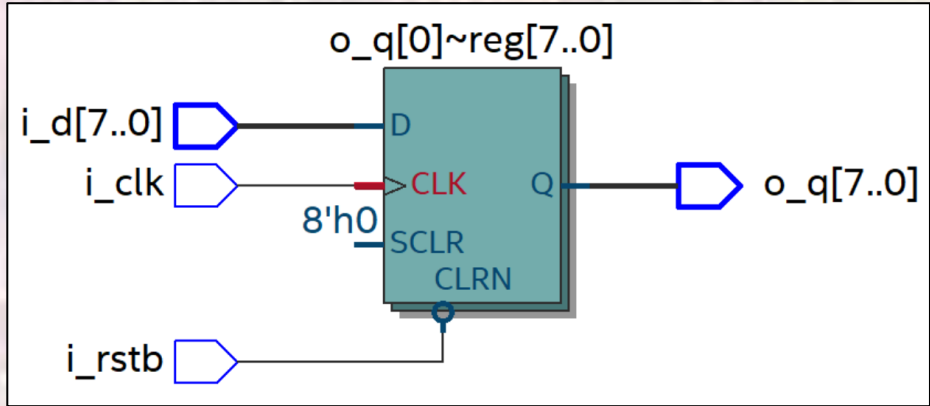

(others => '0') used since N can change

Registers - HDL

- 64 bit register – using instantiation

Component Prototype

```
--  
-- COMPONENT PROTOTYPE -----  
--  
component reg_n_bit is  
  generic(  
    N: integer := 8  
  );  
  port (  
    i_d   : in std_logic_vector((N - 1) downto 0);  
    i_clk : in std_logic;  
    i_rstb: in std_logic;  
  
    o_q : out std_logic_vector((N - 1) downto 0)  
  );  
end component;  
-----
```

Instantiation

```
--  
-- COMPONENT INSTANTIATION -----  
--  
myBigRegister: reg_n_bit  
  generic map(  
    N => 64  
  )  
  port map(  
    i_rstb => i_RSTB,  
    i_clk  => i_CLK,  
    i_d    => i_D,  
    o_q    => o_Q  
  );  
-----
```

Generic - overwrite

Explicit port mapping

Registers - HDL



- 64 bit register – using instantiation

```
-----  
-- reg_64_bit.vhd1  
-- created: 1/26/18  
-- by: johnsontimoj  
-- rev: 0  
--  
-- 64 bit register using instantiation  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
  
entity reg_64_bit is  
  port (  
    i_D : in std_logic_vector(63 downto 0);  
    i_CLK : in std_logic;  
    i_RSTB : in std_logic;  
  
    o_Q : out std_logic_vector(63 downto 0)  
  );  
end entity;
```

```
architecture behavioral of reg_64_bit is  
  
  --  
  -- COMPONENT PROTOTYPE -----  
  --  
  component reg_n_bit is  
    generic(  
      N: integer := 8  
    );  
    port (  
      i_d : in std_logic_vector((N - 1) downto 0);  
      i_clk : in std_logic;  
      i_rstb : in std_logic;  
  
      o_q : out std_logic_vector((N - 1) downto 0)  
    );  
  end component;  
  
  -----  
begin  
  
  --  
  -- COMPONENT INSTANTIATION -----  
  --  
  myBigRegister: reg_n_bit  
  generic map(  
    N => 64  
  )  
  port map(  
    i_rstb => i_RSTB,  
    i_clk => i_CLK,  
    i_d => i_D,  
    o_q => o_Q  
  );  
  
  -----  
end behavioral;
```

Registers - HDL

- 64 bit register – using instantiation

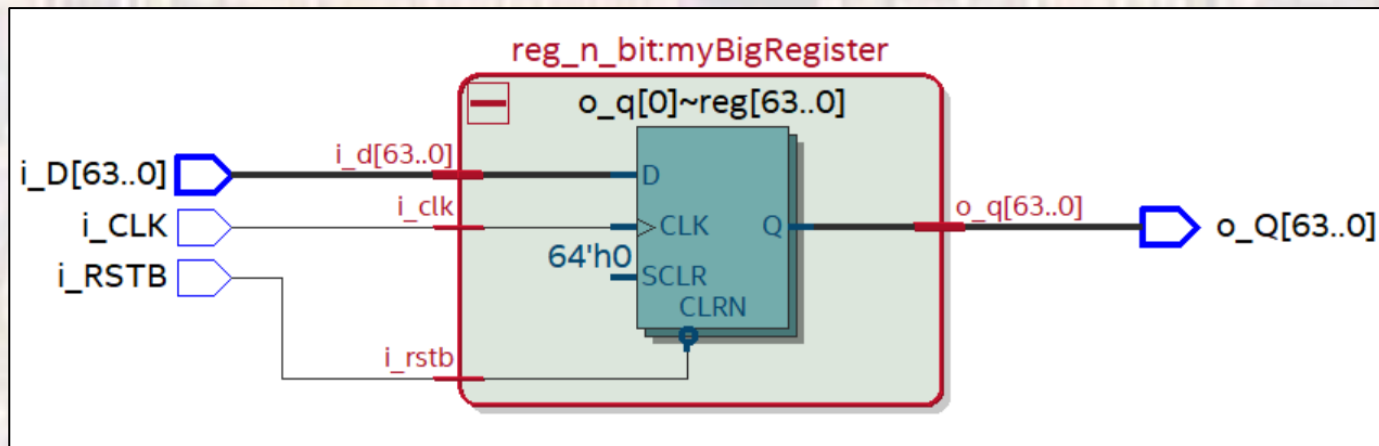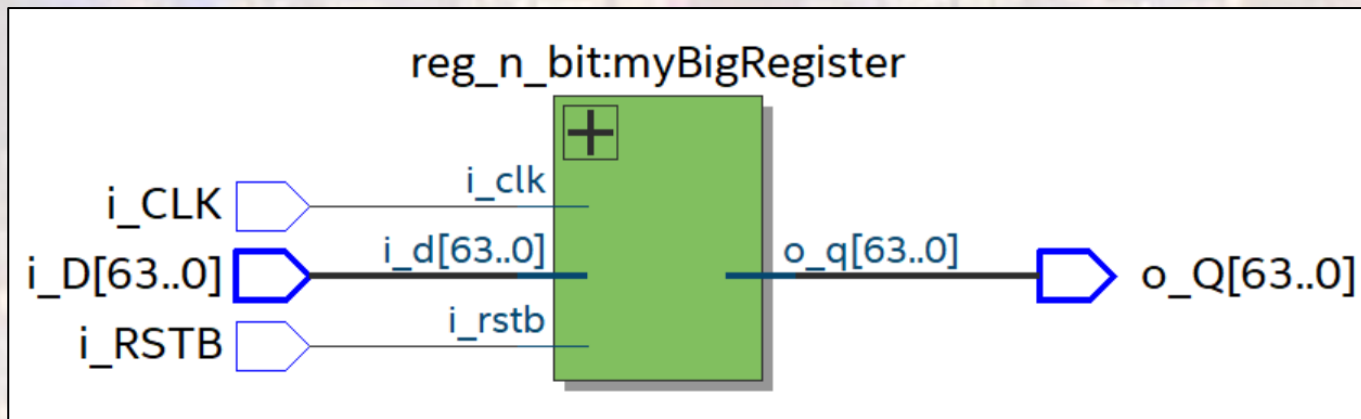

Registers - HDL

- 64 bit register – testbench

```

-----
-- reg_64_bit_tb.vhdl
--
-- created: 1/26/18
-- by: johnsontimoj
-- rev: 0
--
-- testbench for 64 bit register
-- of reg_64_bit.vhdl
--
-- brute force implementation
--
-----
library ieee;
use ieee.std_logic_1164.all;

entity reg_64_bit_tb is
  -- no entry - testbench
end entity;

architecture testbench of reg_64_bit_tb is
  signal CLK:      std_logic;
  signal RSTB:     std_logic;
  signal D:        std_logic_vector(63 downto 0);

  signal Q:        std_logic_vector(63 downto 0);

  constant PER:   time := 20 ns;

  -----
  -- Component prototype
  -----
  COMPONENT reg_64_bit
  port (
    i_D   : in std_logic_vector(63 downto 0);
    i_CLK : in std_logic;
    i_RSTB: in std_logic;

    o_Q   : out std_logic_vector(63 downto 0)
  );
  END COMPONENT;

  -----
begin

```

```

-----
-- Device under test (DUT)
-----
DUT: reg_64_bit
port map(
  i_clk    => CLK,
  i_rstb   => RSTB,
  i_d      => D,

  o_q      => Q
);

-----
-- Test processes
-----

-- Clock process - 50MHz
clock: process -- no sensitivity list
begin
  CLK <= '0';
  wait for PER;
  infinite: loop
    CLK <= not CLK; wait for PER/2;
  end loop;
end process clock;

-- Reset process
reset: process -- no sensitivity list
begin
  RSTB <= '0'; wait for 1.5*PER;
  RSTB <= '1'; wait;
end process reset;

-- Run process
run: process -- no sensitivity list
begin
  -----
  -- Initialize input
  D <= (others => '0');


  wait for PER*3.5; -- wait for reset

  -- setup various D values
  D <= x"A5A5A5A5A5A5A5A5";
  wait for 6*PER;
  D <= x"5A5A5A5A5A5A5A5A";
  wait for 4*PER;
  D <= (others => '1');
  wait for 2*PER;
  D <= (others => '0');
  wait for 2*PER;

end process run;

-----
-- End test processes
-----
end architecture;

```

 


All bits toggling

Registers - HDL

- Shift Register

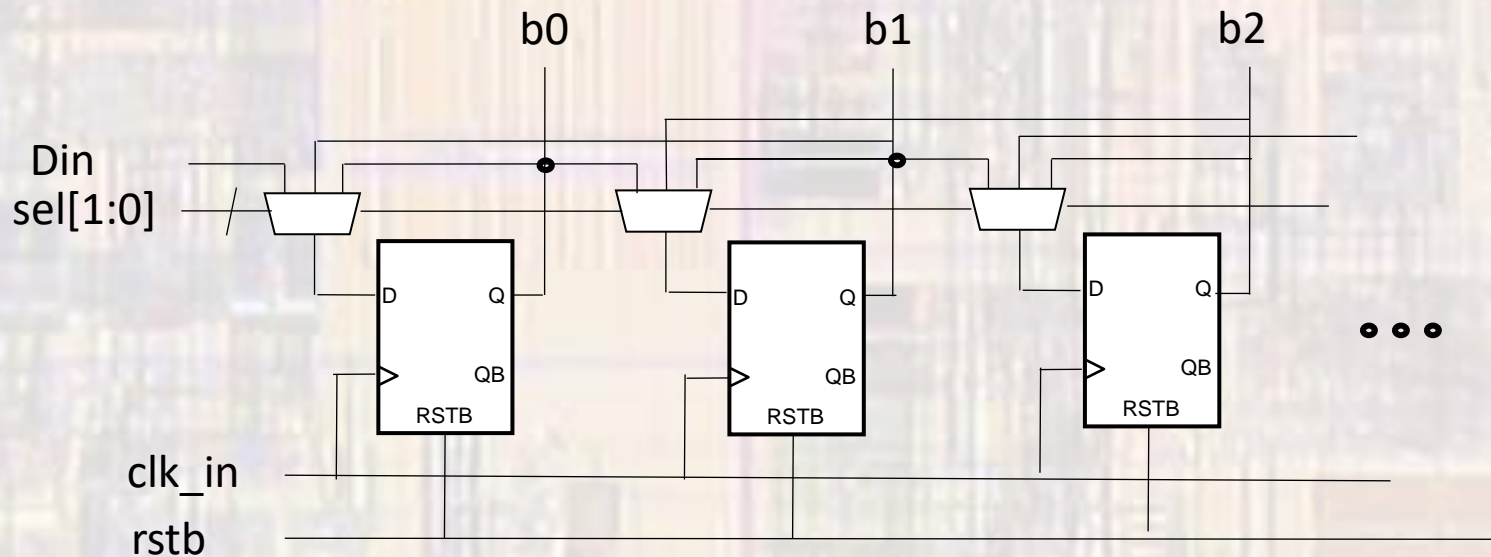- Shift a series of bits within a register
- sel[0]: shift right / left
- sel[1]: shift / no-shift



Registers - HDL

- Shift Register

```
-- shift_reg_8_bit.vhd1
-- created 2/29/17
-- tj
--
-- rev 0
-----
-- 8 bit L/R shift register example
-----
-- Inputs: rstb, clk, bit_in, shift, dir
-- Outputs: data_out[7:0]
-----
library ieee;
use ieee.std_logic_1164.all;

entity shift_reg_8_bit is
  port (
    i_clk : in std_logic;
    i_rstb : in std_logic;
    i_bit_in : in std_logic;
    i_shift : in std_logic;
    i_dir : in std_logic; -- 0 for left, 1 for right

    o_data_out : out std_logic_vector(7 downto 0)
  );
end entity;
```



```
architecture behavioral of shift_reg_8_bit is
  -- internal signals
  signal data_out_sig: std_logic_vector(7 downto 0);
begin
  process(i_clk, i_rstb)
  begin
    -- reset
    if (i_rstb = '0') then
      data_out_sig <= (others => '0');
    -- rising clk edge
    elsif (rising_edge(i_clk)) then
      -- shifting
      if (i_shift = '0') then
        data_out_sig <= data_out_sig;
      elsif (i_dir = '0') then
        data_out_sig <= data_out_sig(6 downto 0) & i_bit_in;
      else
        data_out_sig <= i_bit_in & data_out_sig(7 downto 1);
      end if;
    end if;
  end process;

  -- output logic
  o_data_out <= data_out_sig;
end behavioral;
```

why?

Registers - HDL

- Shift Register

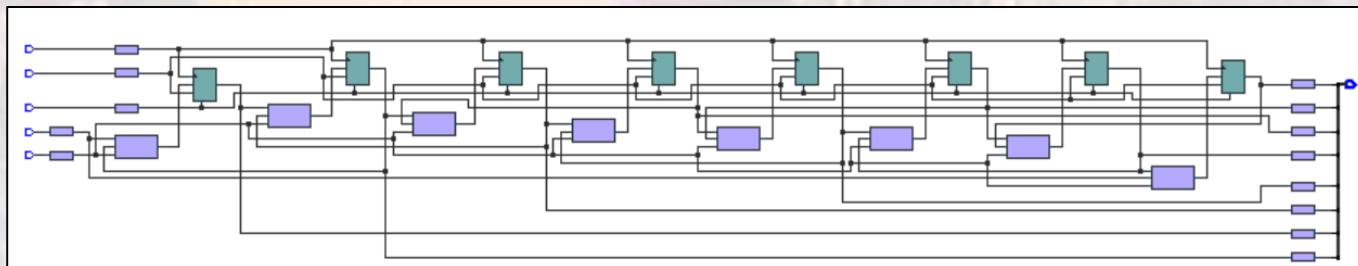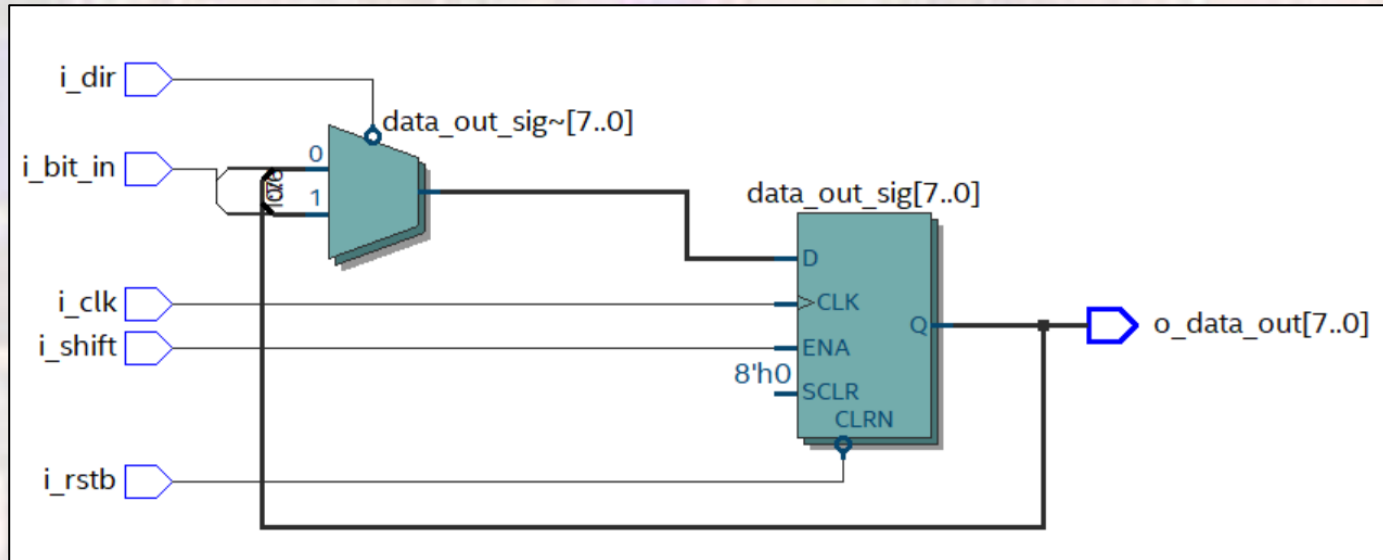

Registers - HDL

- Shift Register - testbench

```
-----  
-- Component prototype  
-----  
COMPONENT shift_reg_8_bit  
  port (  
    i_clk :      in std_logic;  
    i_rstb :     in std_logic;  
    i_bit_in :   in std_logic;  
    i_shift :   in std_logic;  
    i_dir :     in std_logic; -- 0 for left, 1 for right  
  
    o_data_out : out std_logic_vector(7 downto 0)  
  );  
END COMPONENT;  
-----  
  
begin  
-----  
-- Device under test (DUT)  
-----  
DUT: shift_reg_8_bit  
  port map(  
    i_clk      => CLK,  
    i_rstb     => RSTB,  
    i_bit_in   => BIT_IN,  
    i_shift    => SHIFT,  
    i_dir      => DIR,  
  
    o_data_out => DATA_OUT  
  );
```

```
-----  
-- shift_reg_8_bit_tb.vhdl  
-- created: 1/26/18  
-- by: johnsontimoj  
-- rev: 0  
--  
-- testbench for 8 bit shift register  
-- of shift_reg_8_bit.vhdl  
--  
-- brute force implementation  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
  
entity shift_reg_8_bit_tb is  
  -- no entry - testbench  
end entity;  
  
architecture testbench of shift_reg_8_bit_tb is  
  signal CLK:      std_logic;  
  signal RSTB:     std_logic;  
  signal BIT_IN:   std_logic;  
  signal SHIFT:    std_logic;  
  signal DIR:      std_logic;  
  
  signal DATA_OUT:std_logic_vector(7 downto 0);  
  
  constant PER:   time := 20 ns;
```

```
-----  
-- Test processes  
-----  
  
-- Clock process - 50MHz  
clock: process -- note - no sensitivity list allowed  
begin  
  CLK <= '0';  
  wait for PER;  
  infinite: loop  
    CLK <= not CLK; wait for PER/2;  
  end loop;  
end process clock;  
  
-- Reset process  
reset: process -- note - no sensitivity list allowed  
begin  
  RSTB <= '0'; wait for 1.5*PER;  
  RSTB <= '1'; wait;  
end process reset;  
  
-- Run process  
run: process -- note - no sensitivity list allowed  
begin  
  -----  
  -- Initialize inputs  
  BIT_IN <= '0';  
  SHIFT <= '0';  
  DIR <= '0';  
  
  wait for PER*3; -- wait for reset  
  
  -- verify no shift  
  BIT_IN <= '1'; wait for 2*PER;  
  BIT_IN <= '0'; wait for 2*PER;  
  
  -- verify shift lt  
  SHIFT <= '1';  
  DIR <= '0';  
  BIT_IN <= '1'; wait for 40*PER;  
  BIT_IN <= '0'; wait for 40*PER;  
  
  -- verify shift rt  
  SHIFT <= '1';  
  DIR <= '1';  
  BIT_IN <= '1'; wait for 40*PER;  
  BIT_IN <= '0'; wait for 40*PER;  
end process run;  
  
-----  
-- End test processes  
-----  
end architecture;
```

Registers - HDL

- Shift Register - verification

reset

no shift

Big Picture



Signal names visible

1 shifted left

0 shifted left

Registers - HDL

- Shift Register - verification

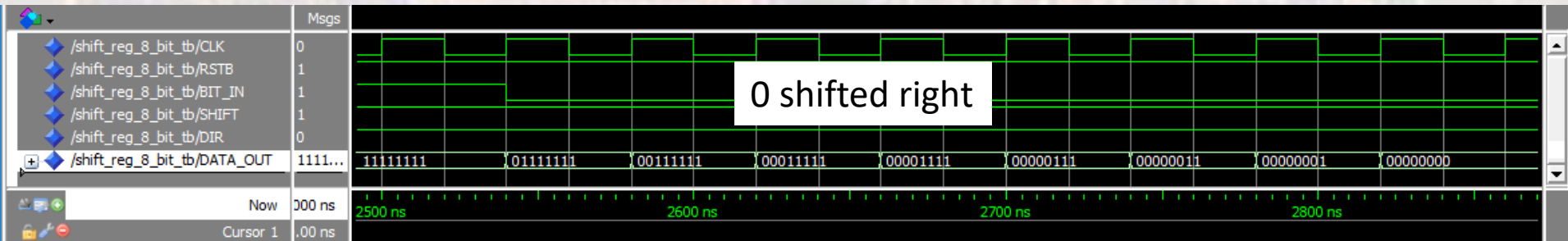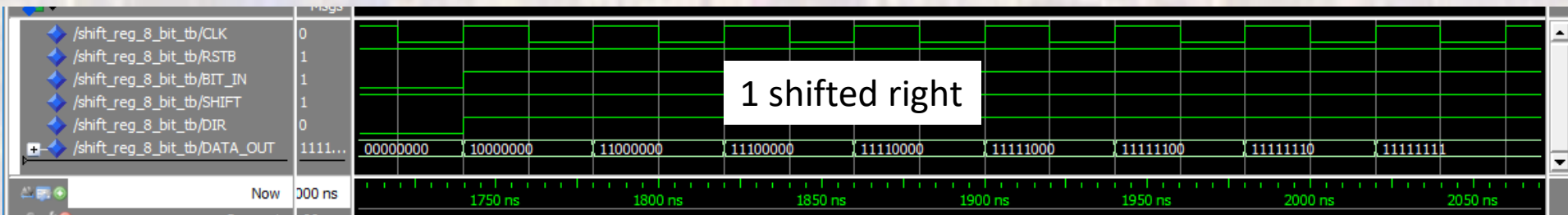

Registers - HDL

- Shift Register - n

```
-----  
-- shift_reg_n_bit.vhdl  
-- created 2/29/17  
-- tj  
--  
-- rev 0  
-----  
--  
-- n bit L/R shift register example  
--  
-----  
-- Inputs: rstb, clk, bit_in, shift, dir  
-- Outputs: data_out[(N-1):0]  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
entity shift_reg_n_bit is  
  generic(  
    N: natural := 8  
  );  
  port(  
    i_clk : in std_logic;  
    i_rstb : in std_logic;  
    i_bit_in : in std_logic;  
    i_shift : in std_logic;  
    i_dir : in std_logic; -- 0 for left, 1 for right  
    o_data_out : out std_logic_vector((N-1) downto 0)  
  );  
end entity;
```

```
architecture behavioral of shift_reg_n_bit is  
  -- internal signals  
  signal data_out_sig: std_logic_vector((N-1) downto 0);  
begin  
  process(i_clk, i_rstb)  
    begin  
      -- reset  
      --  
      if (i_rstb = '0') then  
        data_out_sig <= (others => '0');  
      -- rising clk edge  
      --  
      elsif (rising_edge(i_clk)) then  
        -- shifting  
        --  
        if (i_shift = '0') then  
          data_out_sig <= data_out_sig;  
        elsif (i_dir = '0') then  
          data_out_sig <= data_out_sig(((N-1)-1) downto 0) & i_bit_in;  
        else  
          data_out_sig <= i_bit_in & data_out_sig((N-1) downto 1);  
        end if;  
      end if;  
    end process;  
  -- output logic  
  --  
  o_data_out <= data_out_sig;  
end behavioral;
```