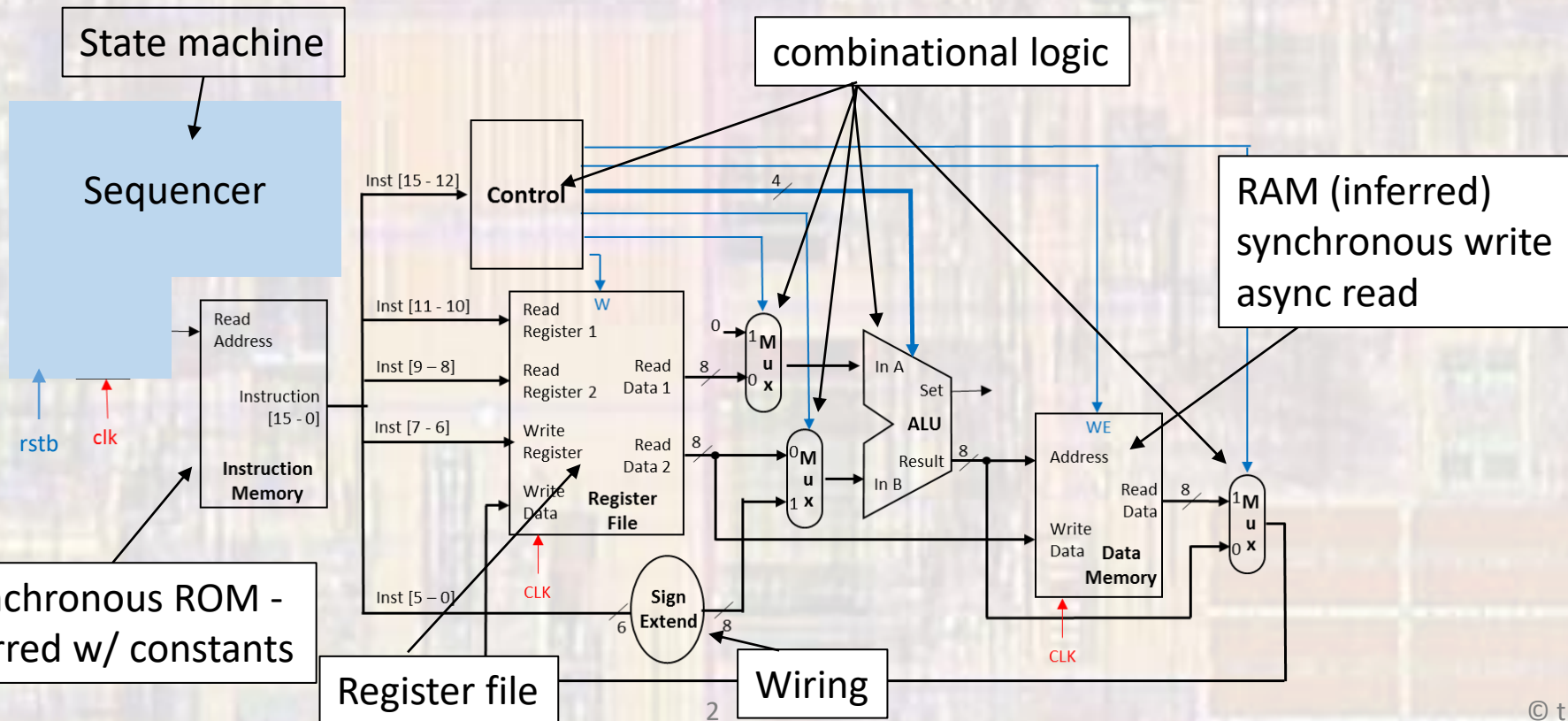


Single Cycle Processor Implementation

Last updated 4/22/21

Single Cycle Processor - Implementation

- Project
 - Build and test each block
 - except maybe the stand alone muxes and sign extend
 - Label all wires and use those names in the top level



Single Cycle Processor - Implementation

- Project
 - Register File
 - 4 additional outputs to directly pass RA, RB, RC, RD to SSEG
 - **No rstb input**
 - Sequencer
 - State machine – 3 states
 - reset – change switches – release reset
 - Starting address
 - Number of instructions to execute
 - start ↓(button) to start program
 - **ONLY place rstb is used**

