

State Diagrams

Last updated 1/10/20


State Diagrams

- These slides introduce State Diagrams
- Upon completion: You should be able to read and create state diagrams for finite state machines

State Diagrams

- Finite State Machine
 - State Diagram – Moore


- State

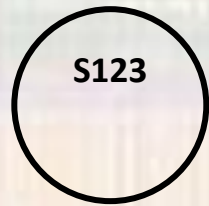

- Outputs



- Inputs
- Conditions

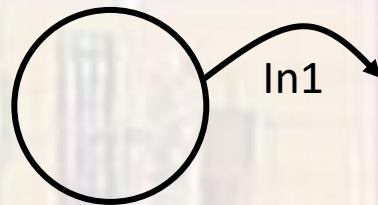


State Diagrams

- Finite State Machine

- State Transition Diagram – Moore

- Transitions ONLY occur on clock edges (rising)
- Transitions occur on EVERY clock edge (rising)
- Priority stop light – Inputs: Reset, Traffic N/S, Traffic E/W

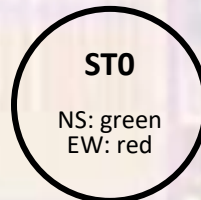- State 0 : NS light state variable (memory) holds code for green
EW light state variable (memory) holds the code for red



- State 1 : NS light state variable (memory) holds code for yellow
EW light state variable (memory) holds the code for red



State Diagrams

- Finite State Machine
 - State Transition Diagram – Moore
 - Transitions ONLY occur on clock edges (rising)
 - Transitions occur on EVERY clock edge (rising)
 - Priority stop light – Inputs: Reset, Traffic N/S, Traffic E/W




State Diagrams

- Finite State Machine

- State Transition Diagram – Moore

- Transitions ONLY occur on clock edges (rising)
- Transitions occur on EVERY clock edge (rising)
- Priority stop light – Inputs: Reset, Traffic N/S, Traffic E/W


- Basic transitions

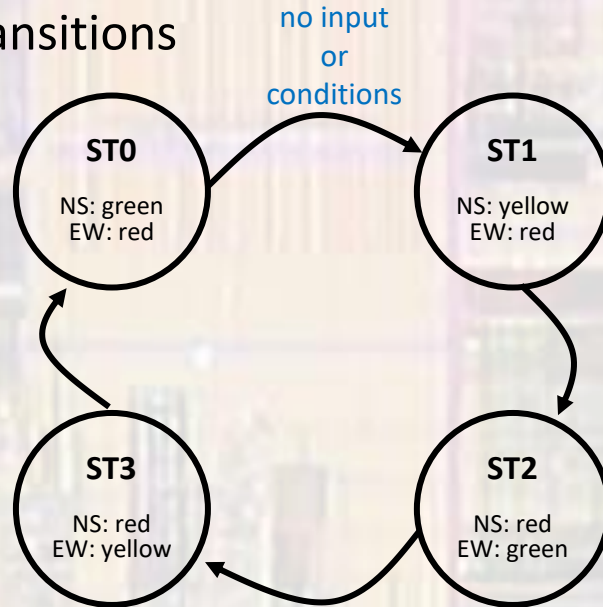

If we did not sense for traffic – this would be complete

State Diagrams

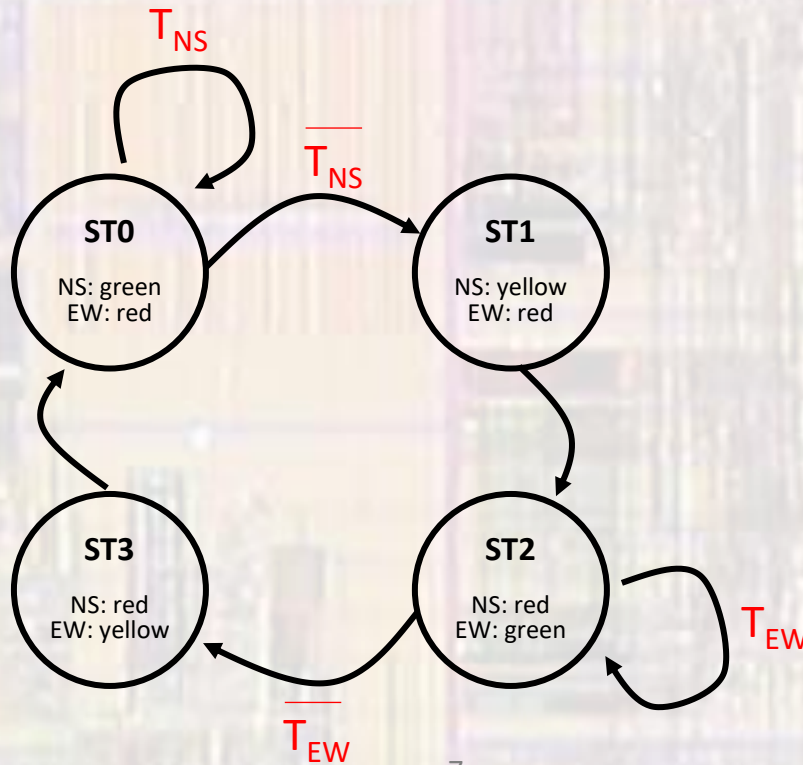- Finite State Machine
 - State Transition Diagram – Moore
 - Transitions ONLY occur on clock edges (rising)
 - Transitions occur on EVERY clock edge (rising)
 - Priority stop light – **Inputs:** Reset, **Traffic N/S**, **Traffic E/W**



State Diagrams

- Finite State Machine
 - State Transition Diagram – Moore
 - Transitions ONLY occur on clock edges (rising)
 - Transitions occur on EVERY clock edge (rising)
 - Priority stop light – **Inputs:** Reset, Traffic N/S, Traffic E/W

