

State Machine Encoding Example

Last updated 1/22/21

State Machine Encoding Examples

- These slides provide examples of various encoding formats

State Machine Encoding Example


- Encoding
 - Comparison – considerations
 - Memory elements (bits) \rightarrow area or fit
 - Coding / Decoding logic \rightarrow area or fit
 - Speed
 - Shorter logic chains \rightarrow faster maximum clock speeds
 - Power
 - $P = v * i$
 - $P = v * c * dv/dt$
 - dv/dt represents a transition $0 \rightarrow 1$
 - Fewer transitions \rightarrow lower power

State Machine Encoding Example

- Sequence Detector
 - Create a state machine that can detect when a specific bit sequence is transmitted on a communications channel
 - Common in coded channels
 - Start sequence: 11001101
 - time →
 - Pulse a bit when the sequence is detected

State Machine Encoding Example

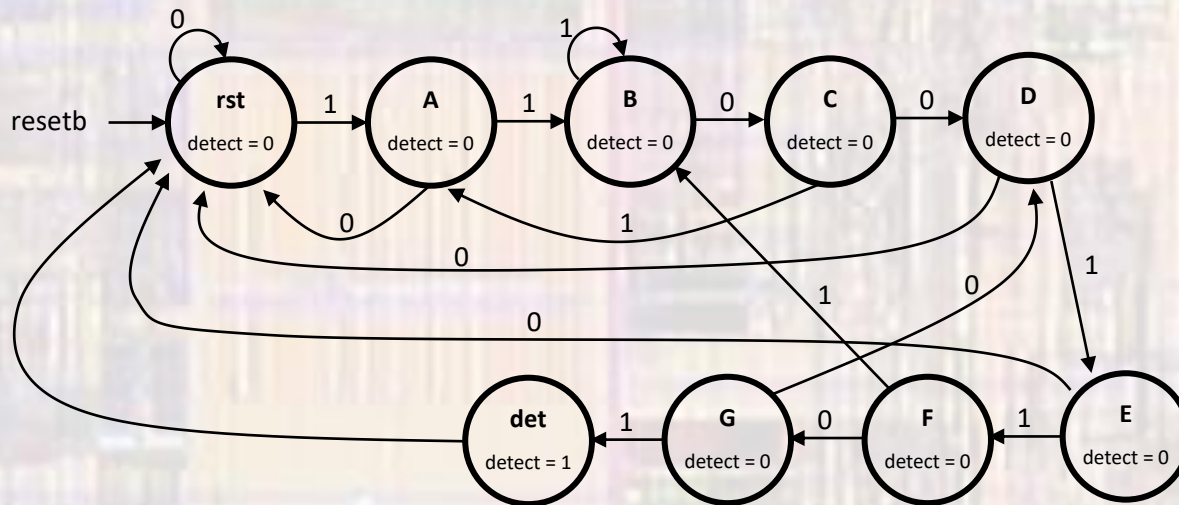- State Diagram
 - Sequence detector 11001101




State Machine Encoding Example

- State Diagram

State	Din	Next State
rst	0	Rst
rst	1	A
A	0	Rst
A	1	B
B	0	C
B	1	B
C	0	D
C	1	A
D	0	Rst
D	1	E
E	0	Rst
E	1	F
F	0	G
F	1	B
G	0	D
G	1	Det
Det	X	rst

Factor 11001101

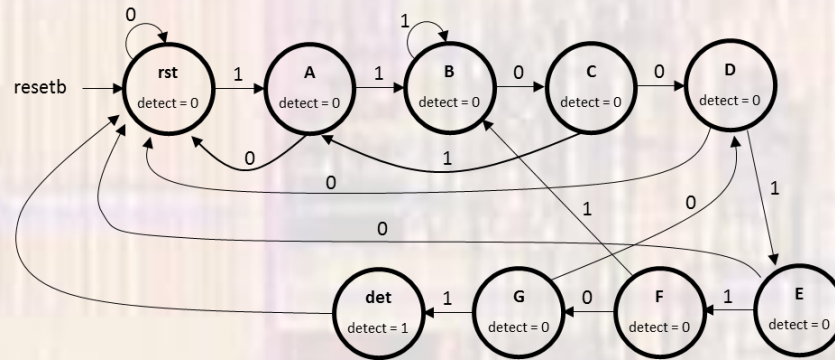

State	Detect
Rst	0
A	0
B	0
C	0
D	0
E	0
F	0
G	0
Det	1

State Machine Encoding Example

- State Diagram
 - Binary encoding
 - 9 states \rightarrow 4 bits

State	Code
Rst	0000
A	0001
B	0010
C	0011
D	0100
E	0101
F	0110
G	0111
Det	1000

State	Din	Next State
0000	0	0000
0000	1	0001
0001	0	0000
0001	1	0010
0010	0	0011
0010	1	0010
0011	0	0100
0011	1	0001
0100	0	0000
0100	1	0101
0101	0	0000
0101	1	0110
0110	0	0111
0110	1	0010
0111	0	0100
0111	1	1000
1000	X	0000

State	Detect
0000	0
0001	0
0010	0
0011	0
0100	0
0101	0
0110	0
0111	0
1000	1

State Machine Encoding Example

- State Diagram
 - Binary encoding
 - 9 states \rightarrow 4 bits

		NS_B3				NS_B0														
		B2		B2'		B2		B2'												
		D	D'	D'	D	D	D'	D'	D											
B3	B1'	2	2	2	2	1	1	1	1	B3	B1'	0	0	0	0	0	0	0	0	B1
	B1	5	4	6	7	9	8	6	7		0	0	0	0	0	0	0	0		
B3'	B1	2	2	3	3	2	2	2	2	B3'	B1	0	0	0	0	0	0	0	0	B1'
	B1'	9	8	0	1	3	2	0	1		0	1	0	0	1	0	1	0		
		1	1	1	1	7	6	4	5					1	0	0	0			
		3	2	4	5									0	0	0	0			
		9	8	1	1	3	2	0	1					0	0	0	1			
		0	0	0	0	0	0	0	0					B0'	B0	B0'				
		0	0	0	0	1	1	1	1											
		1	1	1	1	0	0	0	0											
		0	0	0	0	0	0	0	0											

$$\begin{aligned}
 &B3' B1' B0' D + \\
 &B3' B2 B1 B0' D' + \\
 &B3' B2' B1 B0 D
 \end{aligned}$$

		NS_B3					
		B2		B2'			
		D	D'	D'	D		
B3	B1'	0	0	0	0	0	0
	B1	0	0	0	0	0	0
B3'	B1	0	0	0	1	0	0
	B1'	0	0	0	0	0	0
		B0'	B0	B0'			

$$B3' B2 B1 B0 D$$

		NS_B2					
		B2		B2'			
		D	D'	D'	D		
B3	B1'	0	0	0	0	0	0
	B1	0	0	0	0	0	0
B3'	B1	0	1	1	0	0	1
	B1'	1	0	0	1	0	0
		B0'	B0	B0'			

$$\begin{aligned}
 &B3' B2 B1 D' + \\
 &B3' B2 B1' D + \\
 &B3' B2' B1 B0 D'
 \end{aligned}$$

		NS_B1					
		B2		B2'			
		D	D'	D'	D		
B3	B1'	0	0	0	0	0	0
	B1	0	0	0	0	0	0
B3'	B1	1	1	0	0	0	1
	B1'	0	0	0	1	1	0
		B0'	B0	B0'			

$$\begin{aligned}
 &B3' B1 B0' + \\
 &B3' B1' B0 D
 \end{aligned}$$

State Machine Encoding Example

- State Diagram
 - binary encoding
 - 9 states \rightarrow 4 bits

State	Detect
0000	0
0001	0
0010	0
0011	0
0100	0
0101	0
0110	0
0111	0
1000	1

$$\text{detect} = B3B2'B1'B0'$$

State Machine Encoding Example

- State Diagram
 - One hot encoding
 - 9 states → 9 bits

State	Code
Rst	000000001
A	000000010
B	000000100
C	000001000
D	000010000
E	000100000
F	001000000
G	010000000
Det	100000000

State	Din	Next State
000000001	0	000000001
000000001	1	000000010
000000010	0	000000001
000000010	1	000000100
000000100	0	000001000
000000100	1	000000100
000001000	0	000010000
000001000	1	000000010
000010000	0	000000001
000010000	1	000100000
000100000	0	000000001
000100000	1	001000000
001000000	0	010000000
001000000	1	000000100
010000000	0	000010000
010000000	1	100000000
100000000	X	000000001

State	Detect
000000001	0
000000010	0
000000100	0
000001000	0
000010000	0
000100000	0
001000000	0
010000000	0
100000000	1

State Machine Encoding Example

- State Diagram
 - One hot encoding
 - 9 states \rightarrow 9 bits

$$ns8 = b7 D$$

$$ns7 = b6 D'$$

$$ns6 = b5 D$$

$$ns5 = b4 D$$

$$ns4 = b3 D' + b7 D$$

$$ns3 = b2 D'$$

$$ns2 = b1 D + b2 D$$

$$ns1 = b0 D' + b3 D$$

$$ns0 = b0 D' + b1 D' + b4 D' + b5 D' + b8$$

State	Din	Next State
00000001	0	00000001
00000001	1	00000010
00000010	0	00000001
00000010	1	00000100
00000100	0	00001000
00000100	1	00000100
00001000	0	00001000
00001000	1	00000010
00010000	0	00000001
00010000	1	00010000
00100000	0	00000001
00100000	1	00100000
01000000	0	01000000
01000000	1	00000100
01000000	0	00001000
01000000	1	10000000
10000000	X	00000001

State Machine Encoding Example

- State Diagram
 - One hot encoding
 - 9 states \rightarrow 9 bits

State
00000001
00000010
00000100
00001000
00010000
00100000
01000000
10000000

detect = b8

State Machine Encoding Example

- State Diagram
 - Johnson encoding
 - 9 states \rightarrow 5 bits





State	Code
Rst	10000
A	11000
B	11100
C	11110
D	11111
E	01111
F	00111
G	00011
Det	00001

State	Din	Next State
10000	0	10000
10000	1	11000
11000	0	10000
11000	1	11100
11100	0	11110
11100	1	11100
11110	0	11111
11110	1	11000
11111	0	10000
11111	1	01111
01111	0	10000
01111	1	00111
00111	0	00011
00111	1	11100
00011	0	11111
00011	1	00001
00001	X	10000

State	Detect
10000	0
11000	0
11100	0
11110	0
11111	0
01111	0
00111	0
00011	0
00001	1

State Machine Encoding Example

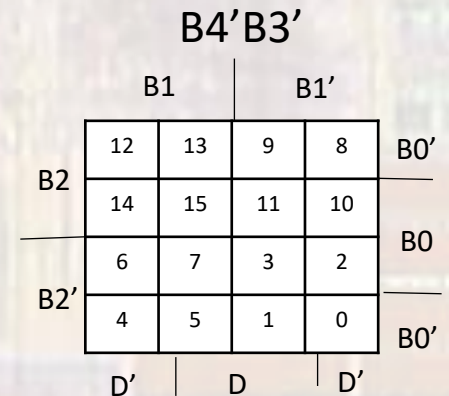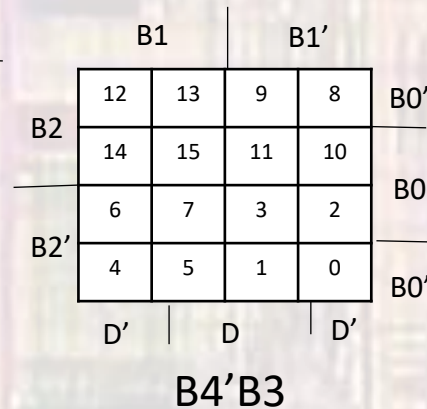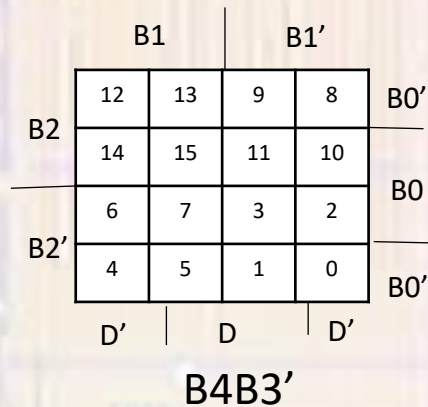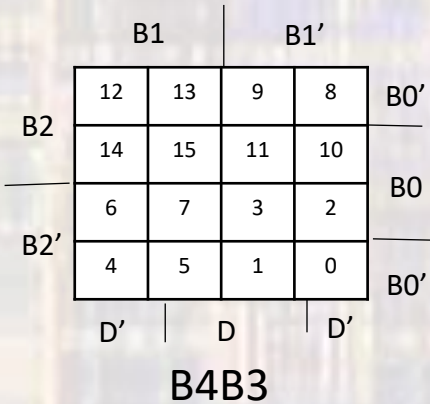- State Diagram
 - Johnson encoding
 - 9 states \rightarrow 5 bits







State Machine Encoding Example

- State Diagram
 - Johnson encoding
 - 9 states \rightarrow 5 bits

State	Din	Next State
10000	0	10000
10000	1	11000
11000	0	10000
11000	1	11100
11100	0	11110
11100	1	11100
11110	0	11111
11110	1	11000
11111	0	10000
11111	1	01111
01111	0	10000
01111	1	00111
00111	0	00011
00111	1	11100
00011	0	11111
00011	1	00001
00001	X	10000

NS_4

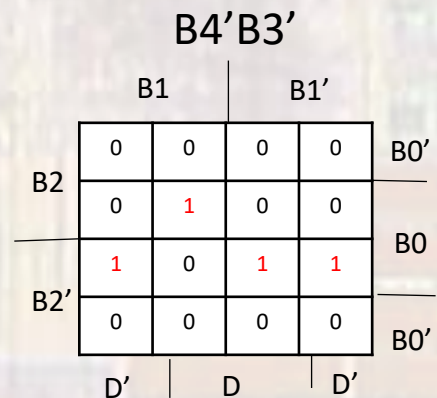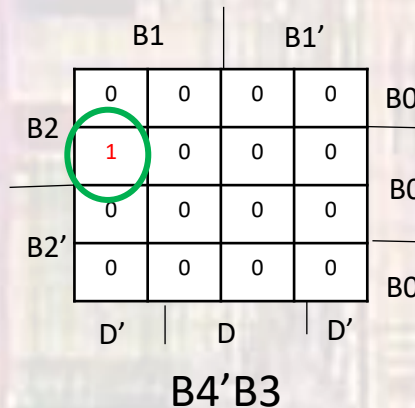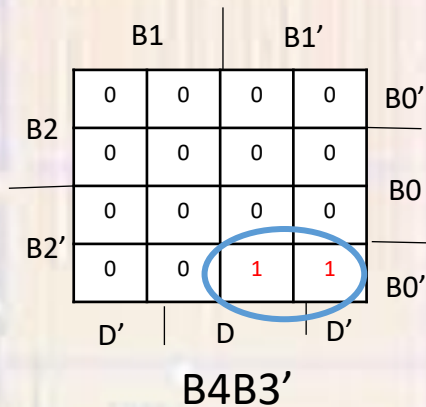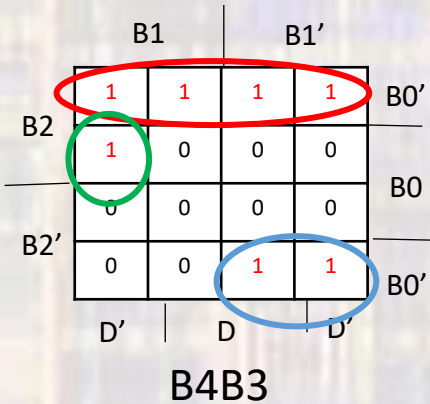

$$B4B3B2B0' + B4B2'B1'B0' + B3B2B1B0D' + B4'B3'B2'B1'B0 + B4'B3'B2'B1B0D' + B4'B3'B2B1B0D$$

State Machine Encoding Example

- State Diagram
 - Johnson encoding
 - 9 states \rightarrow 5 bits

State	Detect
10000	0
11000	0
11100	0
11110	0
11111	0
01111	0
00111	0
00011	0
00001	1

$\text{detect} = b_4'b_3'b_2'b_1'b_0$