

Advanced Testbenches Automation

Last updated 1/28/21

Advanced Testbenches - Automation

- Manual Testbench
 - Results checked by hand
 - Simulation results in waveforms or output file
 - Check expected results to actual results by hand

Advanced Testbenches - Automation

- Automated Testbench
 - Results checked automatically
 - Code results into the test bench
 - Enumerated
 - Calculated
 - Check expected results to actual results in the testbench

Advanced Testbenches - Automation

- Design Verification
 - Enumerated results
 - Explicitly list the expected results

```
-----  
-- counter_nbit_ud_tb1.vhd1  
--  
-- by: johnsontimoj  
--  
-- created: 6/28/2016  
--  
-- version: 0.0  
-----  
--  
-- test bench for 3 bit counter  
-- using enumerated results  
-- inputs: none  
-- outputs: count  
-- sim run time = 370 ns  
-----  
  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
  
entity counter_nbit_ud_tb1 is  
  generic(  
    NN: integer := 3  
  );  
  -- no ports - tb  
end entity;  
  
architecture testbench of counter_nbit_ud_tb1 is  
  signal clk_tb: std_logic;  
  signal rstb_tb: std_logic;  
  signal dir_tb: std_logic := '0'; -- dir=0 is up  
  signal count_tb: std_logic_vector((NN-1) downto 0);  
  signal count_chk: std_logic_vector((NN-1) downto 0);  
  
  constant per: time := 20 ns;  
  constant t_delay: time := 5 ns;  
  constant t_reset: time := per*2;  
  
end architecture;
```

```
-----  
-- 3 bit counter prototype  
-----  
component counter_nbit_ud is  
  generic(N: integer := 3);  
  port ( i_clk: in std_logic;  
         i_rstb: in std_logic;  
         i_dir: in std_logic; -- dir=0 is up  
         o_count: out std_logic_vector(N-1 downto 0)  
       );  
end component;  
  
-----  
begin  
  
-- Device Under Test  
-----  
dut: counter_nbit_ud  
  generic map(  
    N => NN  
  )  
  port map(  
    i_clk => clk_tb,  
    i_rstb => rstb_tb,  
    i_dir => dir_tb,  
    o_count => count_tb  
  );  
  
-----  
-- Clock Process  
clk: process  
begin  
  clk_tb <= '0';  
  wait for PER/2;  
  loop  
    clk_tb <= not clk_tb;  
    wait for per/2;  
  end loop;  
end process;  
  
-- Reset process (active low)  
rstb: process  
begin  
  rstb_tb <= '0';  
  wait for t_reset;  
  rstb_tb <= '1';  
  wait; -- only executes once  
end process;  
  
-- Direction process  
dir: process  
begin  
  wait for t_reset;  
  wait for per*8;  
  dir_tb <= not dir_tb;  
end process;  
|
```

Advanced Testbenches - Automation


- Design Verification
 - Enumerated results
 - Explicitly list the expected results

```
-----  
-- generate expected results  
-----  
count_chk <= "000" after t_reset-per/2 + per*0 + t_delay,  
             "001" after t_reset-per/2 + per*1 + t_delay,  
             "010" after t_reset-per/2 + per*2 + t_delay,  
             "011" after t_reset-per/2 + per*3 + t_delay,  
             "100" after t_reset-per/2 + per*4 + t_delay,  
             "101" after t_reset-per/2 + per*5 + t_delay,  
             "110" after t_reset-per/2 + per*6 + t_delay,  
             "111" after t_reset-per/2 + per*7 + t_delay,  
             "000" after t_reset-per/2 + per*8 + t_delay,  
             "111" after t_reset-per/2 + per*9 + t_delay,  
             "110" after t_reset-per/2 + per*10 + t_delay,  
             "101" after t_reset-per/2 + per*11 + t_delay,  
             "100" after t_reset-per/2 + per*12 + t_delay,  
             "011" after t_reset-per/2 + per*13 + t_delay,  
             "010" after t_reset-per/2 + per*14 + t_delay,  
             "001" after t_reset-per/2 + per*15 + t_delay,  
             "000" after t_reset-per/2 + per*16 + t_delay,  
             "111" after t_reset-per/2 + per*17 + t_delay;  
-----
```

```
-----  
-- check actual results  
-----  
process  
begin  
  -- delay for reset  
  if (now < per*2) then  
    wait for per/2;  
  -- run to end of sim  
  elsif (now < 20*per) then  
    assert (count_tb = count_chk)  
    report "ERROR at t=" & time'image(now) &  
          ", count_tb = " & integer'image(to_integer(unsigned(count_tb))) &  
          ", count_chk = " & integer'image(to_integer(unsigned(count_chk)))  
          severity failure;  
  else  
    assert (false)  
    report "no errors found at t=" & time'image(now)  
    severity note;  
  end if;  
  wait for per;  
end process;  
end architecture;
```


Advanced Testbenches - Automation

 
- Design Verification
 - Enumerated results



```
#
# add wave *
# view structure
# .main_pane.structure.interior.cs.body.struct
# view signals
# .main_pane.objects.interior.cs.body.tree
# run 400 ns
# ** Note: no errors found at t=400000 ps
# Time: 400 ns Iteration: 0 Instance: /counter_nbit_ud_tbl
|VSIM 2>]
```

Advanced Testbenches - Automation

 - Design Verification
 - Enumerated results
 - Changed expected result 4 from 3 to 7



```
#
# add wave *
# view structure
# .main_pane.structure.interior.cs.body.struct
# view signals
# .main_pane.objects.interior.cs.body.tree
# run 400 ns
# ** Failure: ERROR at t= 120000 ps, count_tb = 4, count_chk = 7
# Time: 120 ns Iteration: 0 Process: /counter_nbit_ud_tb1/line_120 File: D:/GDrive/MSOE/19_Q1_EE3921/Projects/Class_Examples/counter_nbit_ud_tb1.vhdl
# Break in Process line_120 at D:/GDrive/MSOE/19_Q1_EE3921/Projects/Class_Examples/counter_nbit_ud_tb1.vhdl line 129
VSIM 2>
```

Advanced Testbenches - Automation

- Design Verification
- Calculated results

```
-----  
-- counter_nbit_ud_tb2.vhd1  
-- by: johnsontimoj  
-- created: 6/28/2016  
-- version: 0.0  
-----  
--  
-- test bench for 3 bit counter  
-- using calculated results  
-- inputs: none  
-- outputs: count  
-- sim run time = 370 ns  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
  
entity counter_nbit_ud_tb2 is  
  generic(  
    NN: integer := 3  
  );  
  -- no ports - tb  
end entity;  
  
architecture testbench of counter_nbit_ud_tb2 is  
  signal clk_tb: std_logic;  
  signal rstb_tb: std_logic;  
  signal dir_tb: std_logic := '0'; -- dir=0 is up  
  signal count_tb: std_logic_vector((NN-1) downto 0);  
  signal count_chk: std_logic_vector((NN-1) downto 0);  
  
  constant per: time := 20 ns;  
  constant t_delay: time := 5 ns;  
  constant t_reset: time := per*2;
```

```
-----  
-- 3 bit counter prototype  
-----  
component counter_nbit_ud is  
  generic(N: integer := 3);  
  port ( i_clk: in std_logic;  
         i_rstb: in std_logic;  
         i_dir: in std_logic; -- dir=0 is up  
         o_count: out std_logic_vector(N-1 downto 0)  
       );  
end component;  
  
-----  
begin  
  
-- Device Under Test  
-----  
dut: counter_nbit_ud  
  generic map(  
    N => NN  
  )  
  port map(  
    i_clk => clk_tb,  
    i_rstb => rstb_tb,  
    i_dir => dir_tb,  
    o_count => count_tb  
  );  
-----  
  
-- Clock Process  
clk: process  
begin  
  clk_tb <= '0';  
  wait for per/2;  
  loop  
    clk_tb <= not clk_tb;  
    wait for per/2;  
  end loop;  
end process;  
  
-- Reset process (active low)  
rstb: process  
begin  
  rstb_tb <= '0';  
  wait for t_reset;  
  rstb_tb <= '1';  
  wait; -- only executes once  
end process;  
  
-- Direction process  
dir: process  
begin  
  wait for t_reset;  
  wait for per*8;  
  dir_tb <= not dir_tb;  
end process;
```

 

Advanced Testbenches - Automation

- Design Verification
 - Calculated results

```
-----  
-- generate expected results  
-----  
process  
begin  
  if (rstb_tb = '0') then  
    count_chk <= (others => '0');  
    wait for per*3/4;  
  else if (dir_tb = '0') then  
    count_chk <= std_logic_vector(unsigned(count_chk) + 1);  
  else  
    count_chk <= std_logic_vector(unsigned(count_chk) - 1);  
  end if;  
end if;  
wait for per;  
end process;  
-----  
  
-----  
-- check actual results  
-----  
process  
begin  
  -- delay for reset  
  if (now < per*2.5) then  
    wait for per/2;  
  -- run to end of sim  
  elsif (now < 20*per) then  
    assert (count_tb = count_chk)  
    report "ERROR at t=" & time'image(now) &  
          ", count_tb = " & integer'image(to_integer(unsigned(count_tb))) &  
          ", count_chk = " & integer'image(to_integer(unsigned(count_chk)))  
          severity failure;  
  else  
    assert (false)  
    report "no errors found at t=" & time'image(now)  
    severity note;  
  end if;  
  wait for per;  
end process;  
end architecture;
```

Advanced Testbenches - Automation

- Design Verification
 - Calculated results



```
#
# add wave *
# view structure
# .main_pane.structure.interior.cs.body.struct
# view signals
# .main_pane.objects.interior.cs.body.tree
# run 400 ns
# ** Note: no errors found at t=400000 ps
# Time: 400 ns Iteration: 0 Instance: /counter_nbit_ud_tb2

|VSIM 2>
Now: 400 ns Delta: 2 sim:/counter_nbit_ud_tb2
```