

C-MOS Circuits

Last updated 4/10/22

C-MOS Circuits

- Parameters

$$K_n = \frac{W\mu_n C_{ox}}{2L}$$

$$K_p = \frac{W\mu_p C_{ox}}{2L}$$

$$K_n = \frac{k'_n}{2} \frac{W}{L} \quad k'_n = \mu_n C_{ox} \quad K_p = \frac{k'_p}{2} \frac{W}{L} \quad k'_p = \mu_p C_{ox}$$

μ_n, μ_p, C_{ox} fixed for a given semiconductor process →

k'_n, k'_p fixed for a given semiconductor process

$$I_D = K_n [2(V_{GS} - V_{tn})V_{DS} - V_{DS}^2]$$

$$I_D = K_p [2(V_{SG} - V_{tp})V_{SD} - V_{SD}^2]$$

$$I_D = \frac{k'_n}{2} \frac{W}{L} [2(V_{GS} - V_{tn})V_{DS} - V_{DS}^2]$$

$$I_D = \frac{k'_p}{2} \frac{W}{L} [2(V_{SG} - V_{tp})V_{SD} - V_{SD}^2]$$

$$V_{DSsat} = V_{GS} - V_{th}$$

$$V_{SDsat} = V_{SD} - V_{th}$$

$$I_D = K_n (V_{GS} - V_{tn})^2$$

$$I_D = K_p (V_{SG} - V_{tp})^2$$

$$I_D = \frac{k'_n}{2} \frac{W}{L} (V_{GS} - V_{tn})^2$$

$$I_D = \frac{k'_p}{2} \frac{W}{L} (V_{SG} - V_{tp})^2$$


$$C_{Gn} = W \times L \times k'_n / \mu_n$$

$$C_{Gp} = W \times L \times k'_p / \mu_p$$

C-MOS Circuits

- Enhancement Mode
 - A bias is required to form the channel

- 4-terminal symbol

 


- In digital applications the Source is typically tied to

- Vdd for P-MOS
 - Gnd for N-MOS




- The simplified logic symbols

 

Note – almost all N-MOS and P-MOS devices used today are enhancement mode – so the dashed line is omitted

C-MOS Circuits

- Inverter - Design

 

Assuming Vdd is big enough to keep M2 and M1 in saturation at the switching point

$$\frac{k'_p}{2} \frac{W_2}{L_2} (V_{sg2} - V_{tp})^2 = \frac{k'_n}{2} \frac{W_1}{L_1} (V_{gs1} - V_{tn})^2$$


Desire a consistent switching point $V_{in} = V_{out} = V_{dd}/2$

$$\frac{k'_p}{2} \frac{W_2}{L_2} (V_{dd}/2 - V_{tp})^2 = \frac{k'_n}{2} \frac{W_1}{L_1} (V_{dd}/2 - V_{tn})^2$$

$$\frac{W_1/L_1}{W_2/L_2} = \frac{k'_p}{k'_n} \left(\frac{V_{dd}/2 - V_{tp}}{V_{dd}/2 - V_{tn}} \right)^2$$

C-MOS Circuits

- Inverter - Design

 

Desire a consistent switching point $V_{in} = V_{out} = V_{dd}/2$

$$\frac{W_1/L_1}{W_2/L_2} = \frac{k'_p}{k'_n} \left(\frac{V_{dd}/2 - V_{tp}}{V_{dd}/2 - V_{tn}} \right)^2$$

If we make $V_{tp} = V_{tn}$, V_{dd} drops out of the equation


$$\frac{W_1/L_1}{W_2/L_2} = \frac{k'_p}{k'_n}$$

And the switching point remains $V_{dd}/2$ regardless of V_{dd} **


** as long as both devices are in saturation

C-MOS Circuits

- Inverter - Design

 

 
$$\begin{aligned}V_t &= 1V \\V_{tn} &= 1V \\V_{tp} &= -1V (1V) \\k'n &= 14\mu A/V^2 \\k'p &= 4.5\mu A/V^2\end{aligned}$$




C-MOS Circuits

- Inverter - Design

 

C-MOS Circuits

- Inverter - Design

 

V_{OL} : Maximum output voltage that will be considered a low

V_{OH} : Minimum output voltage that will be considered a high

V_{IL} : Maximum input voltage that will result in a high output voltage

V_{IH} : Minimum input voltage that will result in a low output voltage


Noise Margin (NM) : The amount of noise in the input signals that the system can tolerate without causing the output to change when it shouldn't

$$NM_L = V_{IL} - V_{OL\text{ unity}}$$

$$NM_H = V_{OH\text{ unity}} - V_{IH}$$

C-MOS Circuits

- Inverter - Design

 

$$V_{dd} = 3.3V$$

$$V_{tn} = -V_{tp} = 1V$$

$$V_{IL} = 1.488V, V_{IH} = 1.813V$$

$$V_{OL\text{Unity}} = 160mV, V_{OH\text{Unity}} = 3.14V$$

$$NML = 1.326V$$

$$NMH = 1.326V$$

$$V_{IL(K_n=K_p)} = V_{tn} + \frac{3}{8}(V_{DD} + V_{tp} - V_{tn})$$

$$V_{IH(K_n=K_p)} = V_{tn} + \frac{5}{8}(V_{DD} + V_{tp} - V_{tn})$$

$$V_{OL\text{Unity}(K_n=K_p)} = \frac{1}{2}(2V_{IH} - V_{DD} - V_{tp} - V_{tn})$$


$$V_{OH\text{Unity}(K_n=K_p)} = \frac{1}{2}(2V_{IL} + V_{DD} - V_{tp} - V_{tn})$$

$$NM_L = V_{IL} - V_{OL\text{Unity}}$$

$$NM_H = V_{OH\text{Unity}} - V_{IH}$$


C-MOS Circuits

- C-MOS Gates

 


C-MOS Circuits

- C-MOS Gates

 

C-MOS Circuits


- C-MOS Gates

 

Total transistor gate area

$$15,000\mu^2$$

NAND gates preferred
over NOR gates

 



Total transistor gate area

$$6,000\mu^2$$

C-MOS Circuits

- C-MOS Gates

  - Use a 2 input NAND gate as a reference for size and loading



Relative Size

2 input NAND gate area = $3000\mu^2$ = 1 NAND equivalent

INV gate area = $1000\mu^2$ = 1/3 NAND Eq.

2 input NOR gate area = $7000\mu^2$ = 2.33 NAND Eq.

3 NAND = 2 NAND eq.

4 NAND = 3.33 NAND eq.

3 NOR = 5 NAND eq.

4 NOR = 8.66 NAND eq.

Input Load (relative capacitance – 1 input)

2 input NAND gate area/input = $1500\mu^2$ = 1 NAND equivalent

INV gate area/input = $1000\mu^2$ = 2/3 NAND Eq.

2 input NOR gate area/input = $4000\mu^2$ = 2.33 NAND Eq.

3 NAND/input = 1.33 NAND eq.



4 NAND/input = 1.66 NAND eq.

3 NOR/input = 3.33 NAND eq.

4 NOR/input = 4.33 NAND eq.


C-MOS Circuits

  - N-MOS Transmission Gates
 - Use a single N-MOS device as a “pass gate”
 - Passes a ‘0’
 - Reduced value for a ‘1’
 - Bi-directional





C-MOS Circuits

 - N-MOS Transmission Gates
 - Chained N-MOS device as a “pass gate”
 - Passes a ‘0’
 - Reduced value for a ‘1’, but no further reduction
 - Multiplexer




C-MOS Circuits

  - C-MOS Transmission Gates
 - Use parallel P-MOS and N-MOS devices as a “pass gate”
 - Passes both ‘0’s and ‘1’s
 - Bi-directional
 - Requires `ctl` and `ctlB`




C-MOS Circuits

 - C-MOS Flip-Flop
 - Logical Circuit
 - 2, SR latches



C-MOS Circuits

- C-MOS Flip-Flop
 - Common Circuit

 

C-MOS Circuits

- C-MOS Tristate Inverter
 - Common Circuit

