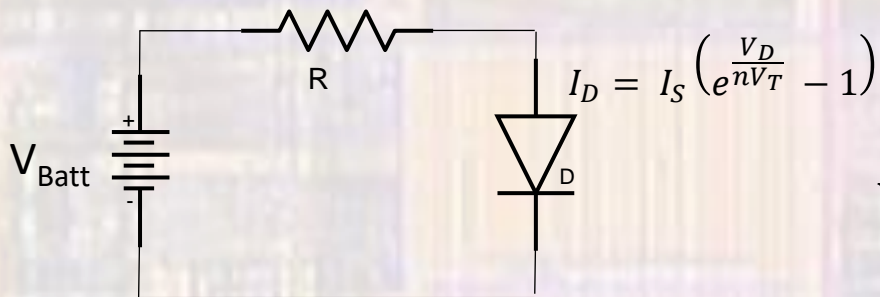


Diode Circuit Analysis

Last updated 1/25/22

Diode Circuit Analysis

- “Exact” Solution
 - Transcendental Equation
 - You have the tools to solve this



$$V_{Batt} = I_D R + V_D$$


$$V_{Batt} = I_S \left(e^{\frac{V_D}{nV_T}} - 1 \right) R + V_D$$

$$I_S = 5.3e-15, n = 1, V_{batt} = 3.3V, R = 1K\Omega$$
$$V_D = 0.6999V, I_D = 2.601mA$$

Diode Circuit Analysis

- Ideal Solution

- $V_D = V_{Th} = 0V$

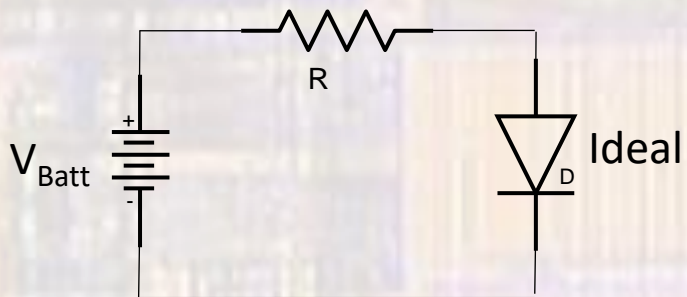

$$V_{Batt} = I_D R + V_D$$


$$V_{Batt} = I_D R$$

$$I_D = V_{Batt} / R$$

$$V_{batt} = 3.3V, R = 1K\Omega, V_{Th} = 0.7V, R_F = 5\Omega$$
$$I_D = 3.3mA$$

Diode Circuit Analysis

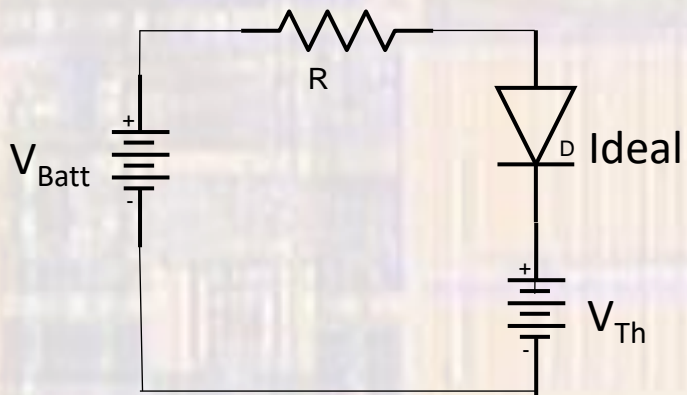- Ideal Solution (with V_{Th})
 - $V_D = V_{Th} = 0.7V$



$$V_{Batt} = I_D R + V_{Th}$$


$$I_D = (V_{Batt} - V_{Th})/R$$

$$V_{batt} = 3.3V, R = 1K\Omega, V_{Th} = 0.7V, R_F = 5\Omega$$
$$I_D = 2.60mA$$

Diode Circuit Analysis

- Piecewise Linear Solution

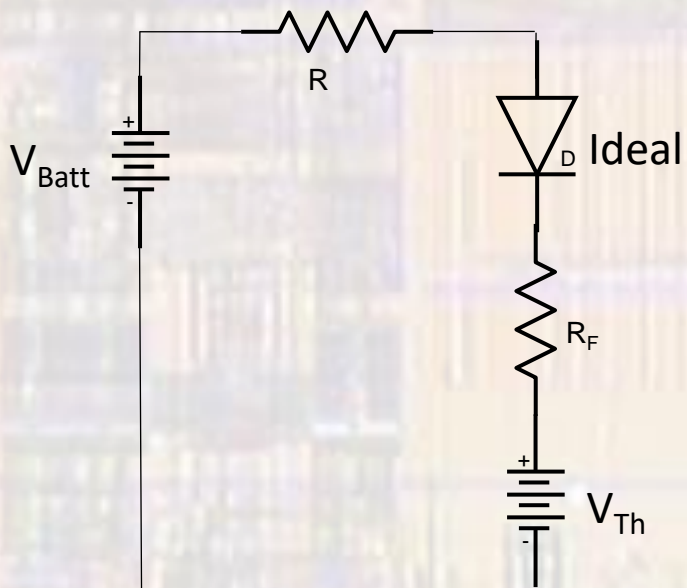- $V_{Th} = V_y = 0.7V$
- $R_F = 5\Omega$



$$V_{Batt} = I_D R + I_D R_F + V_{Th}$$

$$I_D = (V_{Batt} - V_{Th}) / (R + R_F)$$

$$V_{batt} = 3.3V, R = 1K\Omega, V_{TH} = 0.7V, R_F = 5\Omega$$
$$I_D = 2.587mA$$

Diode Circuit Analysis

- Comparison

Exact

Simulate instead

$$V_{Batt} = I_S \left(e^{\frac{V_D}{nV_T}} - 1 \right) R + V_D$$

$$I_S = 5.3e-15, n = 1, V_{batt} = 3.3V, R = 1K\Omega$$

$$V_D = 0.6999V, I_D = 2.601mA$$

Ideal

Only acceptable for determining functionality

$$V_{Batt} = I_D R$$

$$V_{batt} = 3.3V, R = 1K\Omega, V_{TH} = 0.7V, R_F = 5\Omega$$

$$I_D = 3.3mA$$

Ideal w/ V_{Th}

The best choice for almost all situations

$$V_{Batt} = I_D R + V_{Th}$$

$$V_{batt} = 3.3V, R = 1K\Omega, V_{TH} = 0.7V, R_F = 5\Omega$$

$$I_D = 2.60mA$$

Piecewise linear

$$V_{Batt} = I_D R + I_D R_F + V_{Th}$$

$$V_{batt} = 3.3V, R = 1K\Omega, V_{TH} = 0.7V, R_F = 5\Omega$$

$$I_D = 2.587mA$$