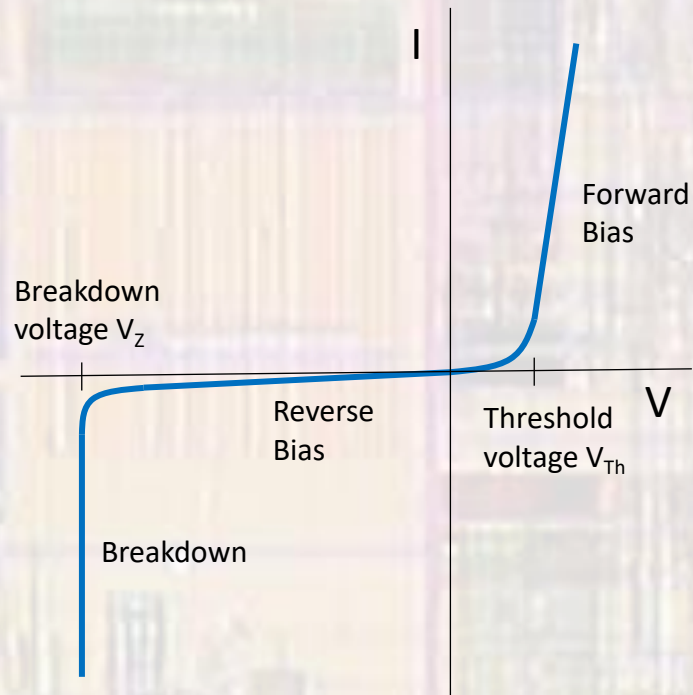


# Diode Models

Last updated 3/8/23


# Diode Models

- Real diode behavior



# Diode Models

- Real diode behavior


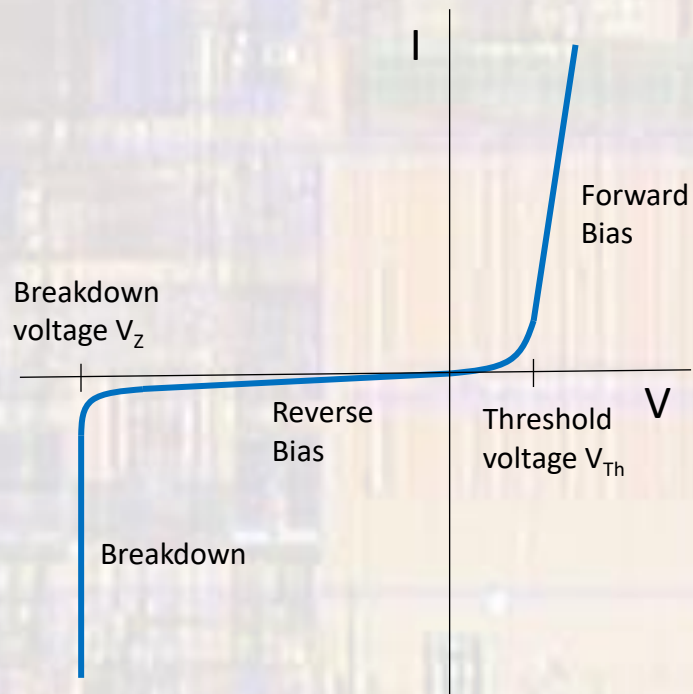


$$I_D = I_S \left( e^{\frac{V_D}{nV_T}} - 1 \right)$$

$V_D > V_Z$



# Diode Models

- Ideal diode models
  - Switch model

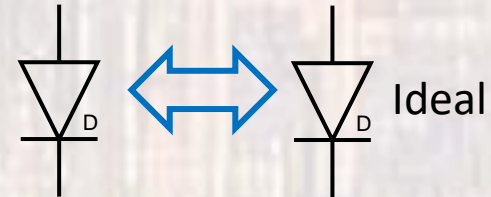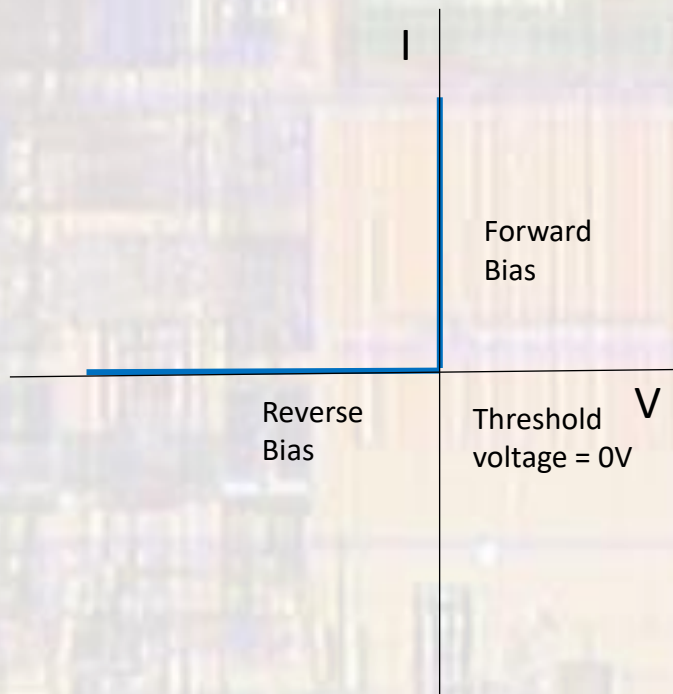
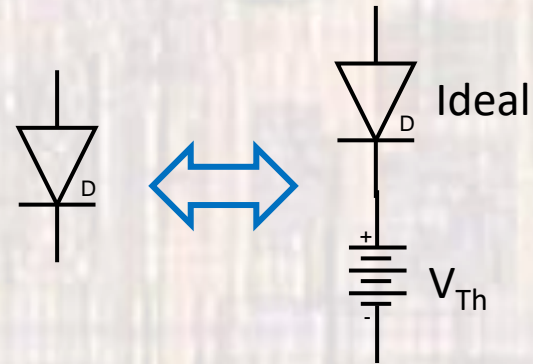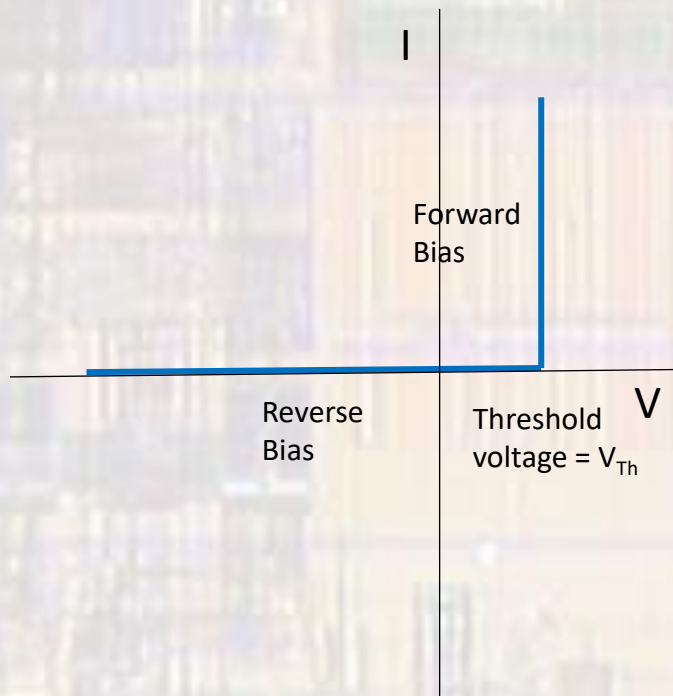
# Diode Models



- Ideal diode models
  - Switch model with Turn-on voltage





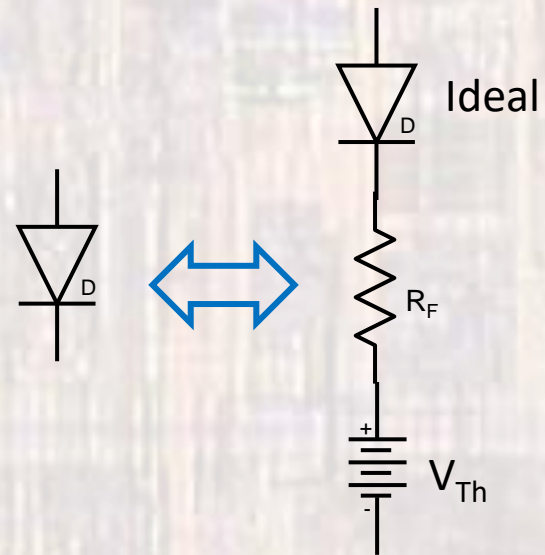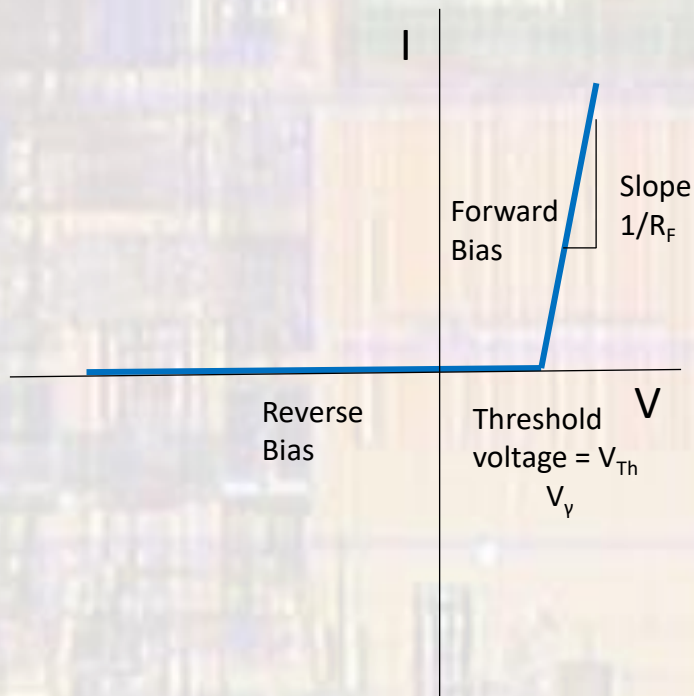
# Diode Models

- Ideal diode models
  - Piecewise Linear model




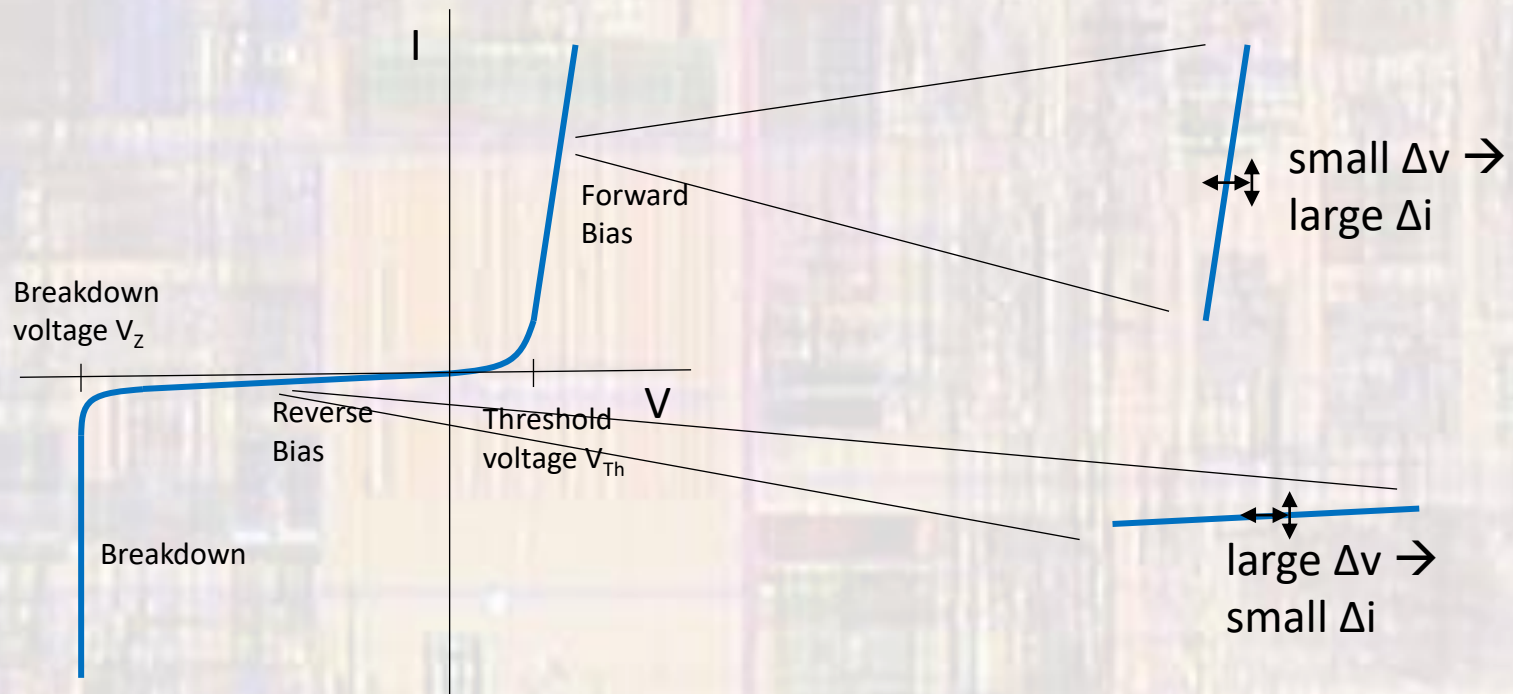
# Diode Models

- Small Signal Model
  - Consider the I-V characteristics constant



# Diode Models


- Small Signal Model

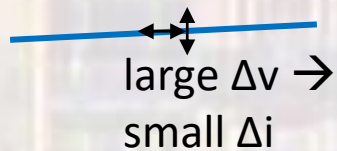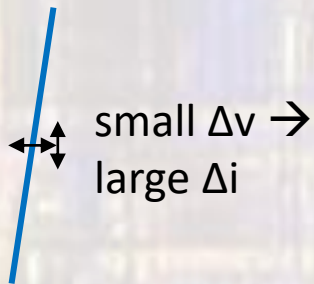

$I_D$  – DC current  
 $V_D$  – DC voltage  
 $i_d$  – small signal current  
 $v_d$  – small signal voltage

$$i_d = \left( \frac{I_D}{V_T} \right) v_d = \left( \frac{1}{r_d} \right) v_d$$

$$r_d = \left( \frac{V_T}{I_D} \right)$$

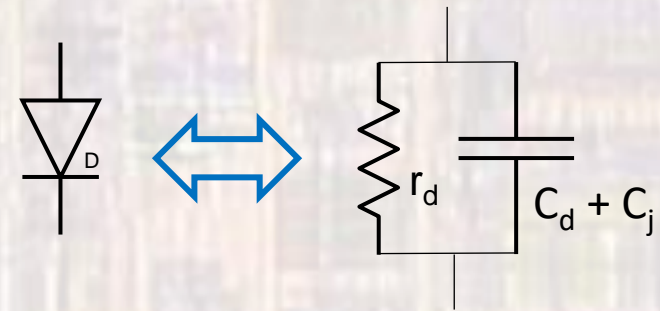

$C_j$  – Junction Capacitance  
 $C_d$  – Diffusion Capacitance

$C_j$  – dominant in reverse bias  
 $C_d$  – dominant in forward bias