

Emitter Coupled Logic Basics

Last updated 3/8/22


Emitter Coupled Logic - Basics

- History
 - Invented by IBM in the 1950s
 - High Speed logic solution of the 60s and 70s
 - Due to power concerns – used only where required
- 500ps gate delays possible by the mid 70s
- Replaced by NMOS and then CMOS in the 80s

Emitter Coupled Logic - Basics

- Inverter / Buffer Core Circuit

Configured for 0, -5.2V operation


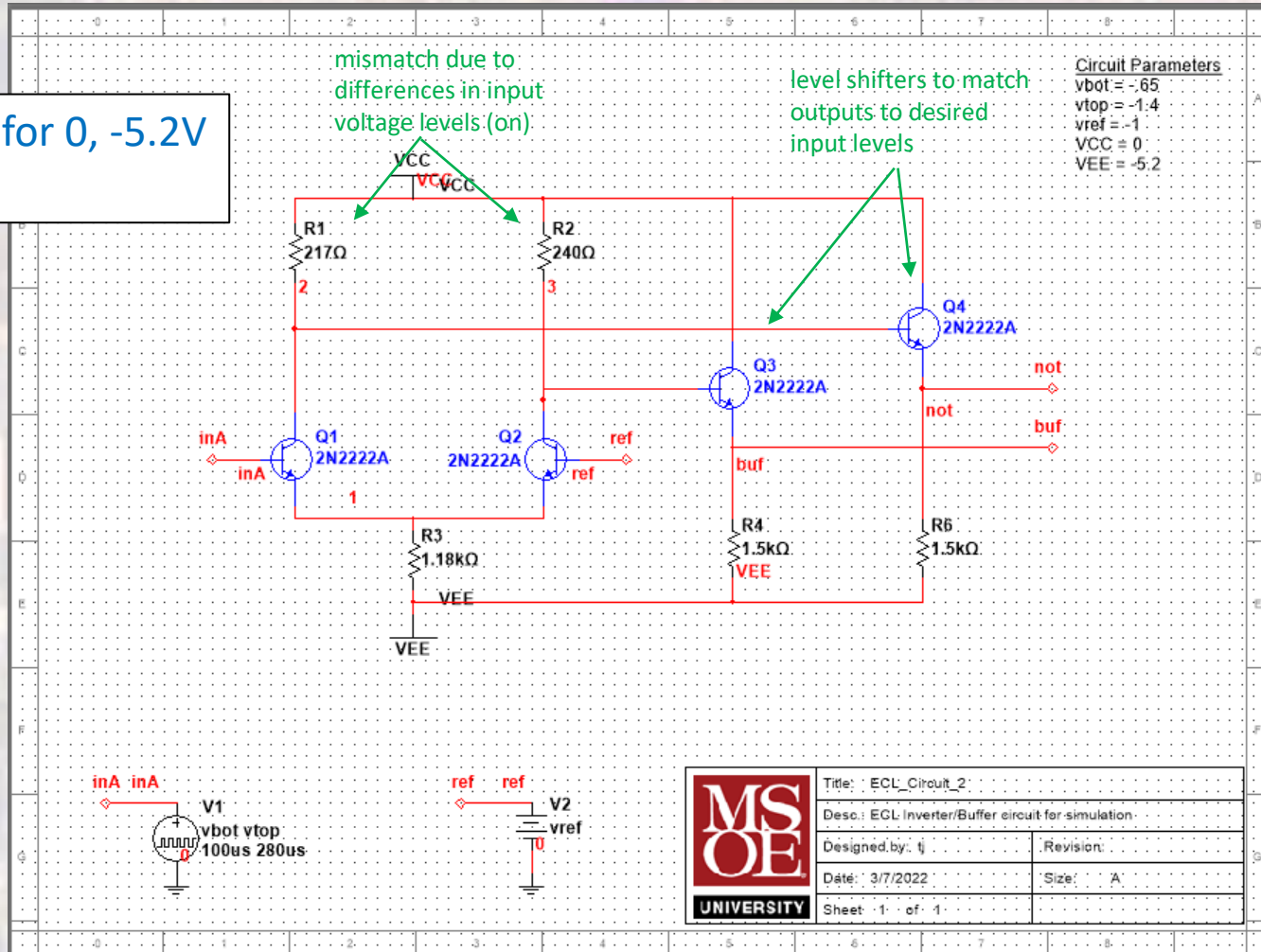


Emitter Coupled Logic

- Inverter / Buffer Core Circuit

- Low Speed
- 0V, -5.2V





Note symmetric switching points

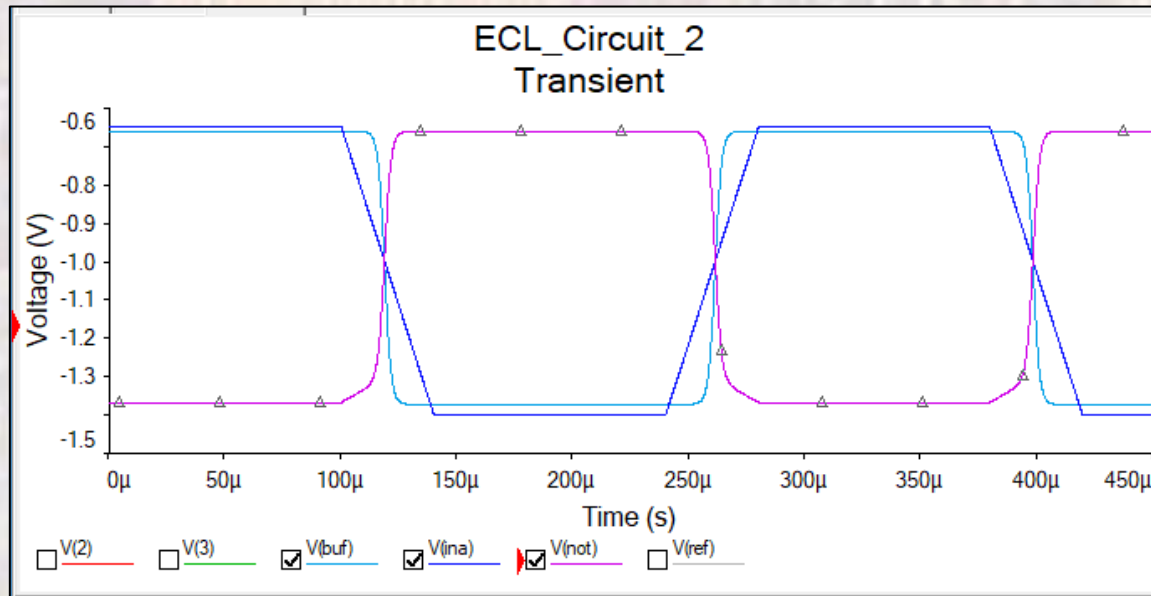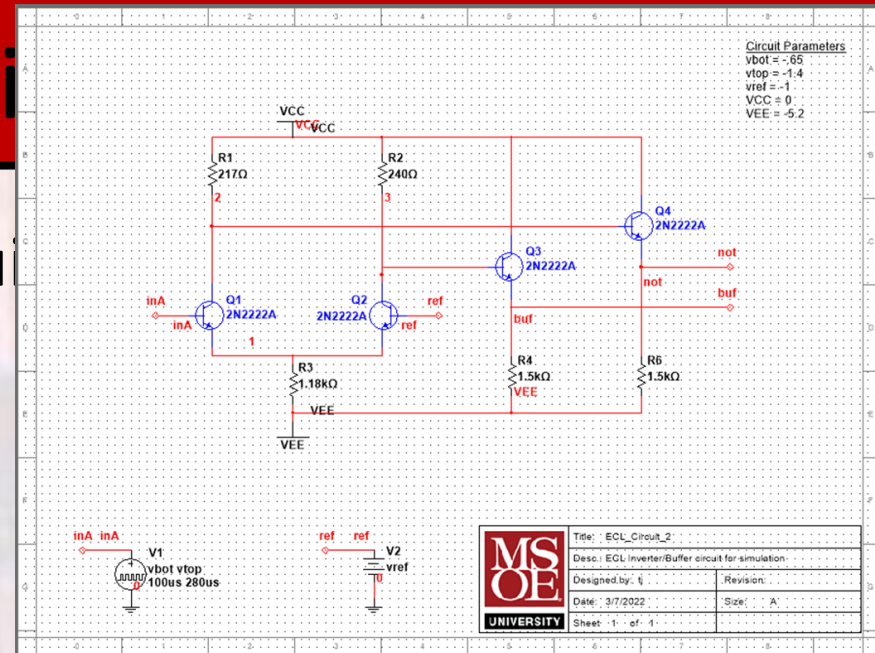

Emitter Coupled Logic

- Inverter / Buffer Core Circuit
- High speed switching
- 0V, -5.2V



Why spikes on v(not) but not v(buf)?

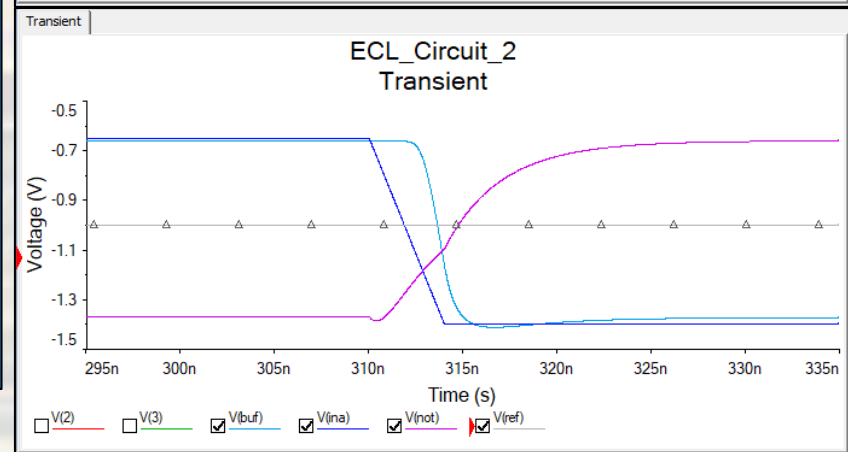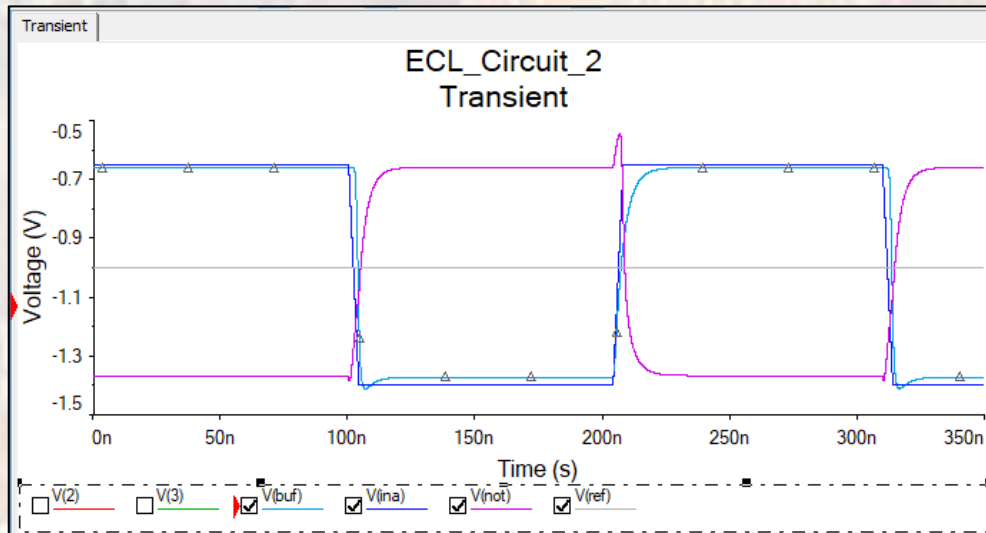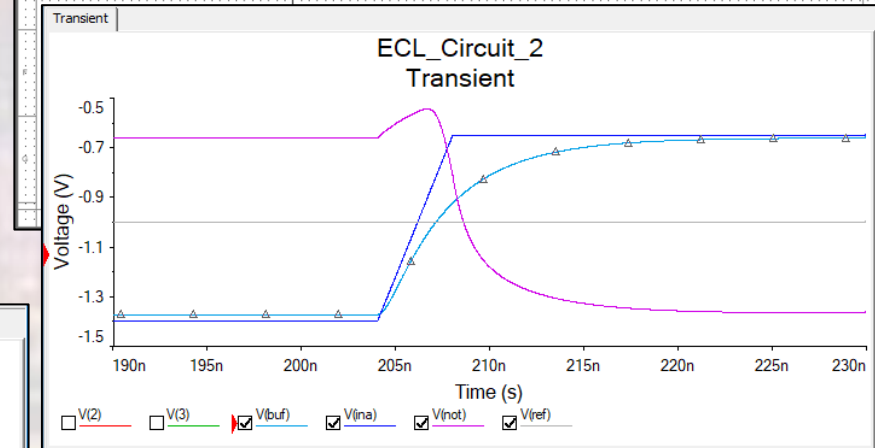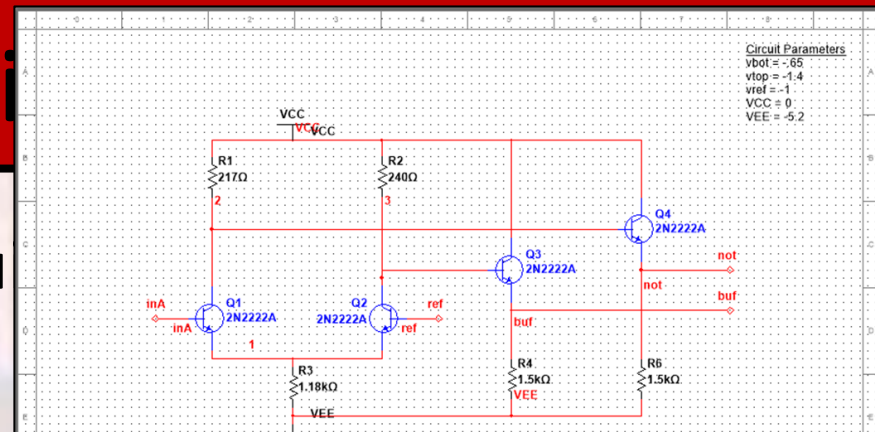

Emitter Coupled Load

- Inverter / Buffer Core Circuit
 - Low Speed
 - 3.3V, 0V
 - No circuit changes

Note symmetric switching points

 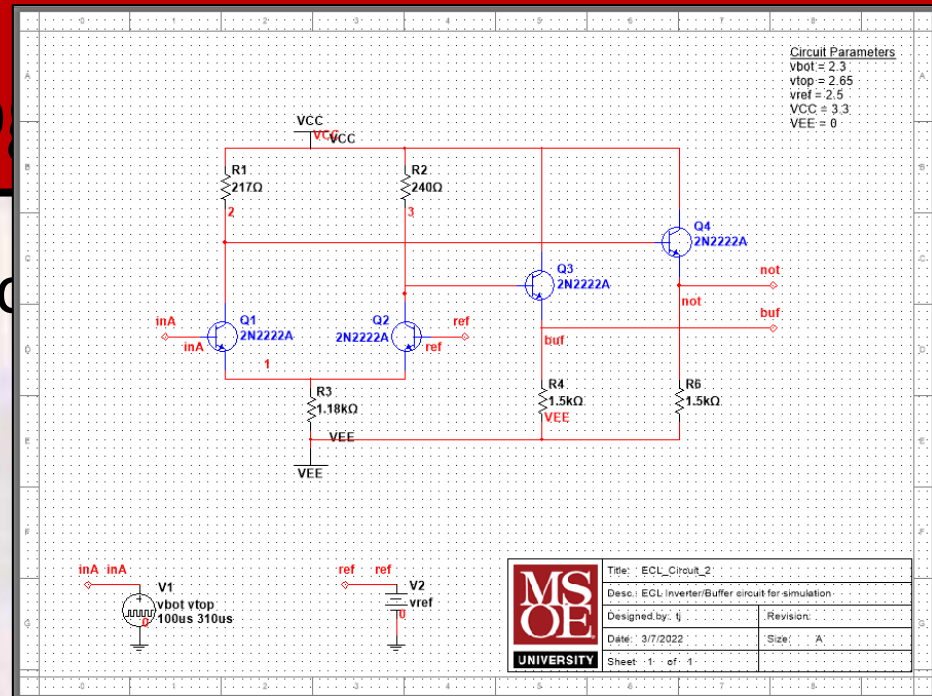

Emitter Coupled Logic - Basics

- Inverter / Buffer Core Circuit
- High speed switching
- 3.3V, 0V
- No circuit changes

Why spikes on v(not) but not v(buf)?

