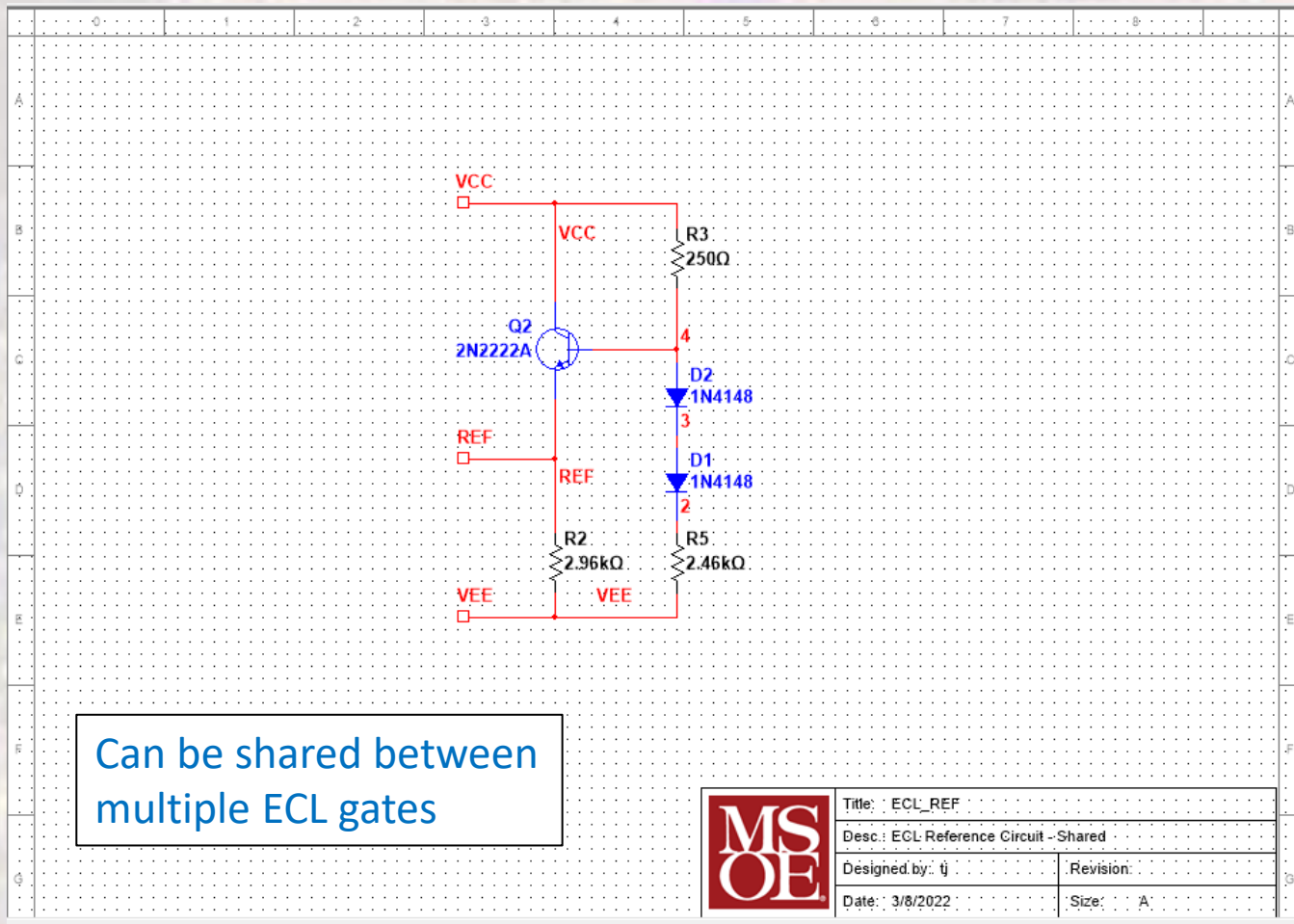


Emitter Coupled Logic Implementation

Last updated 3/8/22


Emitter Coupled Logic - Implementation

- Reference Generator




Emitter Coupled Logic - Implementation

- Reference Generator

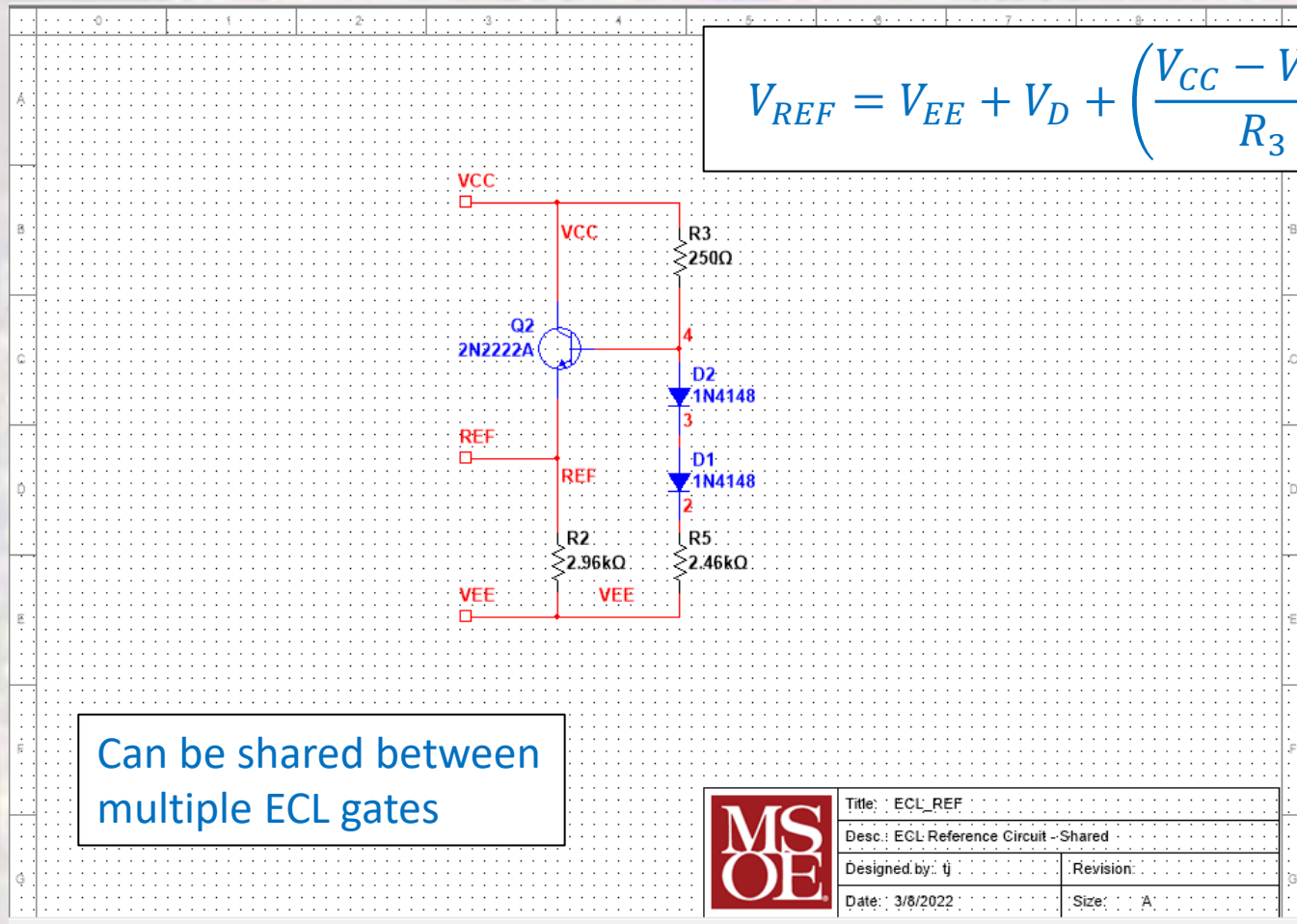


Emitter Coupled Logic - Implementation

- Inverter

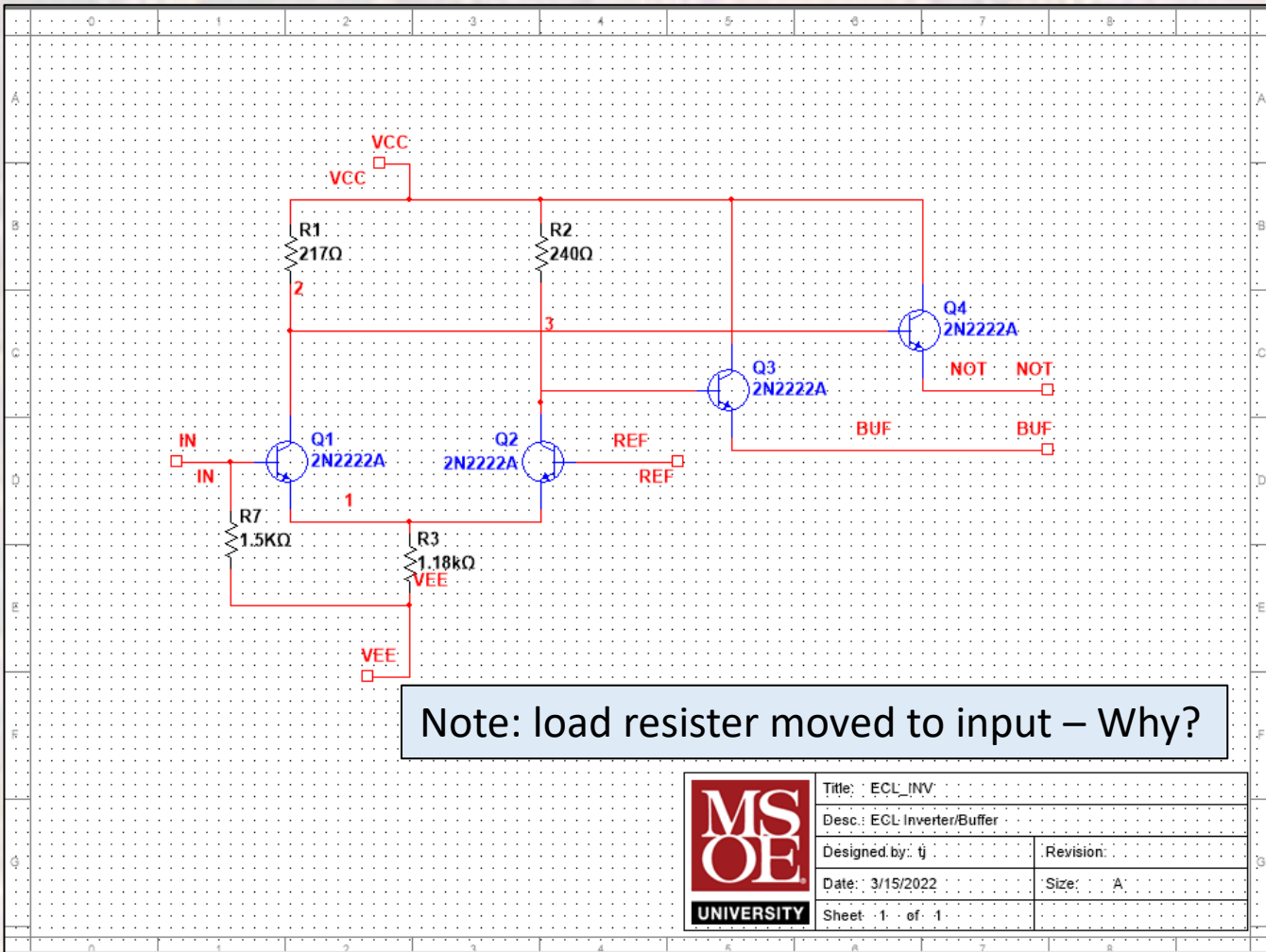


Emitter Coupled Logic - Implementation

- 2 Input NOR/OR

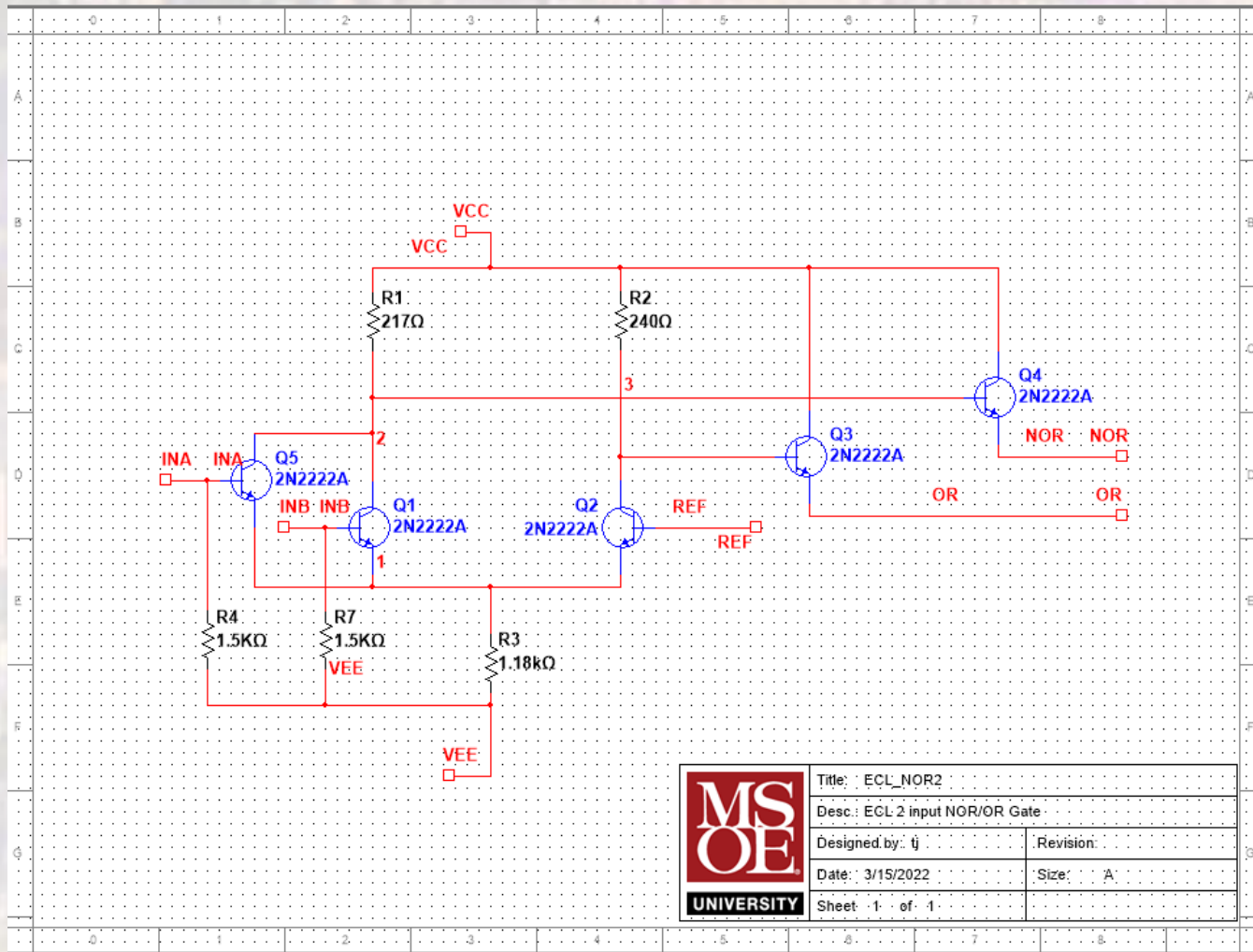


Emitter Coupled Logic - Implementation

- 3 Input NOR/OR

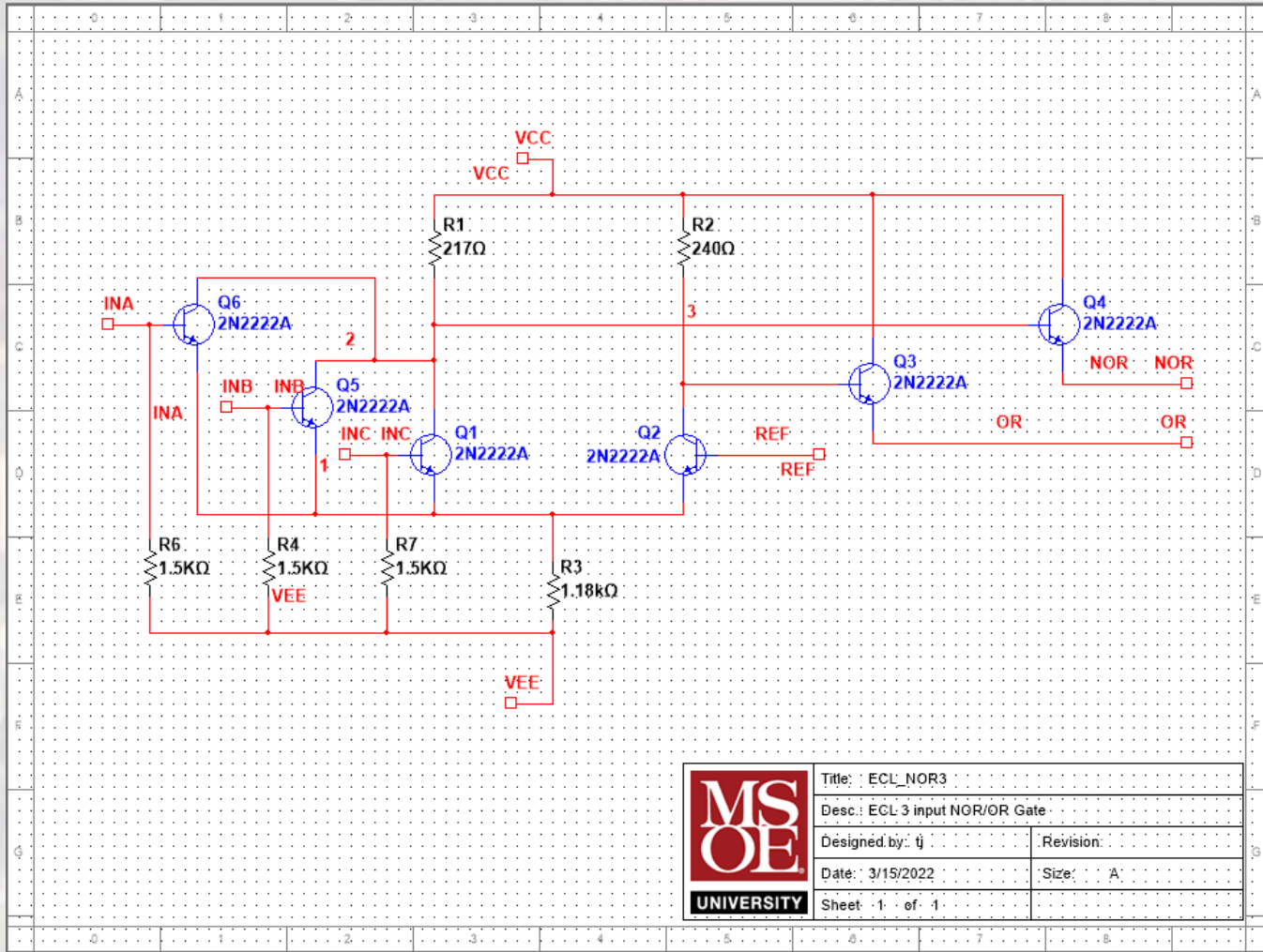


Emitter Coupled Logic - Implementation

- 3 Input NOR/OR

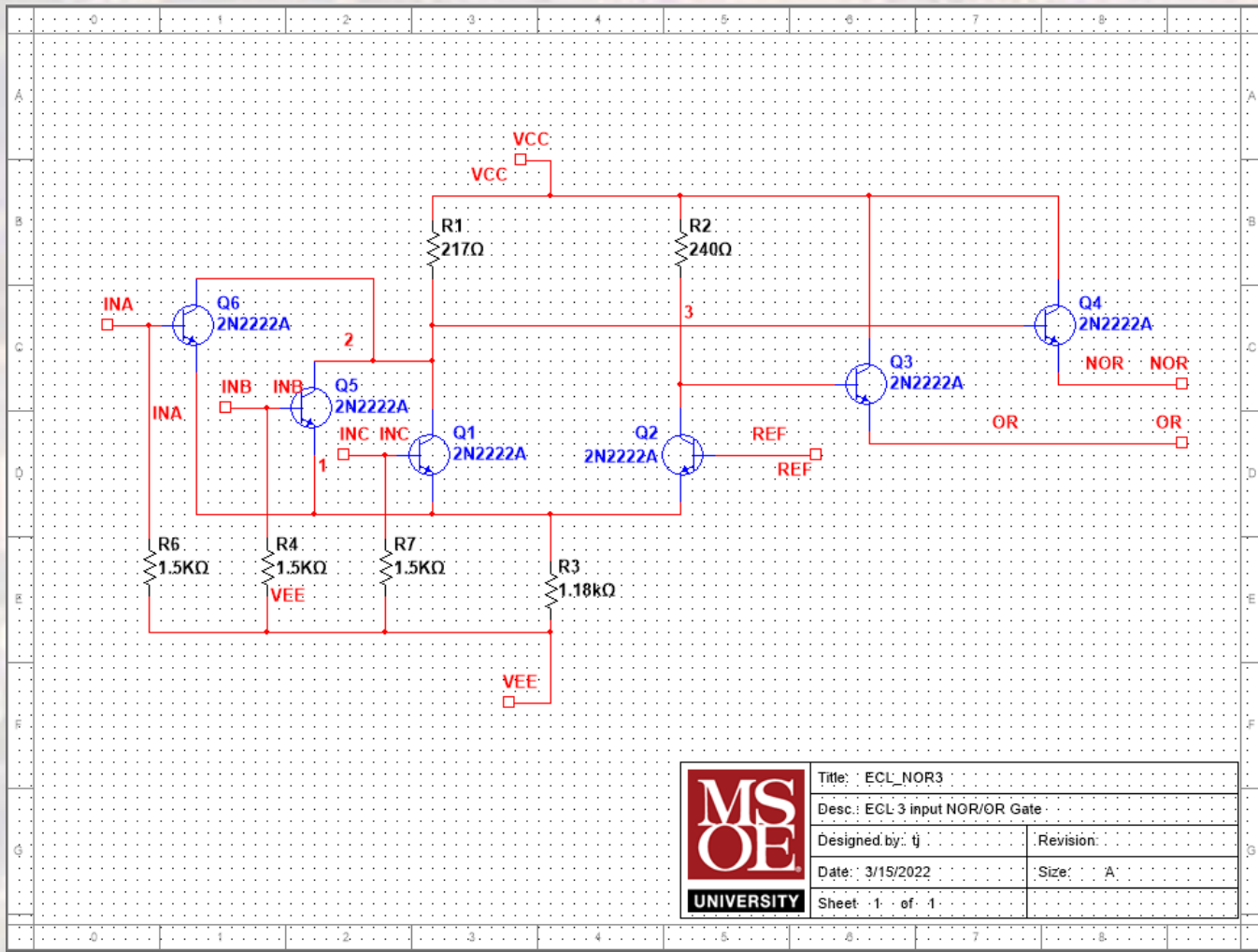

Emitter Coupled Logic - Implementation

- 2 Input NAND/AND

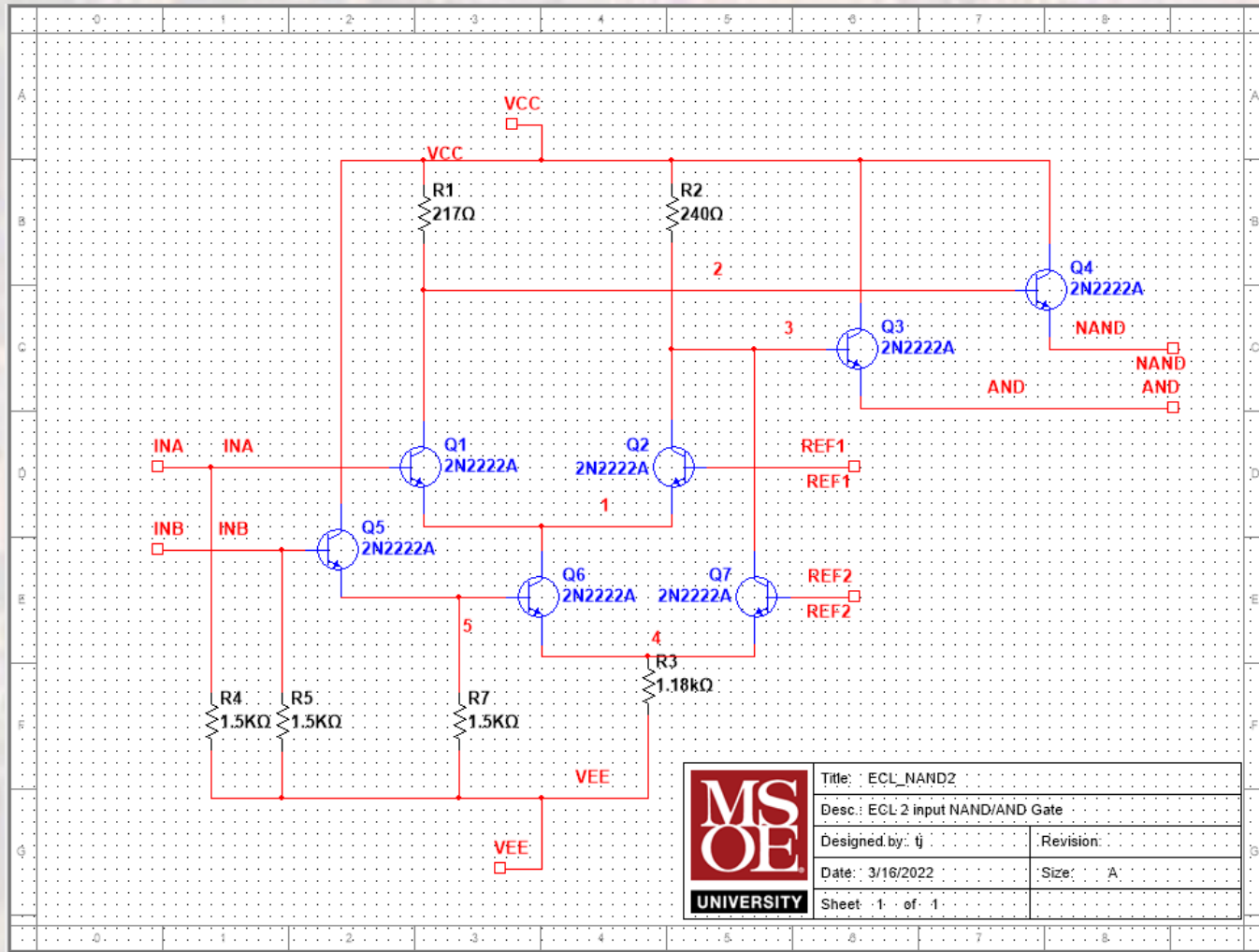

Emitter Coupled Logic - Implementation

- Reference Generator - 2

