
Last updated 4/26/22


- Filter (electronics)
 - A filter is a circuit capable of passing certain signal frequencies while attenuating others
 - Some filters amplify the passed signal frequencies
 - Audio filters
 - Anti-alias filters
 - Signal selection filters
 - Noise reduction filters

Low Pass Filter

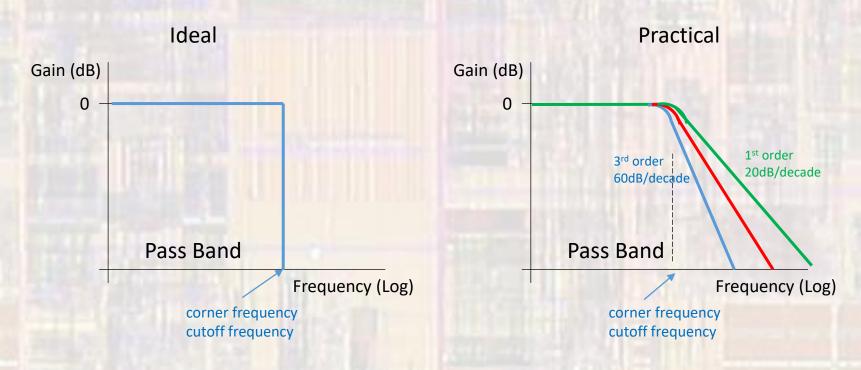- Allows low frequency signals to pass, attenuates high frequency signals
 - Corner frequency defined as passband gain 3dB




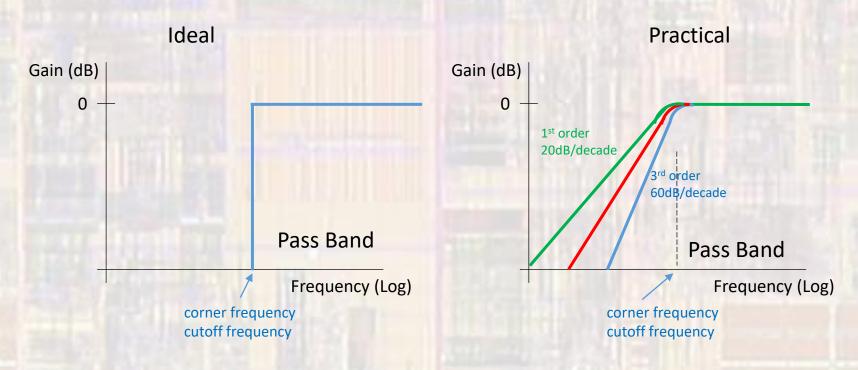- High Pass Filter
 - Allows high frequency signals to pass, attenuates low frequency signals
 - Corner frequency defined as passband gain 3dB




Band Pass Filter

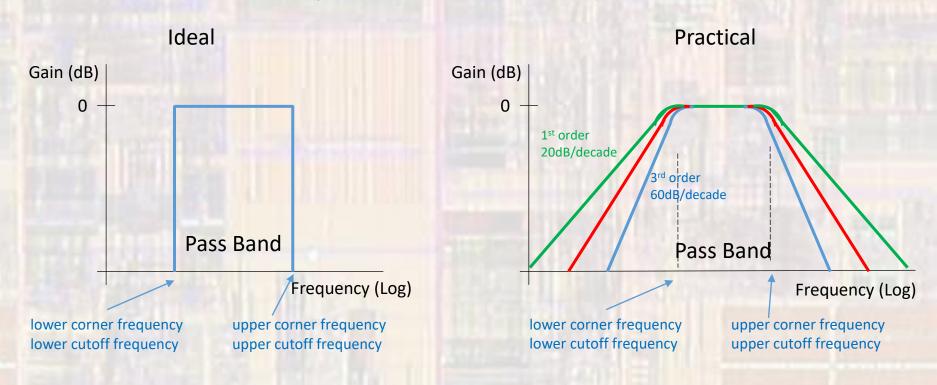- Allows mid frequency signals to pass, attenuates low and high frequency signals
 - Corner frequency defined as passband gain 3dB




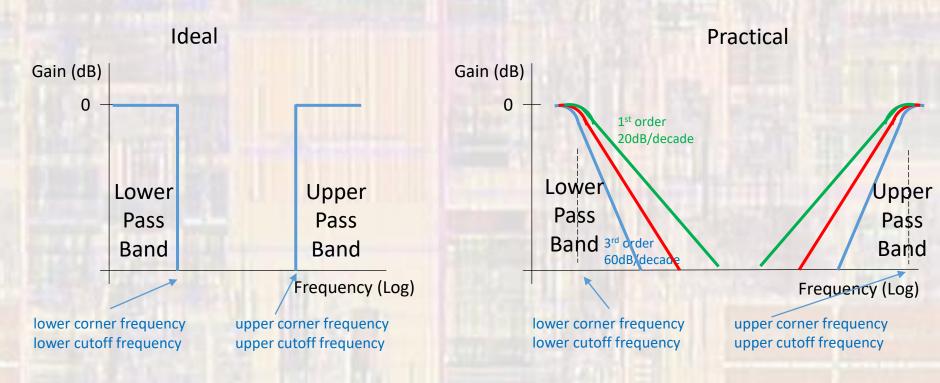
- Band Stop Filter (notch, band reject)
 - Allows high and low frequency signals to pass, attenuates mid frequency signals
 - Corner frequency defined as passband gain 3dB





Phase Shift

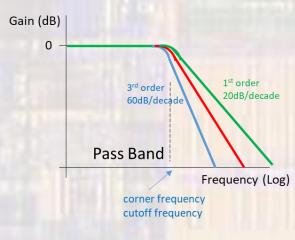 Each type of filter also causes a phase shift in the signal as it passes through



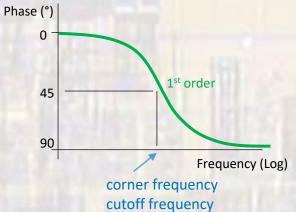

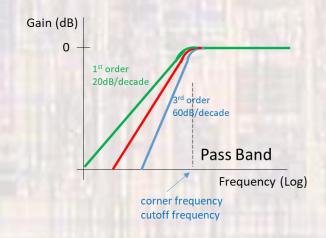

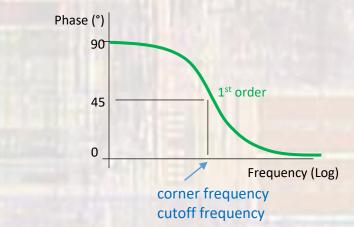

Phase Shift

 Each type of filter also causes a phase shift in the signal as it passes through

