
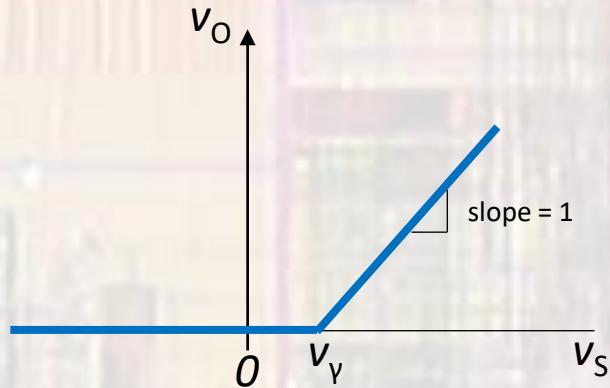


Half-Wave Rectifier

Last updated 12/8/21


Half-Wave Rectifier

- Basic Implementation


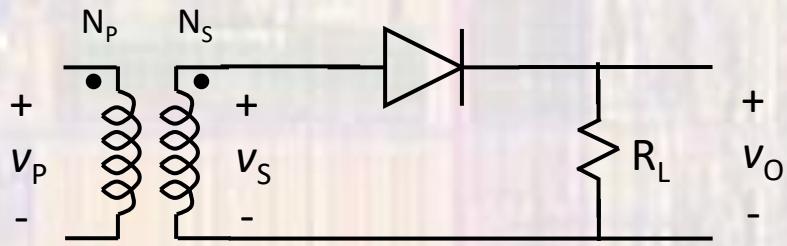


Half-Wave Rectifier

- Basic Implementation


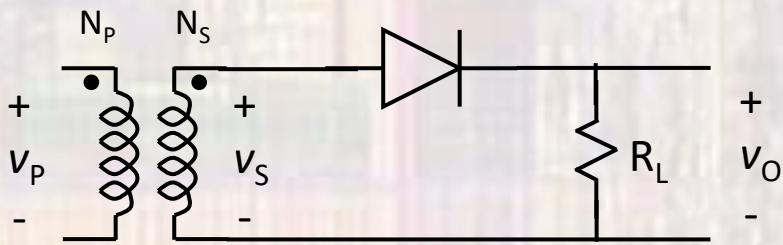


$$v_S = \pm 3V$$

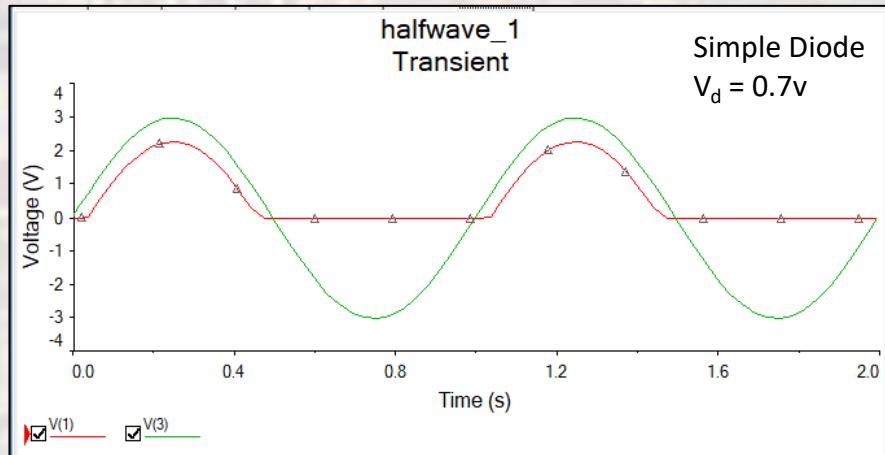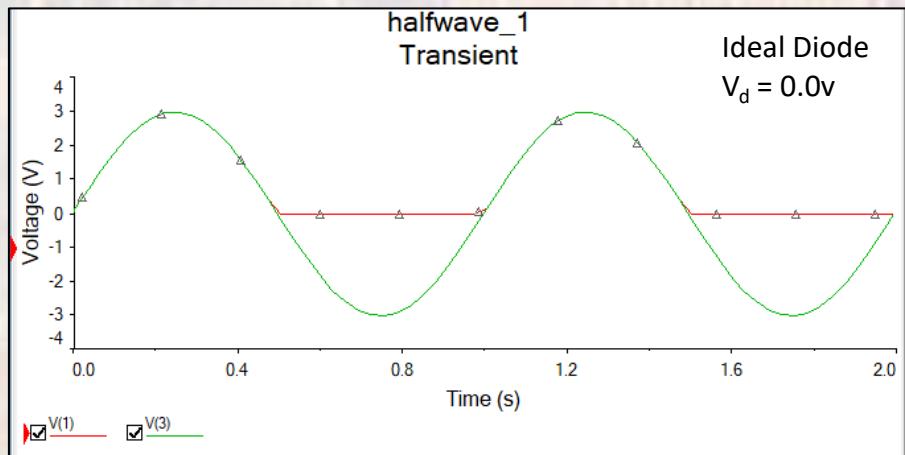

Half-Wave Rectifier

- Design Considerations

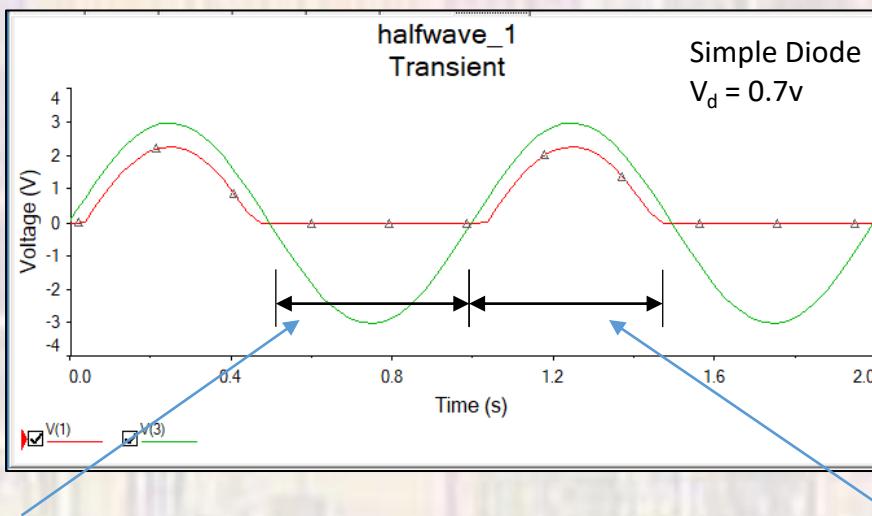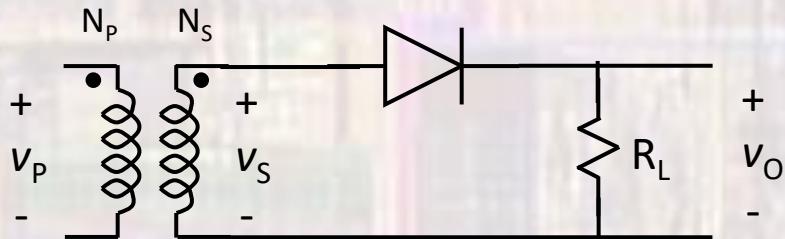


Reversed biased region
 $v_{D\max} = -v_{speak}$
→ breakdown requirement

Forward biased region
 $i_{D\max} = (v_{speak} - v_D)/R$
→ current requirement

Half-Wave Rectifier

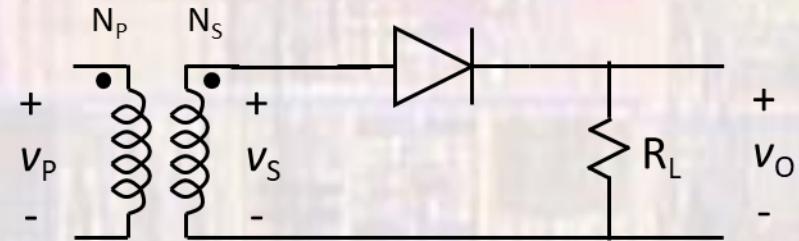- Design Example
 - 120v rms primary voltage
 - Transformer turns ratio: 12
 - Load resistance: $1\text{K}\Omega$
 - What are the diode requirements?



Breakdown:

$$120\text{v rms, 12 turns ratio} \rightarrow v_s = 10\text{v rms}$$

$$10\text{v rms} \rightarrow v_{s\text{peak}} = 14.14\text{v}$$

Current:

$$(14.14\text{v} - v_D)/1\text{K}\Omega \rightarrow 14.14\text{ma} - v_D/1\text{K}\Omega$$

$$\text{typical } v_F \text{ is } 0.6\text{v} \rightarrow 13.54\text{ma}$$

guard band the design:

$$v_F \approx 0.6\text{v}$$

$$V_{\text{breakdown}} > 20\text{v (14v rms)}$$

$$I_{\text{max}} > 20\text{ma}$$