
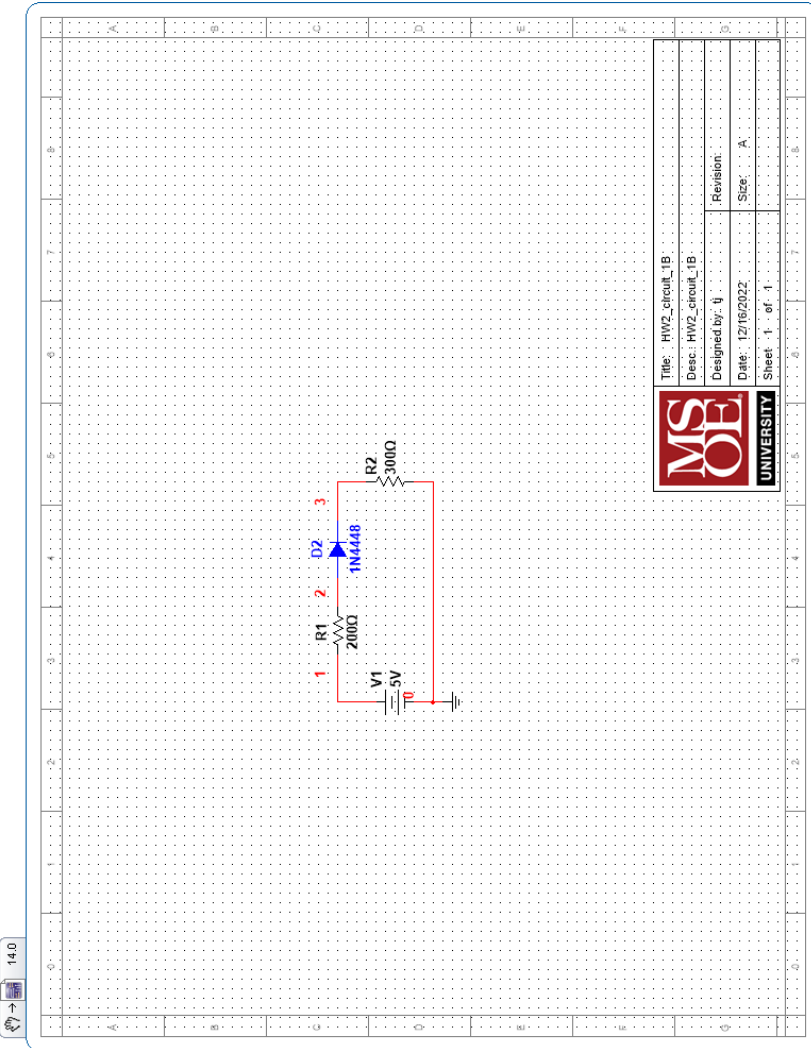


Circuit for parts 1-4

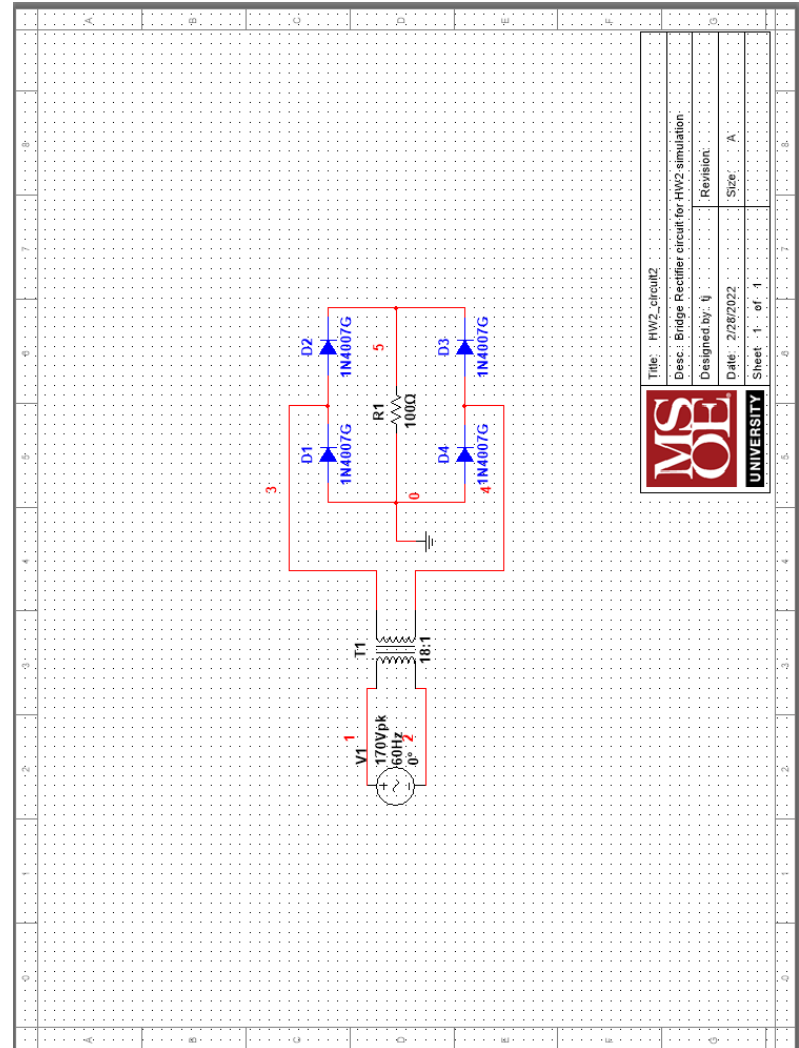

Circuit for part 5



1 – Calculate the current in D2 (assume $V_D = 0.7V$)

10pts

2 – If I_S for D2 is $3 \times 10^{-8}A$ and $n = 2$, calculate the current in D2 with $V_D = 0.7V$
(ignore the rest of the circuit)

20 pts

3 – Calculate the expected V_D for D2 with the current from part 1, and I_S , n from
part 2

20pts

- 4 – Simulate the circuit for part 1 and verify your results for problems 1 and 3.
Provide a screenshot of the DC analysis 20pts

- 4 – Simulate the circuit for part 2 and verify the operation of the bridge rectifier (plot V3, V4, V5) for at least 2 full input periods
- Explain the difference in peak voltages between V3/V4 and V5 30pts