

- 1 – Design: Design and simulate a second order low pass filter with a cutoff (3dB) frequency of 100KHz, and a gain of 1.5
Use a UA741CD opamp
40pts

- 2 – Design: Design and simulate a fourth order high pass filter with a cutoff (6dB) frequency of 20KHz
Use a UA741CD opamp

60pts