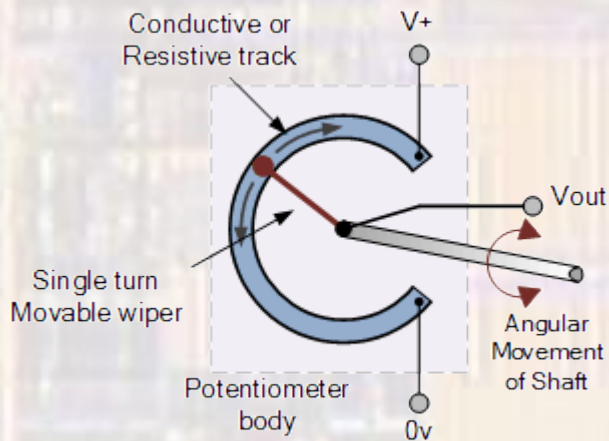


Interfaces Inputs


Last updated 5/2/22

Interfaces - Inputs


- Potentiometer



Voltage Divider


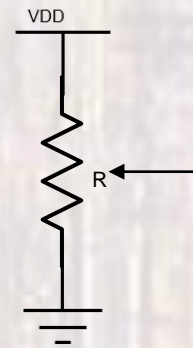


Reostat

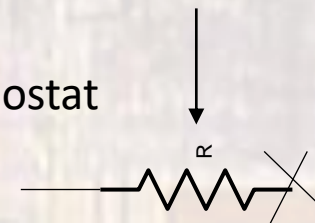

Interfaces - Inputs



- Simple Switch

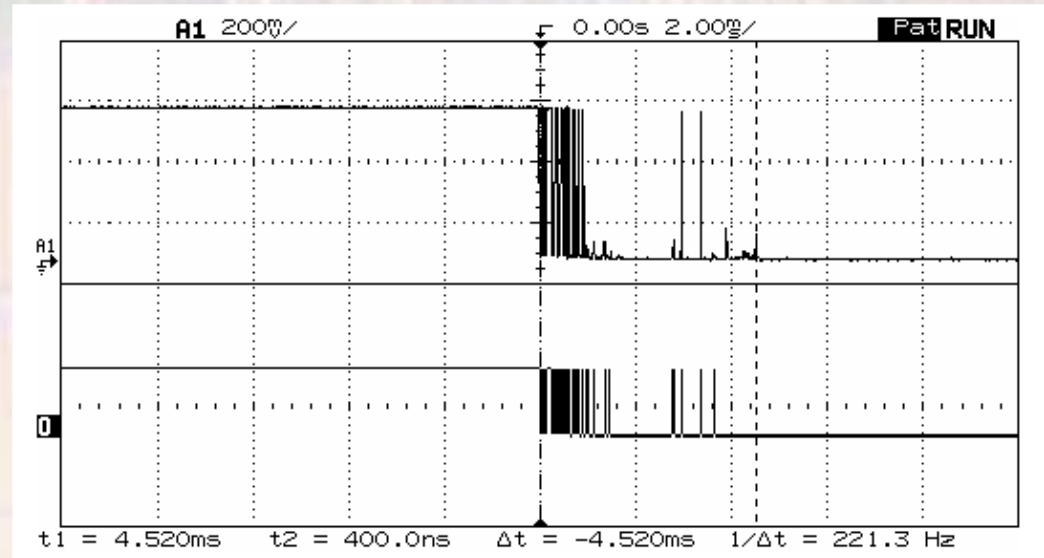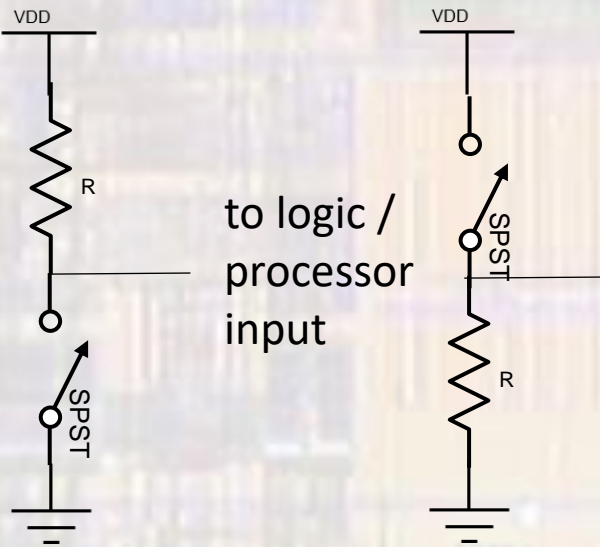

src: The Ganssle Group


Interfaces - Inputs

- Schmitt Trigger Inverter

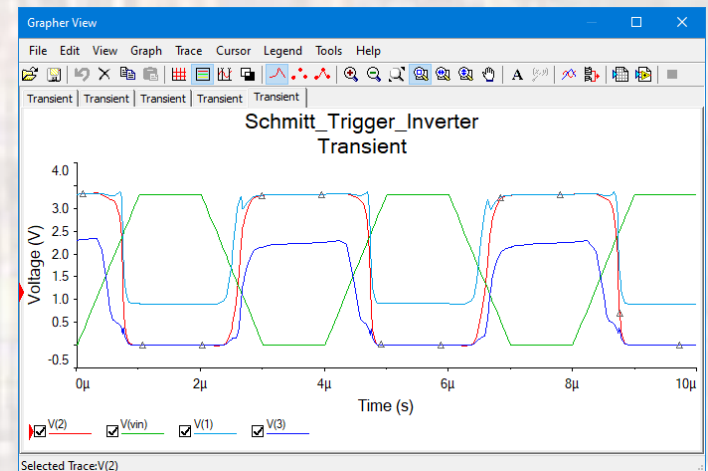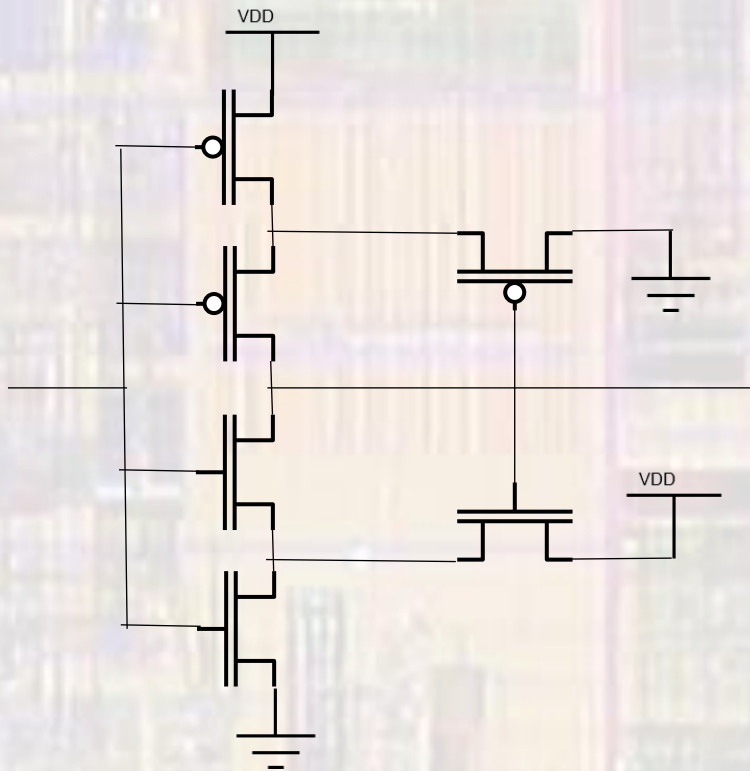


Interfaces - Inputs

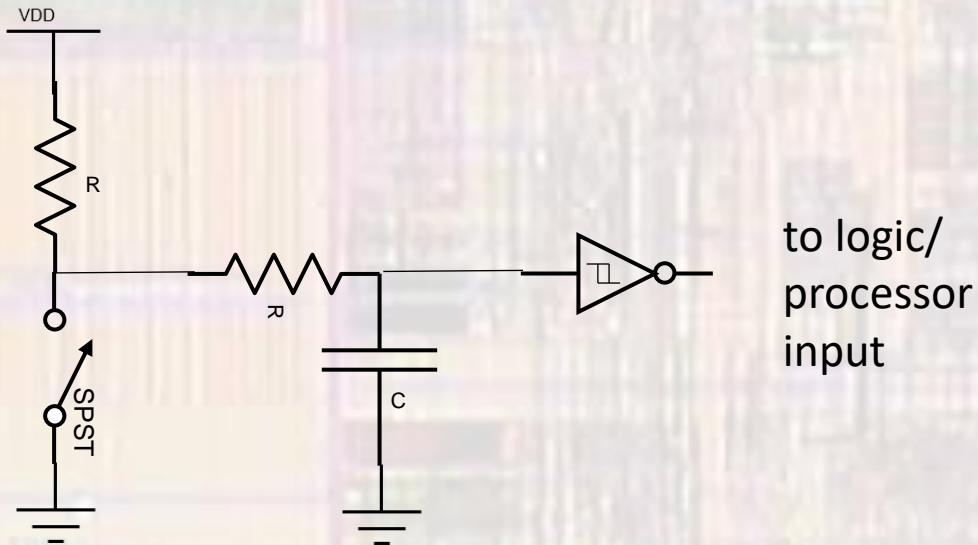- Debounced Switch 1
 - Slows the transition (filters it)
 - Delays the switching time






Interfaces - Inputs

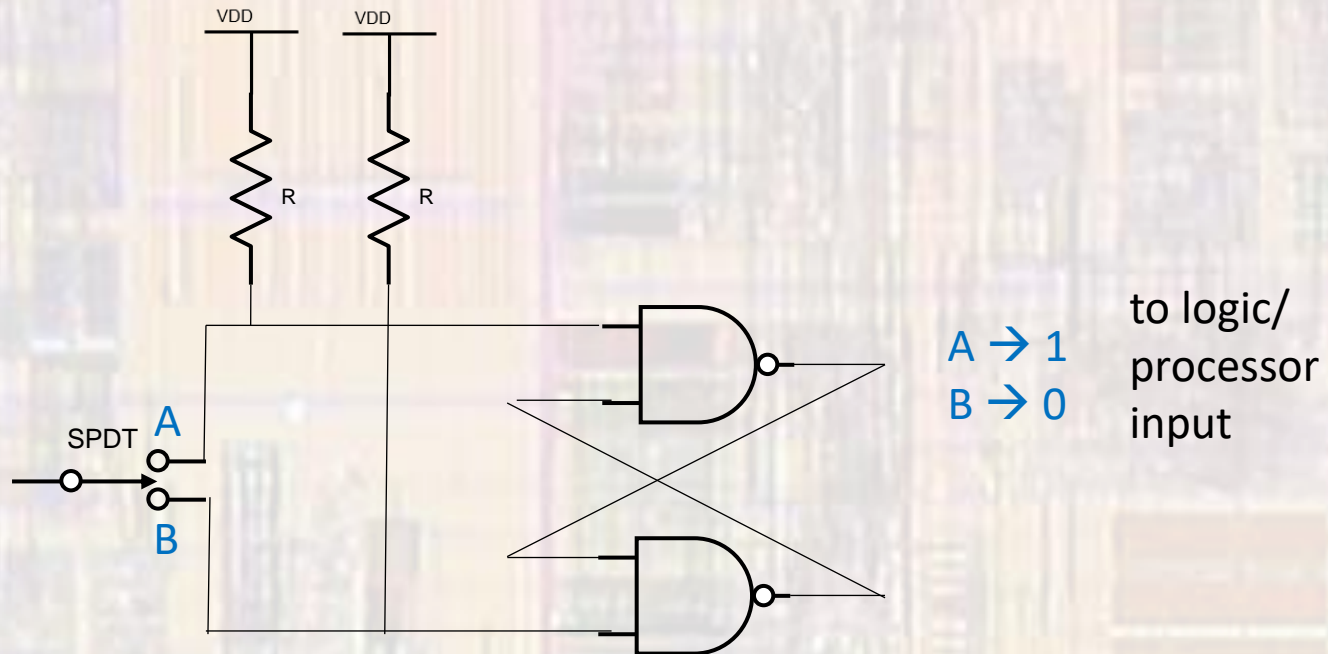- Debounced Switch 2
 - SR latch
 - Requires an SPDT switch





Interfaces - Inputs

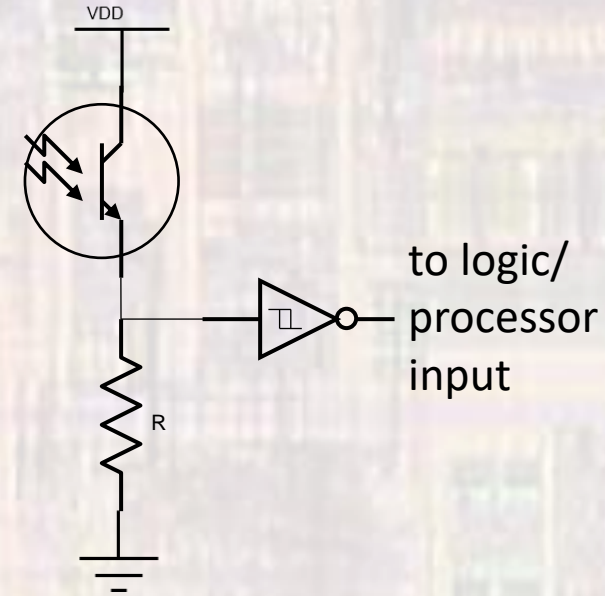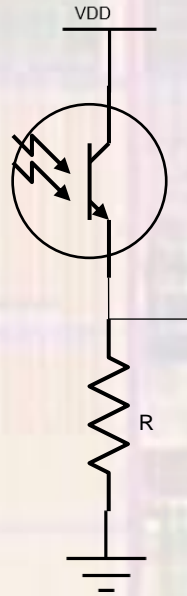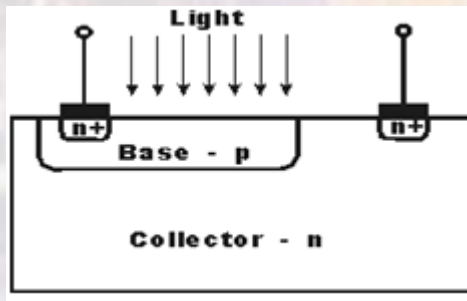- Photo-Transistor
 - Converts light to current




Interfaces - Inputs

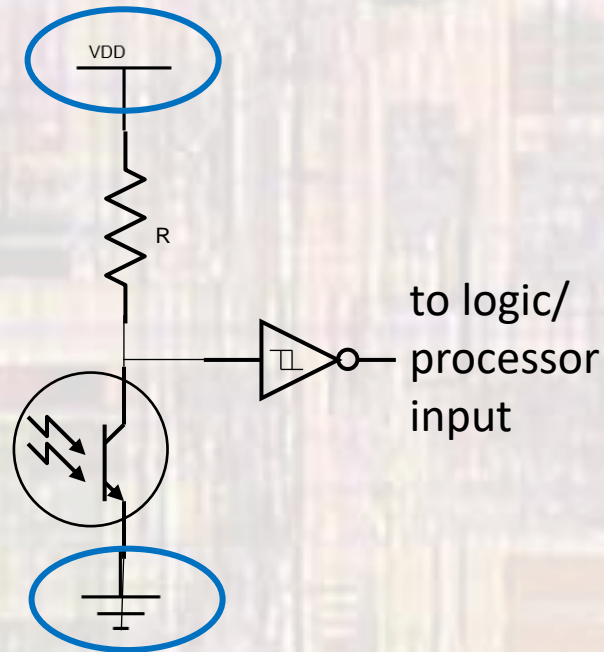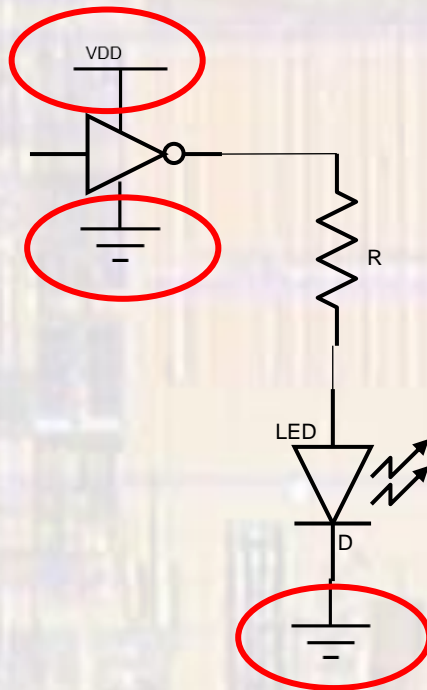- Opto-coupler
 - Transmits a signal using light
 - Isolates Supplies



Interfaces - Inputs

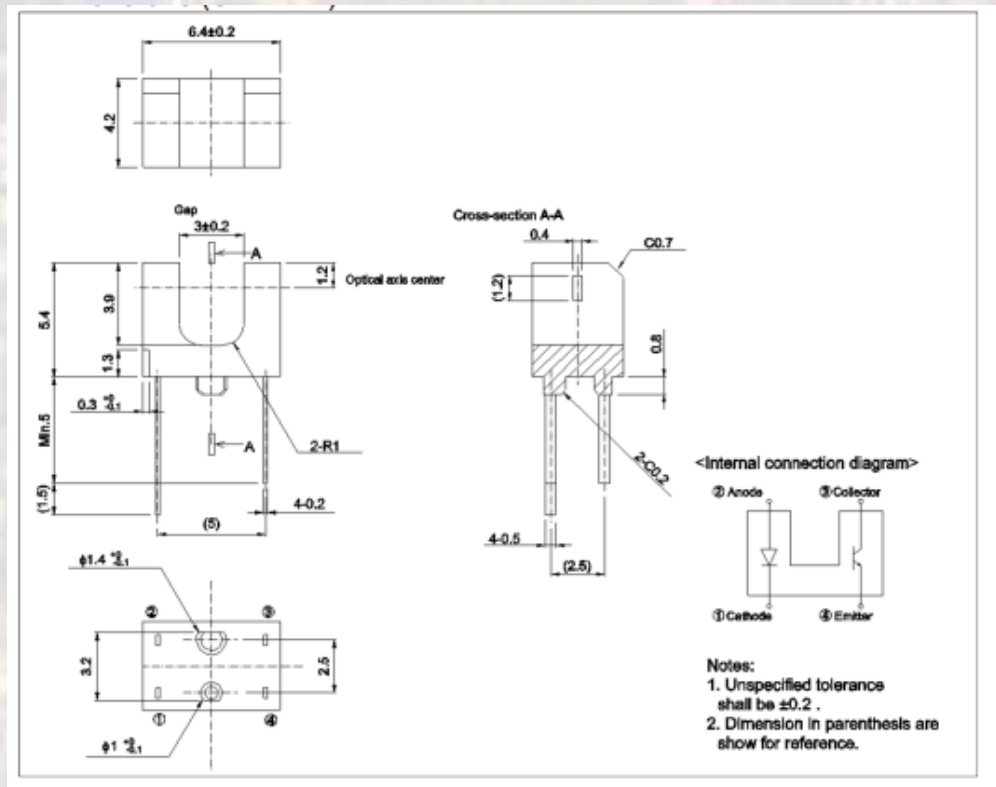- Slotted Opto-coupler
 - Transmits a signal using light
 - Isolates Supplies






● Outline






Interfaces - Inputs

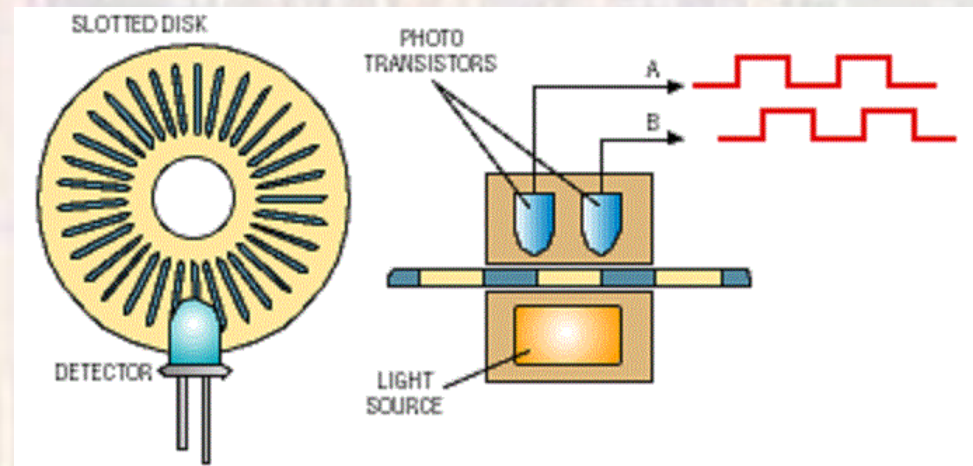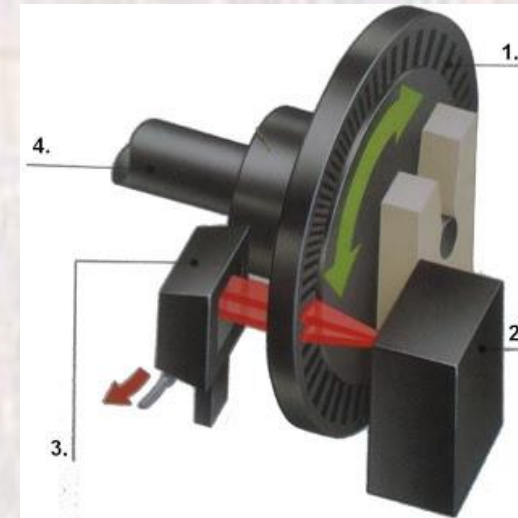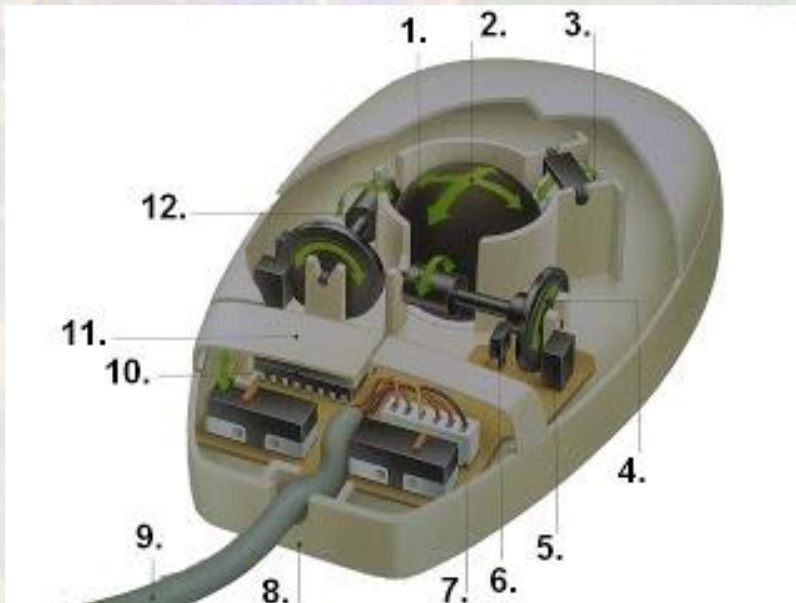- Rotary Encoder
 - Direction
 - Distance





Interfaces - Inputs

- Reflective Coupler
 - Line sensor

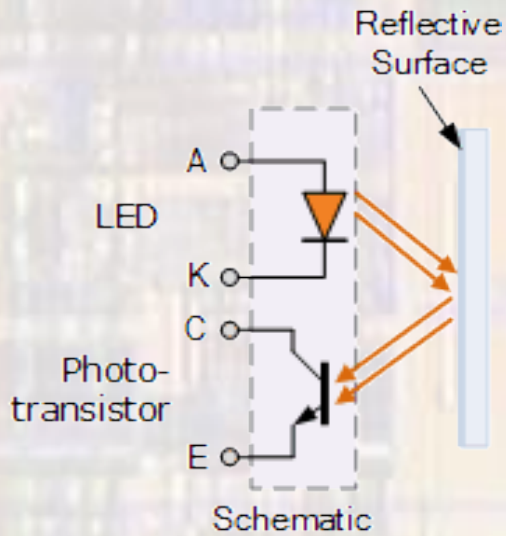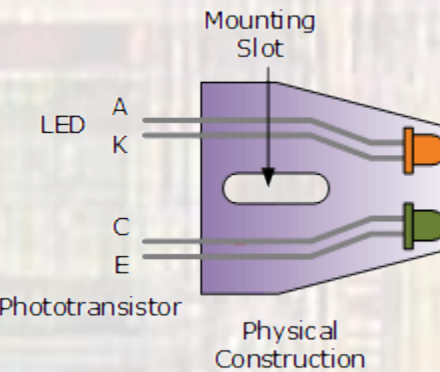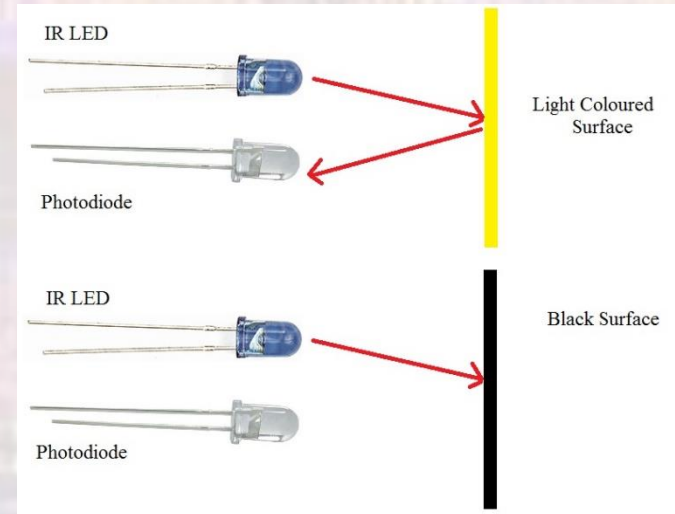


Interfaces - Inputs

- Photo Resistor

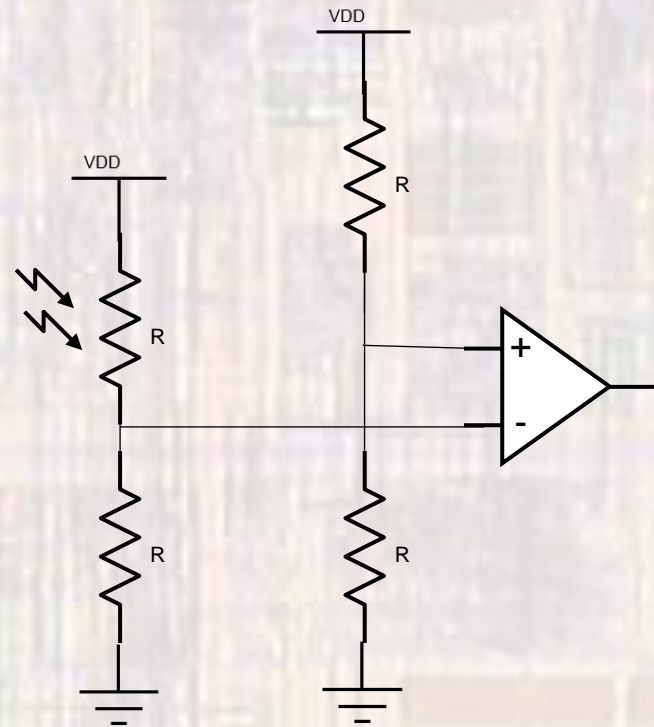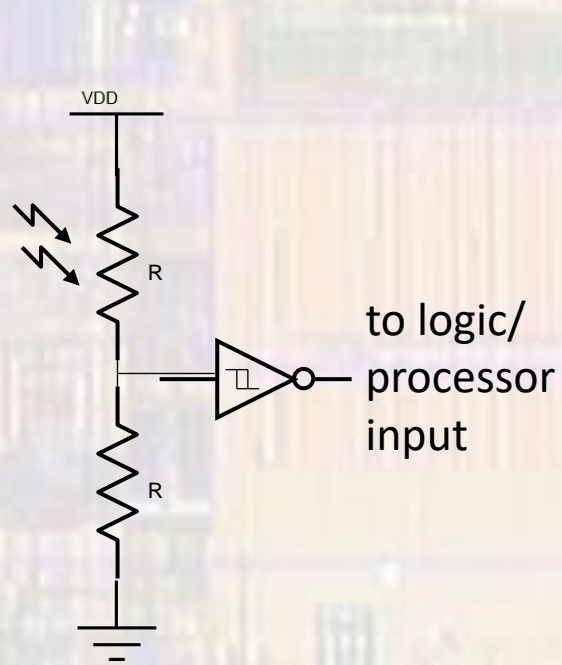


Interfaces - Inputs

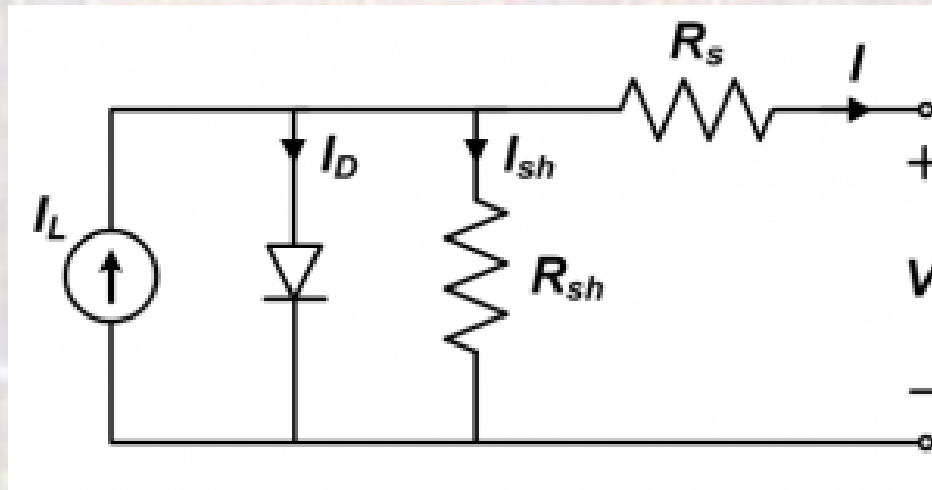- Photovoltaic Cell (Solar Cell)
 - Generates a voltage that is the \ln of the photo-current
 - Put cells in series to generate usable voltages




Interfaces - Inputs

- Moving Coil Microphone

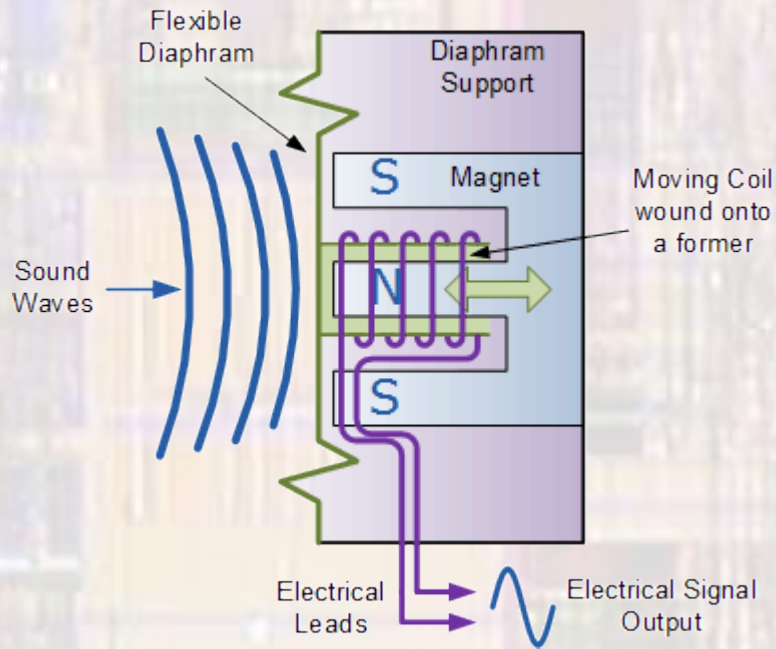


Interfaces - Inputs

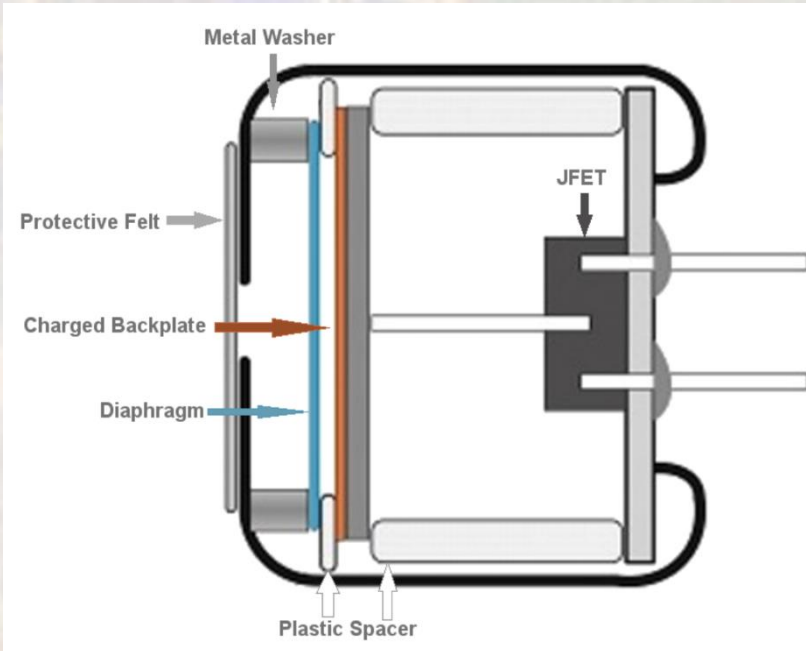- Electret Microphone
 - Sound pressure moves the diaphragm → dC




Fixed Q
 $Q = CV$
 $V = Q/C$
 $dV = QdC$

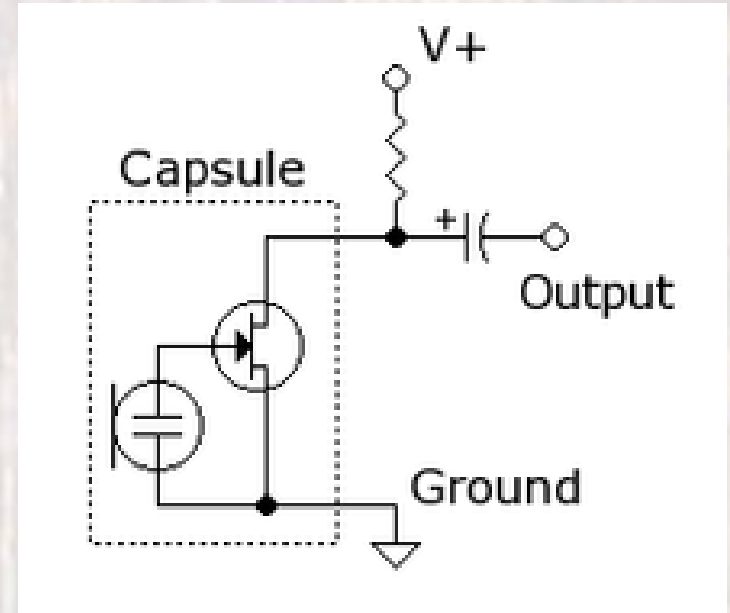

Interfaces - Inputs

- Logic Interfaces – Discrete

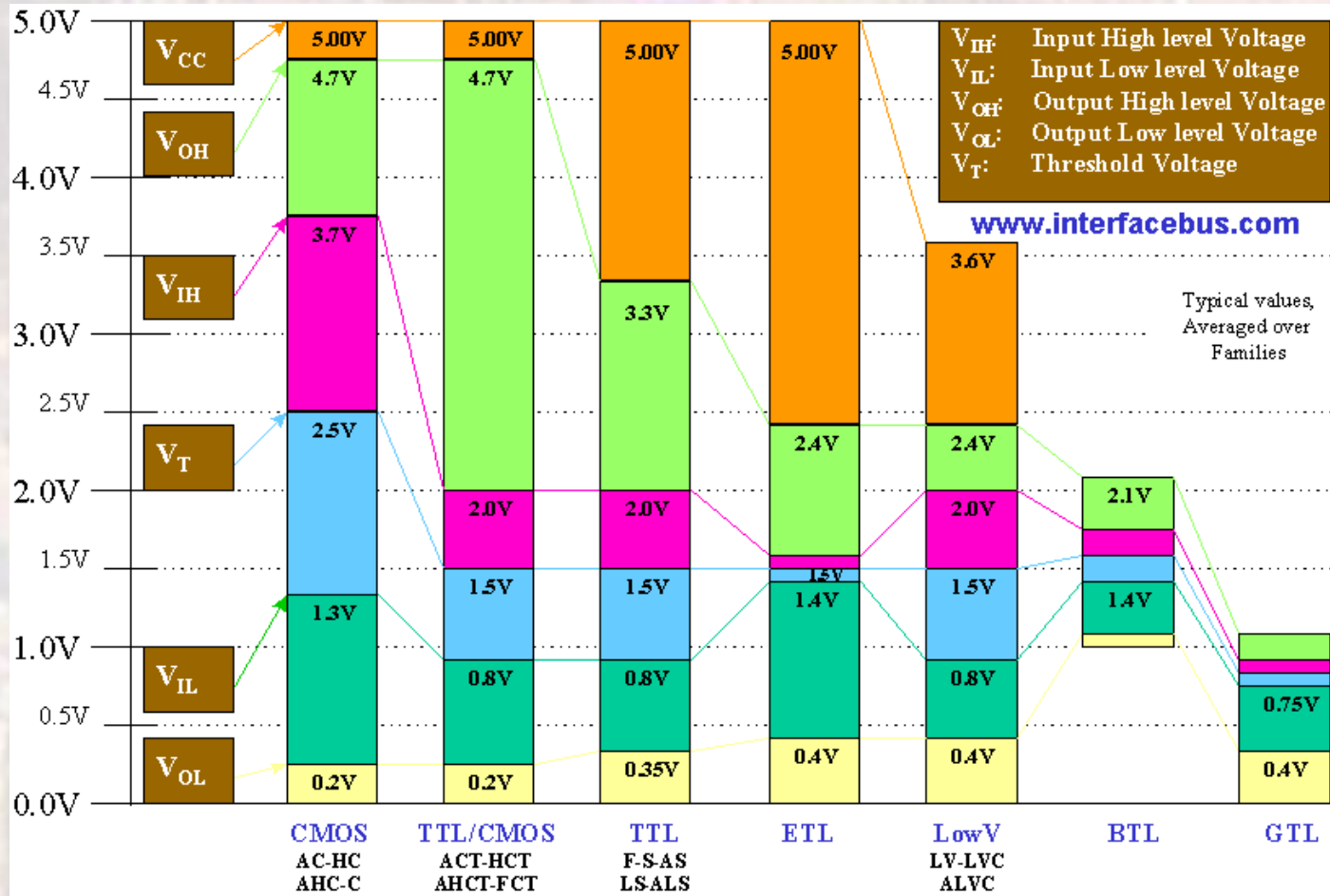

Interfaces - Inputs

- Logic Interfaces – IC

SCEA035A


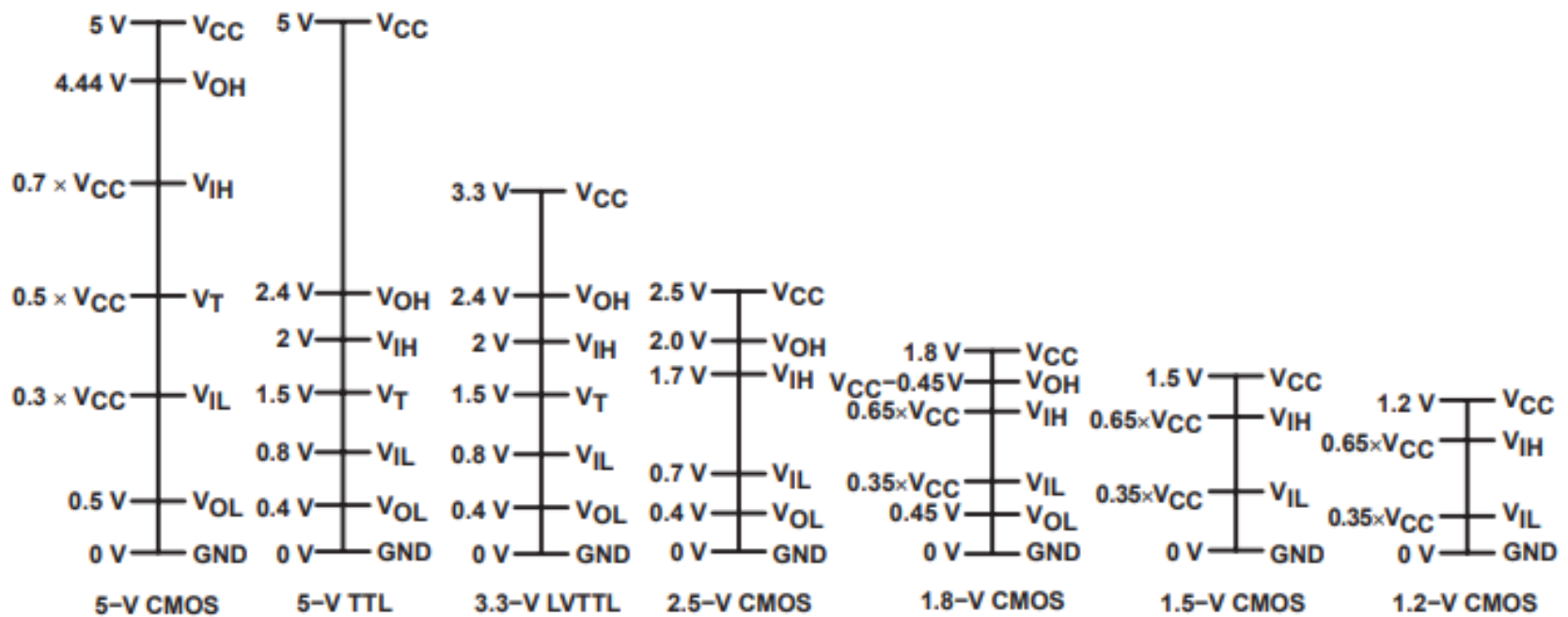


Figure 2. Digital Switching Levels


Interfaces - Inputs

- Logic Interfaces
 - Open Drain

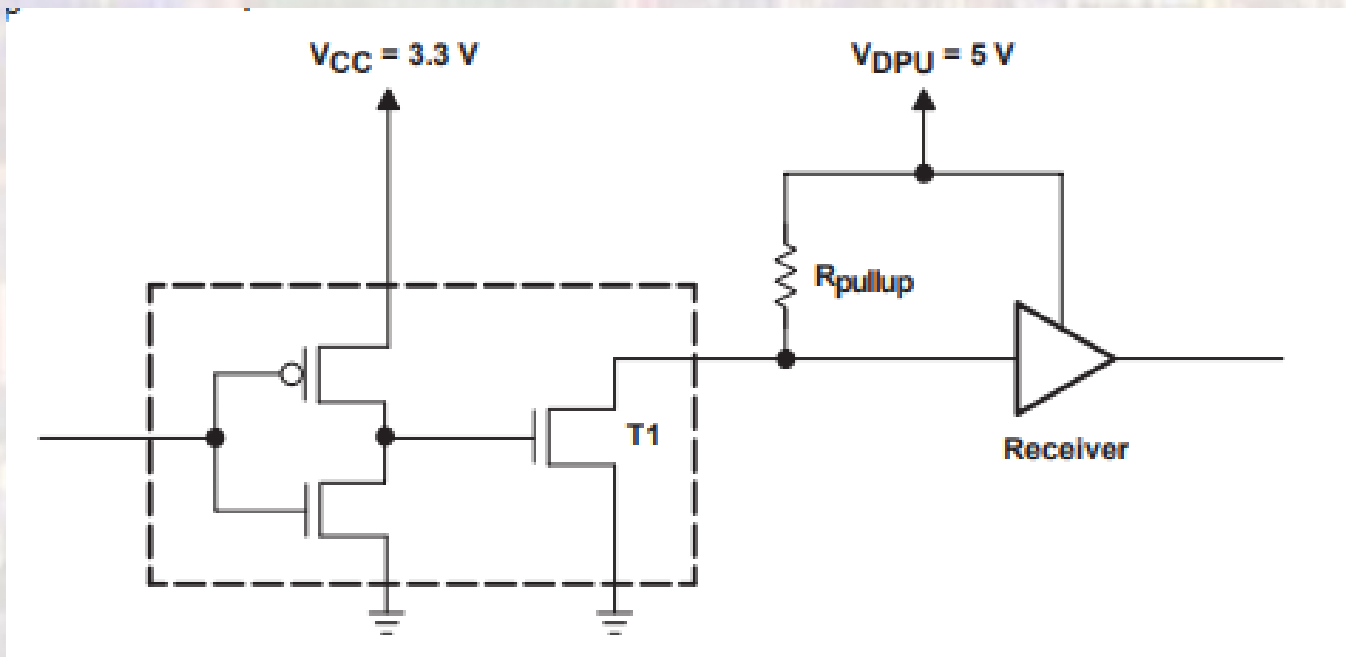

Interfaces - Inputs

- Logic Interfaces
 - Open Drain

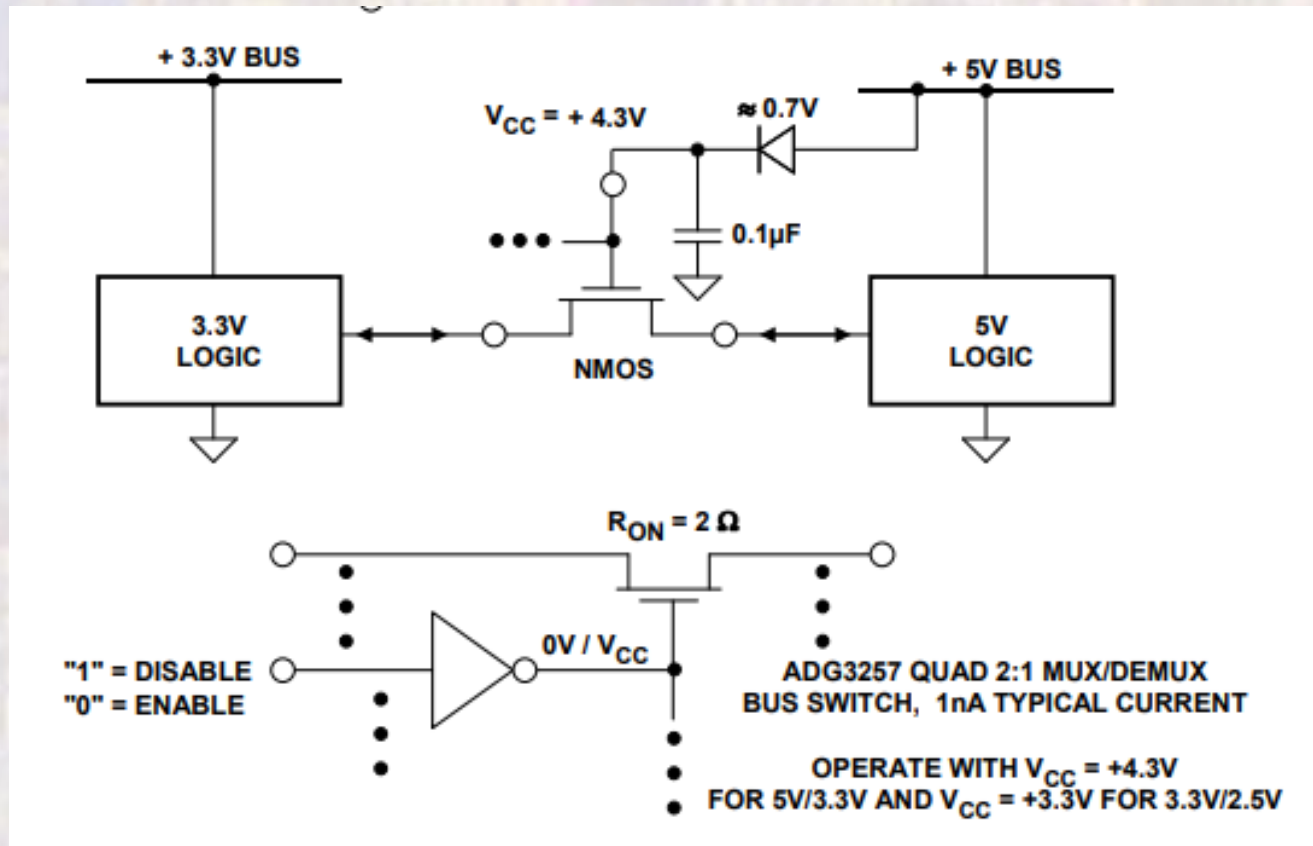


Touch Screens


- Technologies
 - Resistive
 - Capacitive
 - Optical
 - Surface wave

Touch Screens

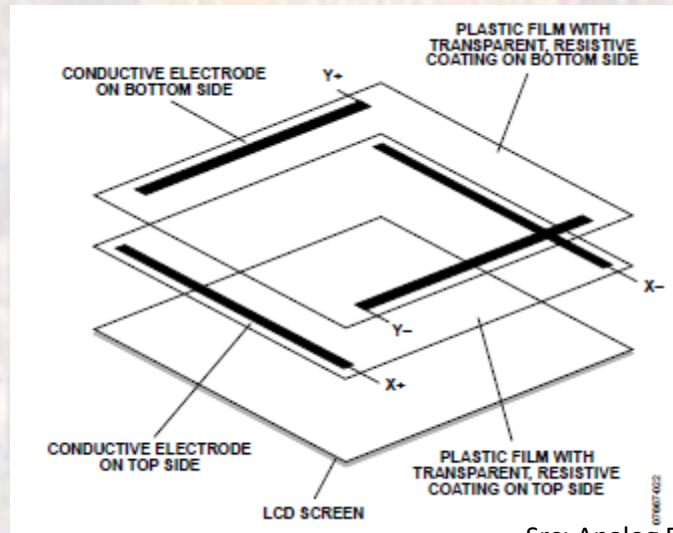- Resistive Touch – 4 wire
 - 2 layers of resistive material
 - 1 with connections at top/bottom
 - 1 with connections at sides
 - Separated by air/spacers




Src: Analog Devices

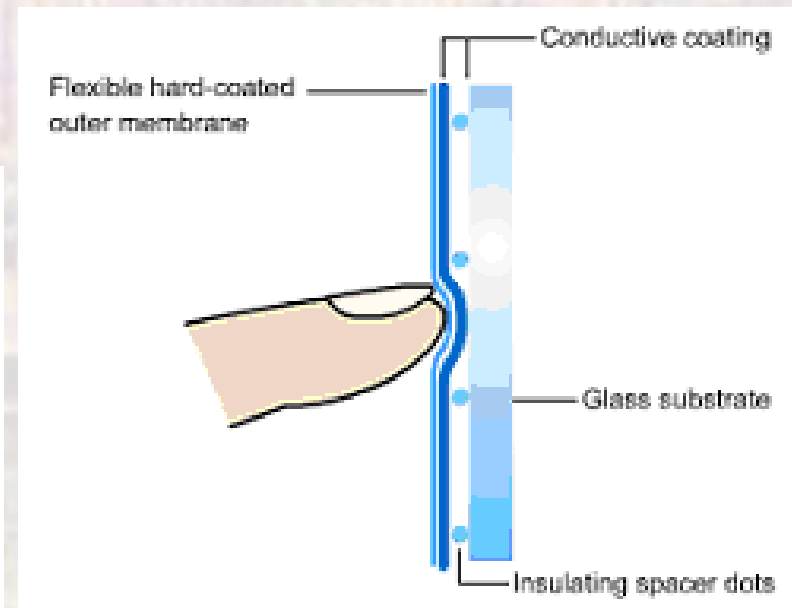

Src: ELO

Touch Screens

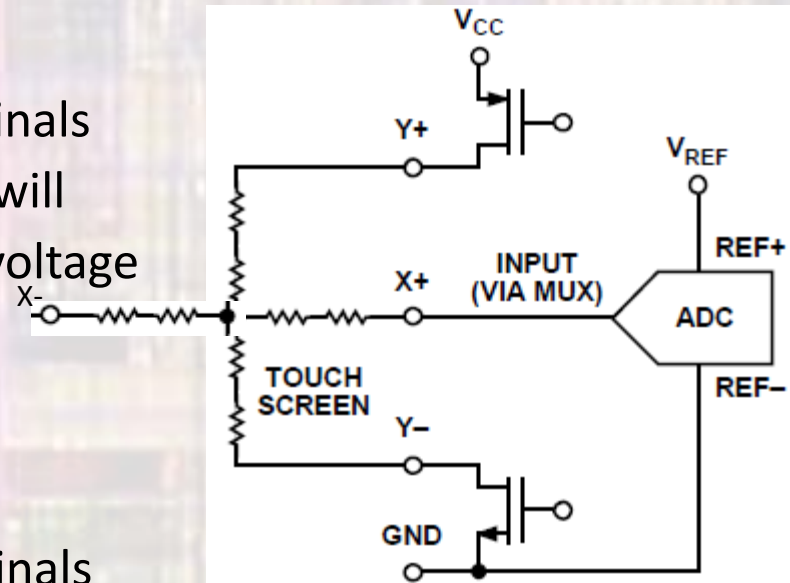
- Resistive Touch – 4 wire
 - Measure Y position
 - Place a voltage across Y terminals
 - Where touched, X+ terminal will measure relative voltage
 - Measure X position
 - Place a voltage across X terminals
 - Where touched, Y+ terminal will measure relative voltage



Src: Analog Devices

Touch Screens


- Resistive Touch – 4 wire

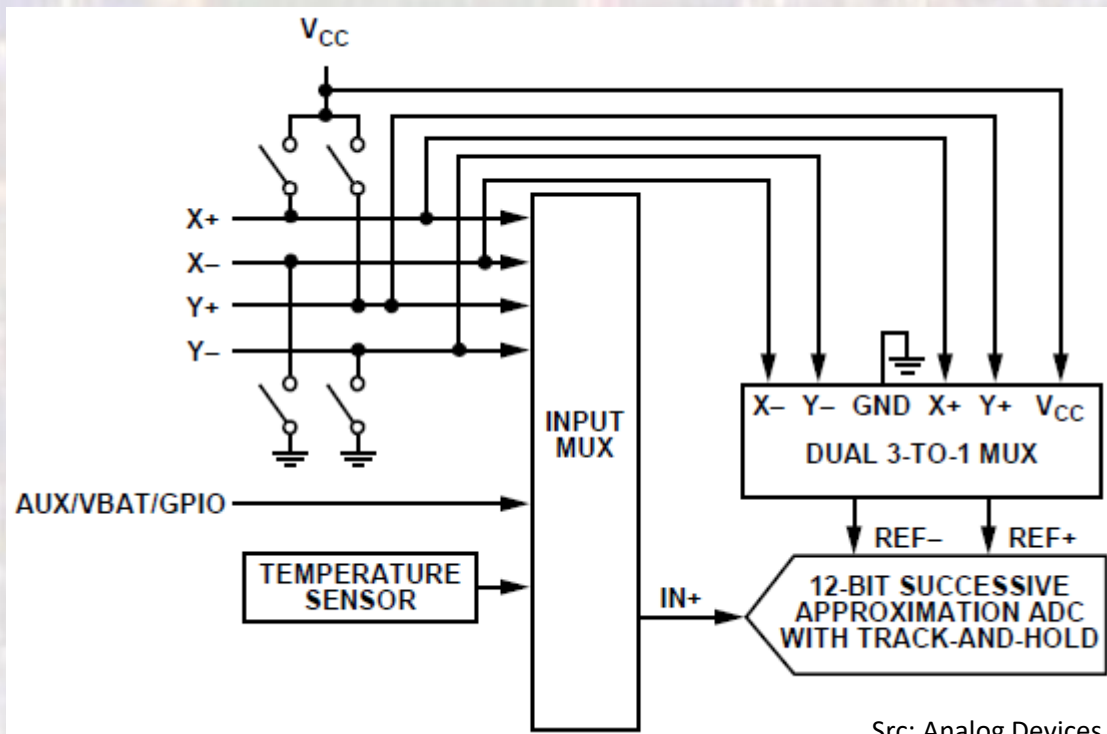

Src: Analog Devices

Touch Screens

- Resistive Touch – 4 wire

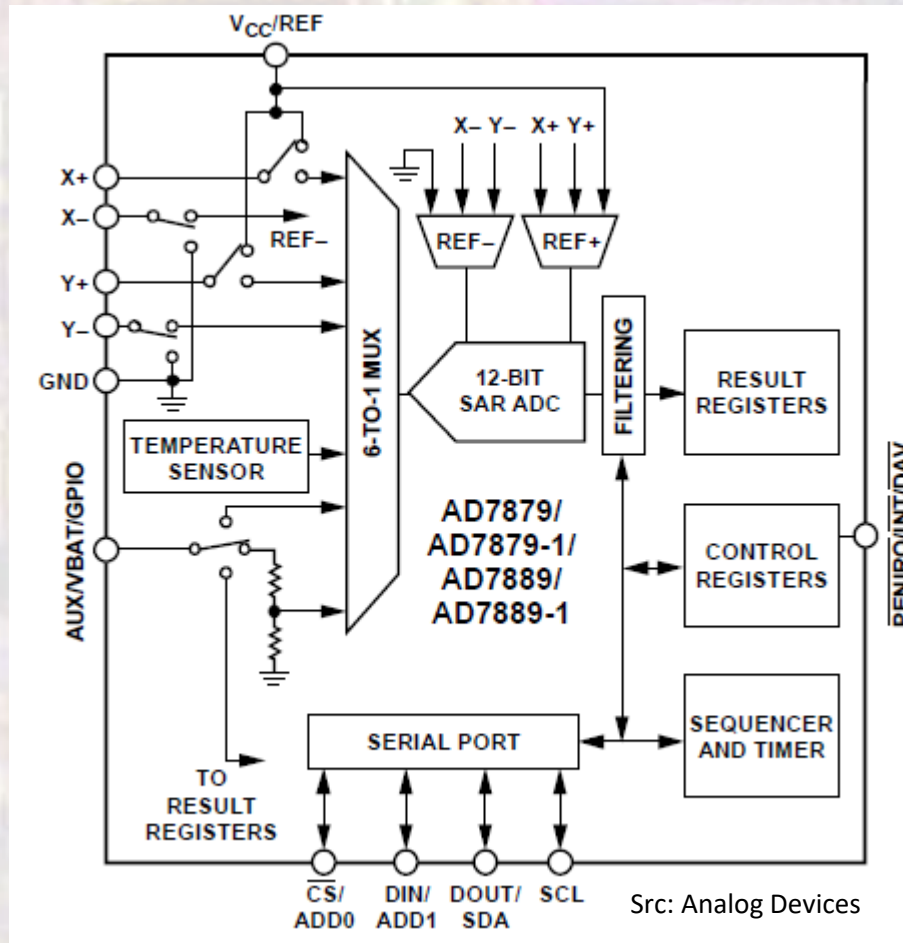


Touch Screens


- Resistive Touch – 4 wire
 - Pro
 - Flexible screen material
 - Any material can be used for touch
 - Can be very accurate
 - Con
 - Surface easy to damage
 - Low endurance
 - Limited light transmission
 - SINGLE TOUCH

Touch Screens

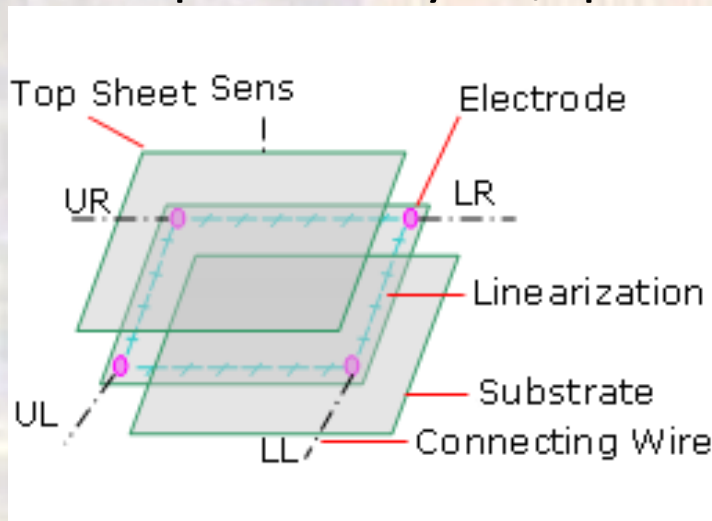- Resistive Touch – 5 wire
 - 1 layer of resistive material
 - 1 with connections at 4 corners
 - 1 layer of conductive material
 - Separated by air/spacers




Src: ewinsonic

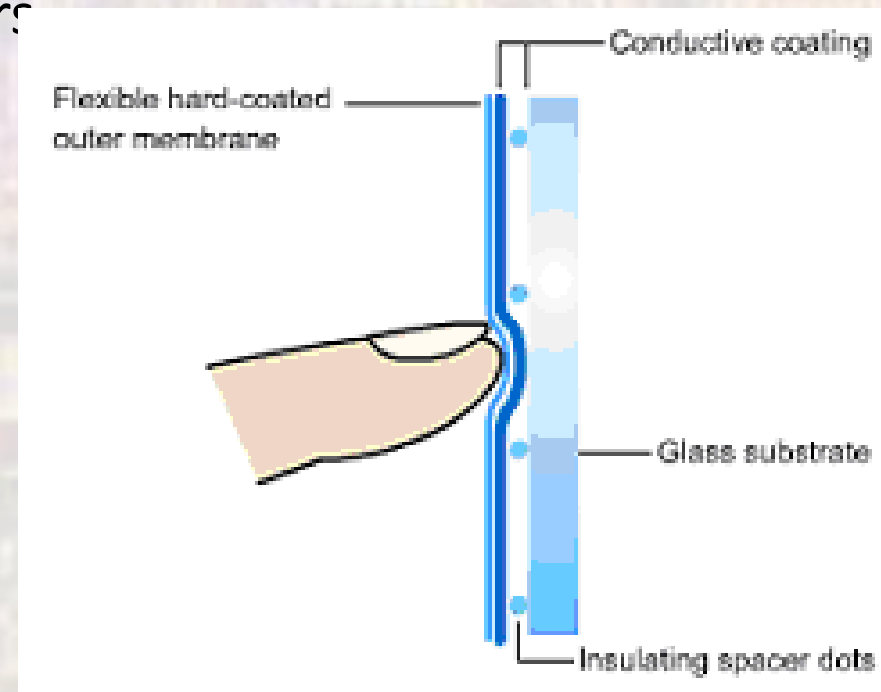

Src: ELO

Touch Screens

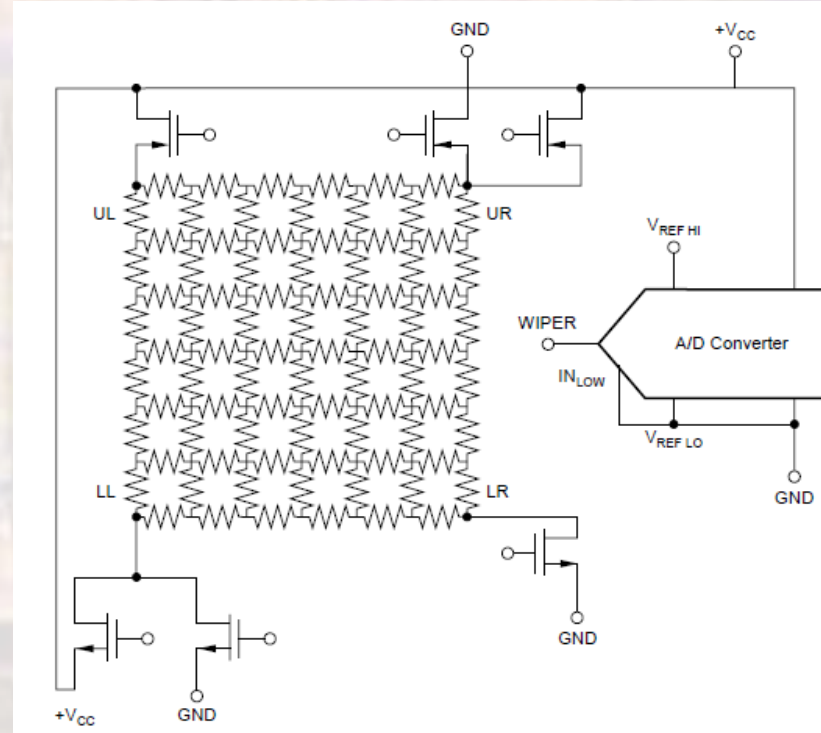
- Resistive Touch – 5 wire
 - Measure Y position
 - LR – gnd, UL - Vdd
 - LL – gnd, UR – Vdd
 - Where touched, wiper terminal will measure relative voltage
 - Measure X position
 - LR – gnd, UL - Vdd
 - LL – Vdd, UR – gnd
 - Where touched, wiper terminal will measure relative voltage



Src: TI

Touch Screens

- Resistive Touch – 5 wire

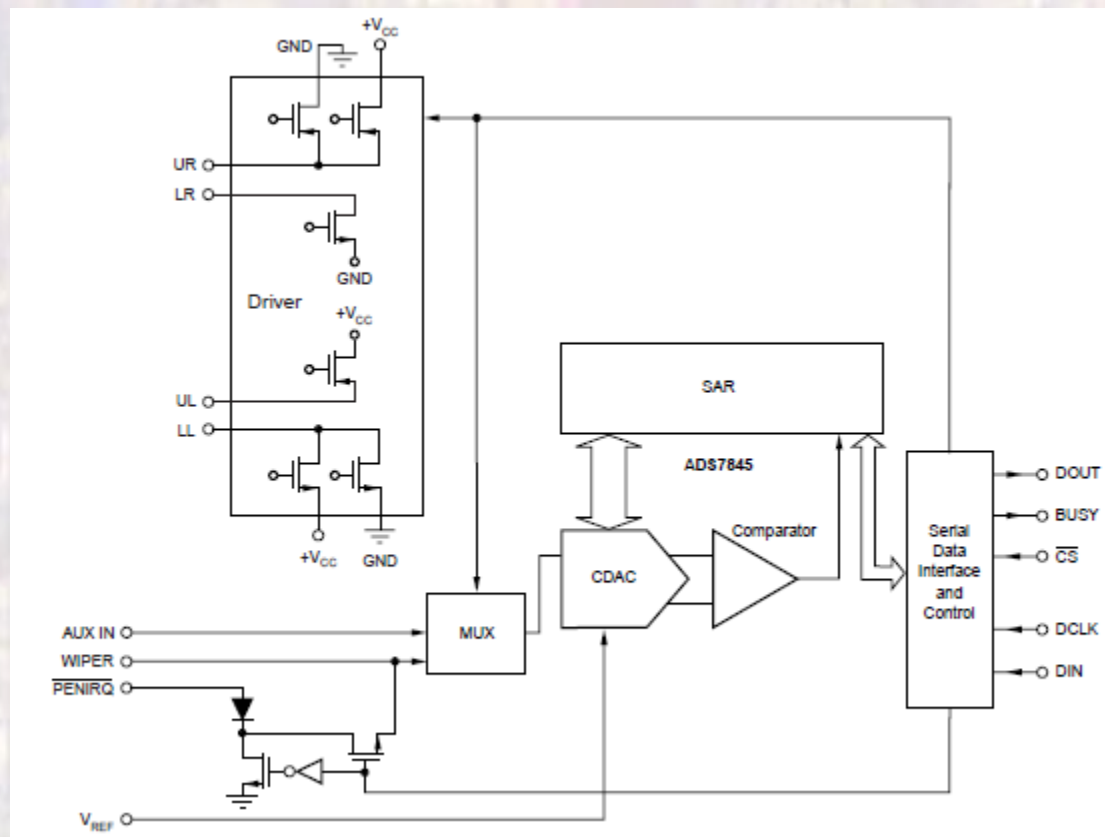

Src: TI

Touch Screens


- Resistive Touch – 5 wire
 - Pro
 - Flexible screen material
 - Any material can be used for touch
 - Can be very accurate
 - Con
 - Surface easy to damage
 - Better but still limited endurance
 - Damage to the top layer does not impact performance
 - Better light transmission
 - SINGLE TOUCH

Touch Screens

- Surface Capacitive

- Uniform conductive material
 - On glass

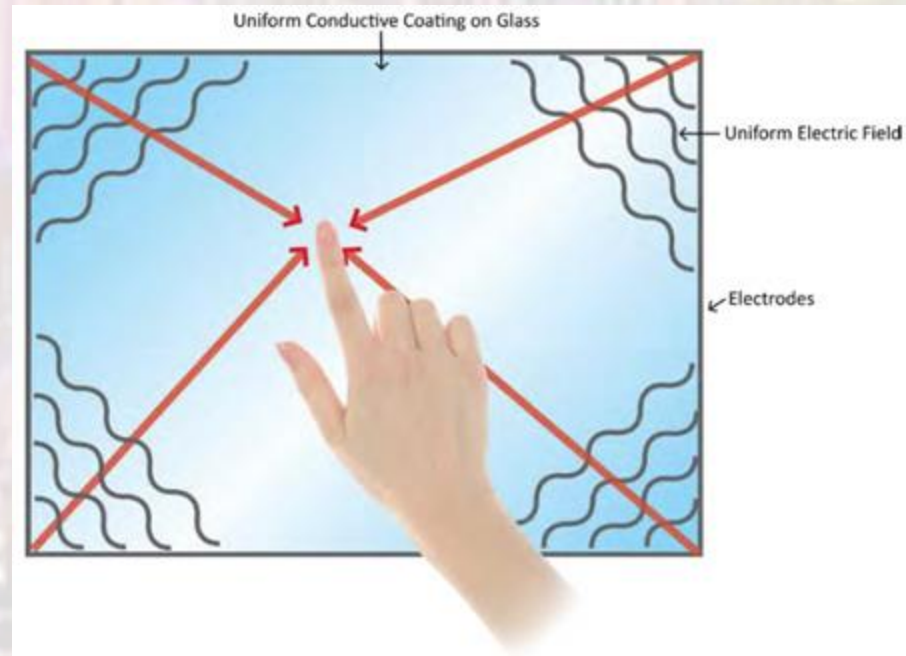- Common ac voltage applied at all 4 corners
 - uniform electric field



- When touched, finger modifies the field (creates a capacitor)
 - current from each corner
- Calculate position based on relative current values – $1/r$

Touch Screens


- Surface Capacitive

- Setup a sine wave on all 4 corners

- $i = C \, dv/dt$


- When touched, finger modifies C
→ Δi

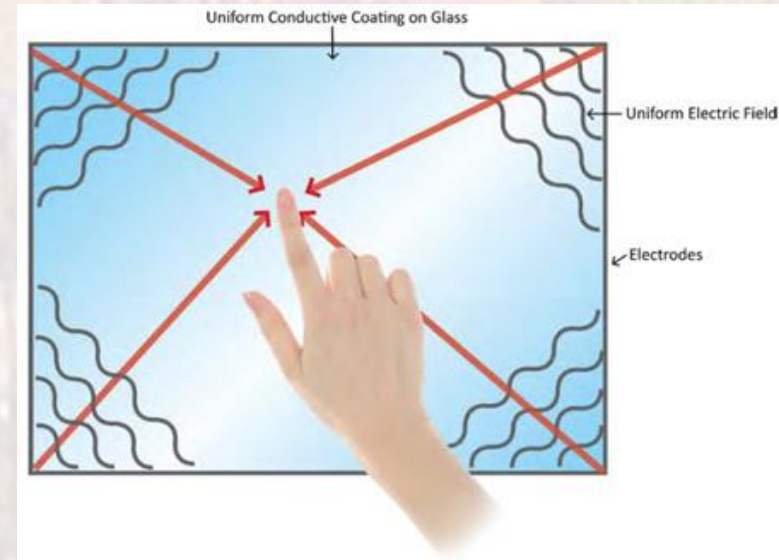- Calculate position based on relative current values – $1/r$



Touch Screens


- Surface Capacitive

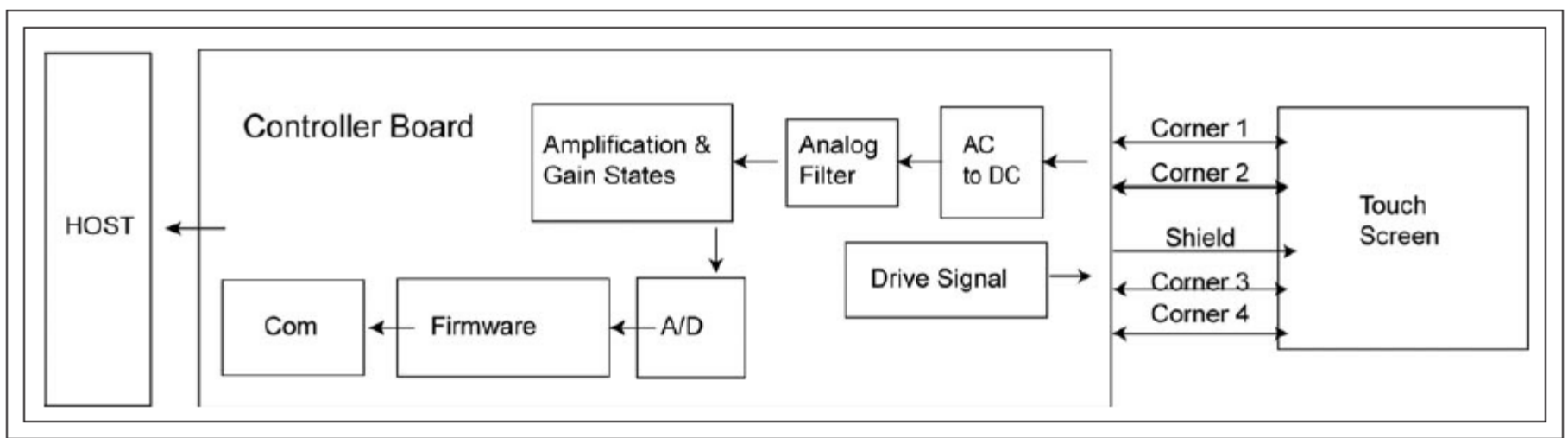

Src: Information Display

Touch Screens

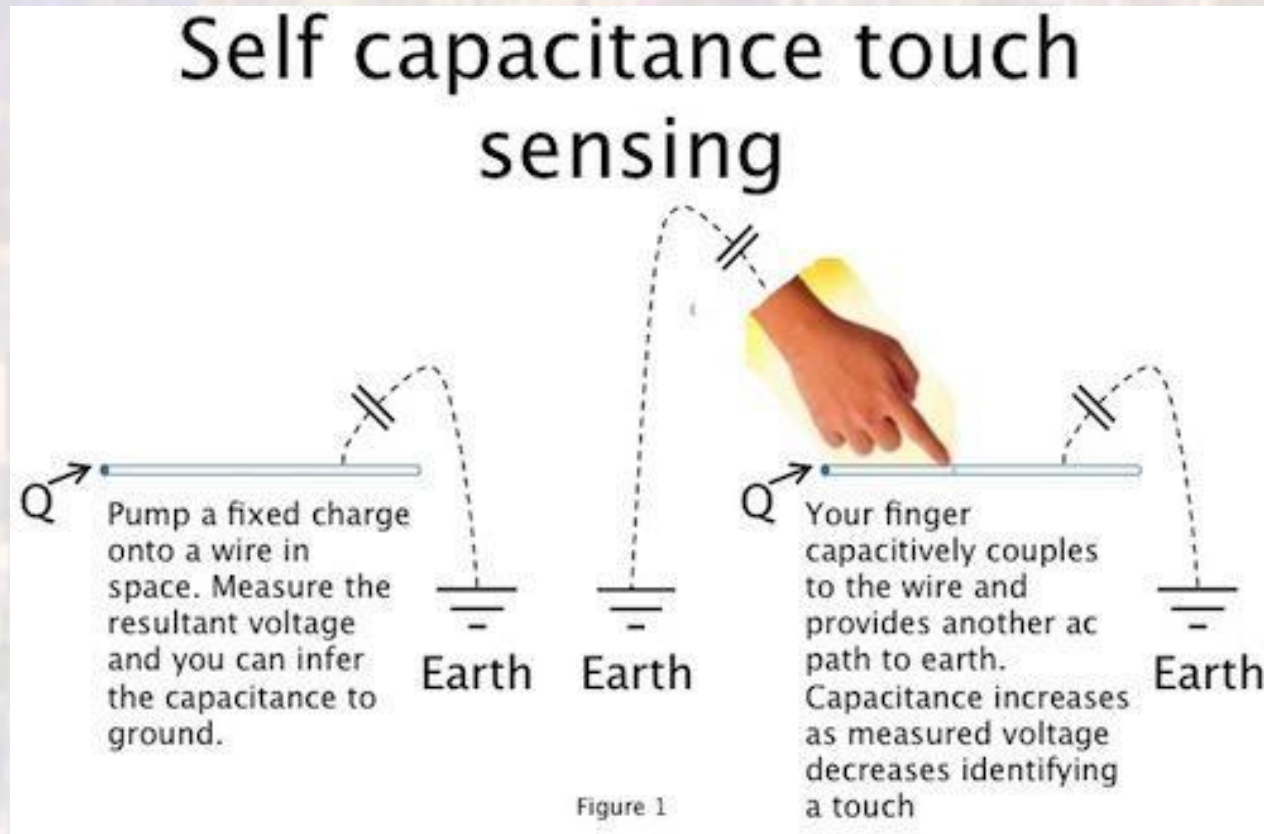
- Projected Capacitive – Self Capacitance



Src: Design News

Touch Screens

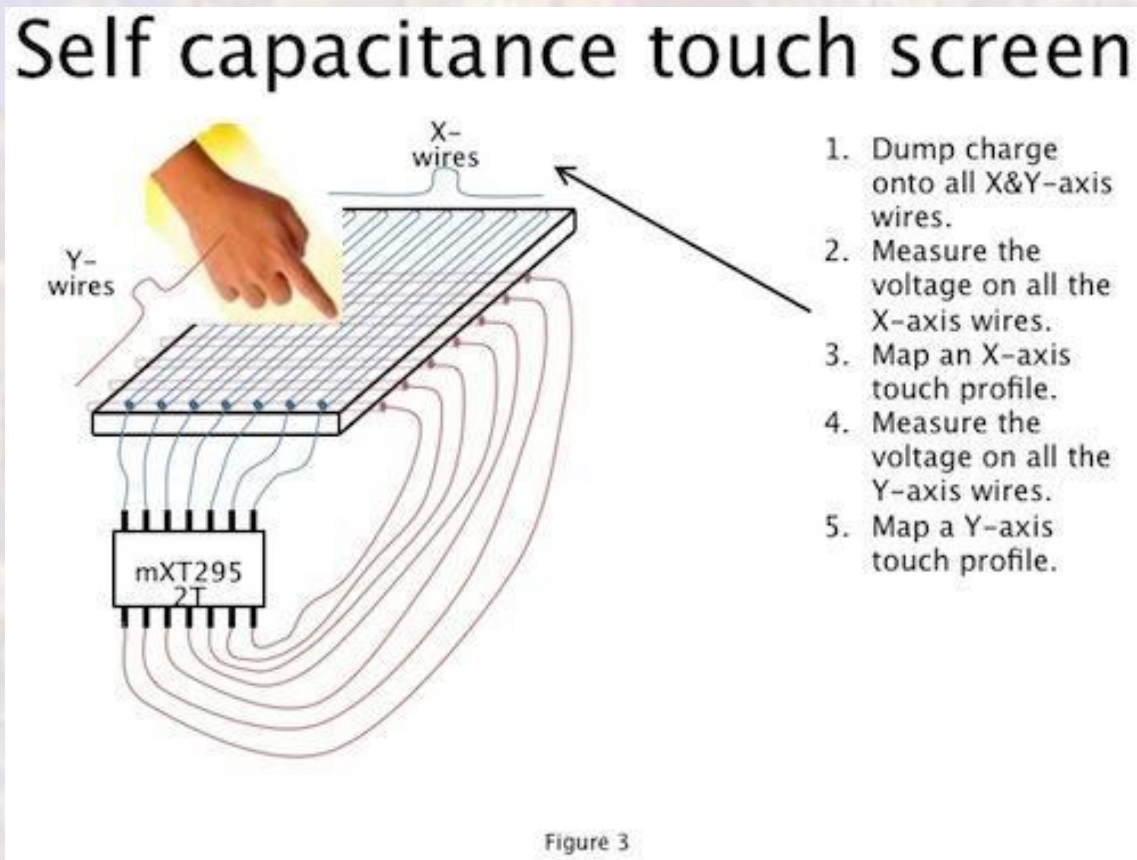
- Projected Capacitive – Self Capacitance



Src: Design News


Touch Screens

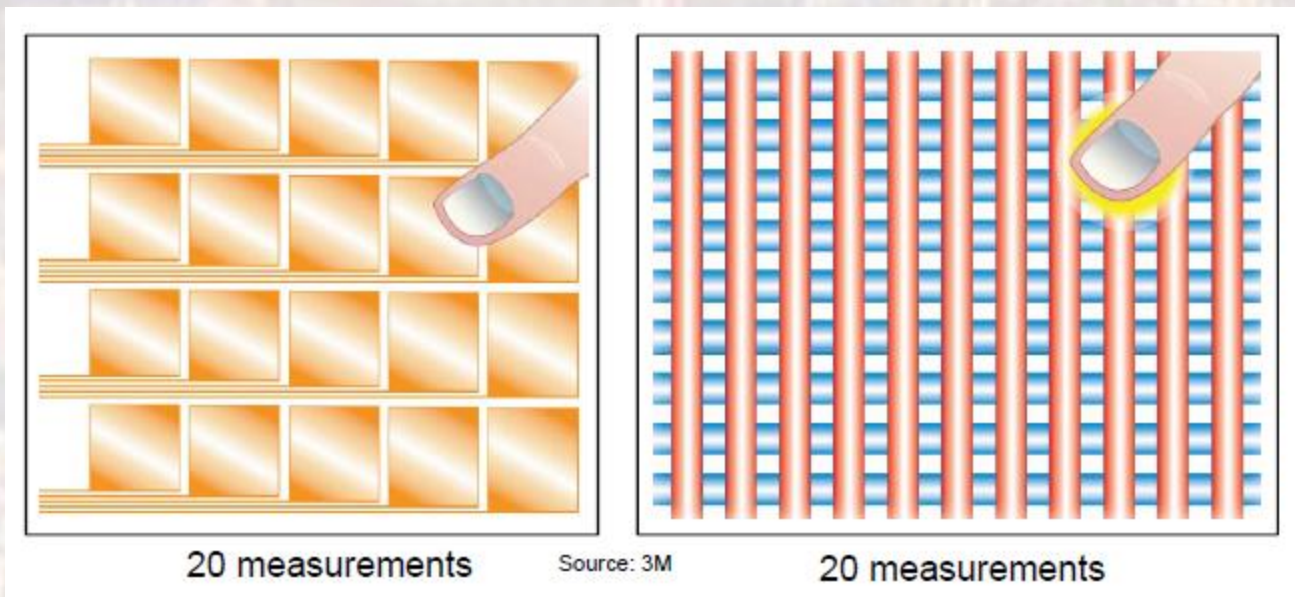- Projected Capacitive – Self Capacitance



Touch Screens

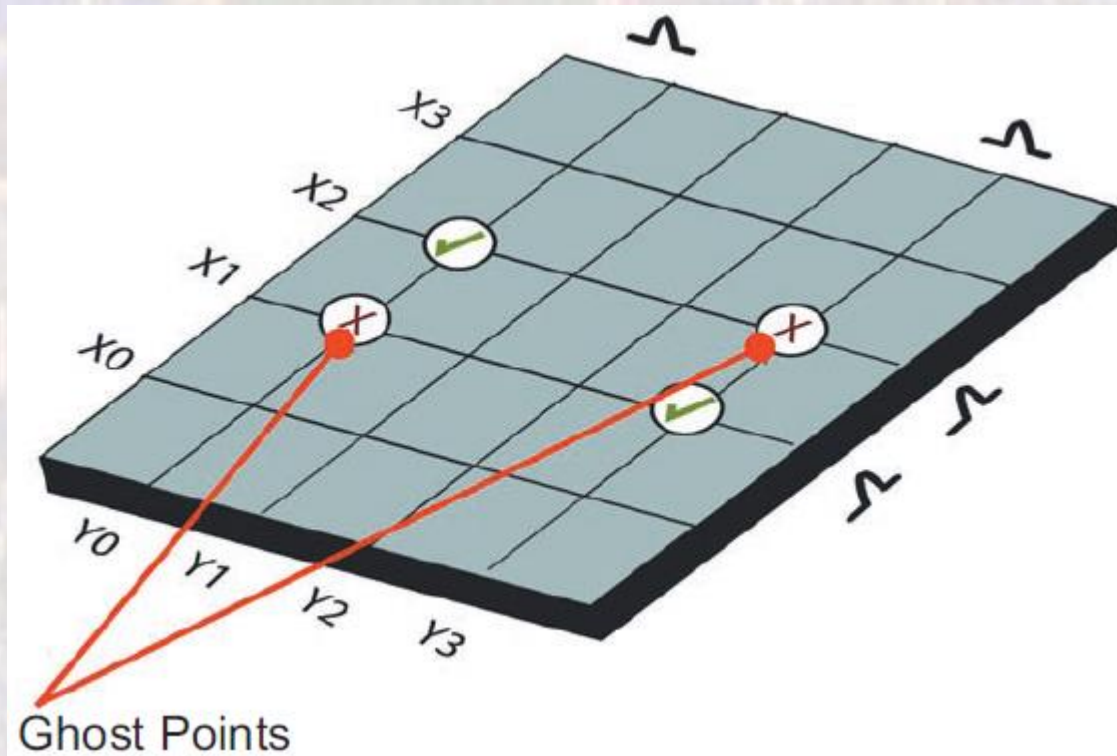
- Projected Capacitive – Self Capacitance
 - Single Touch only



Src: Stanford

Touch Screens


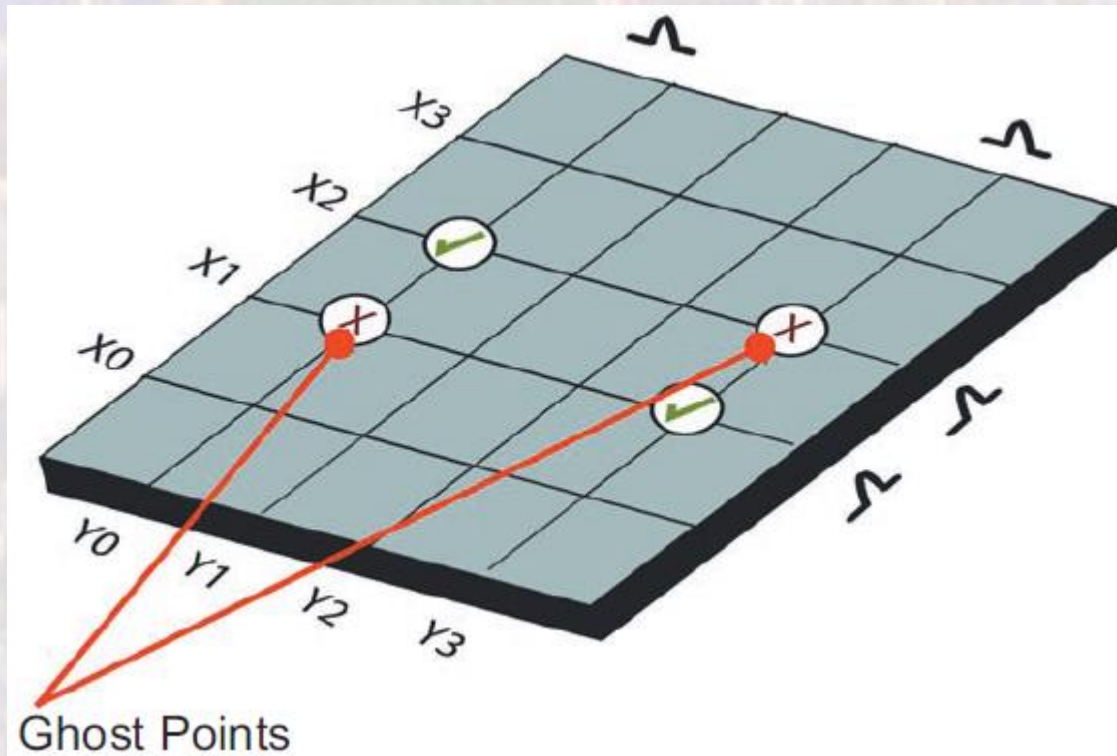
- Projected Capacitive – Self Capacitance
 - With SW can do 2 touch swipes (pinch, expand)



Src: Stanford

Touch Screens

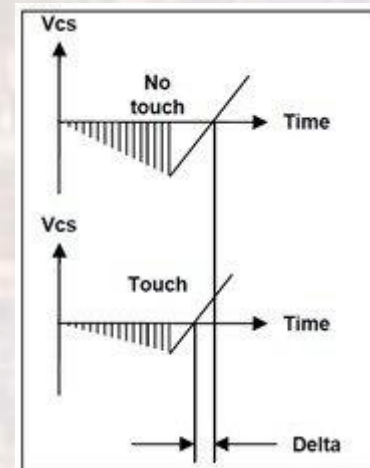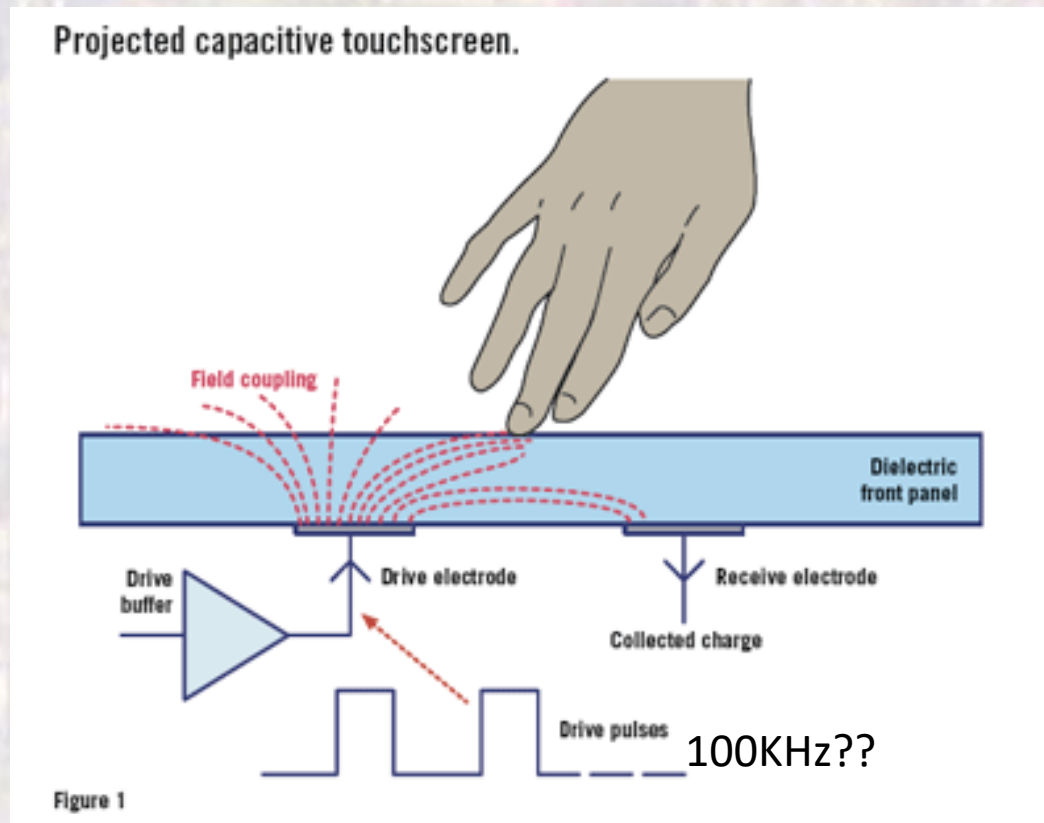
- Projected Capacitive – Mutual Capacitance
 - Reduce the apparent capacitance



Src: Embedded Design

Touch Screens

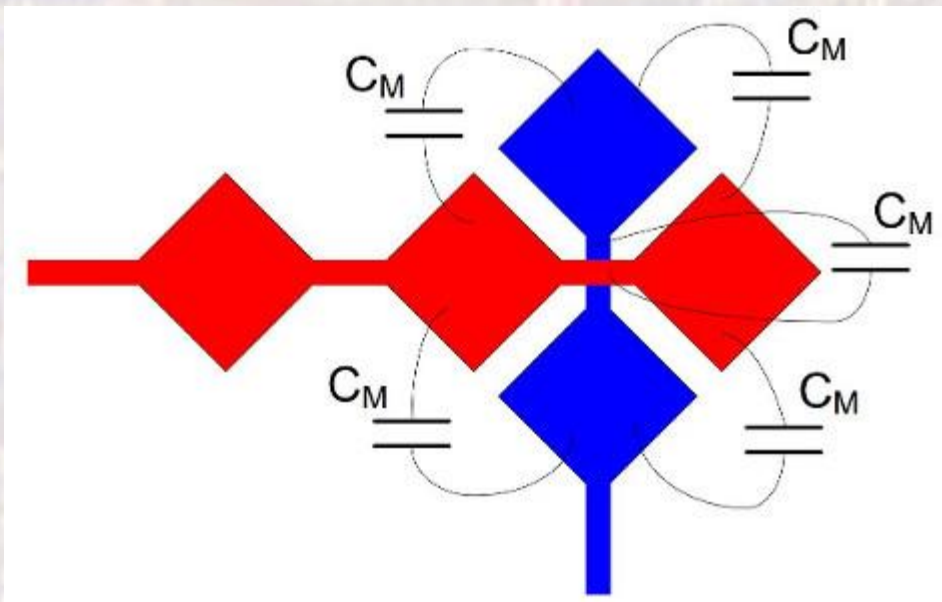
- Projected Capacitive – Mutual Capacitance
- Single intersection – 2 layer ITO



Src Electronic Design

Touch Screens

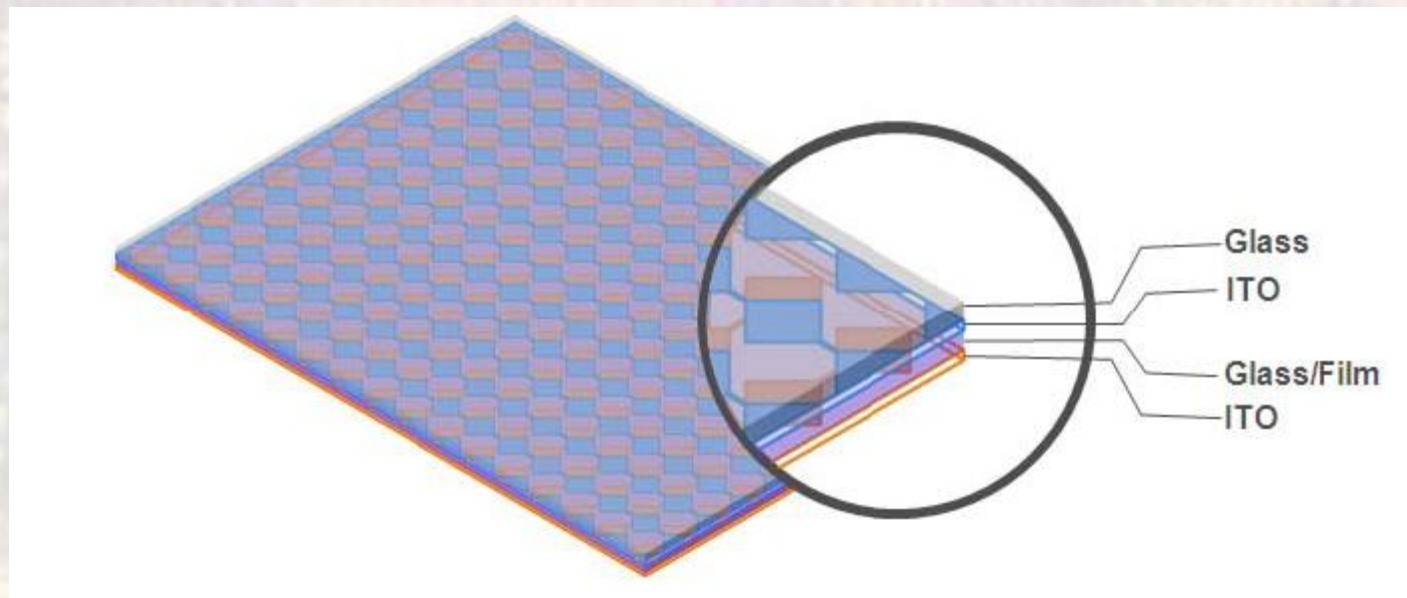- Projected Capacitive – Mutual Capacitance
- Matrix Structure




Src: Cypress

Touch Screens

- Projected Capacitive – Mutual Capacitance
 - Matrix Structure
 - Drive 1 row – Scan each column
 - Measure capacitance
 - Provides for multiple touches as each row/column can be detected
 - Operate at a 20 – 200Hz full screen cycle rate

Touch Screens

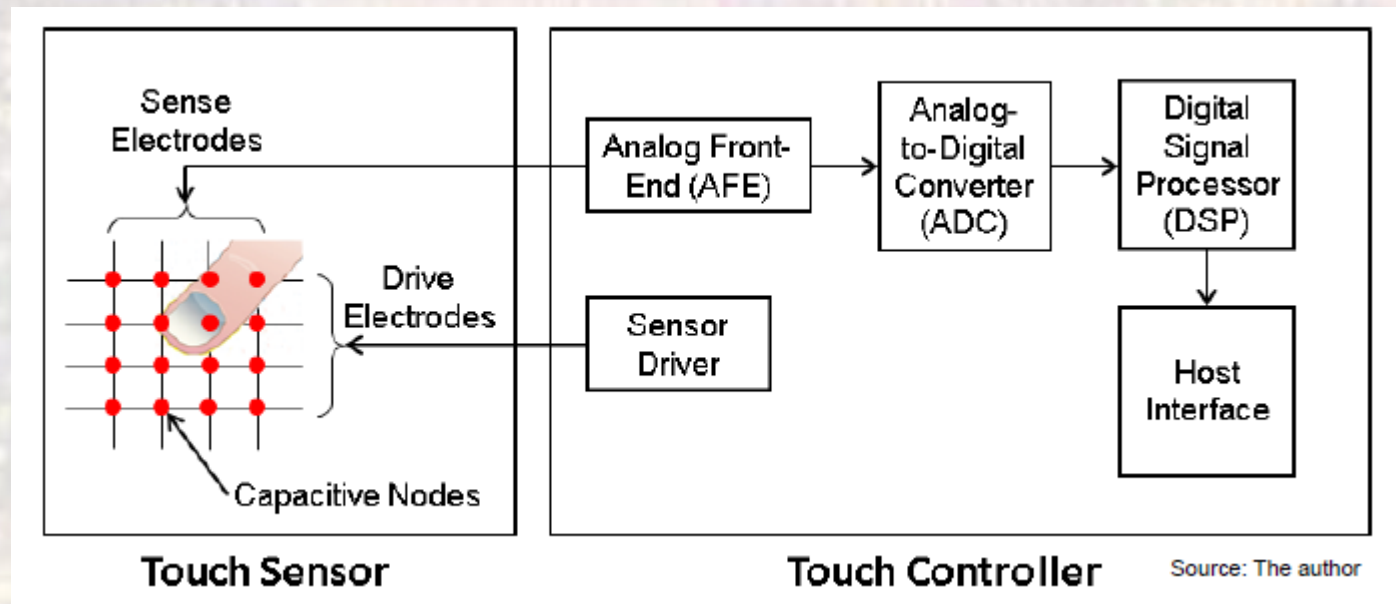
- Projected Capacitive – Mutual Capacitance
- Controller



Src: Intel – Goeff Walker


Touch Screens

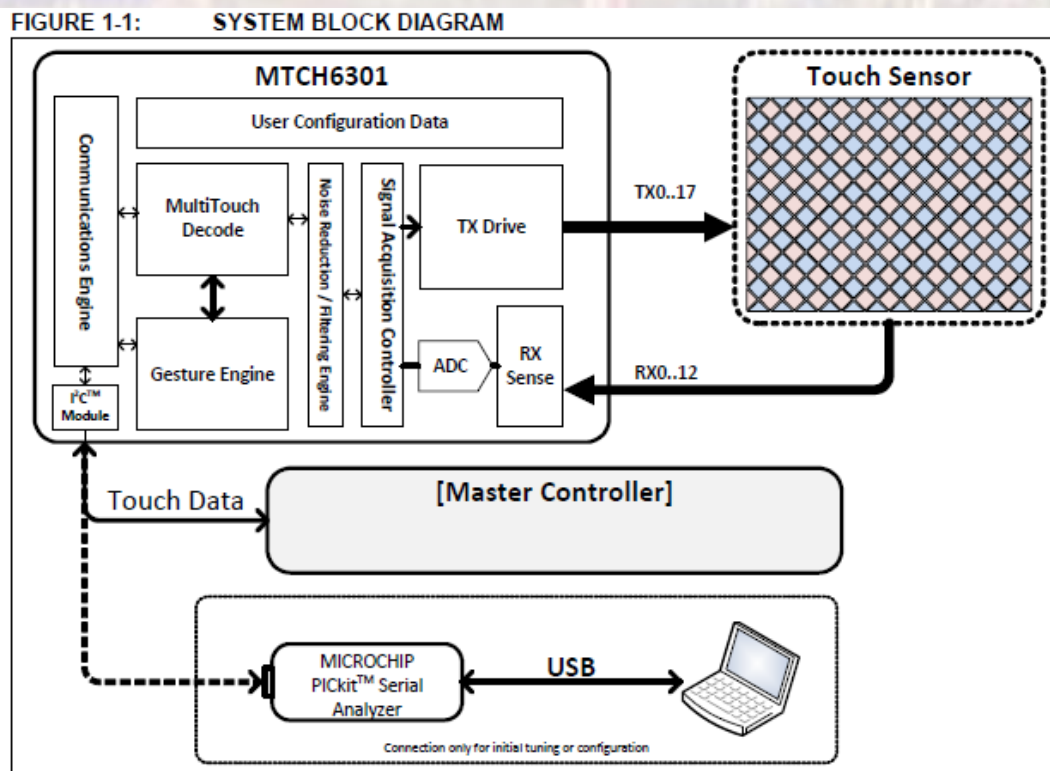- Projected Capacitive – Mutual Capacitance
- Controller




Touch Screens

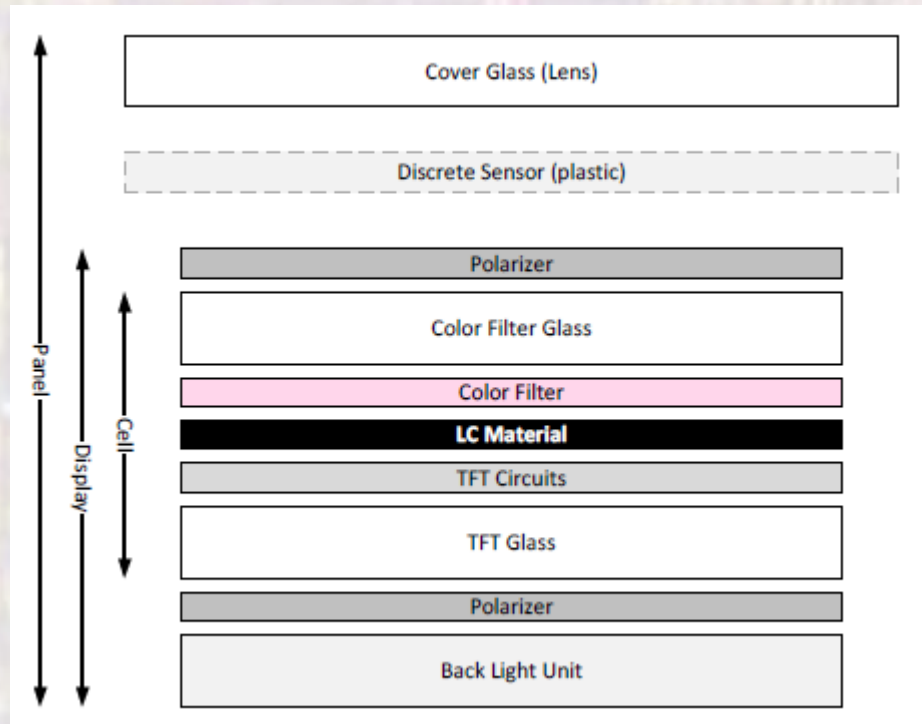- Projected Capacitive – Mutual Capacitance
 - On Panel




Touch Screens

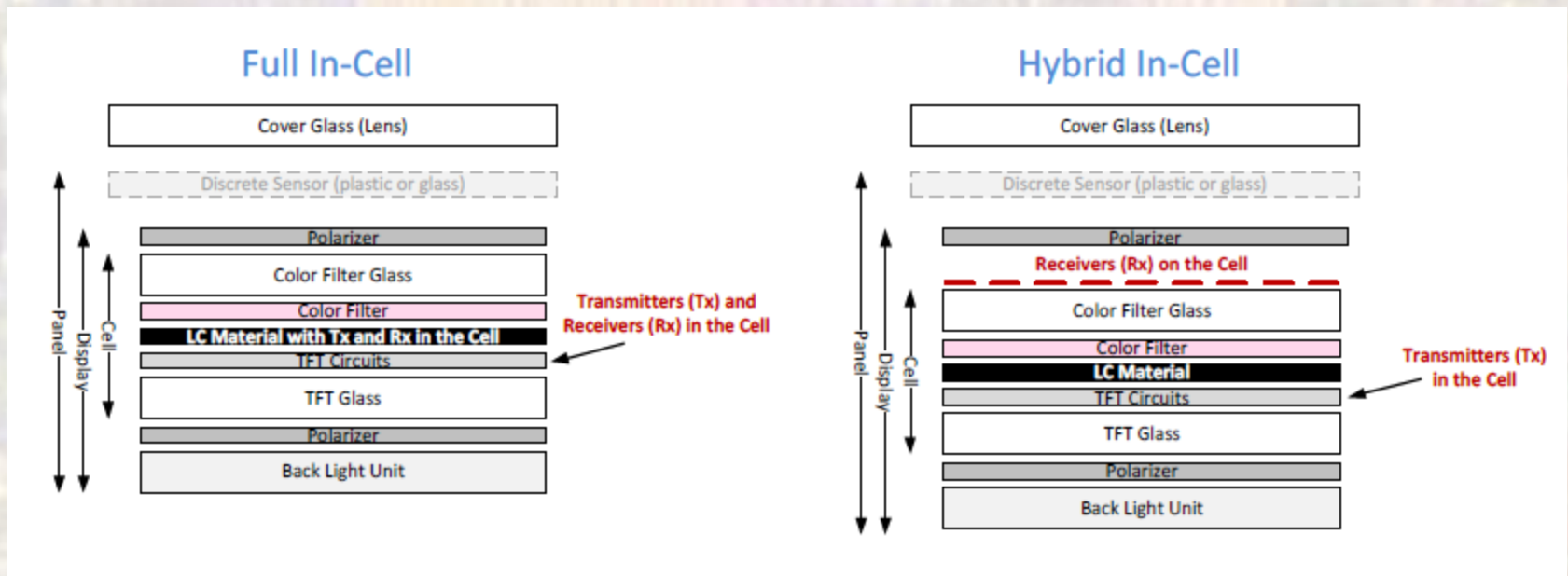- Projected Capacitive – Mutual Capacitance
 - In Cell
 - Critical to design as a part of the display – noise, interference



Touch Screens


- Surface Acoustic Wave

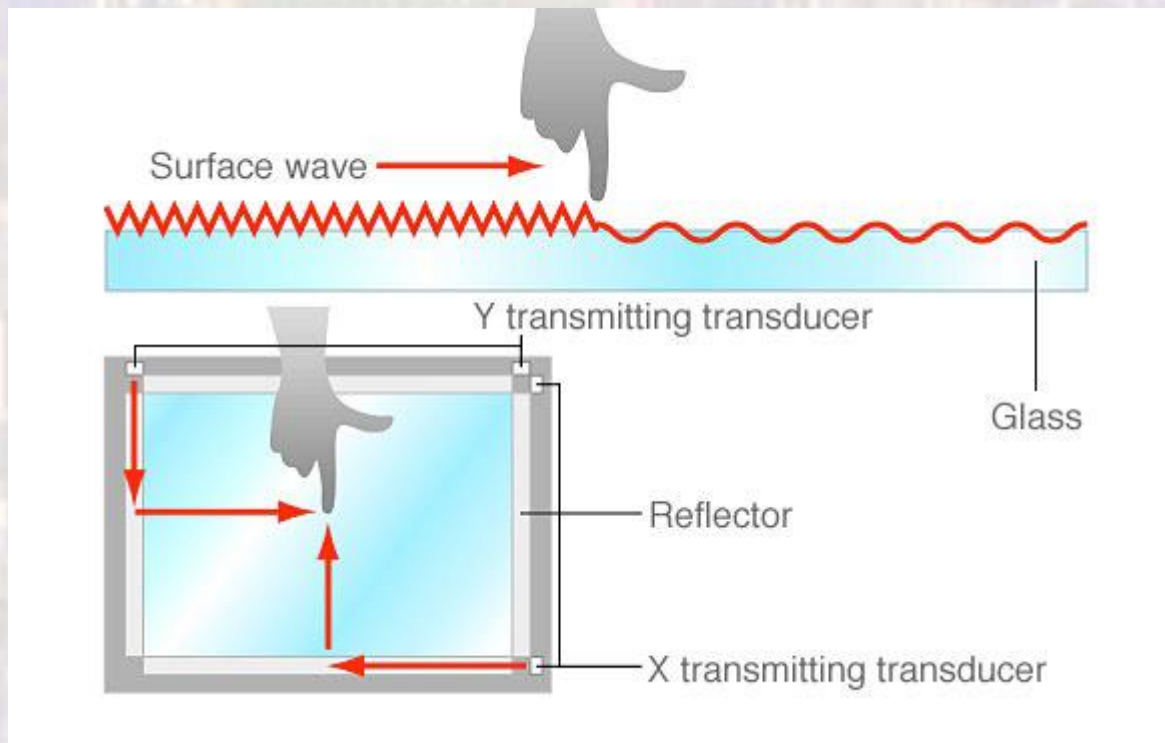

Src: Touch Screen Basics

Touch Screens

- Infrared

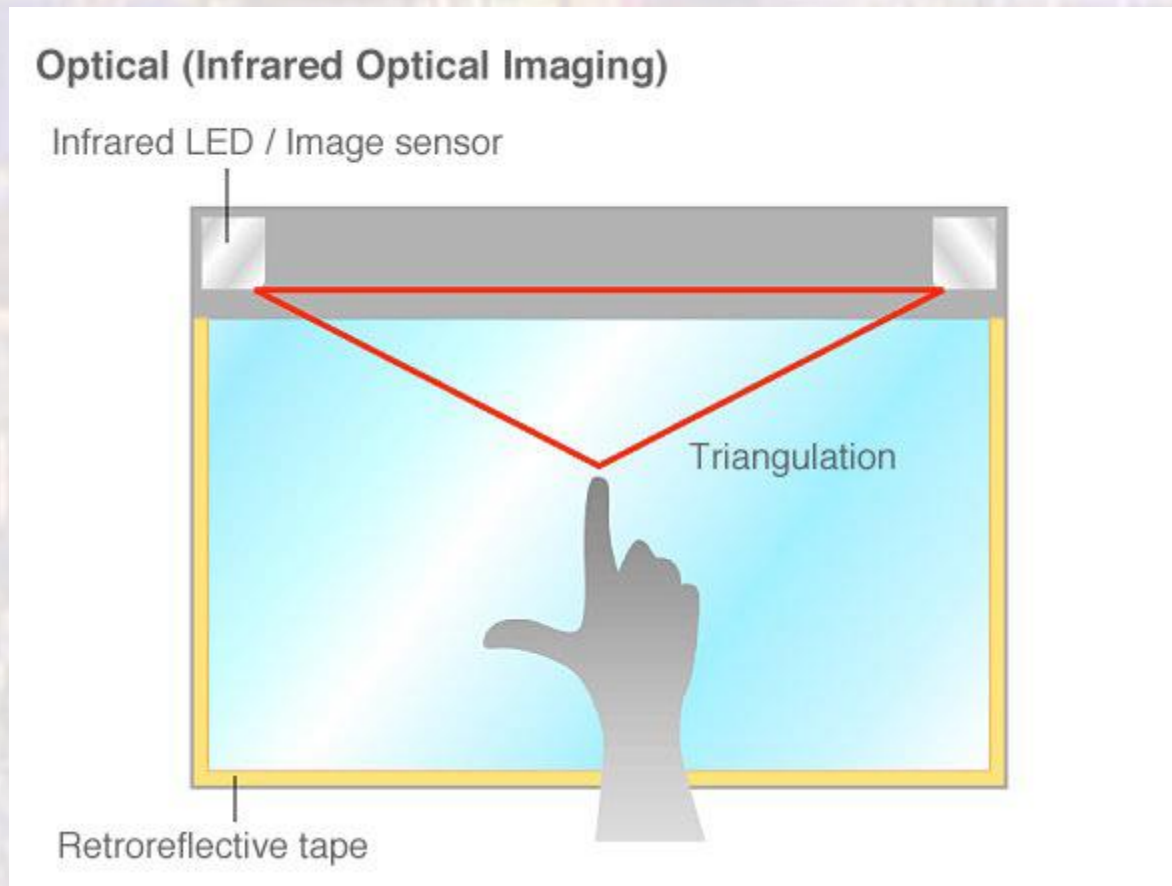

Src: Touch Screen Basics

Touch Screens

- Sensor Comparison

Method	Linearity	Accuracy	Size Scalability	Optical Clarity	Damage Resistant	Multitouch
Infrared	★★★★★	★★★	★★★★★	★★★★★	★★★	Yes (expensive)
Surface Acoustic Wave (SAW)	★★★★	★★★★	★★	★★★	★★★★★	No
Surface Capacitance	★★	★★	★★	★★★★★	★★★★★	No
Resistive	★★★★	★★★★	★★★★	★★	★	Yes (expensive)
Projected Capacitance	★★★★★	★★★★	★★★	★★★★★	★★★★★	Yes

Src: Cypress