

	Title: Lab5_Part2	
	Desc.: 2N7000 I-V curves	
	Designed by: tj	Revision:
	Date: 3/31/2022	Size: A
	Sheet 1 of 1	

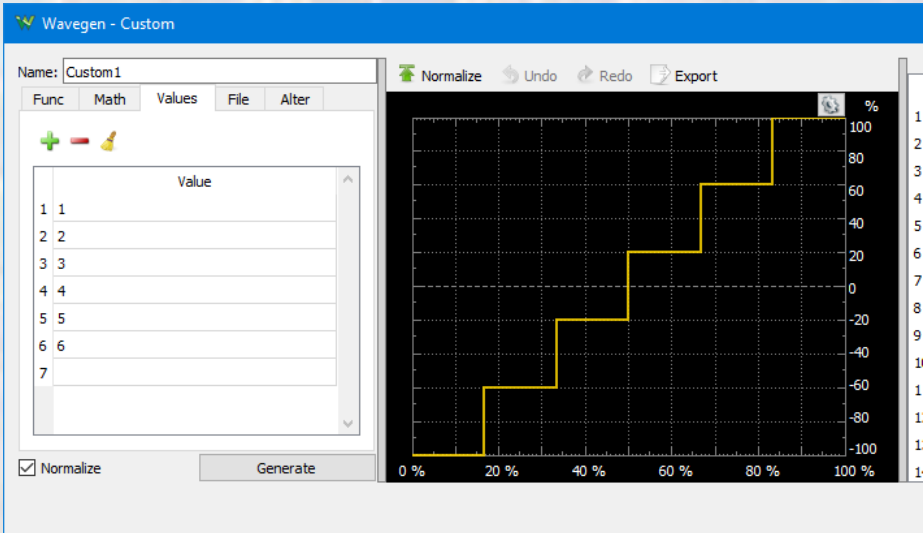

You will need to adjust the offset value to correspond with your individual MOSFET (trial and error)

W1 Setup

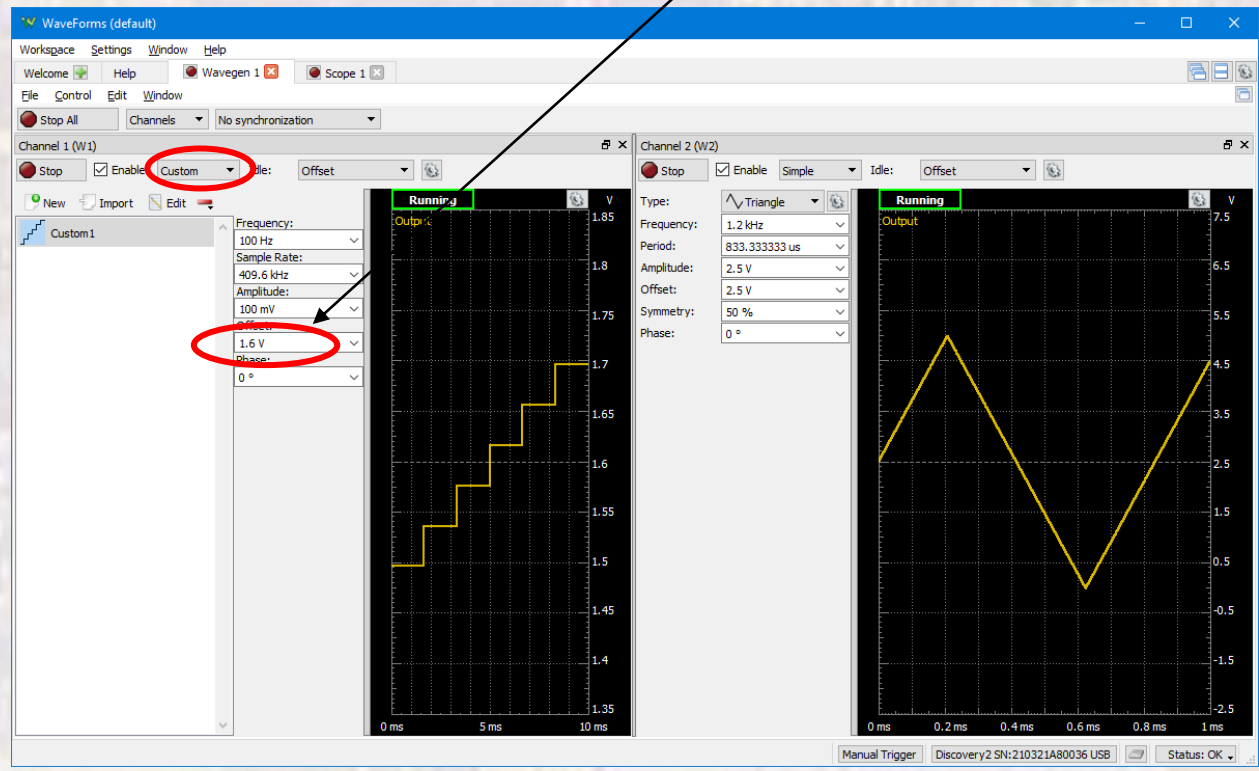

W2 Setup

Adjust the W1 "offset" until you have several curves

Math 1 → C1/330, amps

