

CE3101 Lab 5: MOS transistors

Objectives

- Explore MOSFETs and Circuits

Prelab

- Checkout an Analog Discovery 2 kit from the Tech Center
- Checkout needed components from the Tech Center

student
check off

Assignment

Part 1: Simulation: MOSFET I-V Curves

Create a DC Sweep simulation of the 2n7000 n-mos device. With the source grounded, sweep the drain from 0 – 5v in 0.2V increments (source 1), sweep the gate from 0 – 5V at 0.1V increments (source 2).

- a) Estimate V_{th} , then estimate K_n
- b) Verify your estimates with at least 3 points on the I-V curves (3 gate voltages)
- c) Assuming $K'n = 20\mu A$, what is the W/L ratio for this device

Part 2: Implementation: MOSFET I-V Curves

Due to current limitations on the AD2 we can only replicate the I-V curves for gate voltage very close to the threshold voltage.

Set W1 (use custom mode) to create six gate voltage steps. Initially center (offset) the steps on your calculated V_{th} from part 1, with a 100Hz frequency and 100mv amplitude.

Set W2 to a 1.2KHz triangle wave with 0-5v amplitude.

(You will need to move the W1 offset to match your particular MOSFET. It will probably be below your calculated value. Shift it until you get a “good” looking I-V curve set.)

- a) Estimate V_{th} , then estimate K_n
- b) Verify your estimates with at least 3 points on the I-V curves (3 gate voltages)

Check Off

- Demo and document part 1 40%
- Demo and document part 2 60%

Demo (in-person or via Teams chat) and Report (in the box) due by 4:00 pm Wednesday of the week following the lab.