

CE3101 Lab 6: CMOS Gates

Objectives

- Explore CMOS Gates

Prelab

- Checkout an Analog Discovery 2 kit from the Tech Center
- Checkout needed components from the Tech Center

**student
check off**

Assignment

Part 1: CMOS Inverter

- a) Simulation: Simulate the Part1 circuit in MultiSim. First determine the switching point, then measure the gate delay(s) of the middle inverter. Note the 1M Ω resistors are present to help the simulation converge.
- b) Implementation: Build the circuit from part a (without the resistors) and measure the middle inverter gate delays(s) using the simulated switching point as your reference.

Part 2: CMOS Integrated Circuit

- a) Implementation: Using the schematics for Part2, measure the gate delays and rise/fall times for the second inverter for each part.

Check Off

- Demo and document part 1 50%
- Demo and document part 2 50%

**Demo (in-person or via Teams chat) and Report (in the box) due by 4:00 pm
Wednesday of the week following the lab.**