

CE3101 Lab 7: OpAmps

Objectives

- Explore basic OpAmp characteristics

Prelab

- Checkout an Analog Discovery 2 kit from the Tech Center
- Checkout needed components from the Tech Center

**student
check off**

Assignment

Part 1: Voltage Follower

- a) Simulation: Simulate the Part1 circuit in MultiSim.
 - 1) Verify the basic operation using a 1KHz, 1V sine wave input
 - 2) Measure the output saturation voltage (+ and -) by increasing the amplitude of the input until the output saturates
 - 3) Determine the slew rate using a 2V sine wave input by increasing the frequency until the output starts to slew
 - 4) Measure the gain-BW product doing an AC sweep of the input
 - 5) Verify the 3dB frequency using a 20mV sine wave input and a transient simulation
- b) Implementation: Build the Part1 circuit and measure items 1,2,3, 4, and 5 on the real part. (use the network analyzer for part 4)

Part 2: Inverting Amplifier

- a) Repeat all of the part 1a simulations using the Part2 circuit (be sure to scale the input voltages for parts 1,2,3)
- b) Repeat all of the part 1b measurements using the Part2 circuit (use the network analyzer for part 4)

Check Off

- Demo and document part 1 50%
- Demo and document part 2 50%

**Demo (in-person or via Teams chat) and Report (in the box) due by 4:00 pm
Wednesday of the week following the lab.**