


OpAmp Circuits

Last updated 4/14/22

OpAmp Circuits

- Most opamps are operated in negative feedback configurations
 - Output feeds back to the - input

- Voltage Follower

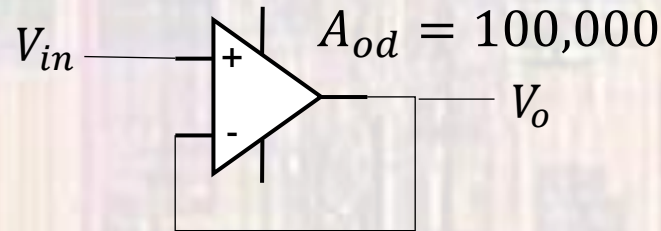

$$V_o = A_{od}(V_+ - V_-)$$

$$V_o = A_{od}(V_{in} - V_o)$$


$$V_o = \frac{A_{od}}{1 + A_{od}} V_{in} = V_{in} |_{A_{od} \gg 1}$$

$$A_v = \frac{V_o}{V_{in}} = \frac{A_{od}}{1 + A_{od}} = 1$$

OpAmp Circuits

- Fixed Gain Inverting Amplifier

- Gnd ref

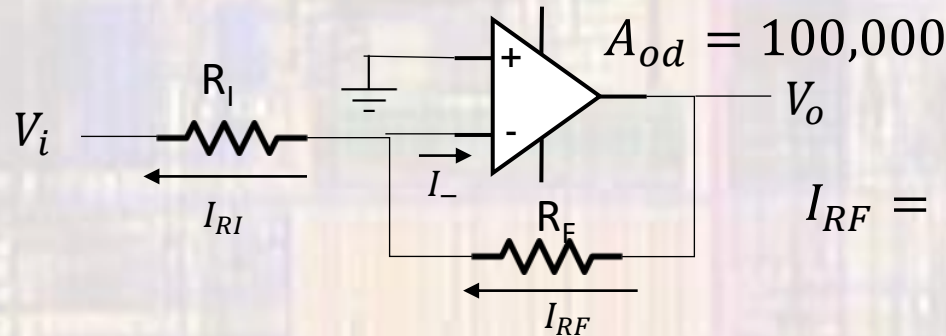

$$I_{RF} = I_{RI} + I_- = I_{RI}$$

$$I_{RF} = \frac{V_o - V_-}{R_F} = \frac{V_o - \left(V_+ - \frac{V_o}{A_{od}} \right)}{R_F}$$

$$I_{RI} = -\frac{V_i - V_-}{R_I} = -\frac{V_i - \left(V_+ - \frac{V_o}{A_{od}} \right)}{R_I}$$


$$\frac{V_o - \left(V_+ - \frac{V_o}{A_{od}} \right)}{R_F} = -\frac{V_i - \left(V_+ - \frac{V_o}{A_{od}} \right)}{R_I}$$

$$V_o = -\frac{R_F}{R_I} V_i$$

$$A_v = -\frac{R_F}{R_I}$$

OpAmp Circuits

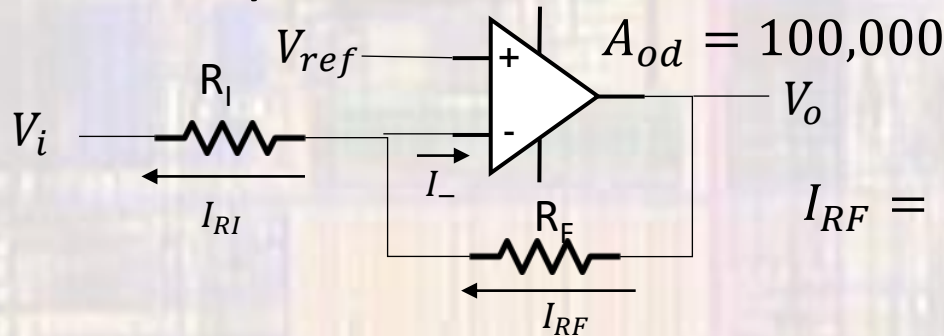- Fixed Gain Inverting Amplifier
 - Arbitrary ref



$$I_{RF} = I_{RI} + I_- = I_{RI}$$

$$I_{RF} = \frac{V_o - V_-}{R_F} = \frac{V_o - \left(V_{ref} - \frac{V_o}{A_{od}} \right)}{R_F}$$


$$I_{RI} = -\frac{V_i - V_-}{R_I} = -\frac{V_i - \left(V_{ref} - \frac{V_o}{A_{od}} \right)}{R_I}$$

$$\frac{V_o - \left(V_{ref} - \frac{V_o}{A_{od}} \right)}{R_F} = -\frac{V_i - \left(V_{ref} - \frac{V_o}{A_{od}} \right)}{R_I}$$

$$V_o = -\frac{R_F}{R_I} V_i + \left(1 + \frac{R_F}{R_I} \right) V_{ref}$$

OpAmp Circuits

- Inverting Amplifier
 - Second look

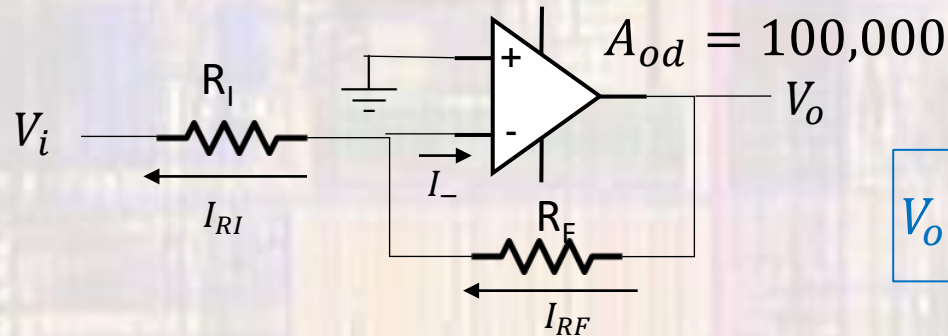

$$V_o = -\frac{R_F}{R_I} V_i$$

$$V_- = V_i + V_{R_I} = V_i + (V_o - V_i) \frac{R_I}{R_I + R_F}$$

$$V_- = \frac{V_i R_I + V_i R_F + V_o R_I - V_i R_I}{R_I + R_F} = \frac{V_i R_F + V_o R_I}{R_I + R_F} = \frac{V_i R_F - \frac{R_F}{R_I} V_i R_I}{R_I + R_F}$$




$$V_- = \frac{V_i R_F - R_F V_i}{R_I + R_F} = 0$$

V_- is called a virtual ground

OpAmp Circuits


- Inverting Amplifier

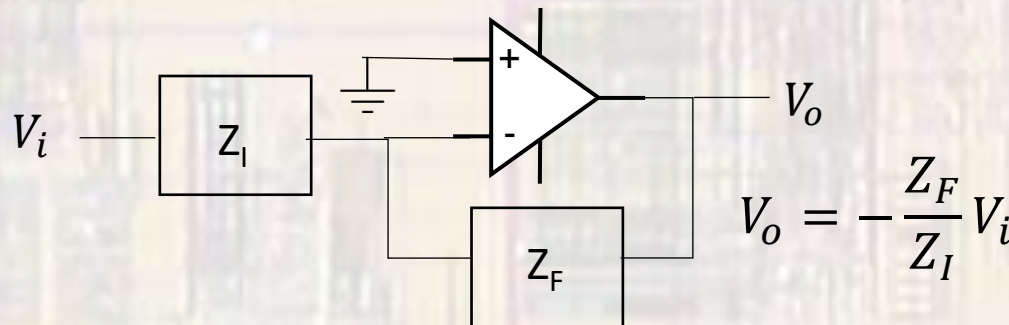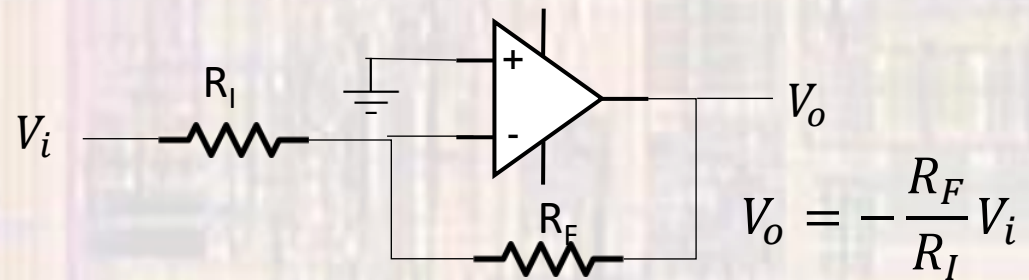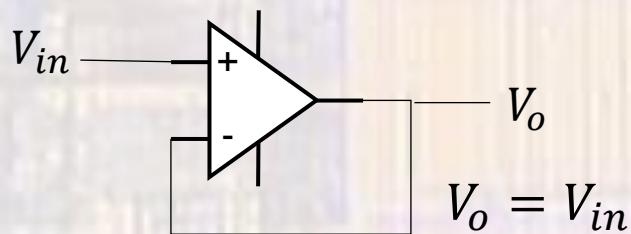An opamp in a negative feedback configuration will drive its output to force the V_+ and V_- inputs to be equal



OpAmp Circuits


- Fixed Gain Inverting Amplifier

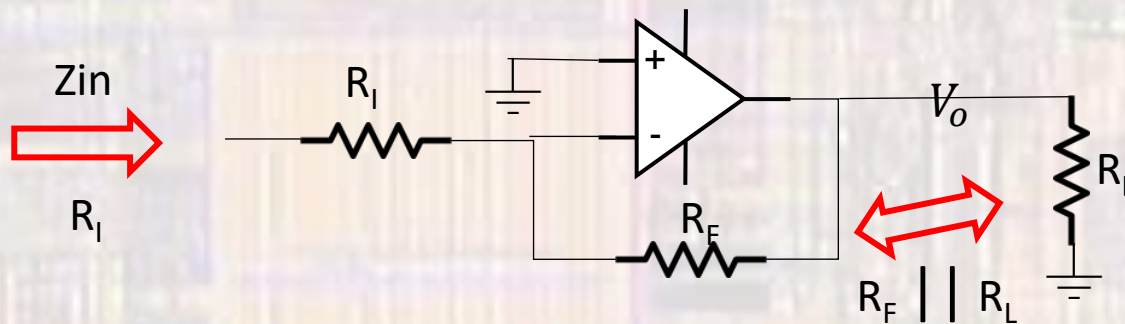

Input impedance concerns
Input current and input offset current concerns
Output impedance concerns

OpAmp Circuits

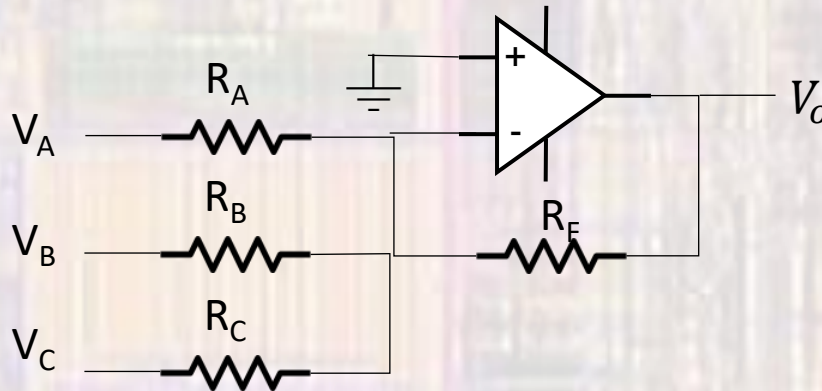
- Fixed Gain Inverting Summing Amplifier
 - By superposition



$$V_O = -\frac{R_F}{R_A} V_A - \frac{R_F}{R_B} V_B - \frac{R_F}{R_C} V_C$$

OpAmp Circuits

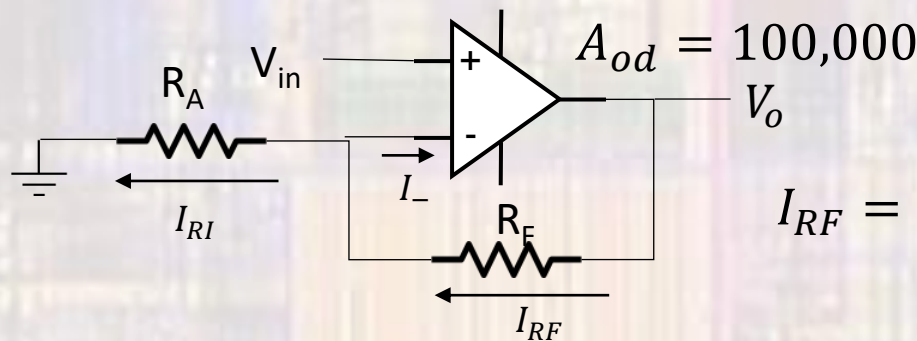- Fixed Gain Non-Inverting Summing Amplifier
 - Full Analysis



$$I_{RF} = I_{RA} + I_- = I_{RA}$$

$$I_{RF} = \frac{V_o - V_-}{R_F} = \frac{V_o - \left(V_{in} - \frac{V_o}{A_{od}} \right)}{R_F}$$

$$I_{RA} = \frac{V_- - 0}{R_A} = \frac{V_{in} - \frac{V_o}{A_{od}}}{R_A}$$


$$\frac{V_o - V_{in} + \frac{V_o}{A_{od}}}{R_F} = \frac{V_{in} - \frac{V_o}{A_{od}}}{R_A}$$

$$V_o = \left(1 + \frac{R_F}{R_A} \right) V_{in}$$

$$A_v = 1 + \frac{R_F}{R_A}$$

OpAmp Circuits

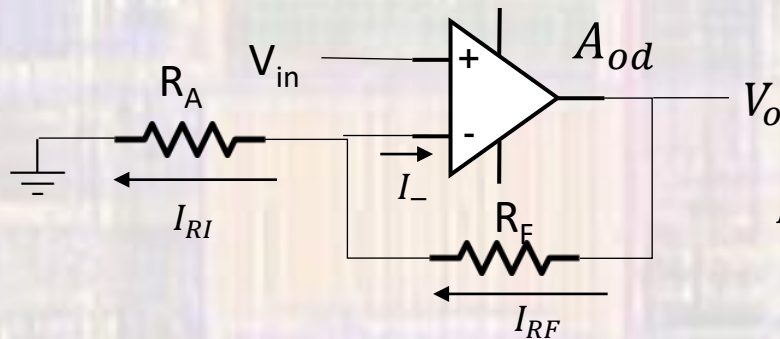- Fixed Gain Non-Inverting Summing Amplifier
 - Simplified analysis
 - Output moves to make the + and – inputs equal



$$I_{RF} = I_{RA} + I_- = I_{RA}$$

$$I_{RF} = \frac{V_O - V_-}{R_F} = \frac{V_O - V_{in}}{R_F}$$

$$I_{RA} = \frac{V_- - 0}{R_A} = \frac{V_{in}}{R_A}$$


$$\frac{V_O - V_{in}}{R_F} = \frac{V_{in}}{R_A}$$

$$V_O = \left(1 + \frac{R_F}{R_A}\right) V_{in}$$

$$A_v = 1 + \frac{R_F}{R_A}$$

OpAmp Circuits

- Difference Amplifier

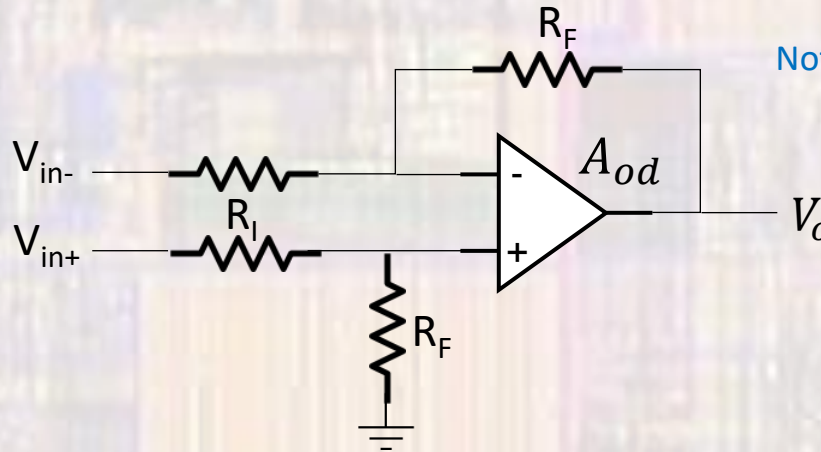


Note: no power pins
Amplifier flipped upside down

$$V_+ = V_{in+} \frac{R_F}{R_I + R_F} = V_- \quad \frac{V_{in-} - V_-}{R_I} = - \frac{V_O - V_-}{R_F}$$

$$V_O = \frac{R_F}{R_I} (V_{in+} - V_{in-})$$

OpAmp Circuits

- Current to Voltage Converter

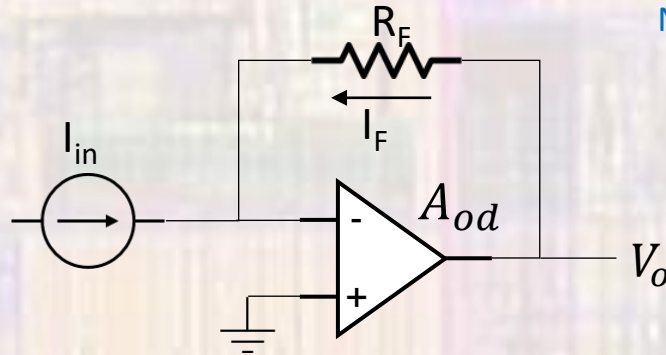

Note: no power pins
Amplifier flipped upside down


$$I_F = \frac{V_o - V_-}{R_F} = -I_{in}$$

The diagram shows a blue arrow pointing from the output node V_o to the inverting input node V_- , indicating the voltage difference used in the equation.

$$V_o = -I_{in}R_F$$

OpAmp Circuits


- Voltage to Current Converter

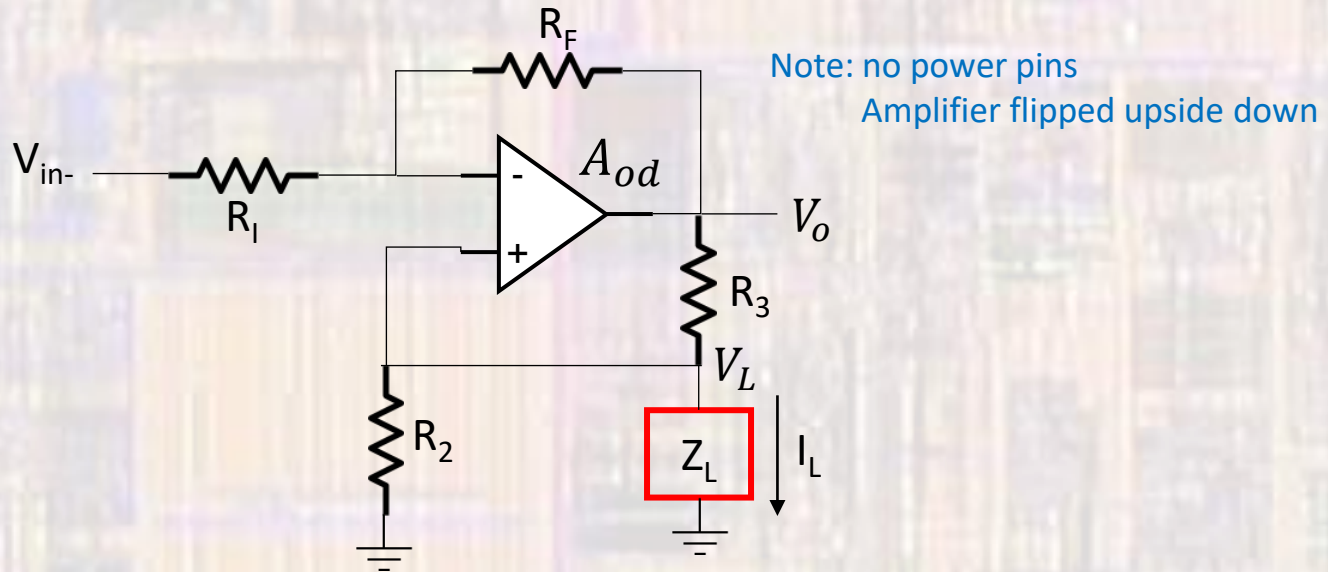

$$I_L = \frac{-V_{in}}{R_2} \left| \frac{R_F}{R_2 R_3} = \frac{1}{R_2} \right.$$

OpAmp Circuits

- Integrator

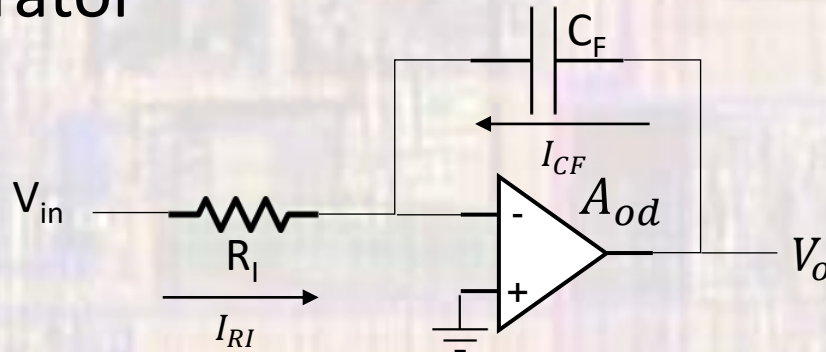


$$I_{CF} = C_F \frac{dv_o}{dt} = -\frac{V_{in}}{R_I}$$

$$dv_o = -\frac{V_{in}}{C_F R_I} dt$$

$$V_o = V_{CF0} - \frac{1}{C_F R_I} \int_0^t V_{in}(t') dt'$$

OpAmp Circuits

- Differentiator

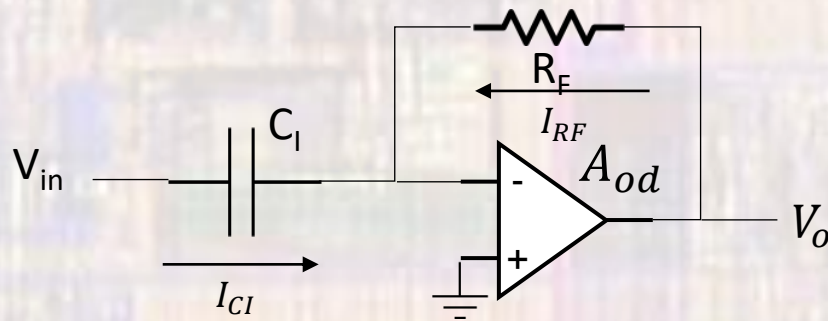

$$I_{CI} = C_I \frac{dv_{in}}{dt} = -\frac{V_o}{R_F}$$

$$V_o = -R_F C_I \frac{dv_{in}}{dt}$$