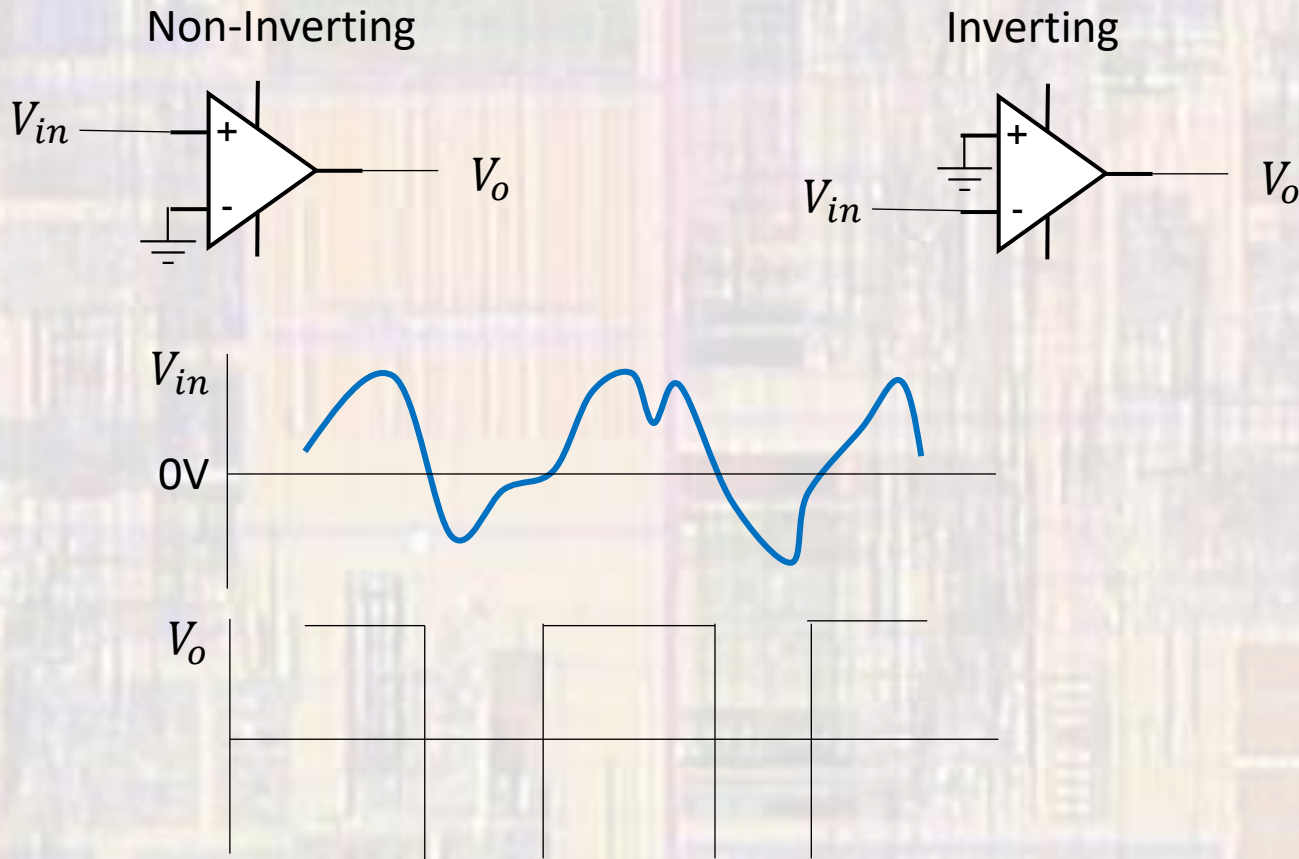


# OpAmp Circuits II

Last updated 4/20/22


# OpAmp Circuits II

- Zero Crossing Detector
  - Open Loop opamp


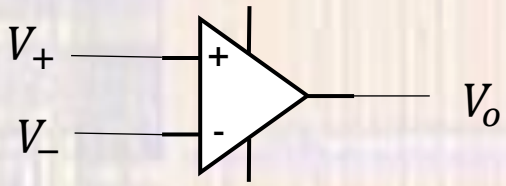
# OpAmp Circuits II


- Comparator
  - Special opamp with non-saturating outputs
    - Reduced delay in switching rail-to-rail



$$V_o = vdd \text{ or } vss$$

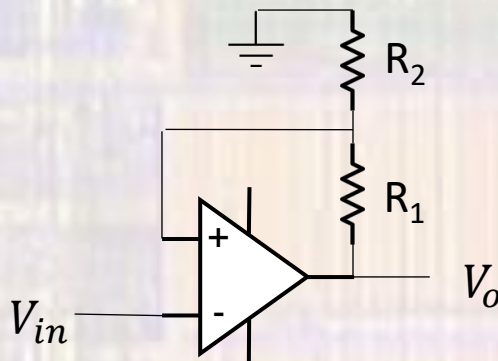
# OpAmp Circuits II

- Schmitt Trigger
  - Positive feedback
  - Non-overlapping switching points



$$\text{when } V_o = v_{dd}, \text{ then } v_+ = v_{dd} \frac{R_2}{R_1 + R_2}$$
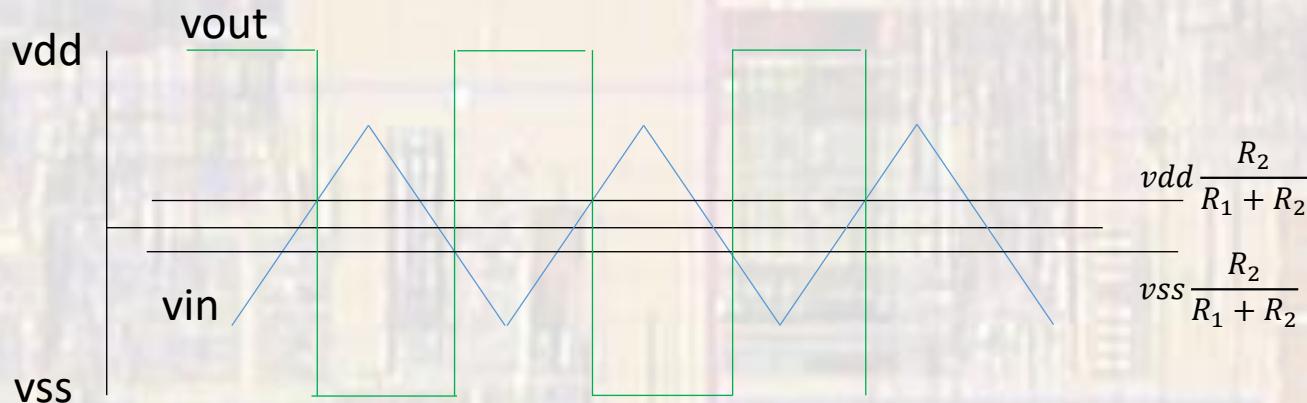
$$\text{when } V_o = v_{ss}, \text{ then } v_+ = v_{ss} \frac{R_2}{R_1 + R_2}$$



# OpAmp Circuits II



- Voltage Controlled Oscillator (VCO)

- Integrator

- Opamp wants  $v_{+input} = v_{-input}$

- When the MOSFET is off

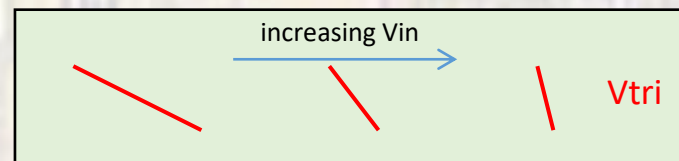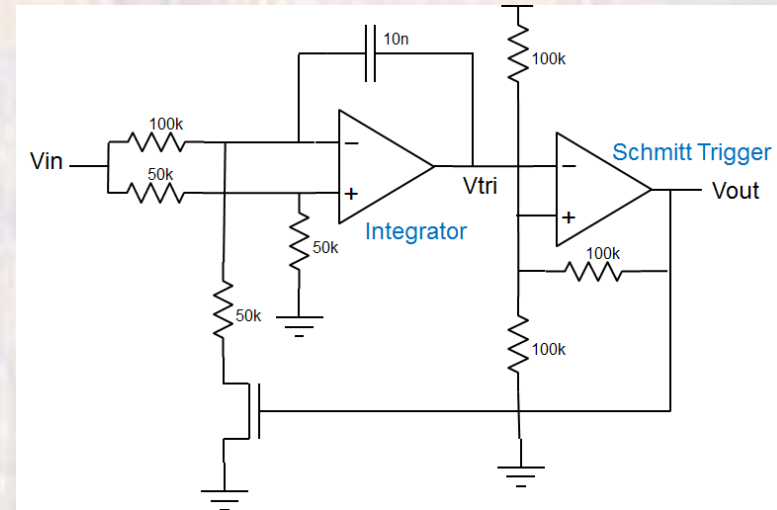- + input is  $V_{in}/2$  (minus input wants to be  $V_{in}/2$ )
- current through 100K resistor must go through C
- current through C  $I_c = -Cdv/dt$
- $-dv/dt$  is proportional to  $V_{in} \rightarrow$  the opamp slews down




# OpAmp Circuits II

- Voltage Controlled Oscillator (VCO)

- Integrator

- Opamp wants  $v_{+input} = v_{-input}$

- When the MOSFET is on

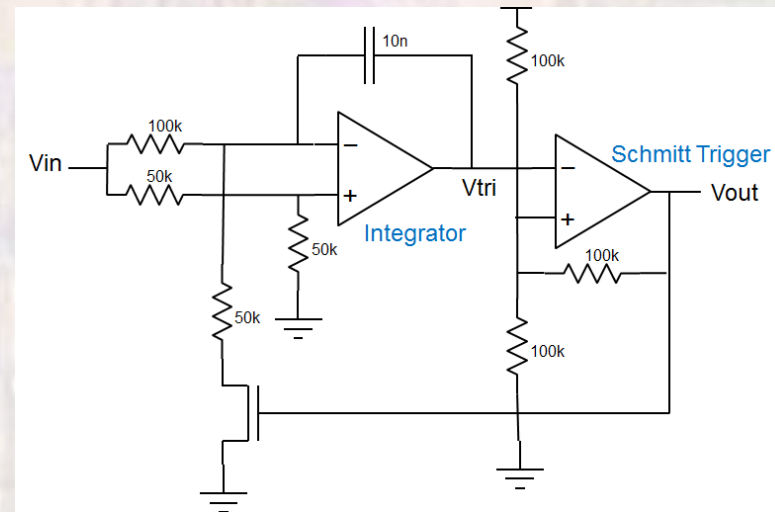


- + input is  $V_{in}/2$  (minus input wants to be  $V_{in}/2$ )

- current through the 100K resistor is  $\frac{1}{2}$  the current through 50K and MOSFET

- the other half the current through the MOSFET must come from the C

- current through C  $I_c = Cdv/dt$

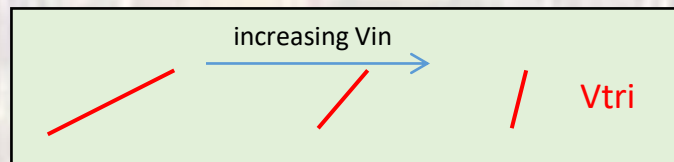- $dv/dt$  is proportional to  $V_{in} \rightarrow$  the opamp slews up



# OpAmp Circuits II

- Voltage Controlled Oscillator (VCO)

- Schmitt Trigger

- When Vout is high




- Mosfet is on → Vtri is slewing up
- + input is  $V_{dd} * 2/3$

- When Vtri goes above  $V_{dd} * 2/3$  the opamp switches to  $V_{out} = 0$
- mosfet turns off → Vtri slews down

- When Vout is low

- Mosfet is off → Vtri is slewing down
- + input is  $V_{dd} * 1/3$

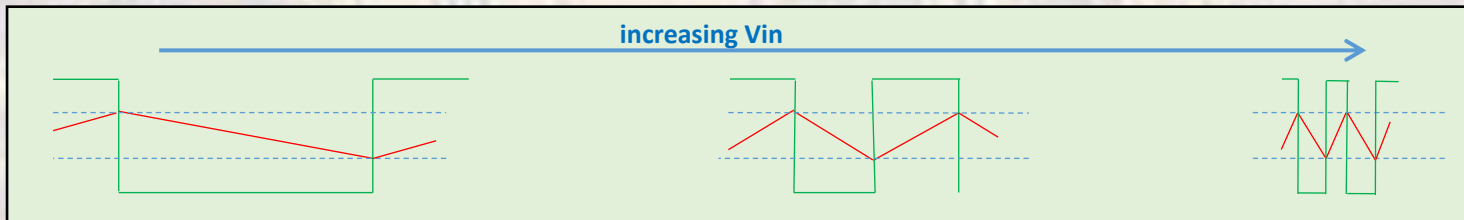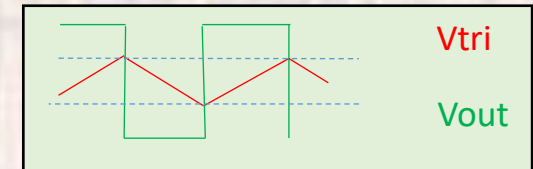
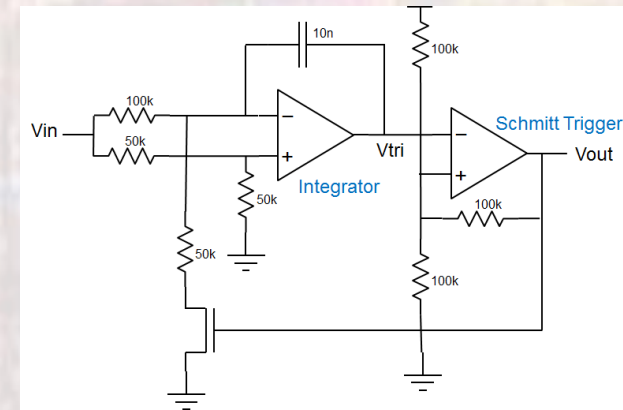
- When Vtri goes below  $V_{dd} * 1/3$  the opamp switches to  $V_{out} = \text{high}$
- mosfet turns on → Vtri slews up



**VCO**

# OpAmp Circuits II



- Voltage Controlled Oscillator (VCO)

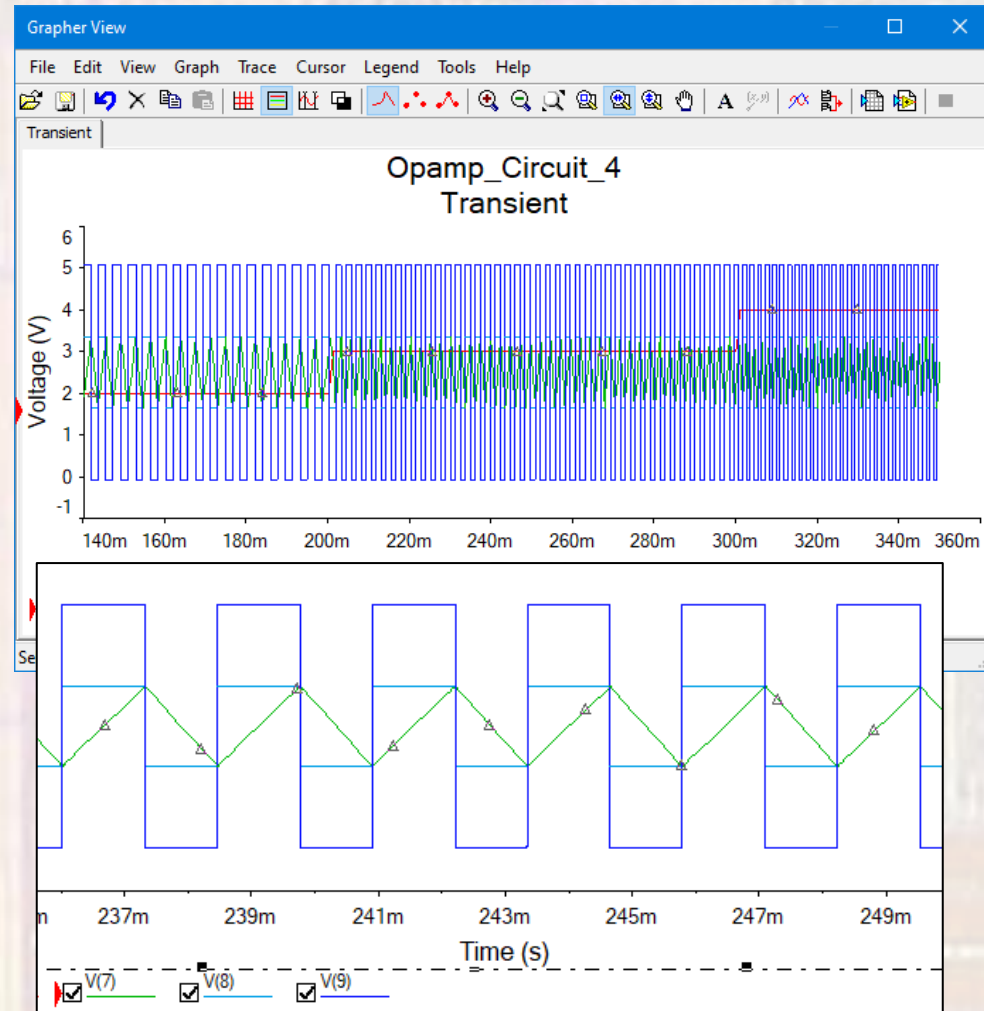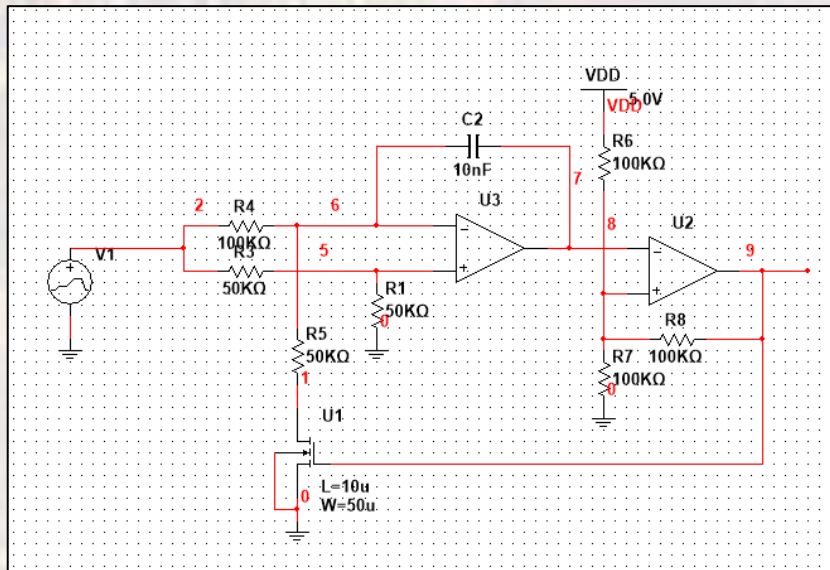





# OpAmp Circuits II

- Peak Detector

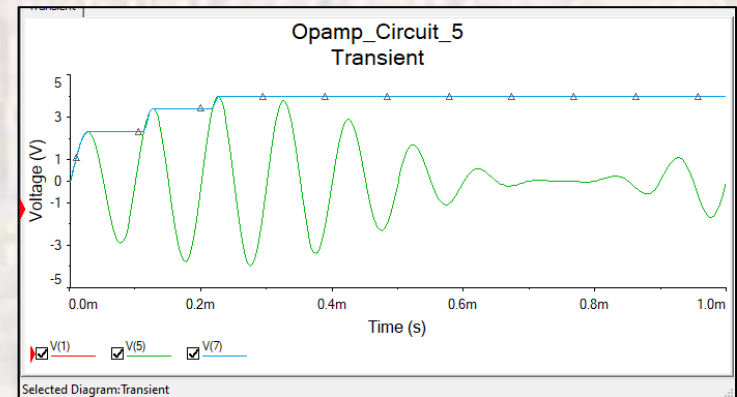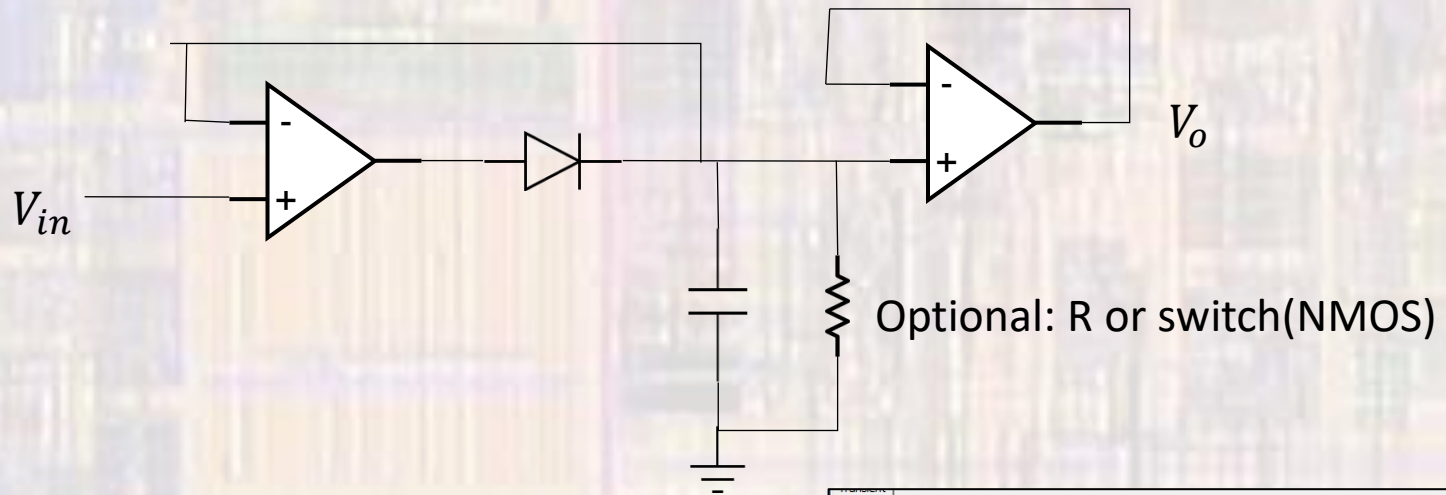

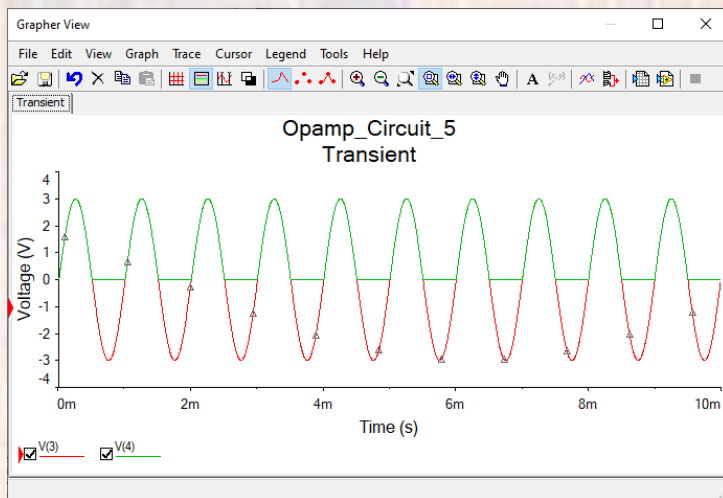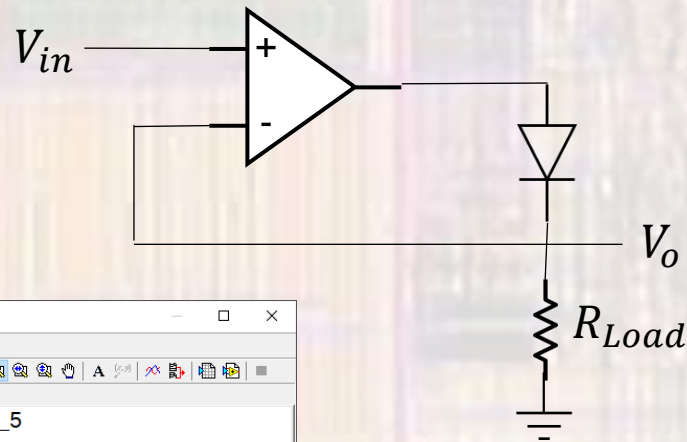
# OpAmp Circuits II

- Half-Wave Precision Rectifier
  - Removes the Diode voltage drop from the output




# OpAmp Circuits II

- Log Amplifier

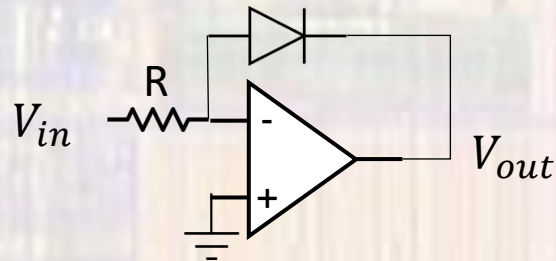


$$V_{in}/R = I_D = I_S e^{\frac{V_D}{nV_T}} = I_S e^{\frac{-V_{out}}{nV_T}}$$
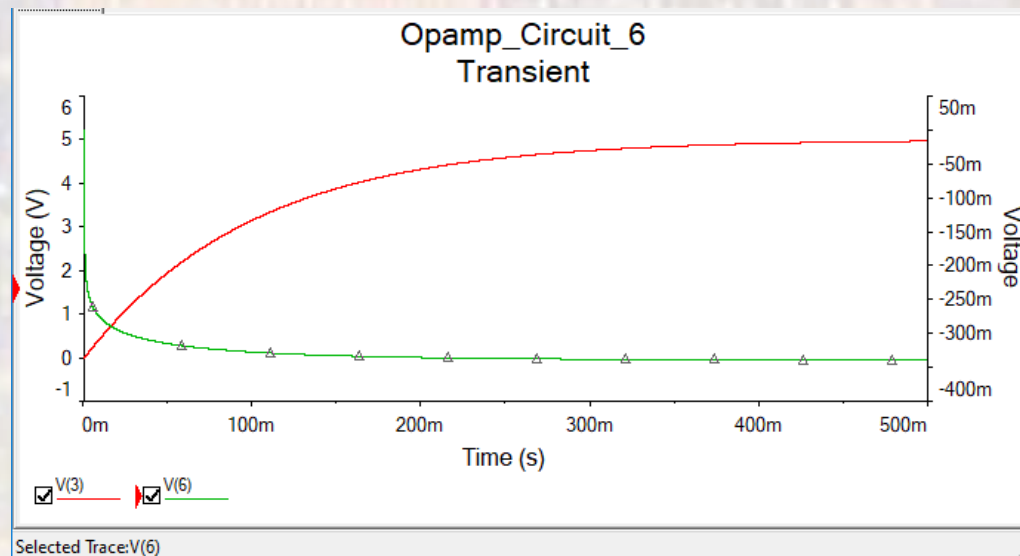
$$V_{out} = -nV_T \ln\left(\frac{V_{in}}{I_S R}\right)$$




# OpAmp Circuits II

- Exponential Amplifier

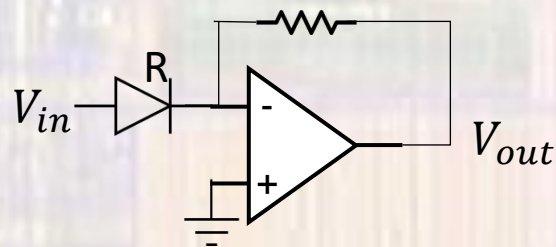


$$V_{out}/R = I_D = I_S e^{\frac{V_D}{nV_T}} = I_S e^{\frac{V_{in}}{nV_T}}$$
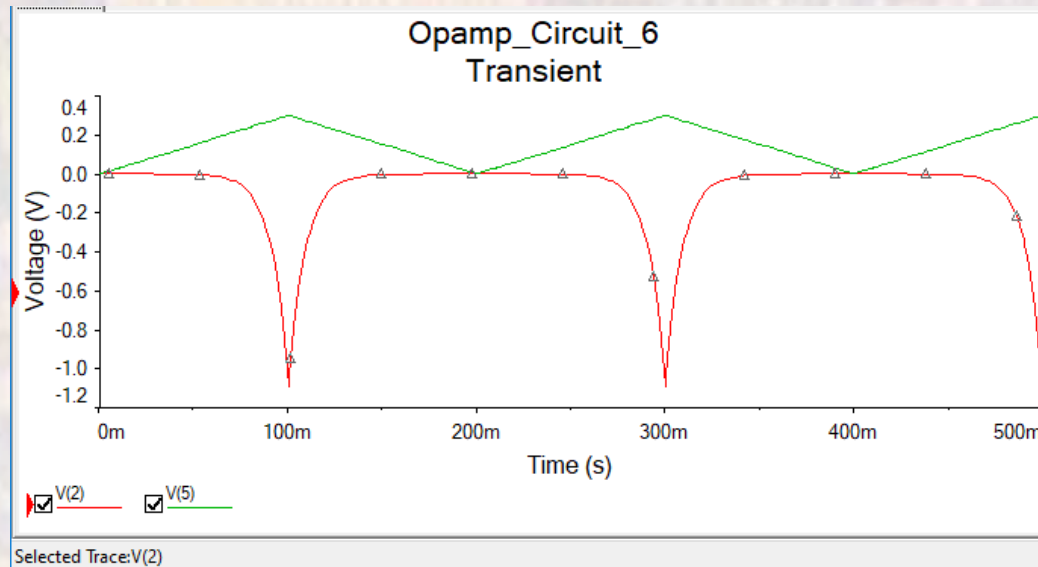
$$V_{out} = -RI_S e^{\frac{V_{in}}{nV_T}}$$



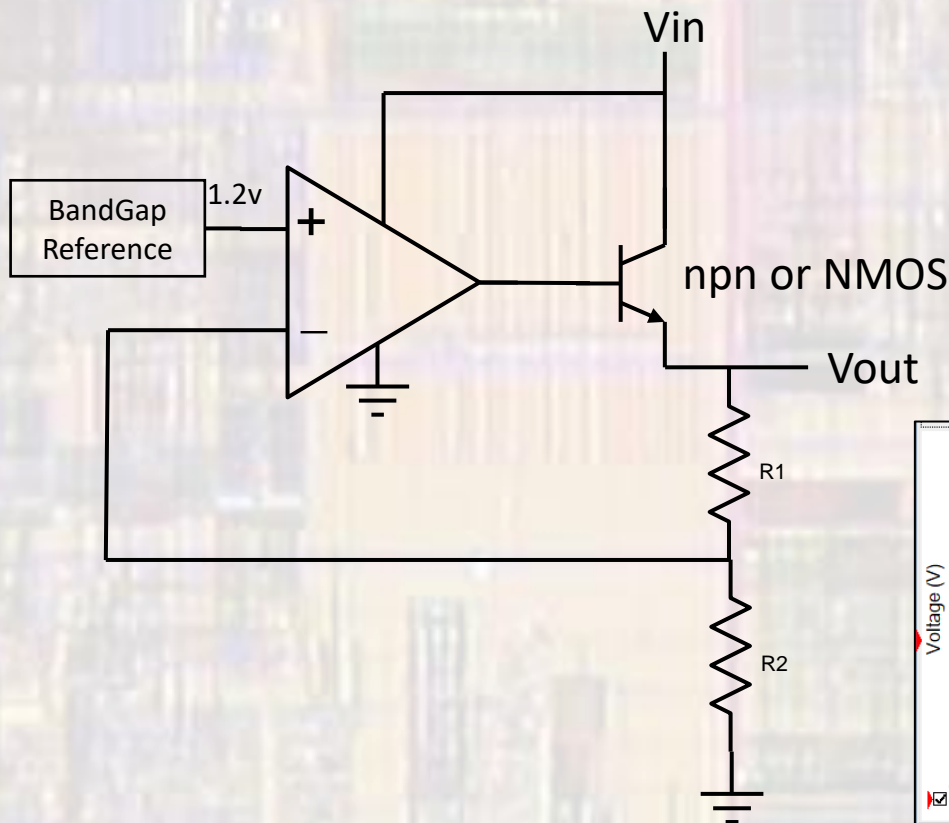
# OpAmp Circuits II

- Regulated Supply
  - Super Simple Regulator





$$\frac{R2}{R1 + R2} V_{out} = V_{bg}$$

$$V_{out} = V_{bg} \frac{R1 + R2}{R2}$$

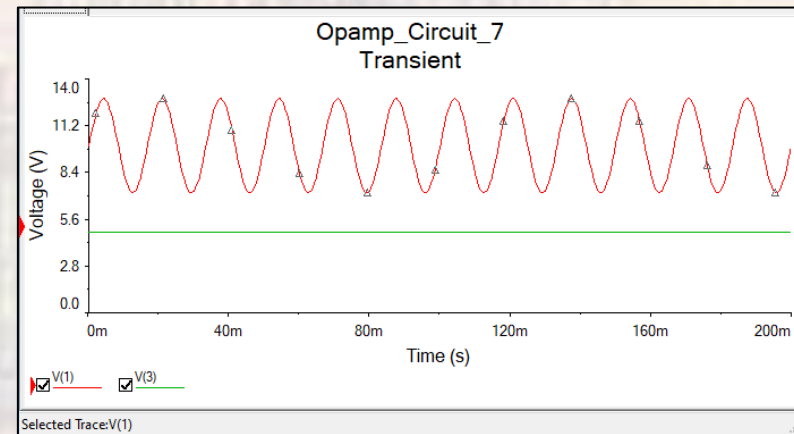

# OpAmp Circuits II

- Instrumentation Amplifier

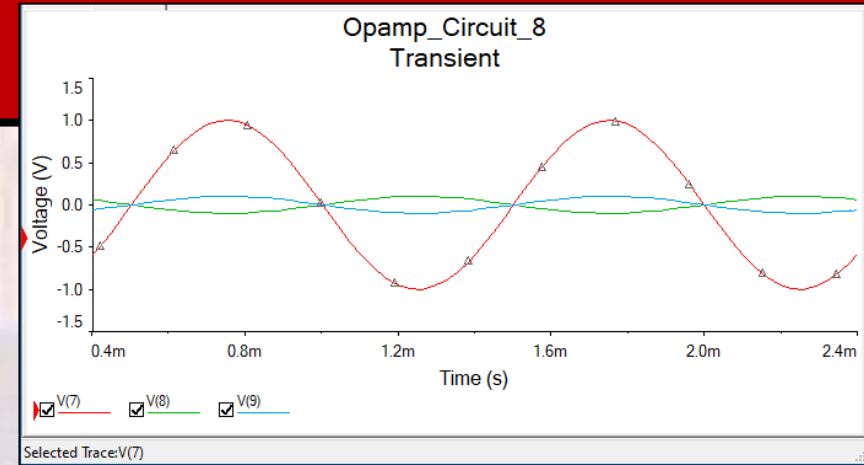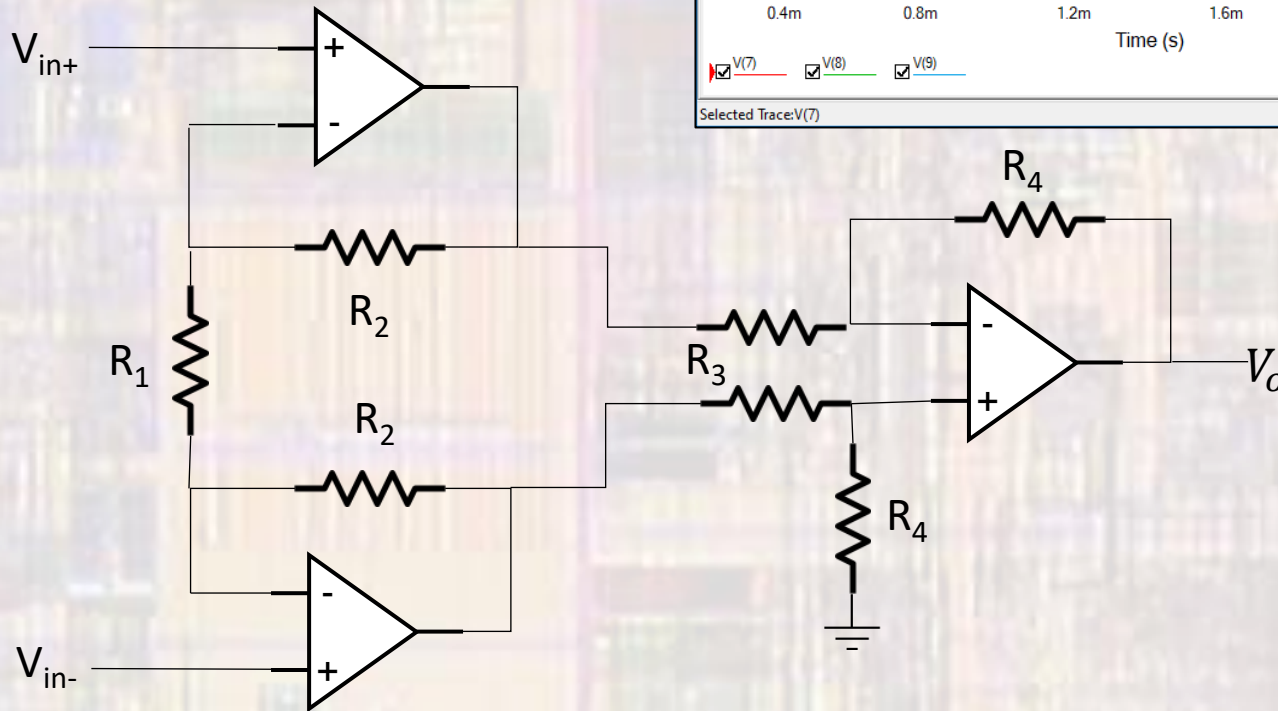

$$V_o = \frac{R_4}{R_3} \left( 1 + \frac{2R_2}{R_1} \right) (V_{in+} - V_{in-})$$