


OpAmps

Last updated 4/14/22


OpAmps

- Operational Amplifier (OpAmp)
 - High Gain difference amplifier

$$V_o = A_{od} (V_+ - V_-)$$

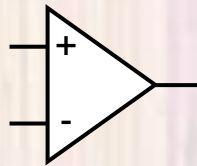

Implied power connections




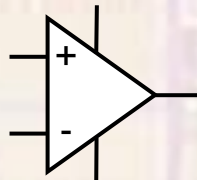


Explicit power connections

OpAmps

- Ideal OpAmp
 - High Gain difference amplifier
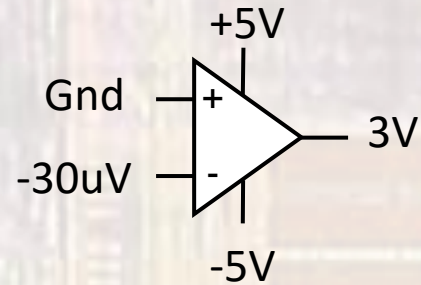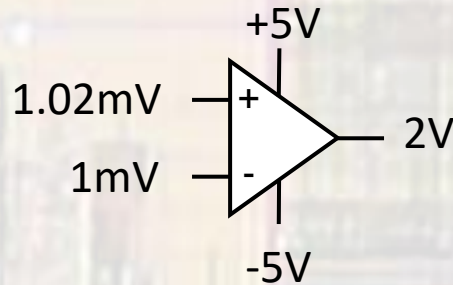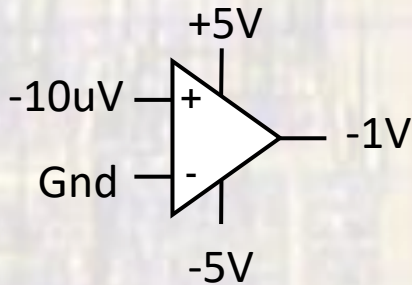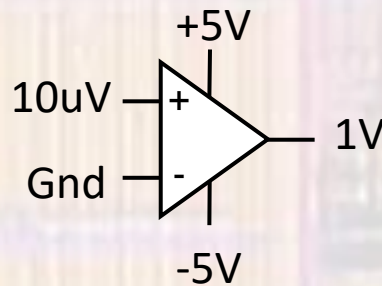
$$V_o = A_{od}(V_+ - V_-) \quad A_{od} = 100,000$$





OpAmps

- OpAmp Limitations


- Output Swing

- Common opamps can only swing the output to about 1V from the positive or negative voltage rails
 - Rail-to-rail opamps can get to within 10s of mv of the rails

$$A_{od} = 100,000$$

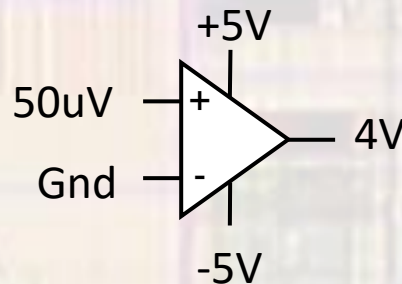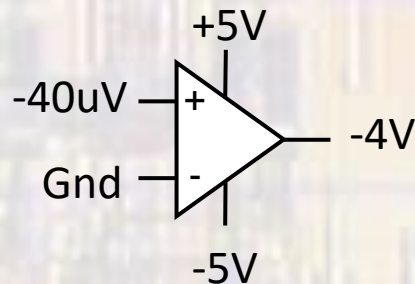

Output Saturated
(clipped, limited)

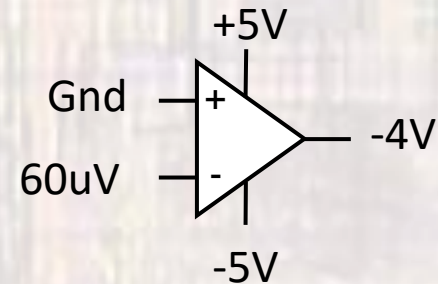

Output Saturated
(clipped, limited)



OpAmps

- OpAmp Limitations

- Slew Rate

- Limit on how fast the output can change
- Limits large signal rise and fall times at the output
 - Typically between 1V/us and 100V/us
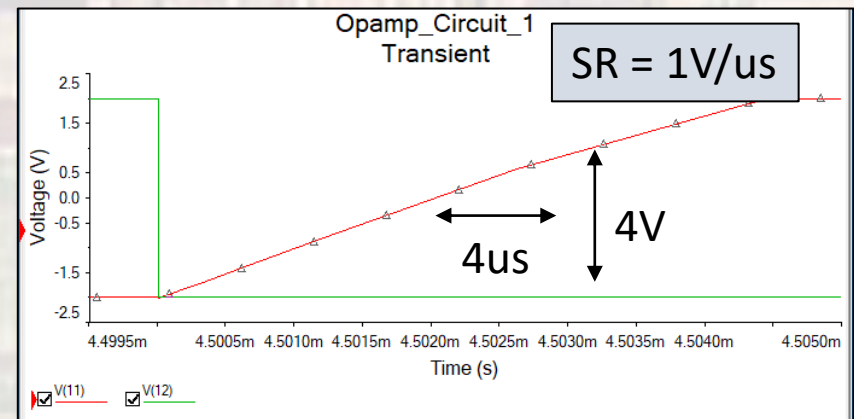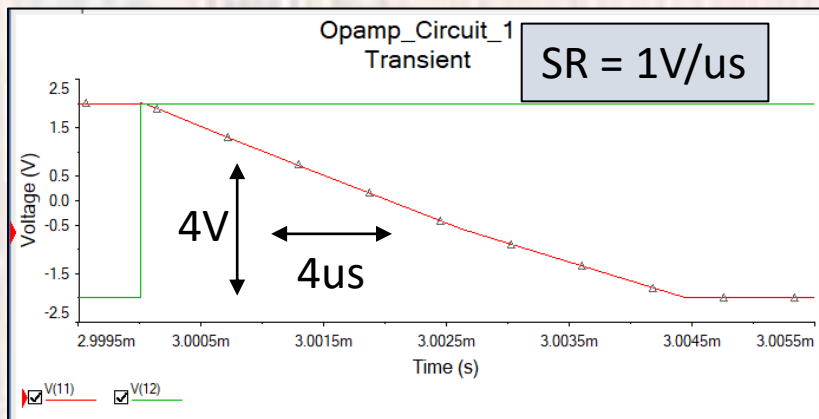
$$\left(\frac{dV_o}{dt}\right)_{max} = SR$$






OpAmps

- OpAmp Limitations

- Input Offset

- This represents a built-in error between the + and – inputs
 - Bipolar: < 20mV
 - CMOS: < 1mV
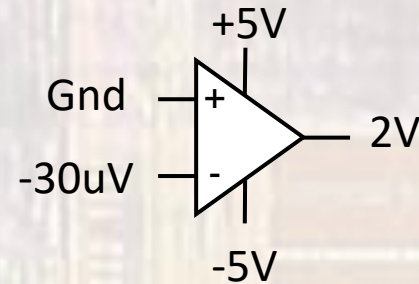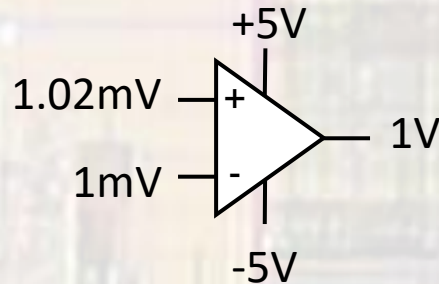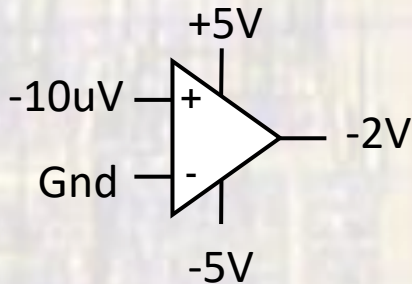
$$V_o = A_{od}(V_+ - V_- - V_{offset}) \quad A_{od} = 100,000$$
$$V_{os} = 10\mu\text{V}$$



OpAmps

- OpAmp Limitations
 - Input bias current / input bias current offset
 - The required input current to operate the opamp
 - The offset from + to – for the input bias currents
 - Bipolar inputs
 - Bias current, typically $< 1\mu\text{A}$
 - Offset, typically 20% - 50% of bias current
 - CMOS inputs, typically $< 1\text{nA}$

OpAmps

- OpAmp Limitations
 - Input Impedance
 - The impedance looking into the inputs
 - Bipolar input opamps typically between $1\text{M}\Omega$ and $10\text{M}\Omega$
 - CMOS input opamps typically $> 10\text{G}\Omega$
 - Output Impedance
 - The impedance looking into the output
 - Typically $< 50\Omega$

OpAmps

- OpAmp Limitations

- Common Mode Rejection Ratio (CMRR)

- This represents the opamps ability to reject signals that are present on both inputs (common)
- CMRR is the ratio of the common-mode gain to differential-mode gain

$$V_o = A_{od}(V_+ - V_-) + A_{CM} \frac{(V_+ + V_-)}{2}$$


$$CMRR = \frac{A_{od}}{A_{CM}}$$

$$CMRR_{dB} = 20 \log \frac{A_{od}}{A_{CM}}$$

$$A_{od} = 100,000$$

$$A_{CM} = 80dB$$

$$(10,000)$$

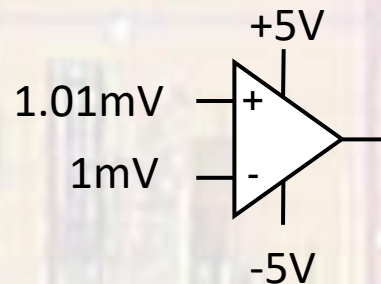


$$1V + \frac{100,000 (1.01mV + 1mV)}{10,000 \cdot 2}$$

$$1V + 10.05mV = 1.01V$$

OpAmps

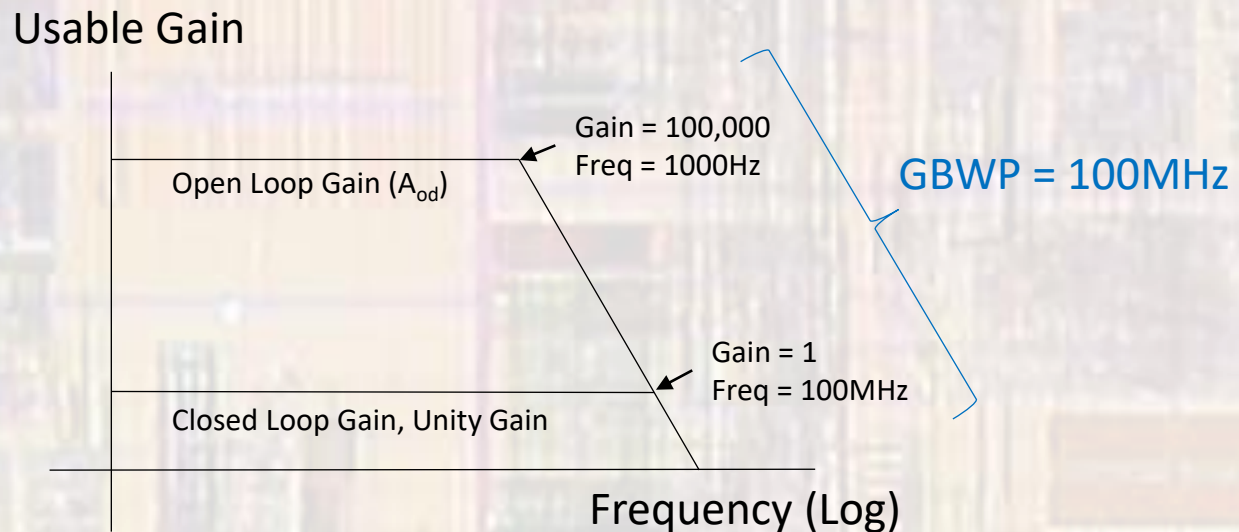- OpAmp Limitations
 - Gain Bandwidth Product
 - Product of the Gain at a specific frequency and the frequency
 - For most negative feedback configurations this is constant
 - Sometimes called the Unity Gain Bandwidth



OpAmps

- OpAmp Models

