


RC Active Filters

1st Order

Last updated 4/28/22

RC Active Filters

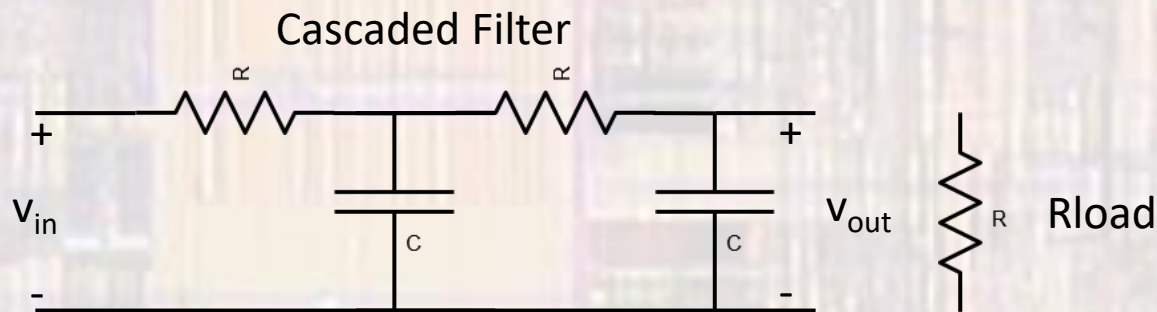- Passive filter concerns
 - Each stage loads the previous stage
 - Best case gain is 1 (0dB)
 - Any non-infinite output load will change the filter output




RC Active Filters

- Why RC
 - It is much easier and cheaper to build integrated circuit capacitors and resistors than inductors

RC Active Filters

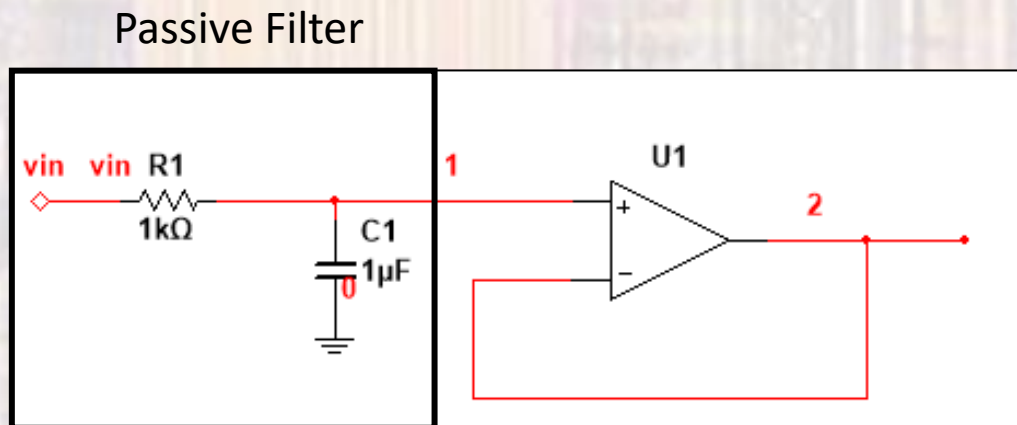- Just buffer the passive filter – Low Pass
 - Non-inverting
 - Load insensitive
 - Can be cascaded
 - Unity Gain




$$f_c = \frac{1}{2\pi RC}$$


$$A = 1$$

$$A_v = \frac{A}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}}$$

RC Active Filters

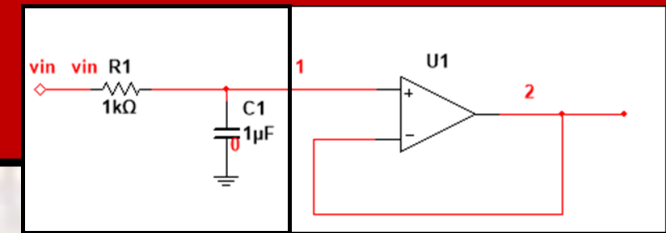


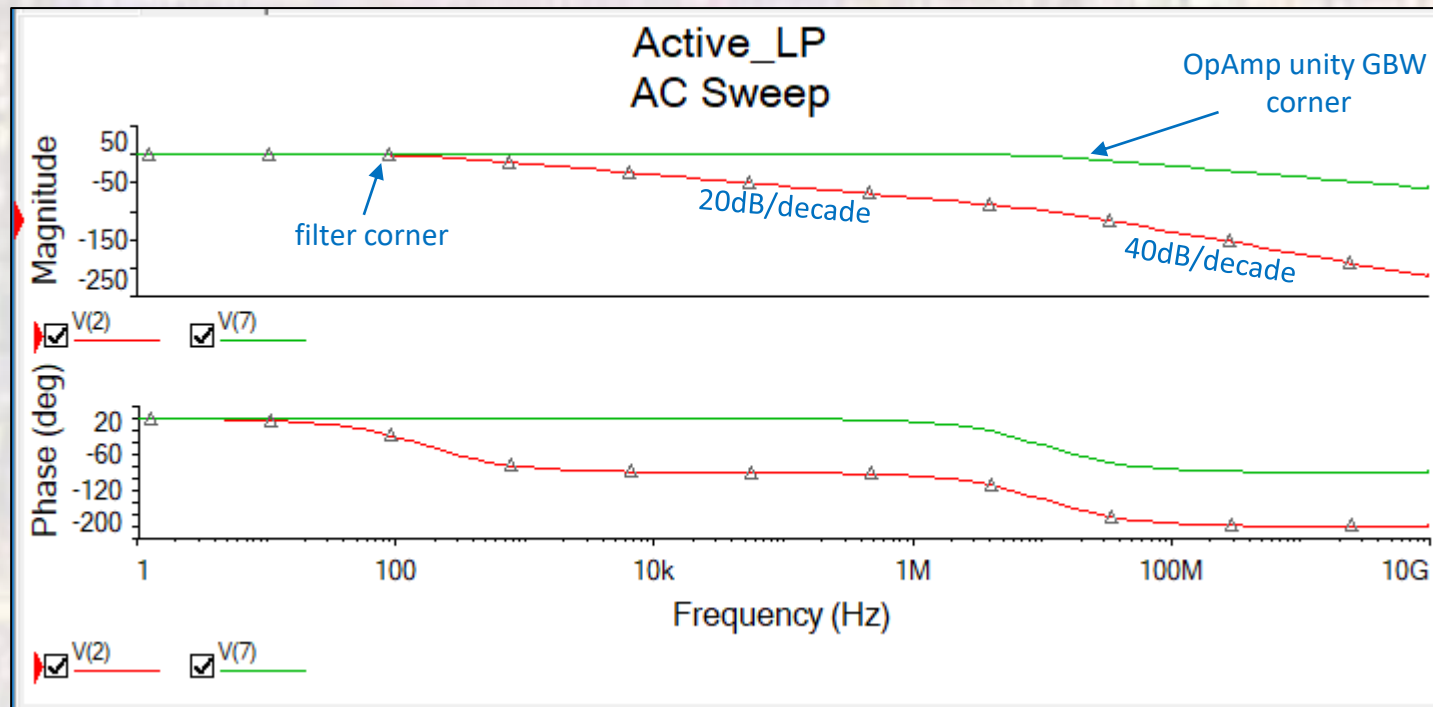- Just buffer the passive filter – **Caveat # 1**
 - The OpAmp has an internal Lowpass characteristic (GBWP)
 - Can be good or bad depending on the situation



RC Active Filters

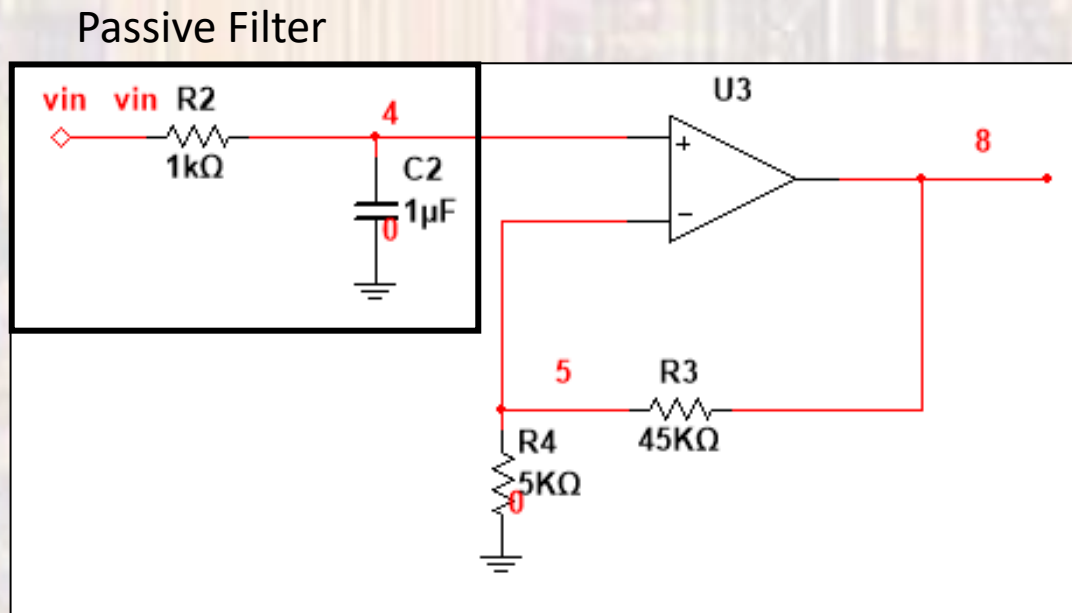- Buffer the passive filter with gain – Low Pass
 - Non-inverting
 - Load insensitive
 - Can be cascaded
 - Selectable Gain




$$f_c = \frac{1}{2\pi RC}$$

$$A = 1 + \frac{R_F}{R_I}$$

$$A_v = \frac{A}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}}$$


RC Active Filters

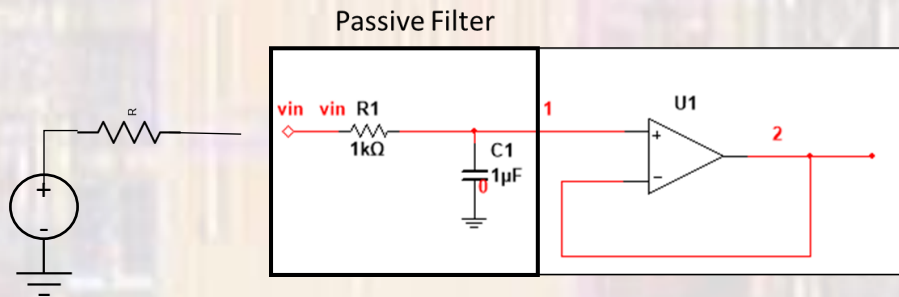- Buffer the passive filter – **Caveat # 2**
 - The filter has a relatively small input impedance
 - Loads the driver
 - Driver output impedance may affect the filter



RC Active Filters

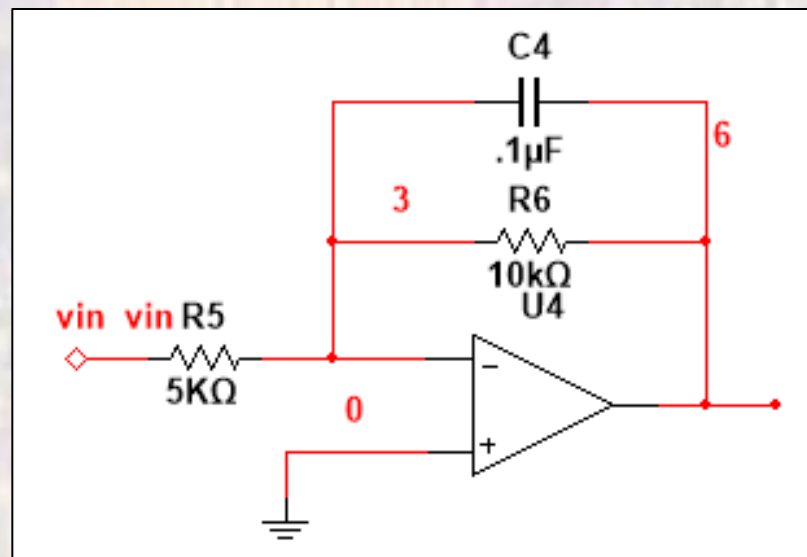- Buffer the passive filter – Low Pass
 - Remove the reactive element from the input
 - Inverting
 - Selectable Gain




$$f_c = \frac{1}{2\pi R_F C}$$

$$A = -\frac{R_F}{R_I}$$

$$A_v = \frac{A}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}}$$

RC Active Filters

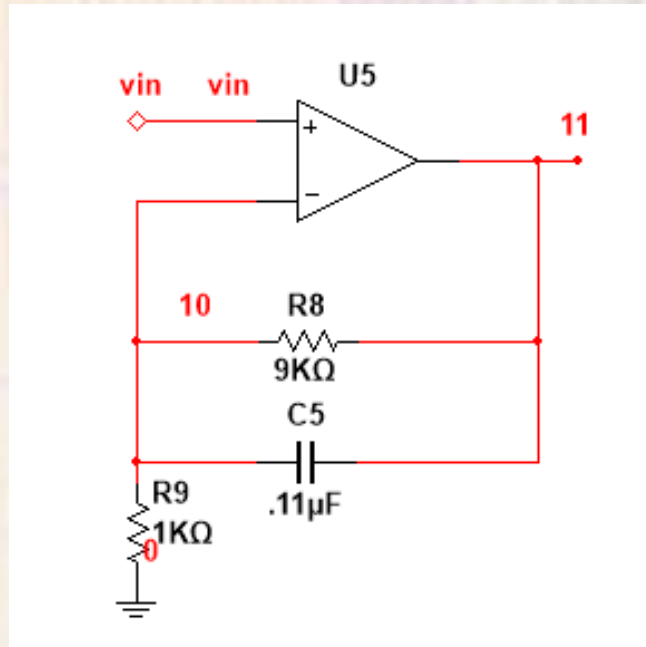- Buffer the passive filter – Low Pass
 - Remove the reactive element from the input
 - Non-inverting
 - Selectable gain
 - High frequencies \rightarrow unity gain



$$f_c = \frac{1}{2\pi R_F C}$$


$$A = 1 + \frac{R_F}{R_I}$$

$$A_v^* = \frac{A}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}}$$

$$* A_{v \min} = 1 = 0dB$$

RC Active Filters

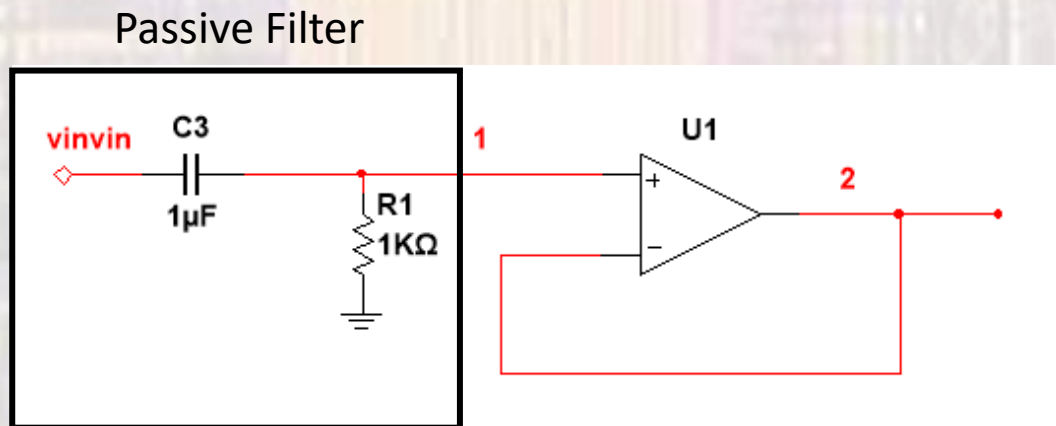- First order – High Pass
 - Non-inverting
 - Unity Gain




$$f_c = \frac{1}{2\pi RC}$$

$$A = 1$$

$$A_v = \frac{A \left(\frac{f}{f_c} \right)}{\sqrt{1 + \left(\frac{f}{f_c} \right)^2}}$$

RC Active Filters

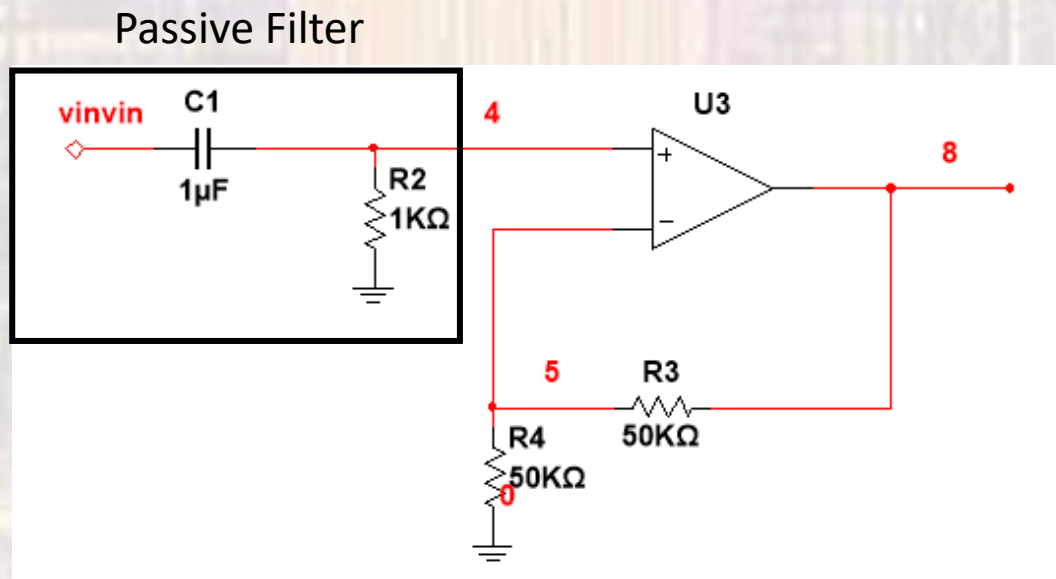- First order – High Pass
 - Non-inverting
 - Selectable Gain




$$f_c = \frac{1}{2\pi RC}$$

$$A = 1 + \frac{R_F}{R_I}$$

$$A_v = \frac{A\left(\frac{f}{f_c}\right)}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}}$$

RC Active Filters

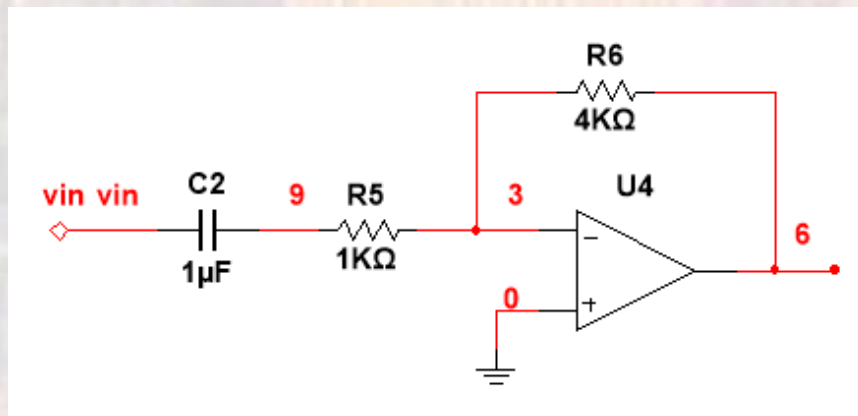- First order – High Pass
 - Inverting
 - Selectable Gain




$$f_c = \frac{1}{2\pi RC}$$

$$A = -\frac{R_F}{R_I}$$

$$A_v = \frac{A\left(\frac{f}{f_c}\right)}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}}$$

RC Active Filters

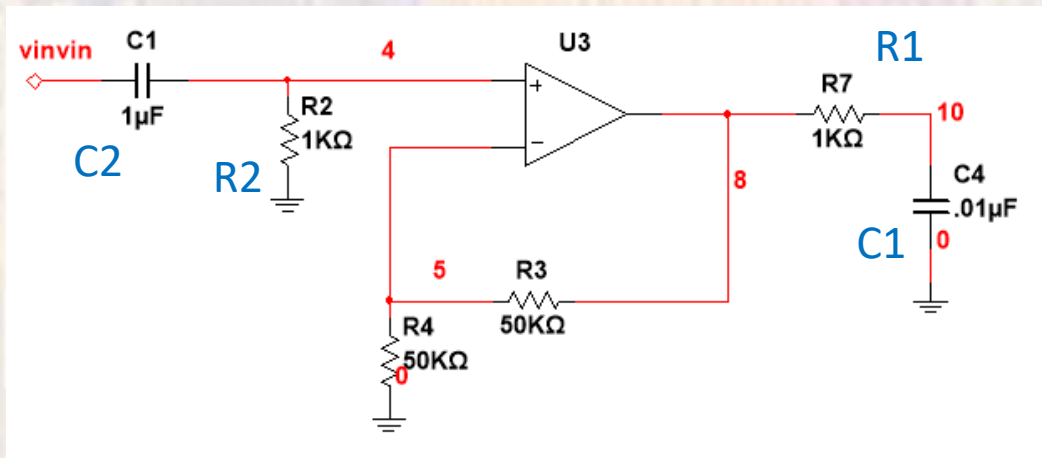- First order – Band Pass
 - Non-inverting
 - Selectable Gain
 - Wide passband



$$f_{CL} = \frac{1}{2\pi R_2 C_2}$$


$$f_{CU} = \frac{1}{2\pi R_1 C_1}$$

$$A = 1 + \frac{R_F}{R_I}$$

$$A_v = \frac{A \left(\frac{f}{f_{CH}} \right)}{\sqrt{1 + \left(\frac{f}{f_{CH}} \right)^2}} \frac{1}{\sqrt{1 + \left(\frac{f}{f_{CL}} \right)^2}}$$

RC Active Filters

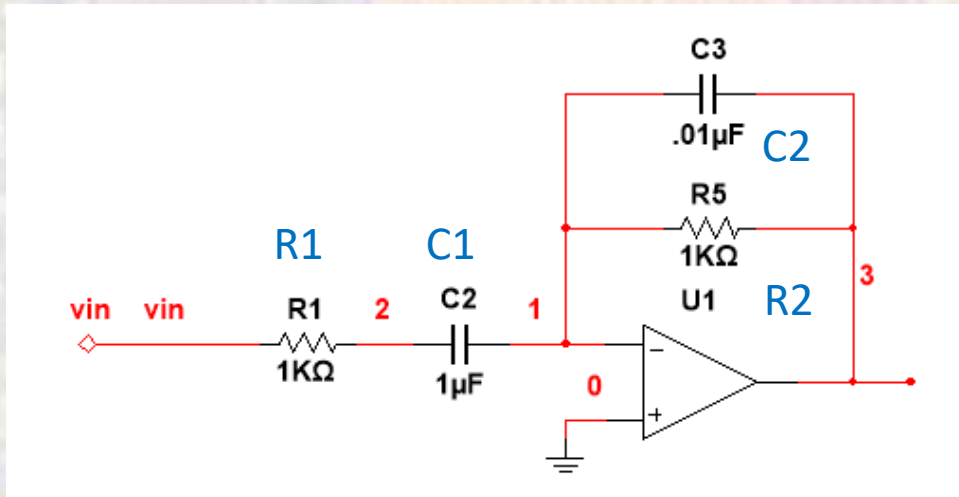- First order – Band Pass
 - Inverting
 - Selectable Gain
 - Narrower passbands possible



$$f_{CL} = \frac{1}{2\pi R1 C1}$$

$$f_{CU} = \frac{1}{2\pi R2 C2}$$


$$A = -\frac{R_F}{R_I}$$

$$A_v^* = \frac{A \left(\frac{f}{f_{CH}} \right)}{\sqrt{1 + \left(\frac{f}{f_{CH}} \right)^2}} \frac{1}{\sqrt{1 + \left(\frac{f}{f_{CL}} \right)^2}}$$

* At high frequencies, the OpAmp internal capacitance limits the rolloff

RC Active Filters

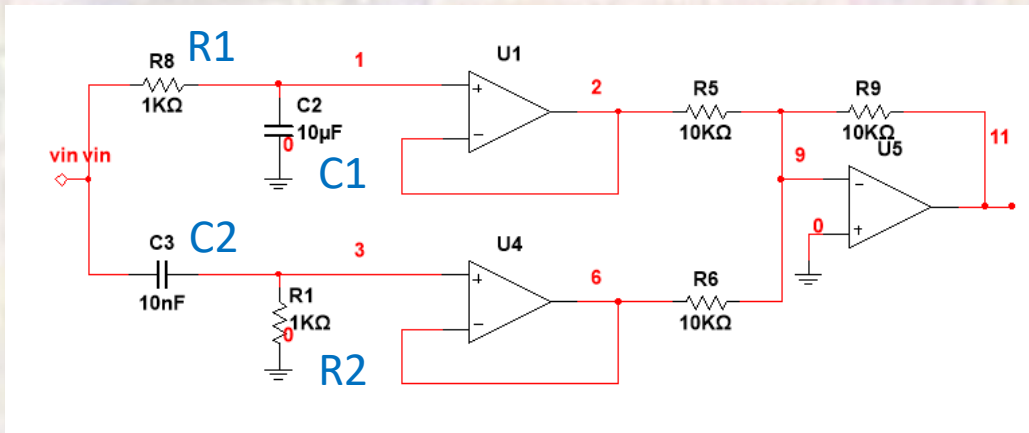- First order – Band Stop
 - Non-inverting
 - Selectable Gain



$$f_{CL} = \frac{1}{2\pi R1 C1}$$

$$f_{CU} = \frac{1}{2\pi R2 C2}$$

$$A = -\frac{R_F}{R_I}$$

$$A_v^* = \frac{A \left(\frac{f}{f_{CH}} \right)}{\sqrt{1 + \left(\frac{f}{f_{CH}} \right)^2}} \frac{1}{\sqrt{1 + \left(\frac{f}{f_{CL}} \right)^2}}$$

* At high frequencies, the OpAmp internal capacitance limits the rolloff