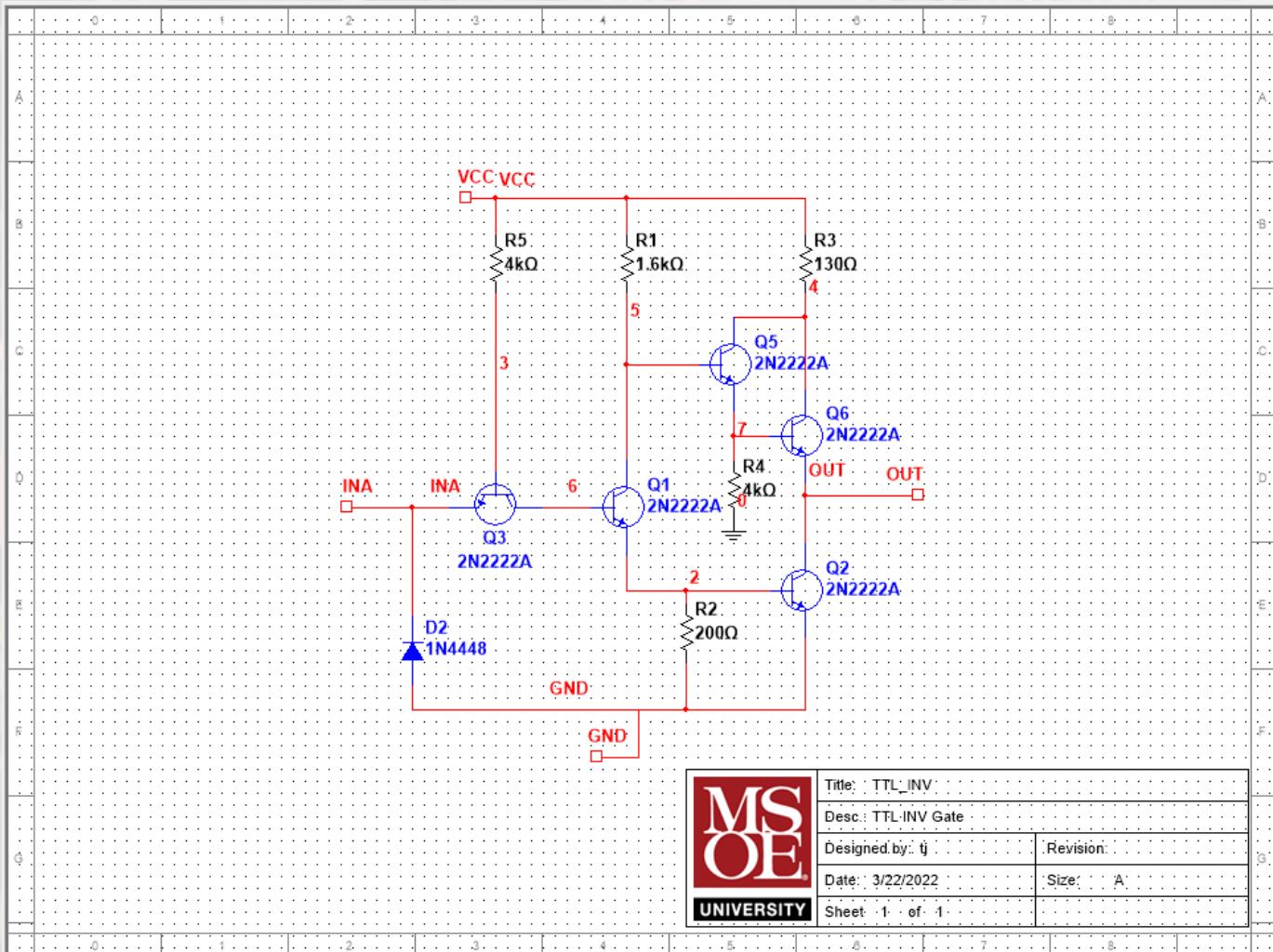


# Transistor Transistor Logic Implementation

Last updated 3/8/22


# TTL - Implementation

- Inverter




# TTL - Implementation

- Nand Gate

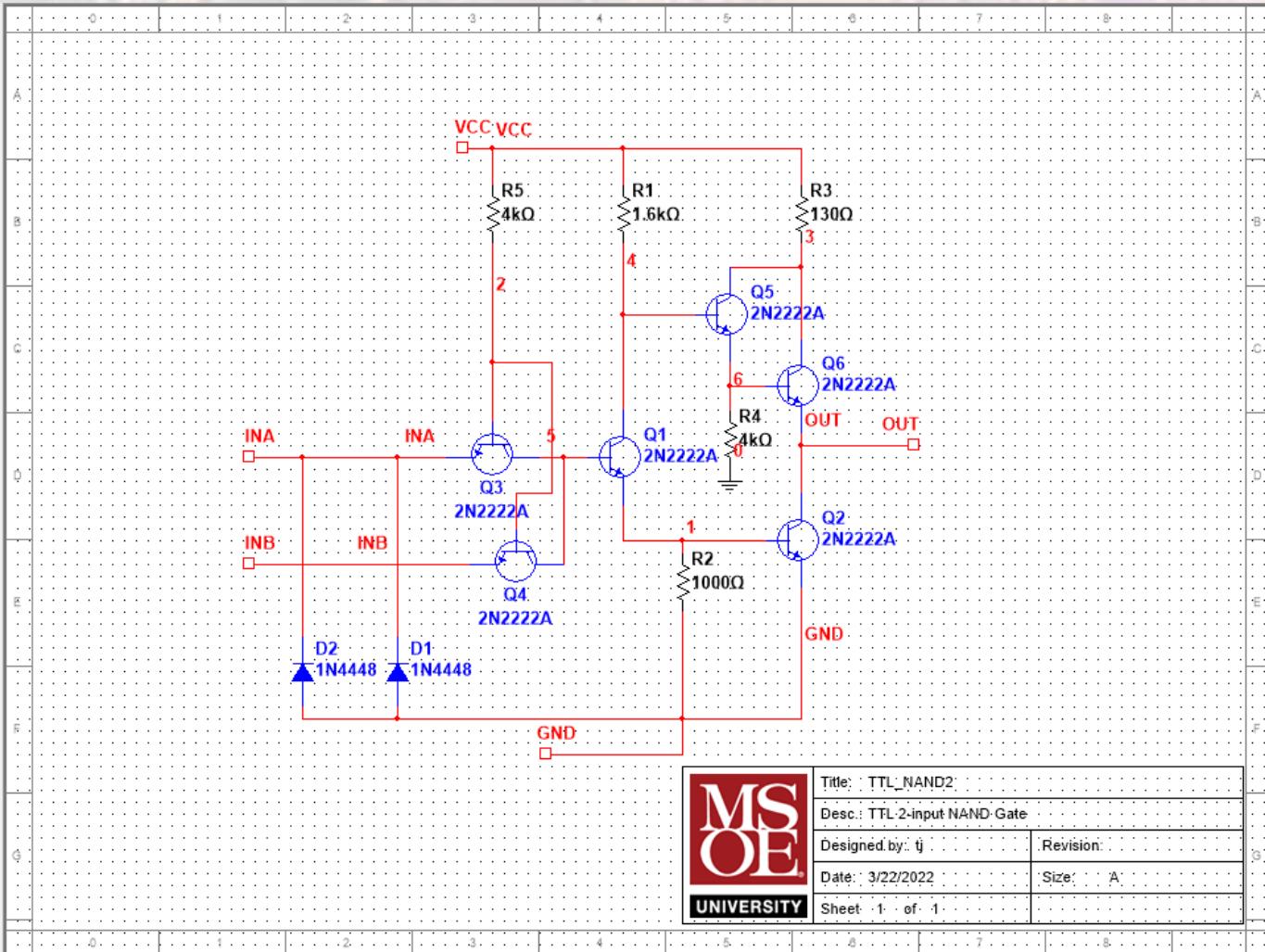

# TTL - Implementation

- Nor Gate

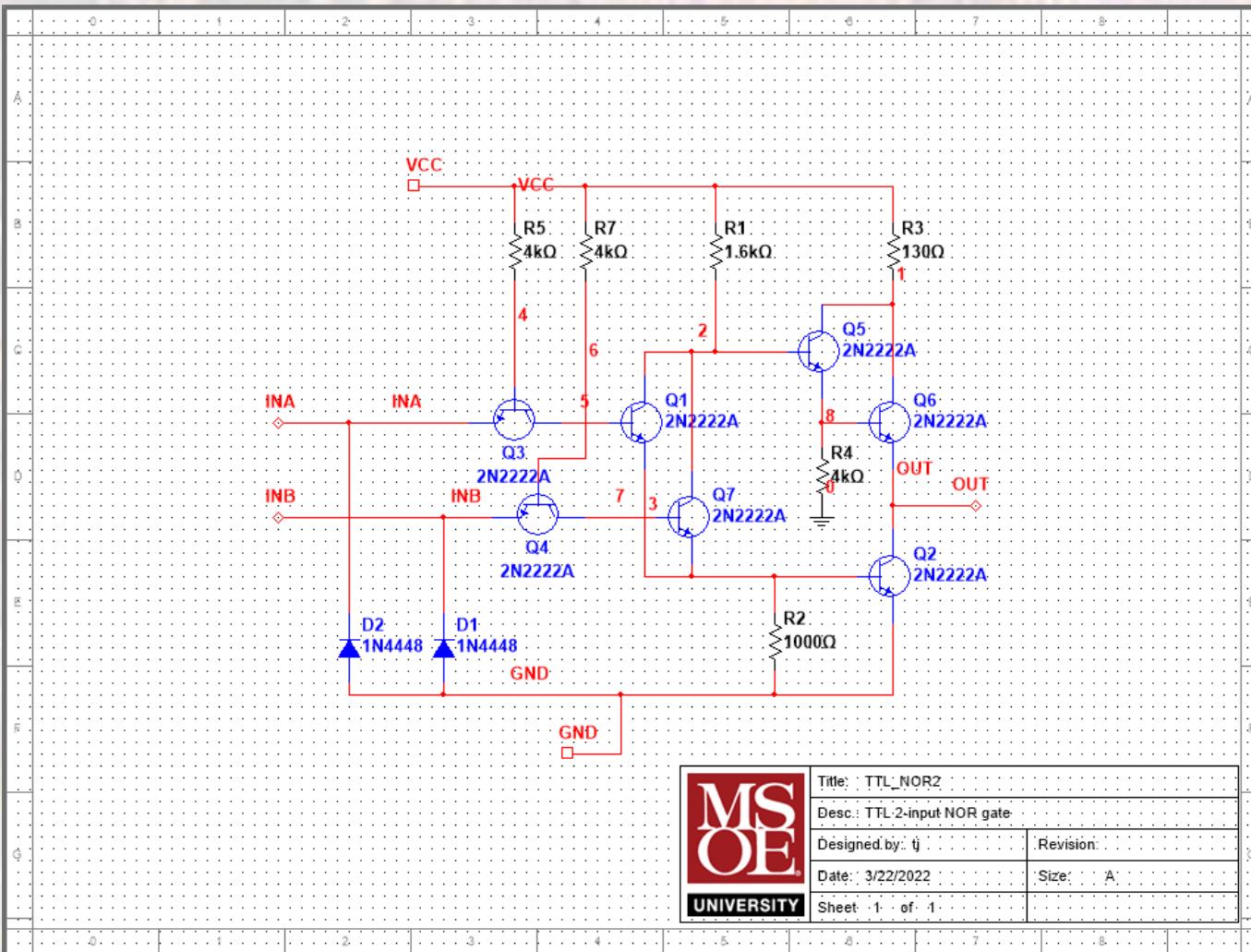

# TTL - Implementation

- Schottky Nand Gate

