


ALU

Arithmetic Logic Unit

Last updated 1/6/25

ALU

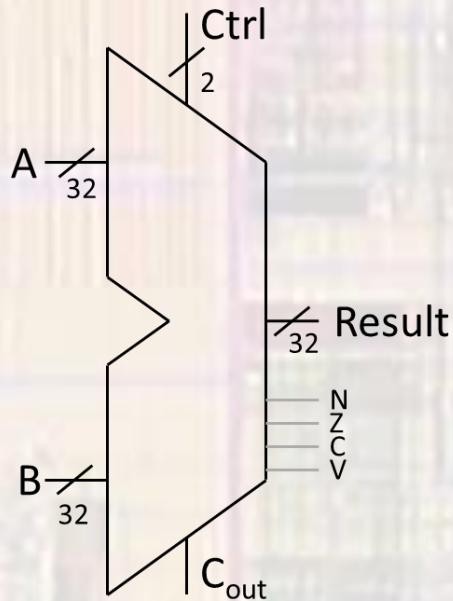- ALU - Arithmetic Logic Unit
 - Calculator on the computer
 - Logical operations
 - Arithmetic operations
 - Status signals




ALU

- Logical Instructions

- AND, OR

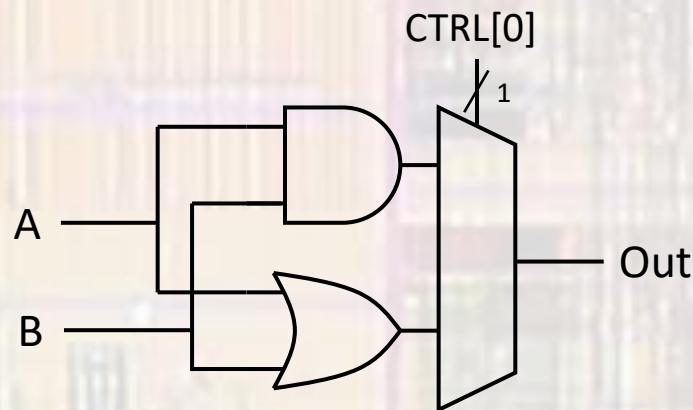- 2 inputs A and B
 - 1 output
 - 1 bit control




ALU

- Arithmetic Instructions

- ADD

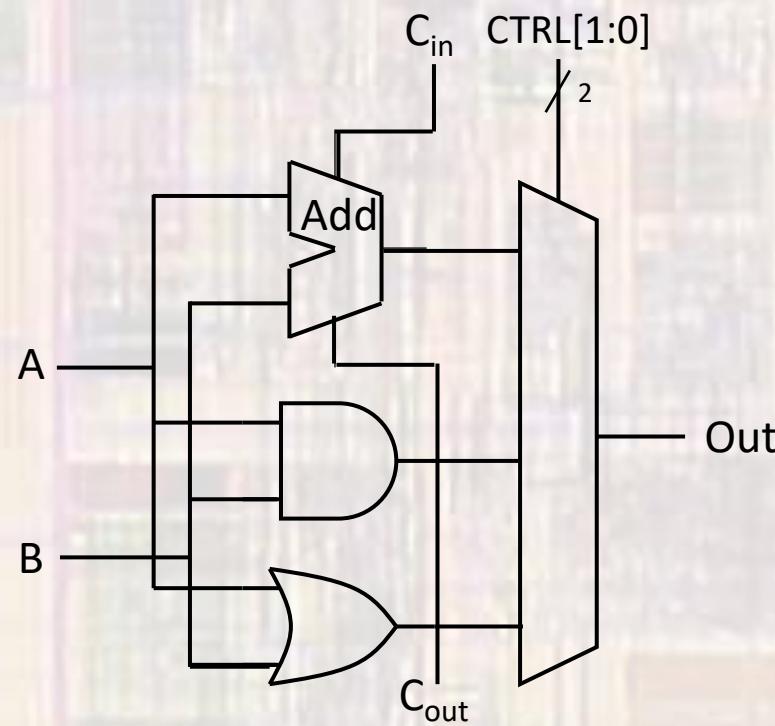- Inputs: A, B, C_{in}
 - Outputs: Out, C_{out}
 - 2 control inputs




ALU

- Arithmetic Instructions – cont'd


- Subtract

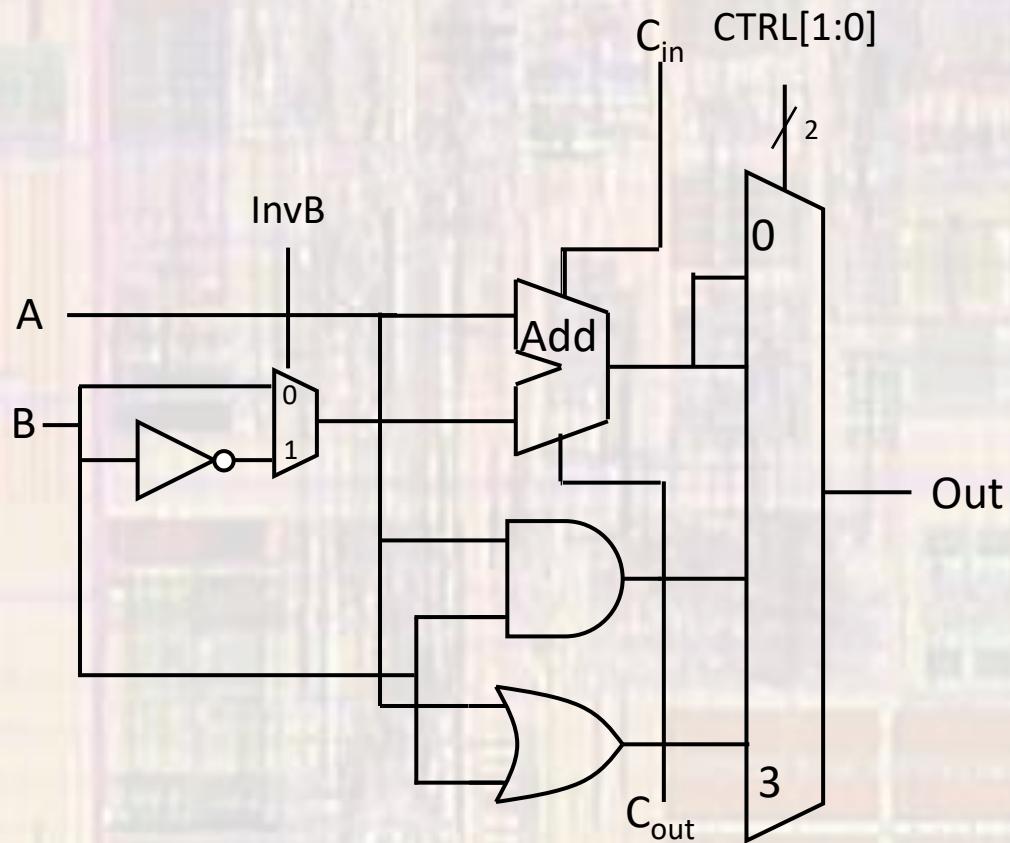- $A + (-B)$
 - Negate (invert) B
 - Carry-in = 1
 - Inputs: A, B, $C_{in} = 1$
 - Outputs: Out, C_{out}
 - 2 control inputs




ALU

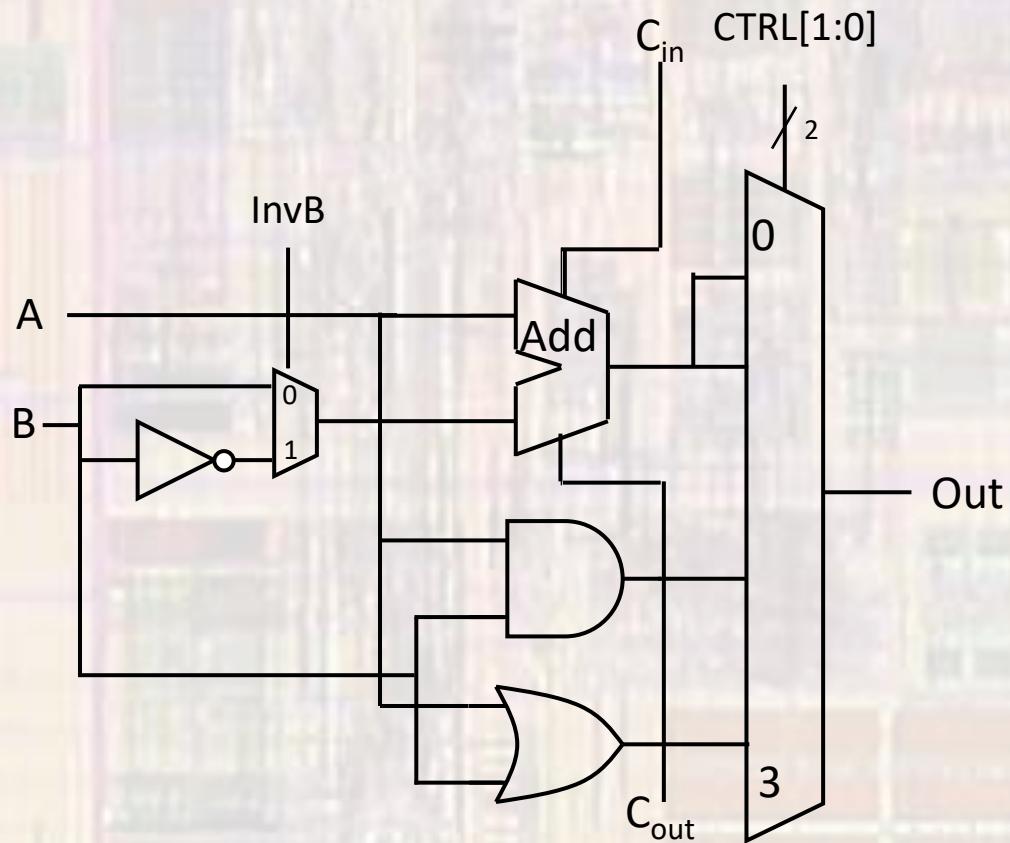- Control
 - $\text{CTRL}[1:0]$
 - 0,0 → subtract
 - 0,1 → add
 - 1,0 → AND
 - 1,1 → OR
 - $\text{CTRL}[1] = 1 \rightarrow \text{logical}$




ALU

- N-bit ALU

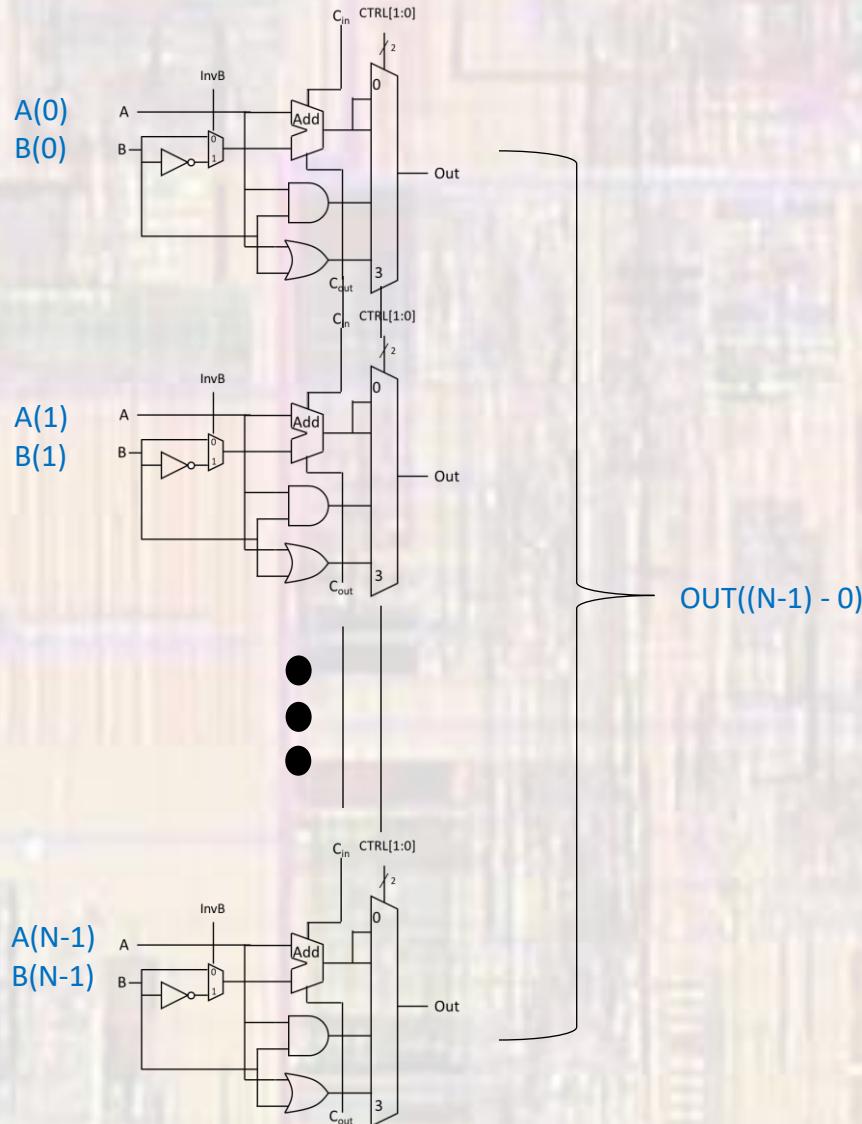


ALU

- Status Signals
 - Overflow Flag (v)

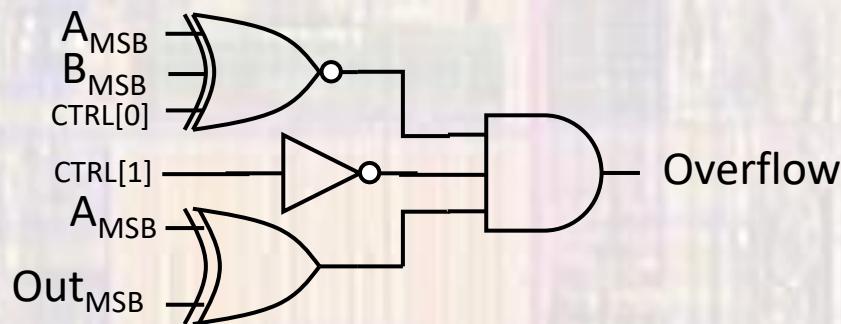

- Carry Flag (c)

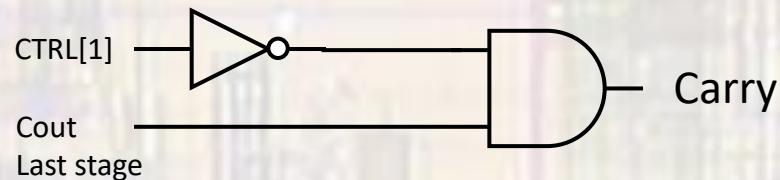

ALU

- Status Signals – cont'd
 - Zero Flag (z)



- Negative Flag (n)


OUT_{MSB} — Negative

ALU

- Control revisited


Operation	invB	Cin	Ctrl[1]	Ctrl[0]
AND	x	x	1	0
OR	x	x	1	1
ADD	0	0	0	0
SUB	1	1	0	1

Operation		Cin	Ctrl[1]	Ctrl[0]
AND			1	0
OR			1	1
ADD			0	0
SUB			0	1

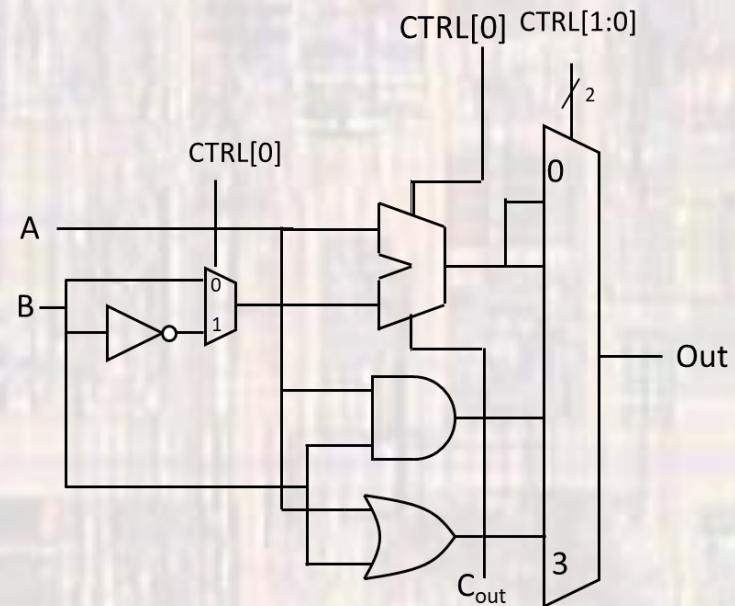

ALU

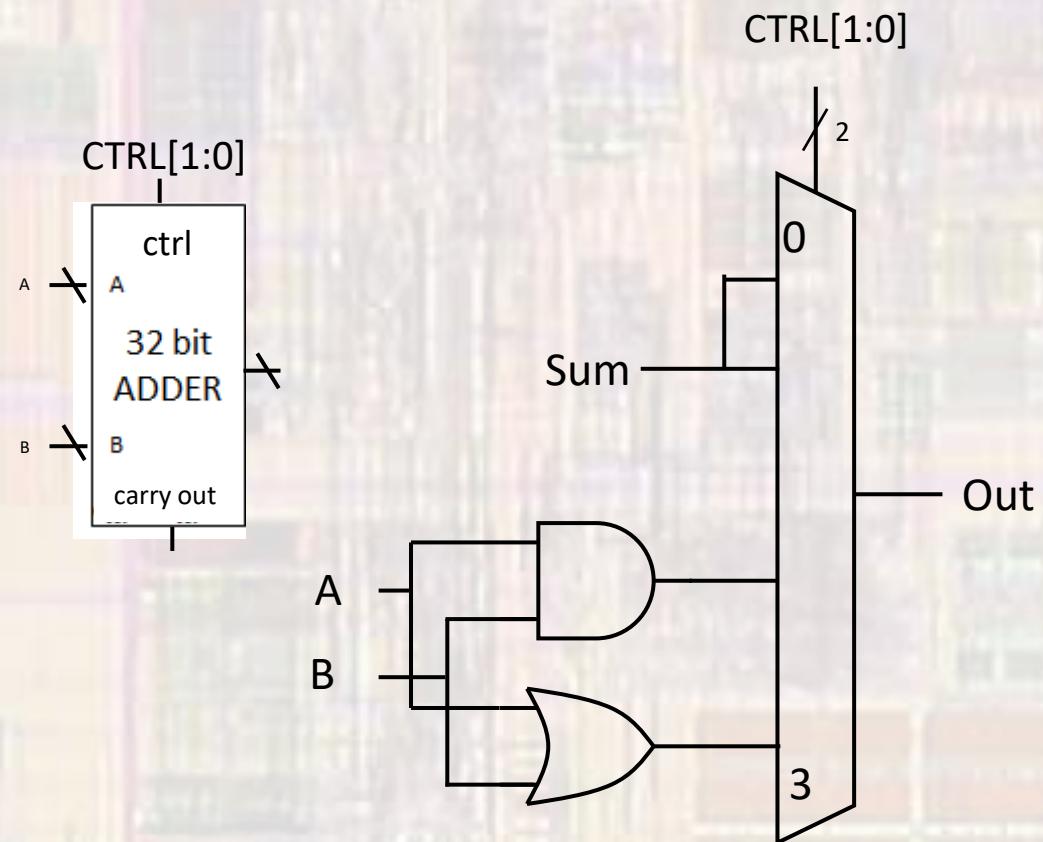- Enhanced Adder
 - Replace the carry chain adder with an efficient adder/subtractor



ALU

- 32 bit representation

