



Capacitor Circuits

Last updated 1/6/25


Capacitor Circuits

- Capacitor
 - Store electrical charge
 - Units: Farads (F)

Schematic Symbol

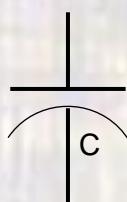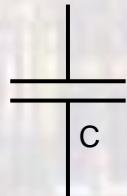


Physical

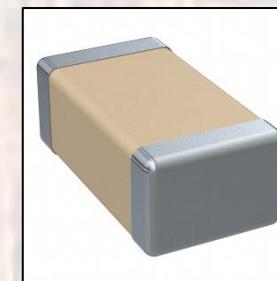

Leaded





Chip

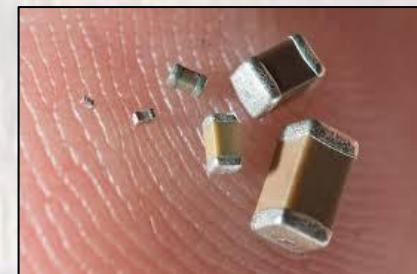

Capacitor Circuits

- DC Circuit Characteristics
 - Capacitors look like open circuits to DC voltages

$$I = 0$$

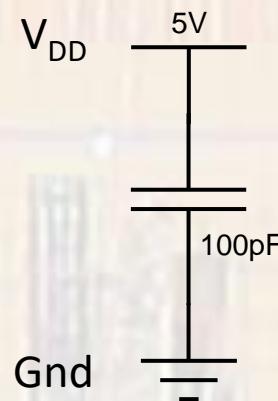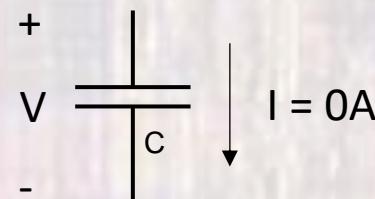


Capacitor Circuits

- Transient Circuit Characteristics

$$I = C \frac{dv}{dt}$$

amps = Farads * volts/sec
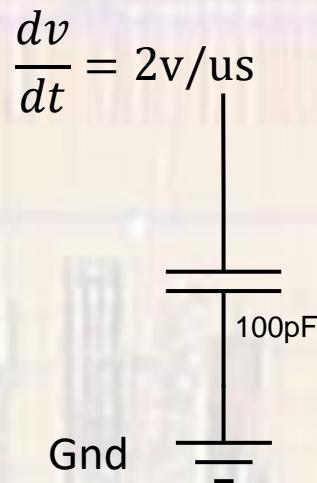
$$\frac{dv}{dt} \frac{+}{-} \text{C} \quad \downarrow \quad I = C \frac{dv}{dt}$$




$$I = 100\text{pF} * 2\text{v/us} = 200\text{ua}$$


Capacitor Circuits

- Capacitor Configurations

Series

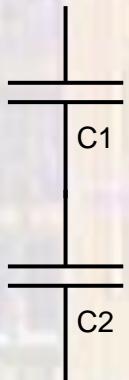

Parallel

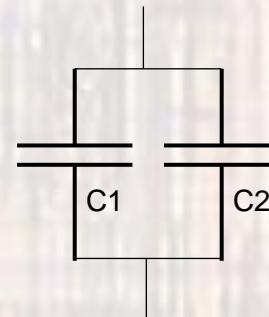

$$C_{eq} = 1/(1/C_1 + 1/C_2)$$

$$C_{eq} = C_1 + C_2$$