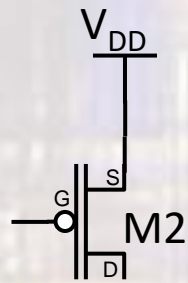


C-MOS Inverter

Last updated 1/6/25

C-MOS Inverter

- MOSFET Digital Configuration
 - Nominal source connections




P-Channel

V_G low:

M2 is ON \rightarrow $M2_D = V_{DD}$

V_G high:

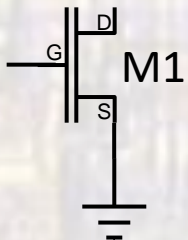M2 is OFF \rightarrow $M2_D = \text{open}$



N-Channel

V_G low:


M1 is OFF \rightarrow $M1_D = \text{open}$

V_G high:

M1 is ON \rightarrow $M1_D = \text{Gnd}$

C-MOS Inverter

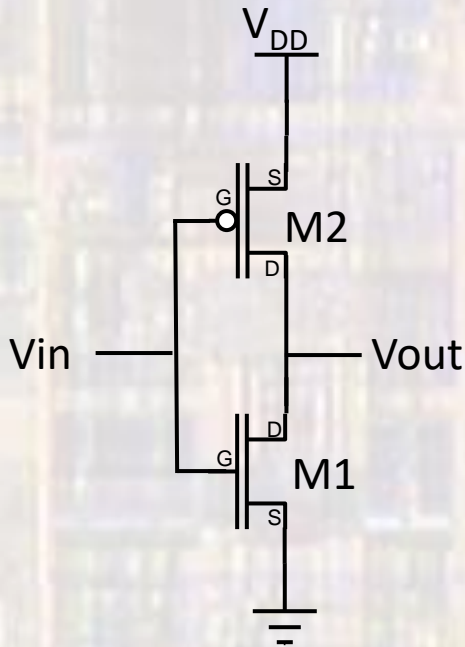- MOSFET Digital Configuration – Inverter
 - Inverts the logical value of the input



V_{in} low:

M2 is on $\rightarrow M2_D = V_{DD}$

M1 is off $\rightarrow M1_D = \text{open}$

$V_{out} = V_{DD}$

V_{in} high:

M2 is on $\rightarrow M2_D = \text{open}$


M1 is off $\rightarrow M1_D = \text{Gnd}$

$V_{out} = \text{Gnd}$


C-MOS Inverter

- C-MOS Inverter

- Circuit Symbol

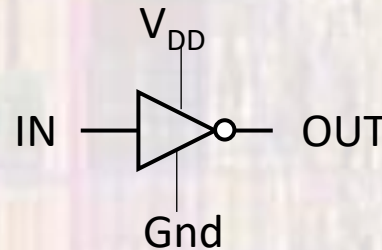

- Logic Symbol

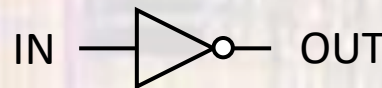


- Truth Table (logic)

IN	OUT
0	1
1	0

C-MOS Inverter


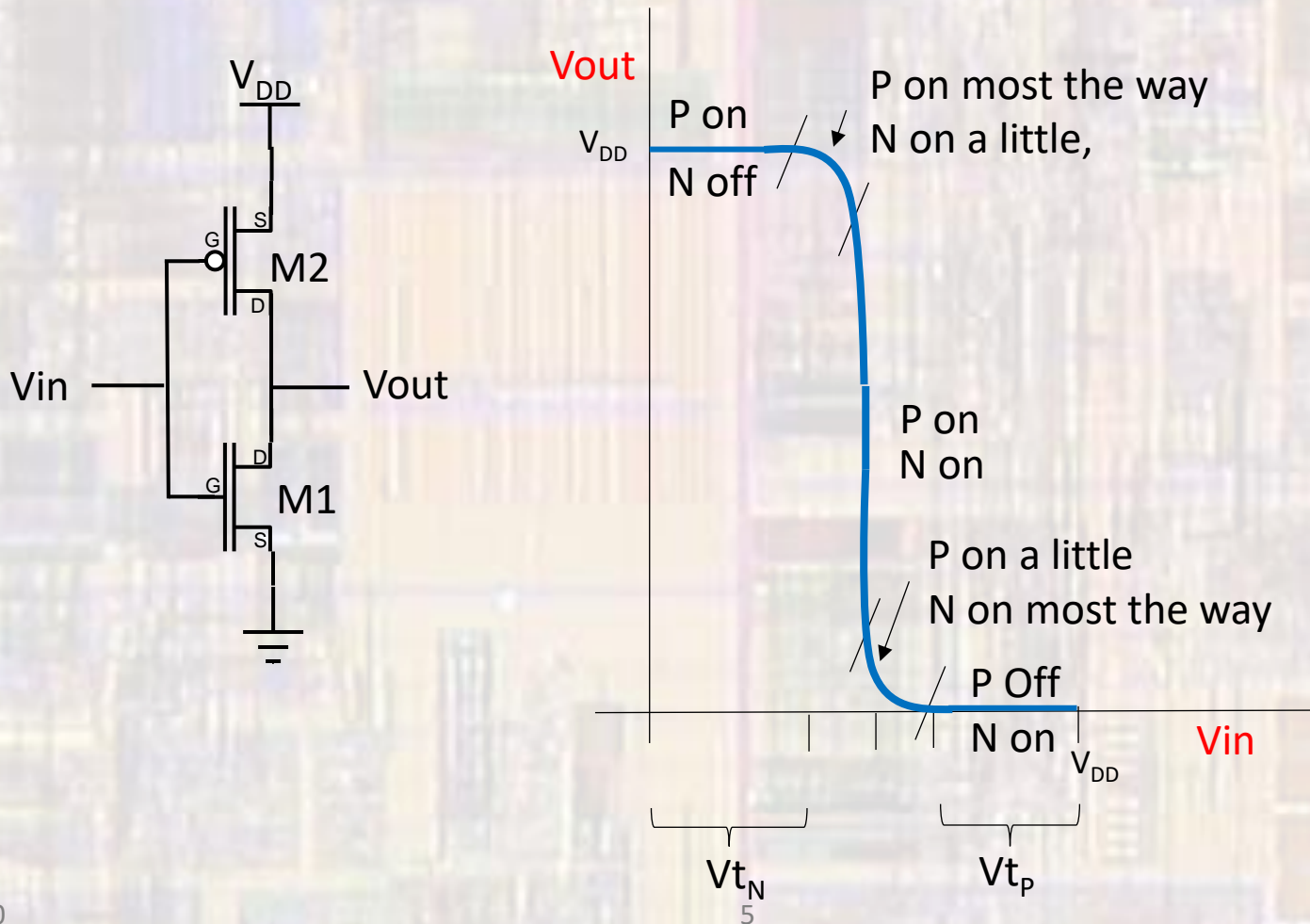
- Inverter – Qualitative – DC Transfer Characteristics



C-MOS Inverter

- Inverter – Qualitative – Transient Characteristics

- $V_{in}: 0 \rightarrow 1$

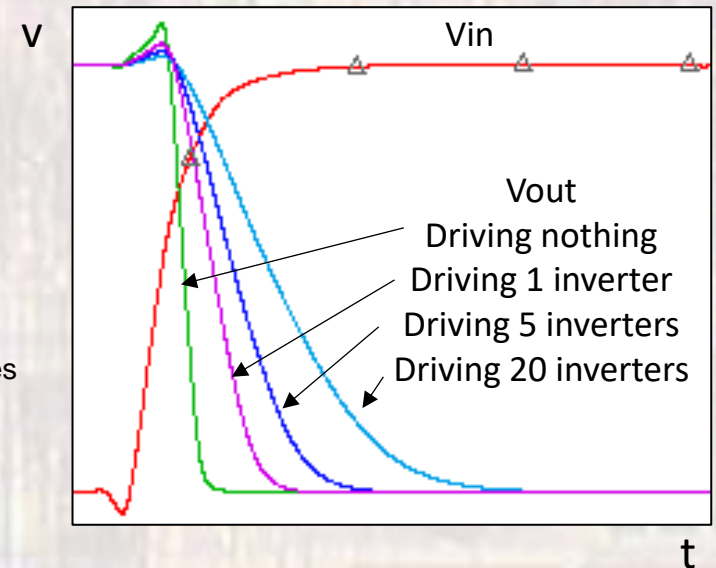
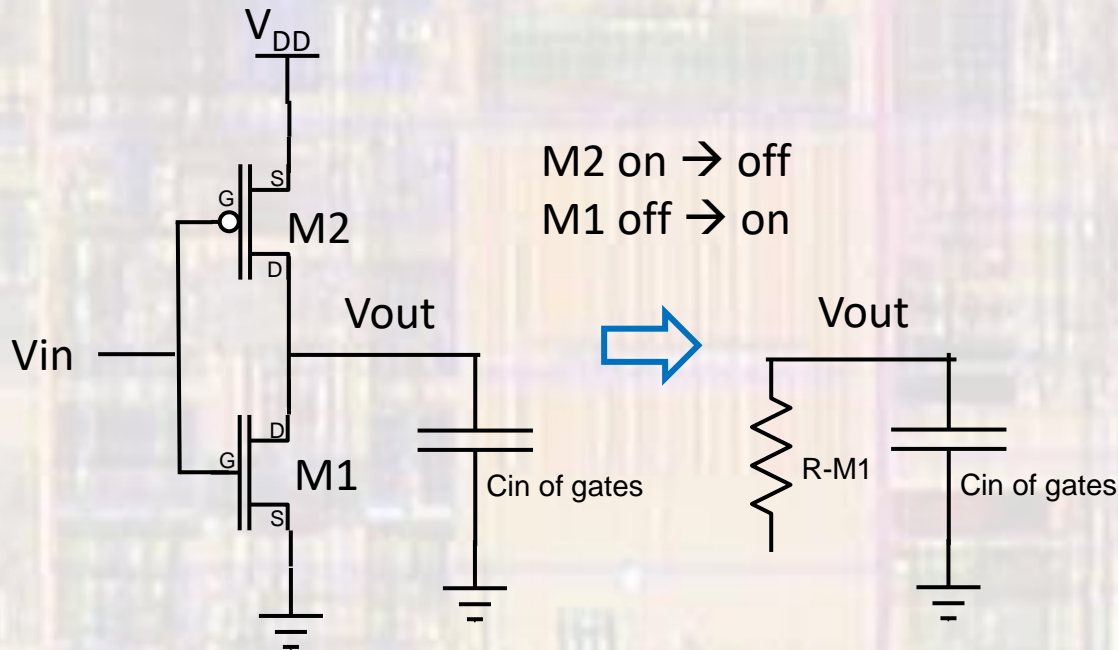


RC Time Constant

$$R_{M1} C_{load}$$

C-MOS Inverter

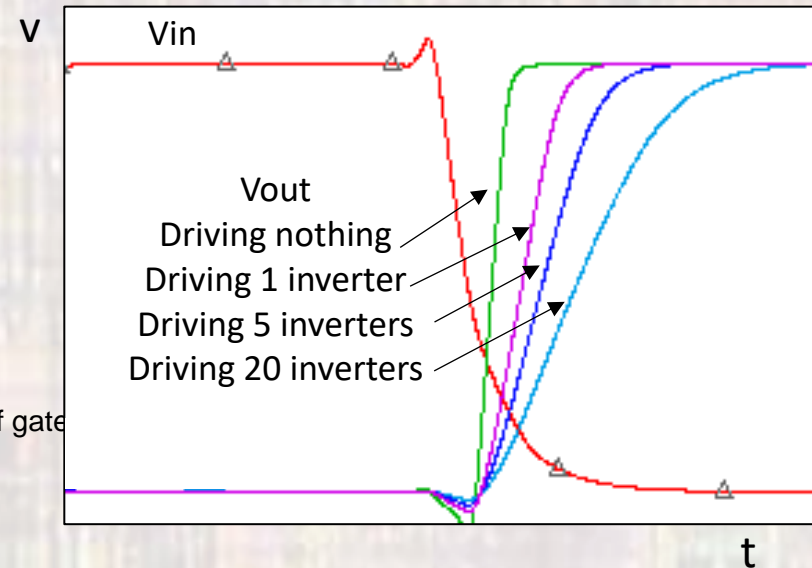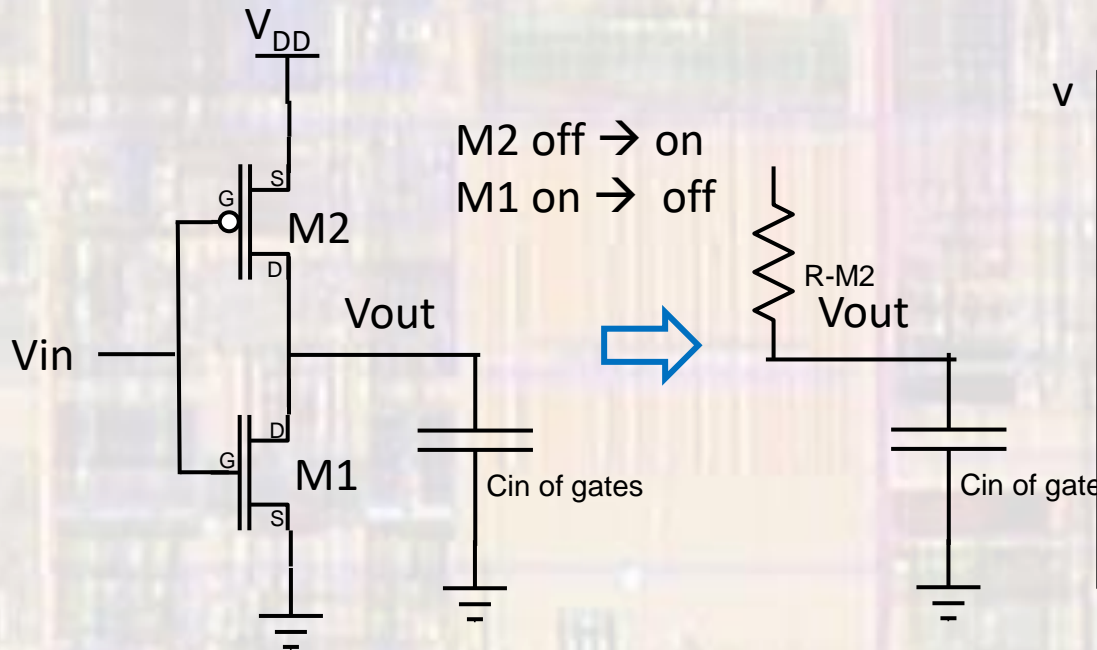- Inverter – Qualitative – Transient Characteristics
 - $V_{in}: 1 \rightarrow 0$



RC Time Constant

$$R_{M2} C_{load}$$