

CMOS Logic Area


Last updated 1/6/25

CMOS Logic Area

- Device area is the key driver for logic area calculations
 - Minimum device lengths and widths set minimum device area
 - In most technologies, P-MOS devices have approximately $1/3$ the strength of N-MOS device
 - To keep gates balanced, P-MOS devices need to be 3x as large as N-MOS devices
 - Devices in series must be made larger due to the need to make the series path through multiple devices the same strength as a single device



CMOS Logic Area

 - CMOS Gates – INV
 - Total area: $4X \text{ nm}^2$




CMOS Logic Area

  - CMOS Gates – NOR₂
 - Total area: $14X \text{ nm}^2$





CMOS Logic Area

 - CMOS Gates – NOR₃
 - Total area: $30X \text{ nm}^2$





CMOS Logic Area

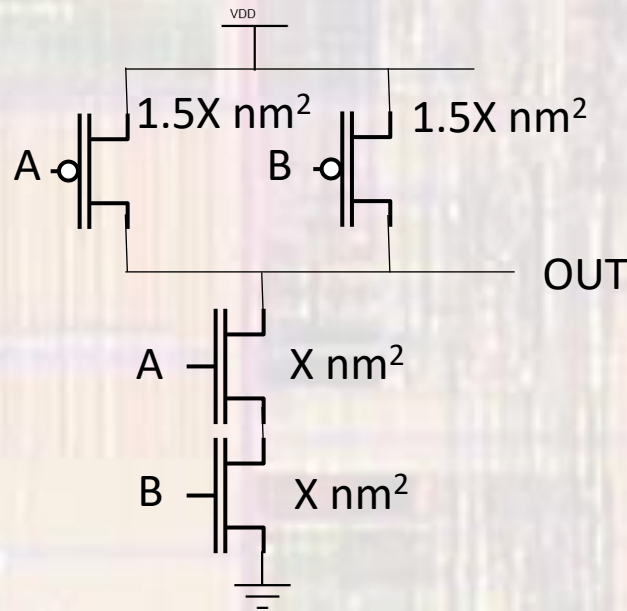 - CMOS Gates – NAND₂
 - Total area: $5X \text{ nm}^2$






CMOS Logic Area

 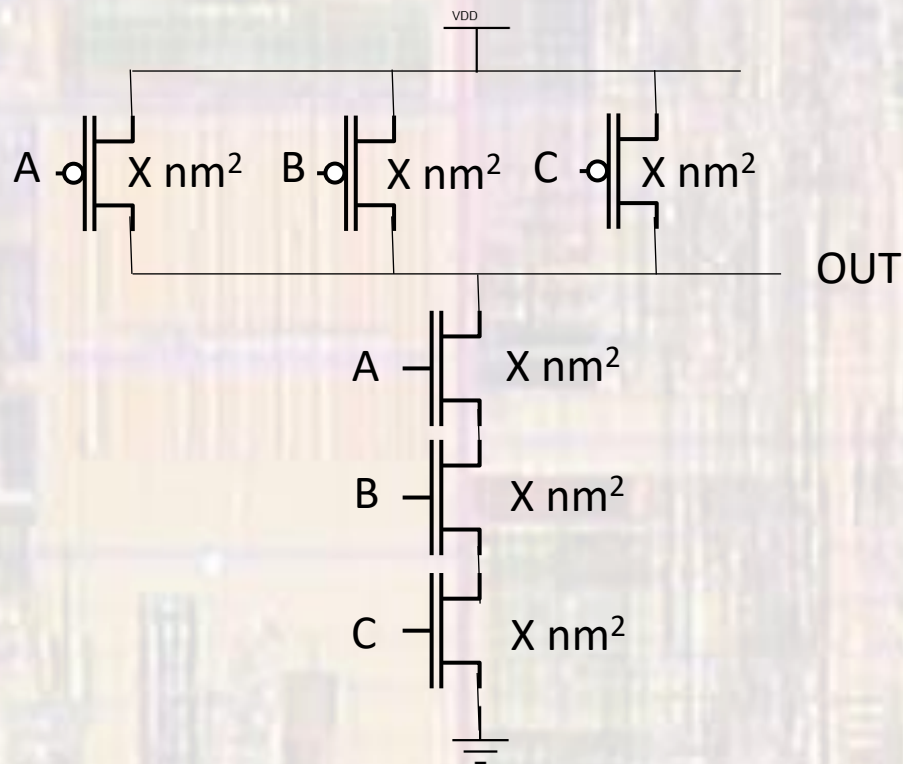- CMOS Gates – NAND₃
 - Total area: $6X \text{ nm}^2$




CMOS Logic Area

  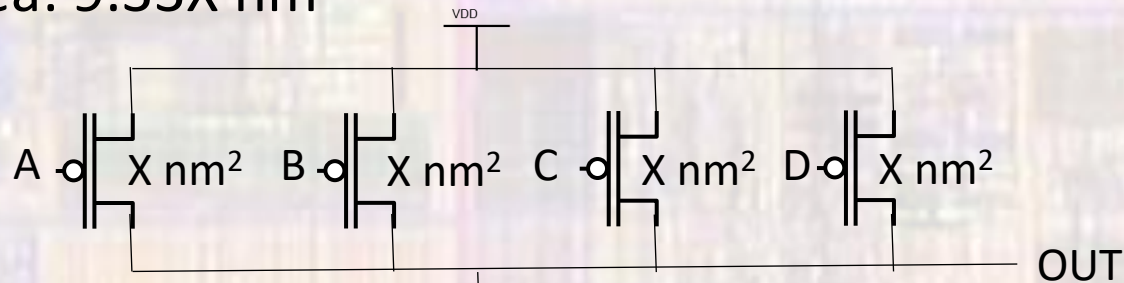- CMOS Gates – NAND_4
 - Total area: $9.33X \text{ nm}^2$



CMOS Logic Area

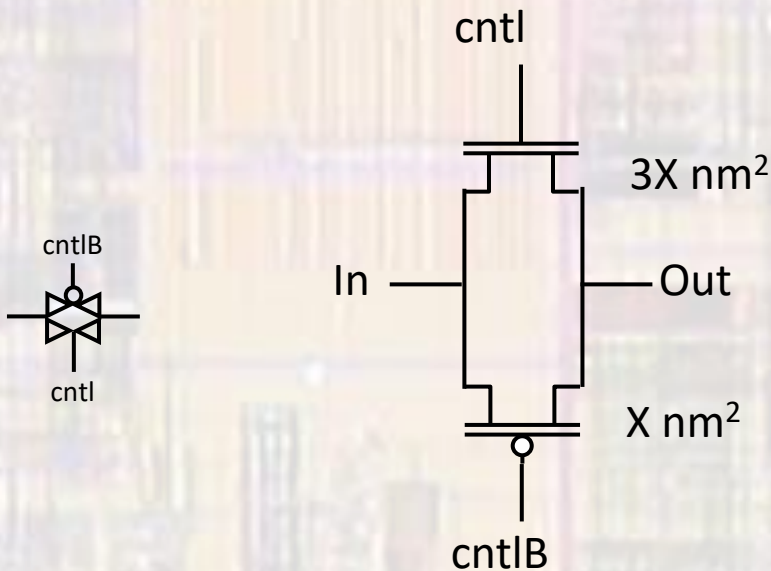- CMOS Transmission Gates
 - Total area: $4X \text{ nm}^2$
 - Often we just make them the same size $\rightarrow 2X \text{ nm}^2$



CMOS Logic Area

- Summary
 - NAND gates preferred over NOR gates

Gate	Area (X nm ²)
INV	4
NOR_2	14
NOR_3	30
NAND_2	5
NAND_3	6
NAND_4	9.33
T-Gate	4