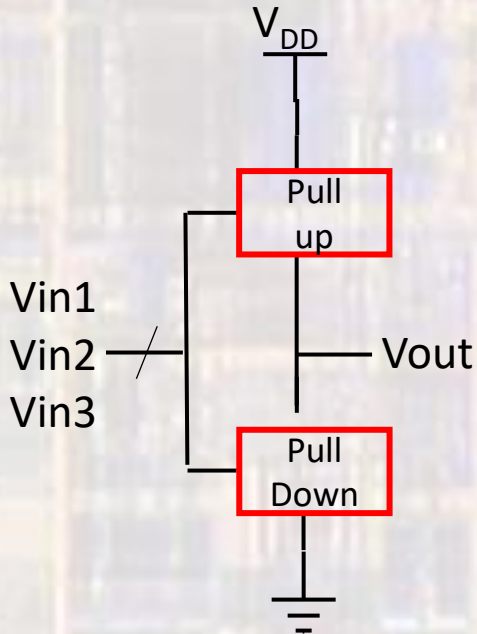


CMOS Logic Circuits

Last updated 10/31/24

CMOS Logic Circuits

- Gate Concepts




We can generalize our inverter results to account for more complex gates

Ensure every input combination results in either:
The Pull-up network provides a path to V_{DD}
or

The Pull-down network provides a path to GND
never
Both

CMOS Logic Circuits

- CMOS Gates - NOR

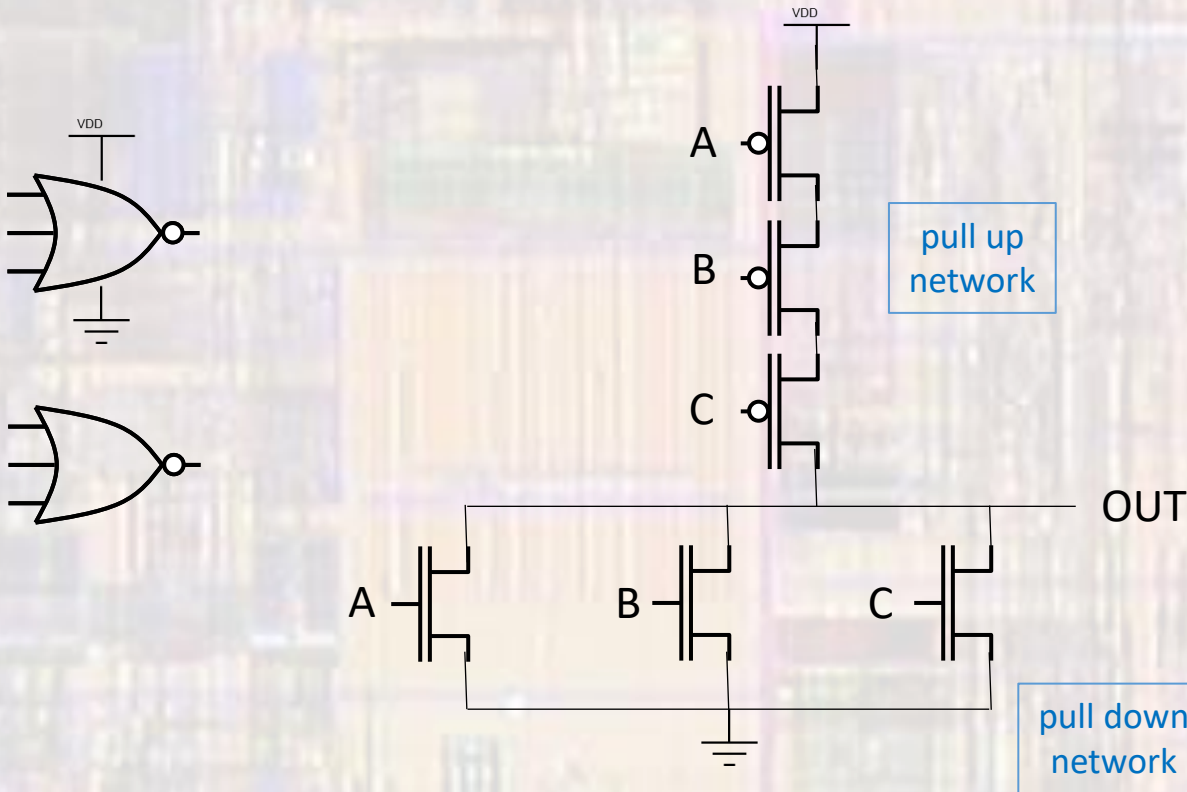


A	B	C	NOR OUT
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

If ANY input is high, pull-down is on, pull-up is off → output is low
If ALL inputs are low, pull-down is off, pull-up is on → output is high

CMOS Logic Circuits

- CMOS Gates - NAND

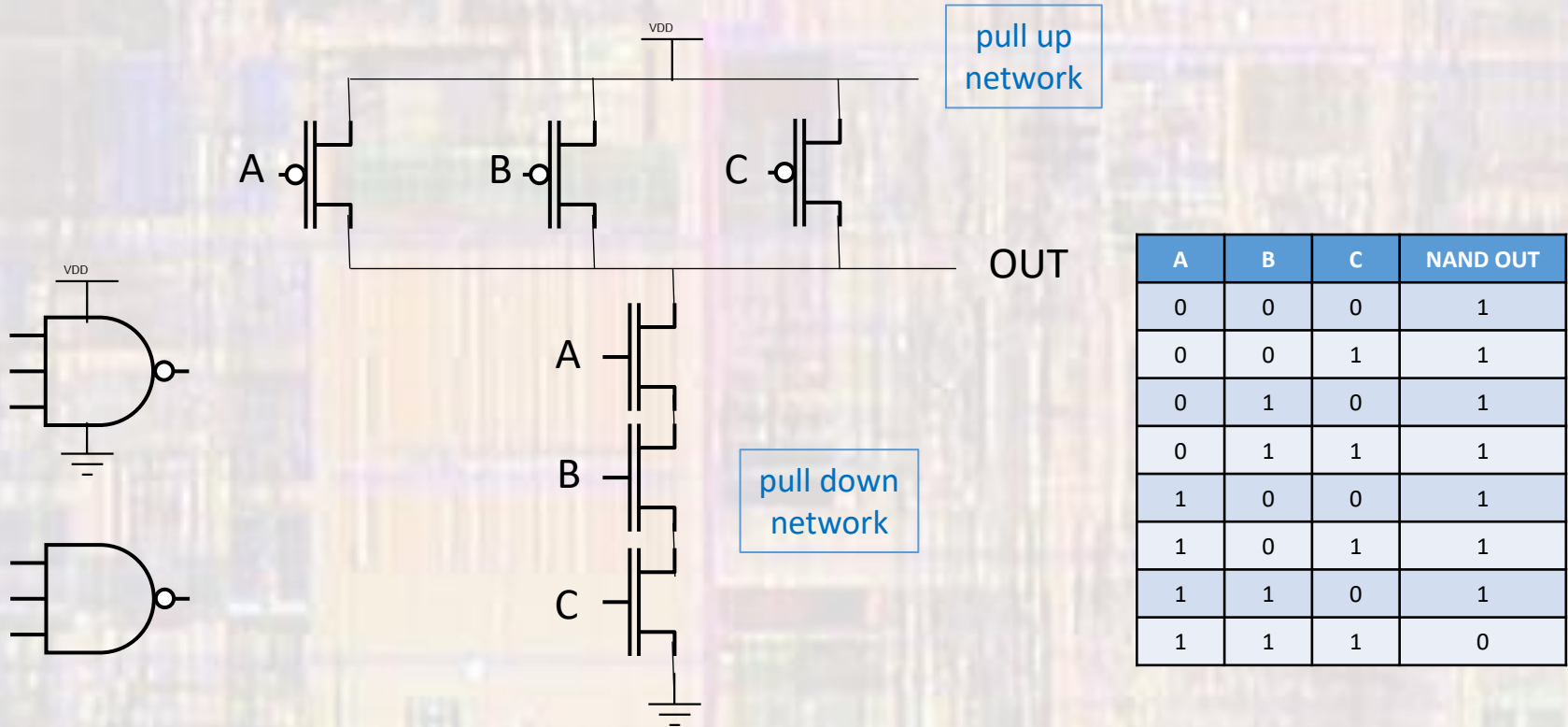

If ANY input is low, pull-up is on, pull-down is off → output is high
If ALL inputs are high, pull-up is off, pull-down is on → output is low

CMOS Logic Circuits

- AND / OR
 - Note – CMOS technology has an inherent inversion operation when configured into a gate
 - AND gates require a NAND gate and an Inverter






- OR gates require a NOR gate and an Inverter



CMOS Logic Circuits

- XOR

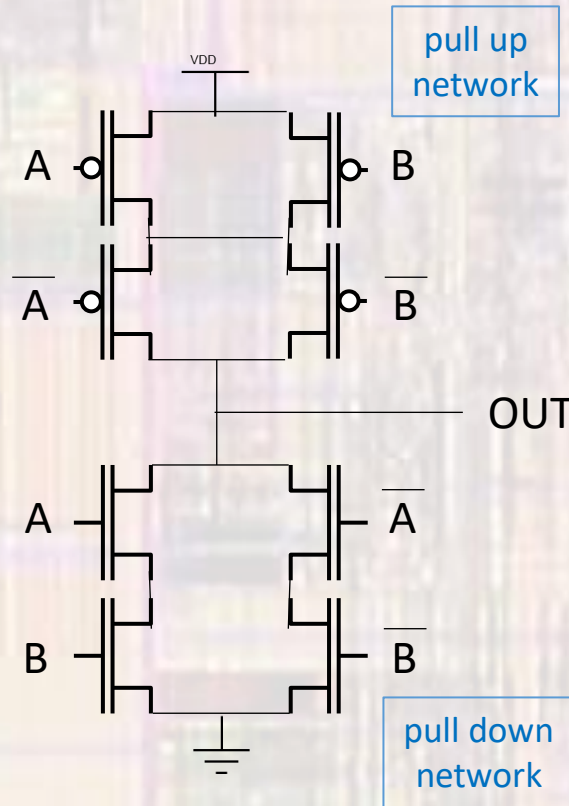
 
 


A	B	$A \oplus B$
1	1	0
1	0	1
0	1	1
0	0	0

If ONLY ONE input is high, pull-up is on, pull-down is off → output is high

CMOS Logic Circuits

- XNOR

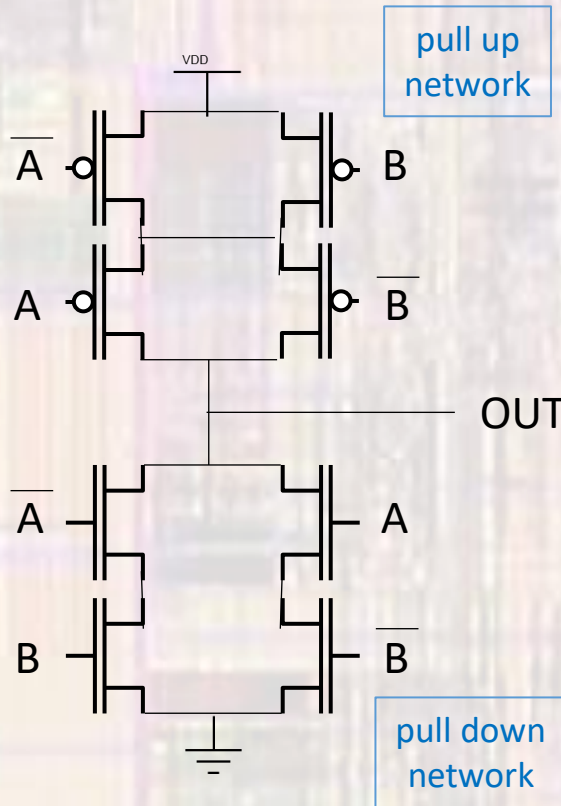  


A	B	$A \odot B$
1	1	1
1	0	0
0	1	0
0	0	1

If ONLY ONE input is high, pull-down is on, pull-up is off → output is low

CMOS Logic Circuits

- Complex Gates

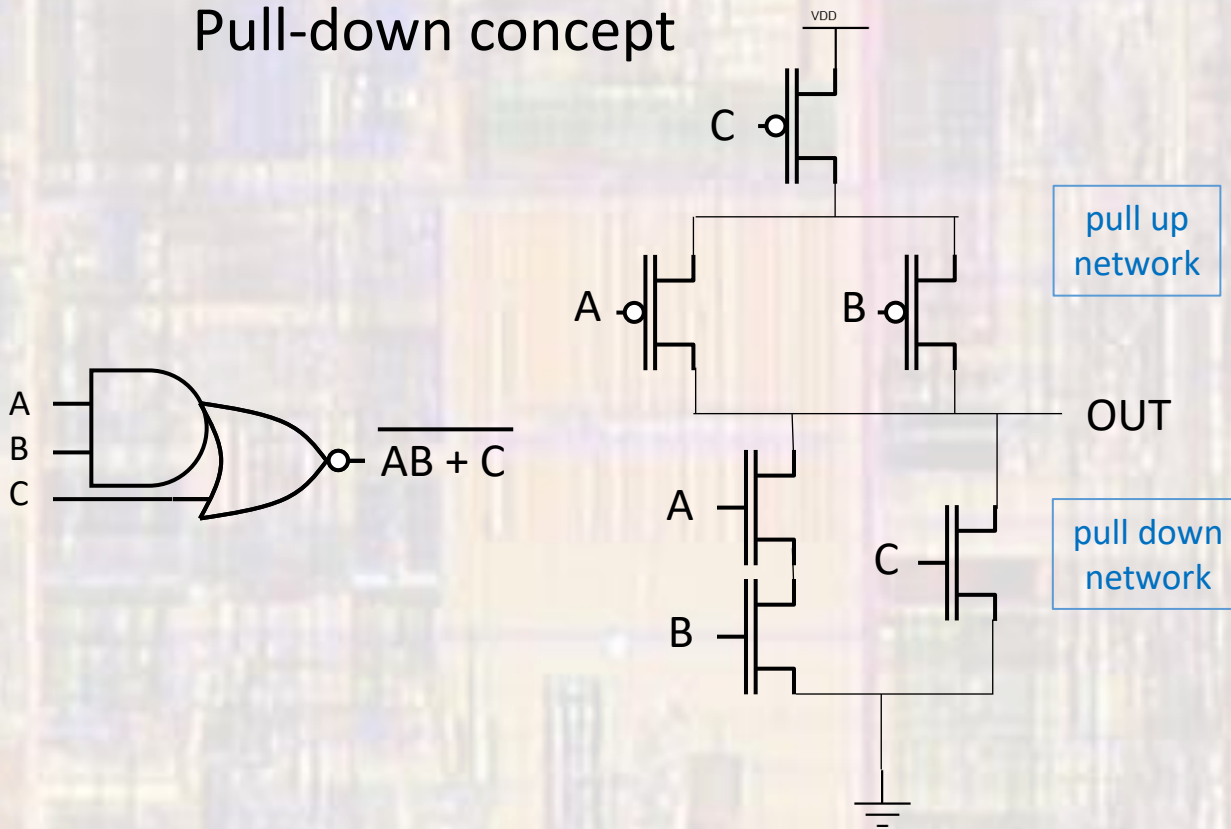- Special function gates can be created using the Pull-up / Pull-down concept




A	B	C	$\overline{AB + C}$
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

CMOS Logic Circuits

- CMOS Tristate Inverter

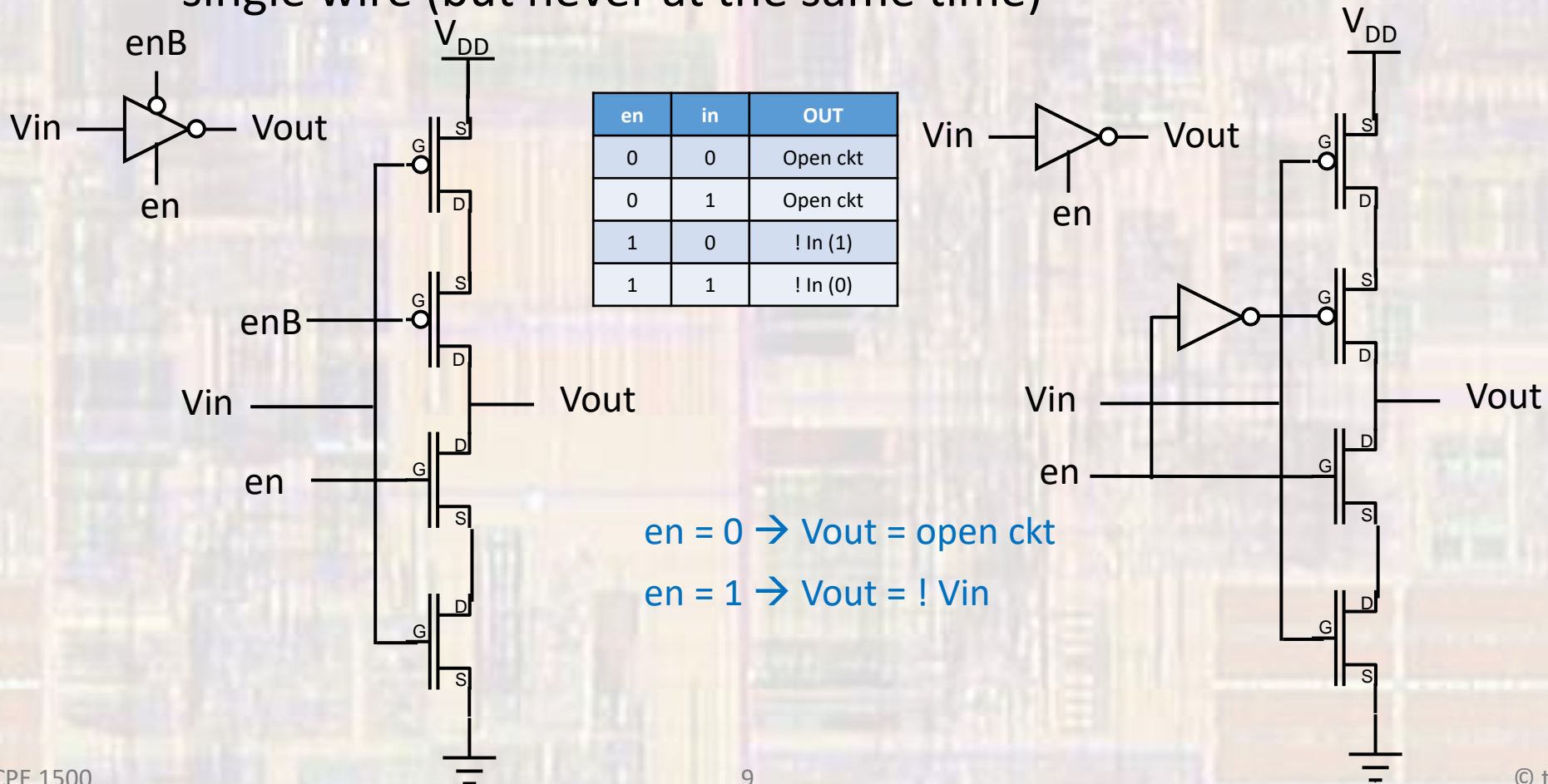- What can we do if we want multiple circuits to drive a single wire (but never at the same time)



CMOS Logic Circuits

- CMOS Transmission Gates

- Use parallel P-MOS and N-MOS devices as a “pass gate”
 - Passes both ‘0’s and ‘1’s
 - Bi-directional
 - Requires cntl and cntlB

