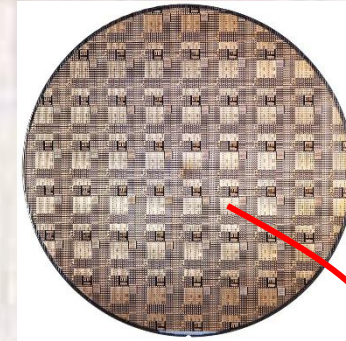


# CMOS Transistor Basics


Last updated 1/6/25

# CMOS Transistor Basics


- Integrated Circuit (IC) technology
  - Built on **wafers**
    - 4" → 12" diameter
    - Multi \$B factories
    - Mostly run with automation – few people
      - See videos on website
  - Cut into individual **die**
  - Packaged into IC '**chips**'




100s to 1000s  
of die per wafer

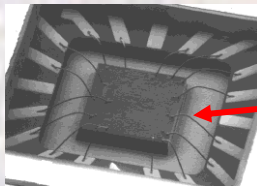

die bonded in package

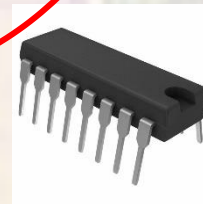

dual in line package

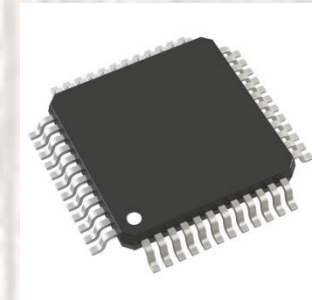

quad flat package

# CMOS Transistor Basics


- Semiconductor Component History
  - 1960s
    - Junction Diodes
    - Bipolar Transistors
      - NPN, PNP
  - 1970s
    - N-MOS Transistors
    - P-MOS Transistors
    - C-MOS Transistors
  - 1990s
    - FinFET Transistors
  - 2000s
    - All Around Gate Transistors
  - Continuous shrinking of technology

# CMOS Transistor Basics

- Modern Day
  - All modern digital ICs (integrated Circuits) are built on CMOS technology
  - Only exception is very small circuits designed to be backward compatible to earlier Bipolar technologies

Basic Logic Gate (NAND-2)


CMOS

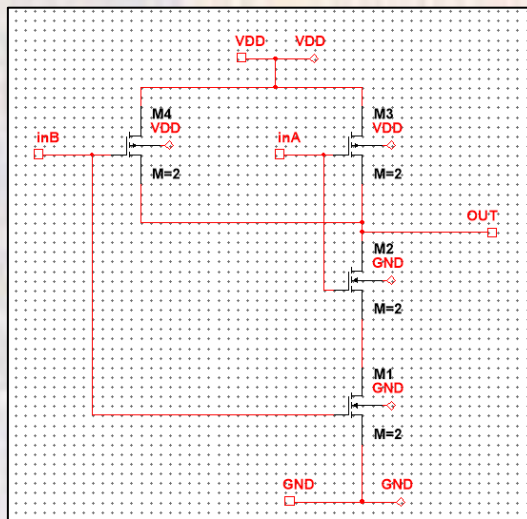

4 transistors

Small, low power

Bipolar

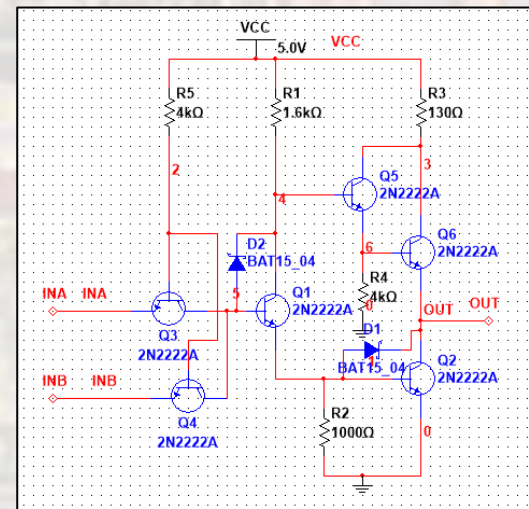

6 transistors  
2 diodes  
5 resistors

Large, high power

# CMOS Transistor Basics

- CMOS
  - Complimentary Metal Oxide Semiconductor
    - Integrated Circuit technology
  - Dominates digital circuit design
    - Small
    - No DC power
  - Many variations
    - Referenced by generation: 1um, 100nm, 10nm, 7nm, 5nm, ...
    - Shrinking sizes lead to more 'stuff' in a fixed area
  - 2 primary devices (complimentary)
    - N-Channel (**NMOS**, N-type)
    - P-Channel (**PMOS**, P-Type)


# CMOS Transistor Basics

- N-Channel (NMOS, N-type)
  - Primary current carrier – electrons
  - 4(3) terminals
    - Gate – control
    - Drain/Source – current flow
    - Body – fixed connection for digital designs



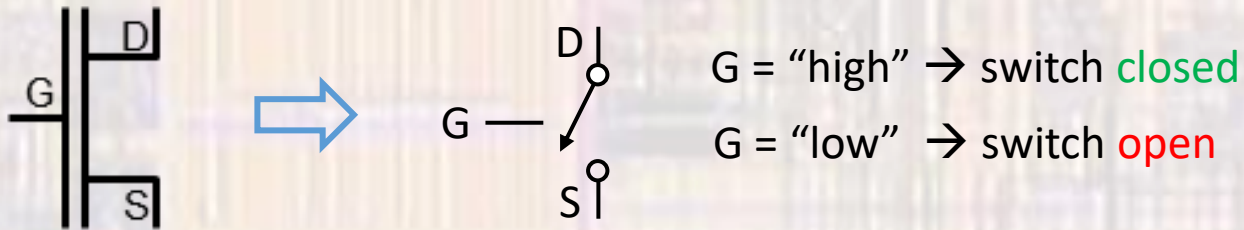
# CMOS Transistor Basics

- N-Channel (NMOS, N-type)
  - Full transistor characteristics very complicated
  - 2 Levels of abstraction
    - Ideal Switch


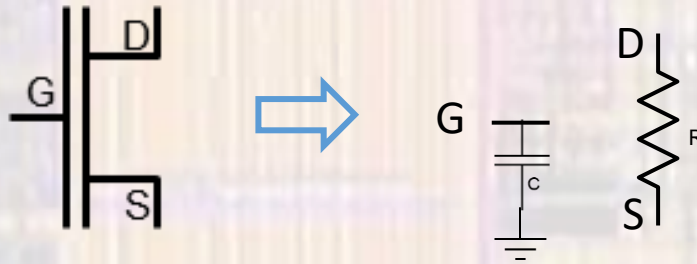
# CMOS Transistor Basics

- N-Channel (NMOS, N-type)
  - Full transistor characteristics very complicated
  - 2 Levels of abstraction
    - Complex Switch



$G = \text{"high"} \rightarrow R \text{ small}$

$G = \text{"low"} \rightarrow R \text{ large}$




$R \downarrow$  as transistor size  $\uparrow$

$C \uparrow$  as transistor size  $\uparrow$


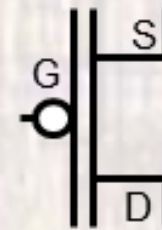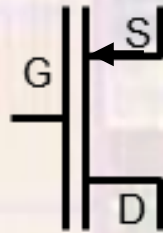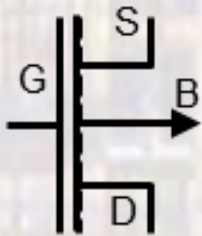
# CMOS Transistor Basics




- P-Channel (PMOS, P-type)
  - Primary current carrier – holes (positive charge)
  - 4(3) terminals
    - Gate – control
    - Drain/Source – current flow
    - Body – fixed connection for digital designs



digital version
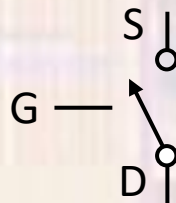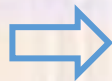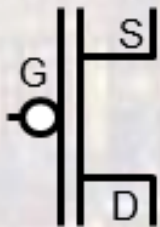
# CMOS Transistor Basics

- P-Channel (PMOS, P-type)
  - Full transistor characteristics very complicated
  - 2 Levels of abstraction
    - Ideal Switch




G = "low" → switch **closed**

G = "high" → switch **open**
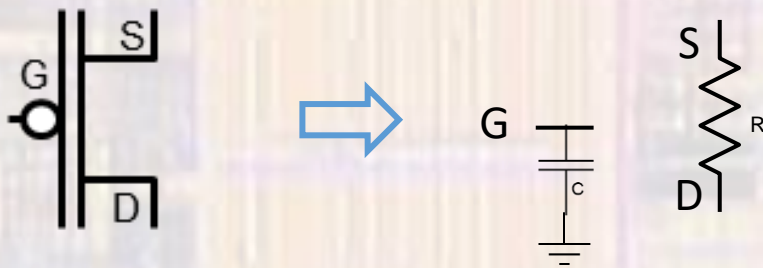
# CMOS Transistor Basics

- P-Channel (PMOS, P-type)
  - Full transistor characteristics very complicated
  - 2 Levels of abstraction
    - Complex Switch



$G = \text{"low"} \rightarrow R \text{ small}$

$G = \text{"high"} \rightarrow R \text{ large}$

$R \downarrow$  as transistor size  $\uparrow$


$C \uparrow$  as transistor size  $\uparrow$

# CMOS Transistor Basics


- Complimentary
  - For the same Gate value
    - One is **on** and the other is **off**

PMOS



G = "high"

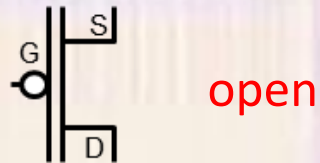

G = "low"

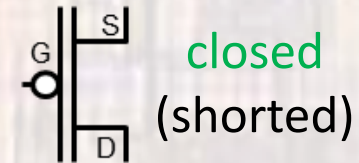

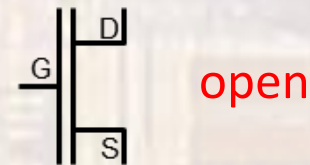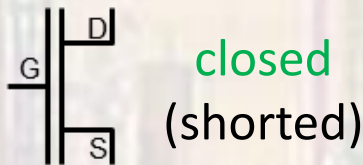

NMOS




# CMOS Transistor Basics

- A little more detail
  - NMOS devices do not turn on (close/short) until the gate voltage reaches a small positive voltage
  - Threshold voltage -  $V_{t_N}$ 
    - 0.7v for 3.3V systems
    - 0.45v for 1.2V systems
  - PMOS devices do not turn on (close/short) until the gate voltage reaches a small voltage below  $V_{DD}$
  - Threshold voltage -  $V_{t_p}$ 
    - 2.7v for 3.3V systems
    - 0.75v for 1.2V systems


# CMOS Transistor Basics

- Digital Iconography
  - In digital circuits, a  (bubble) indicates opposite (inverted) operation
    - The NMOS is ON when the gate is high  $\rightarrow$  active high
    - The PMOS is ON when the gate is low  $\rightarrow$  active low  $\rightarrow$  

PMOS

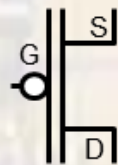

NMOS

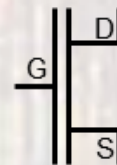

# CMOS Transistor Basics

- CMOS Transistor Parameters
  - Gate terminal
    - Looks like a capacitor to ground
  - S/D terminals
    - Look like a variable value resistor between S/D
  - Size
    - Large transistors
      - Larger gate capacitance
      - Smaller resistance values
    - Small transistors
      - Smaller gate capacitance
      - Larger resistance values
    - P vs. N
      - Same gate capacitance for the same size
      - P is weaker than N for a given size
        - $R_{ON-P}$  2x to 3x  $R_{ON-N}$